

# **ECE 325 – Electric Energy System Components**

## **2- Fundamentals of Electrical Circuits**

Instructor:



Kai Sun

Fall 2016

# Content


- Fundamentals of electrical circuits (Ch. 2.0-2.15, 2.32-2.39)
- Active power, reactive power and apparent power (Ch. 7)
- Three-phase AC systems (Ch. 8)
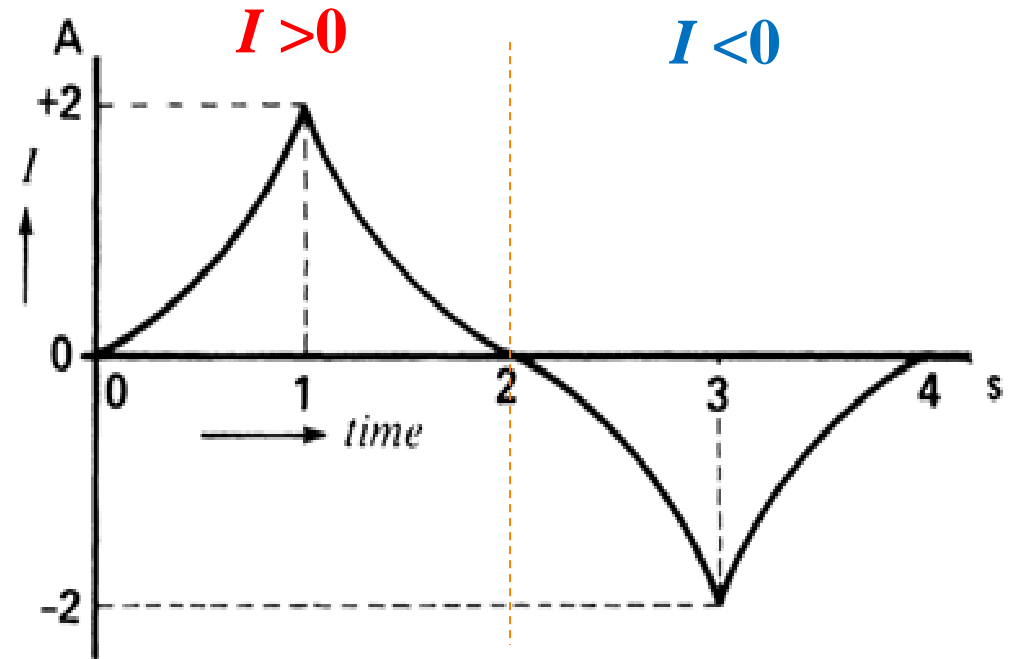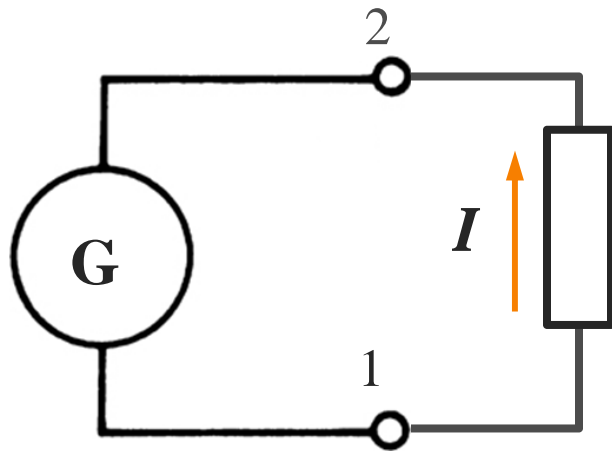
## Notations: Current and Alternating Current



- **Arbitrarily** determine a positive direction, e.g.  $1 \rightarrow 2$ 
  - If a current of 2A flows from 1 to 2,  $I = +2$  A
  - If a current of 2A flows from 2 to 1,  $I = -2$  A


# Notations: Voltage

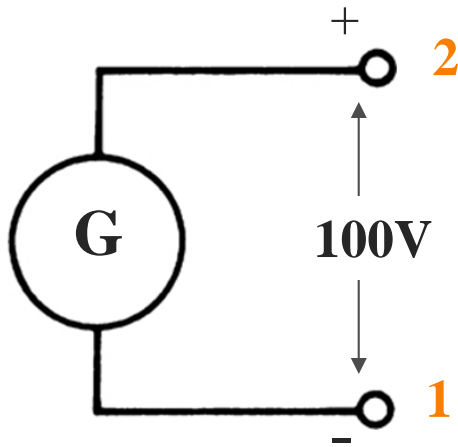

## 1. Double-subscript notation:

$E_{21} = +100\text{V}$  (the voltage between 2 and 1 is 100V, and 2 is positive w.r.t 1)

$$E_{12} = -100\text{V}$$

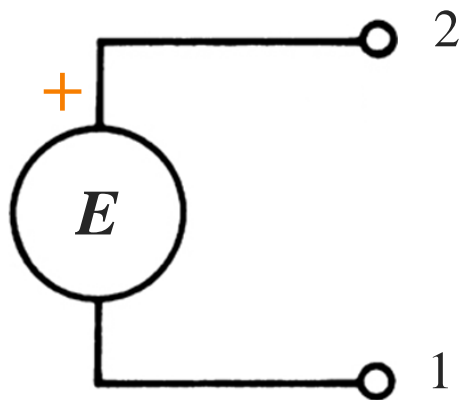


## 2. Sign notation:

**Arbitrarily** mark a terminal with (+);  
 $E > 0$  if and only if that marked terminal is positive w.r.t the other.


E.g. if  $E_{21} = +100\text{V}$ ,  $E = E_{21} = +100\text{V}$ .

Both the double-subscript notation and sign notation apply to alternating voltage

## Notations: Alternating Voltage

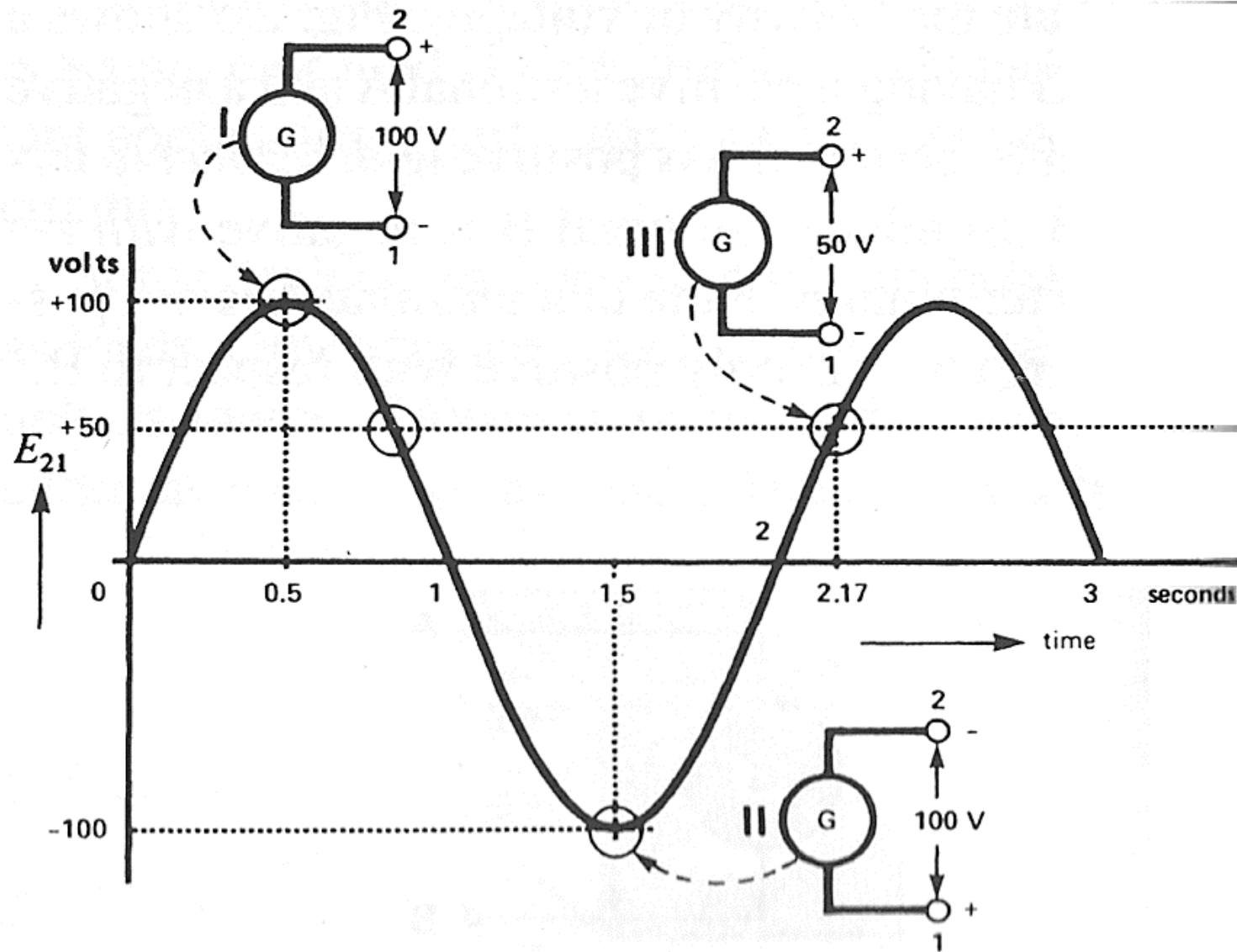


## Notations: Sources and Loads

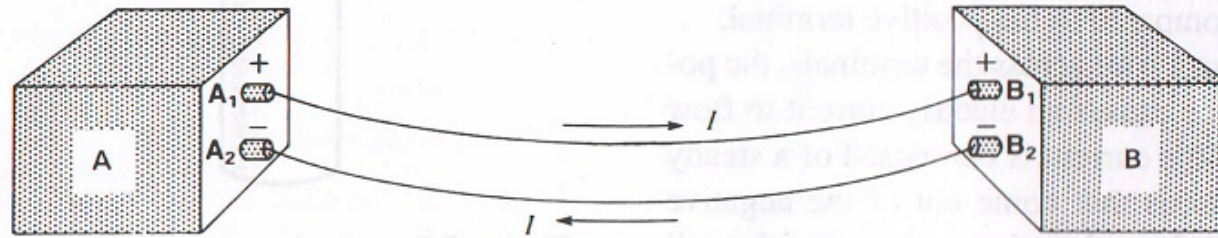


**Figure 2.4**

Distinction between a source and a load.

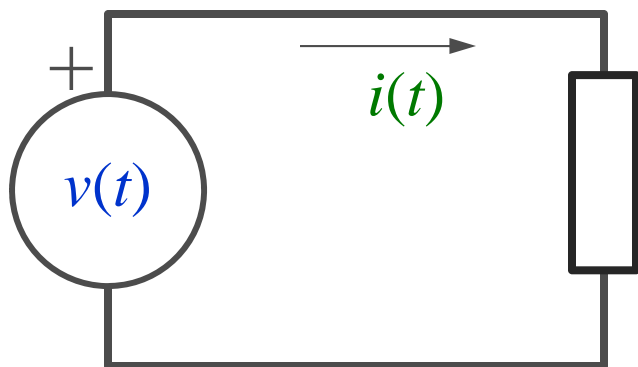
- **Definition:** given the **instantaneous, actual** polarity of voltage and **actual** direction of current
  - **Actual Source:** whenever current flows out of the terminal (+)
  - **Actual Load:** whenever current flows into the terminal (+)
- How about these?
  - Resistor, battery cell, electric motor, capacitor and inductor




## Resistor

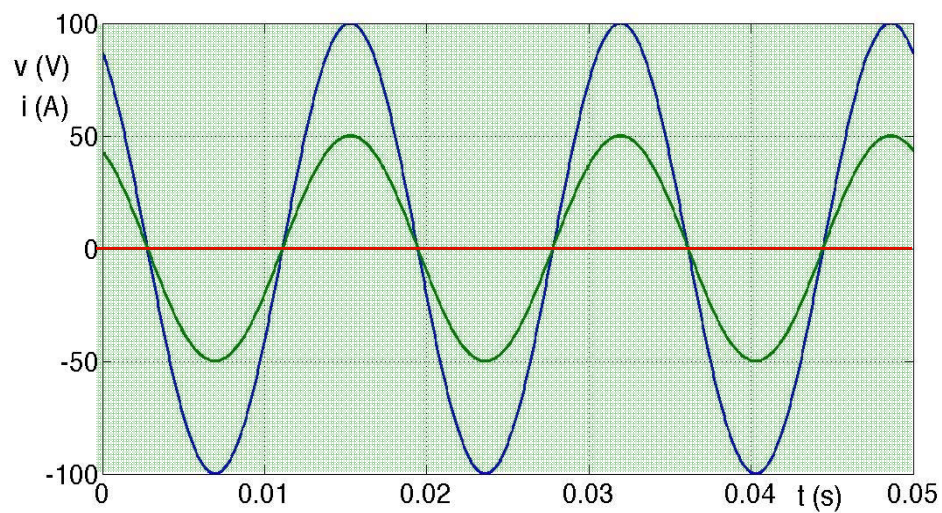


## Inductor

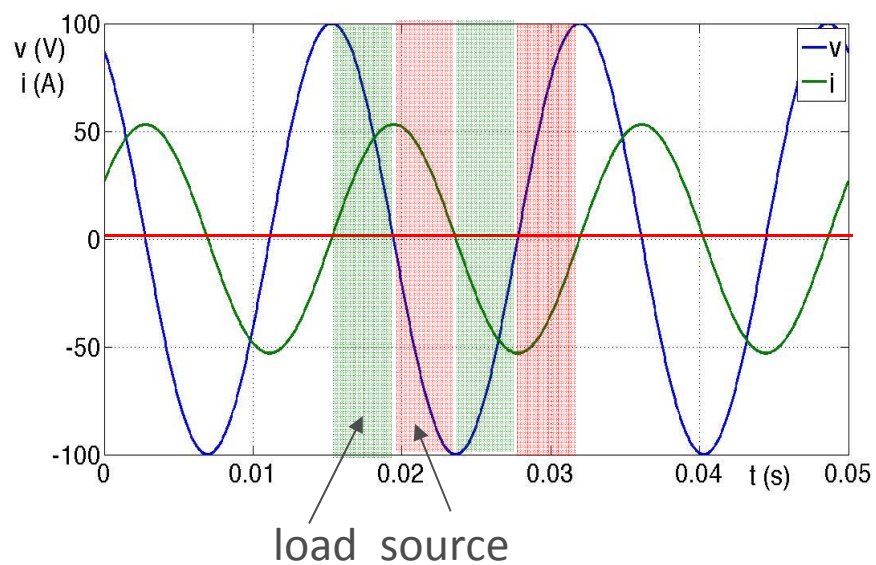

## Capacitor

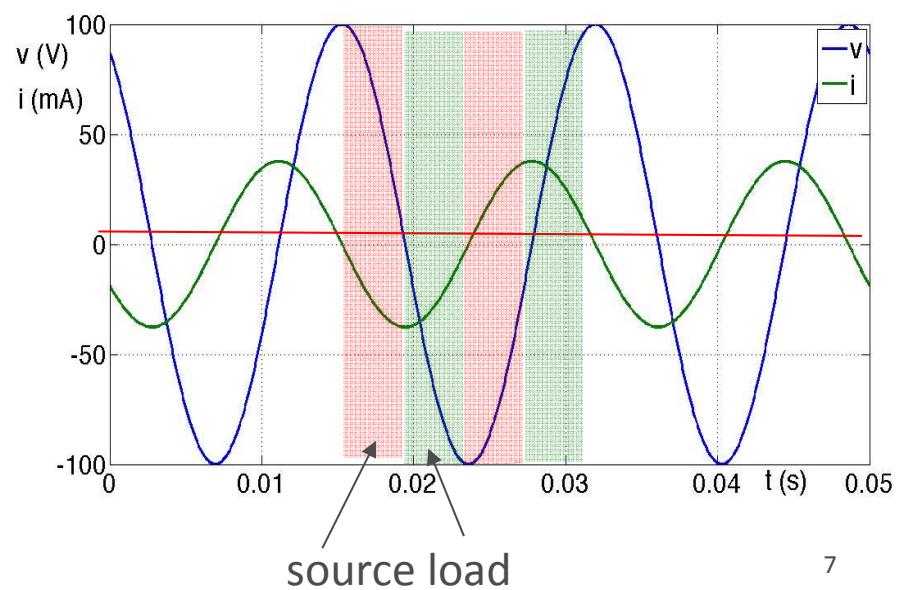
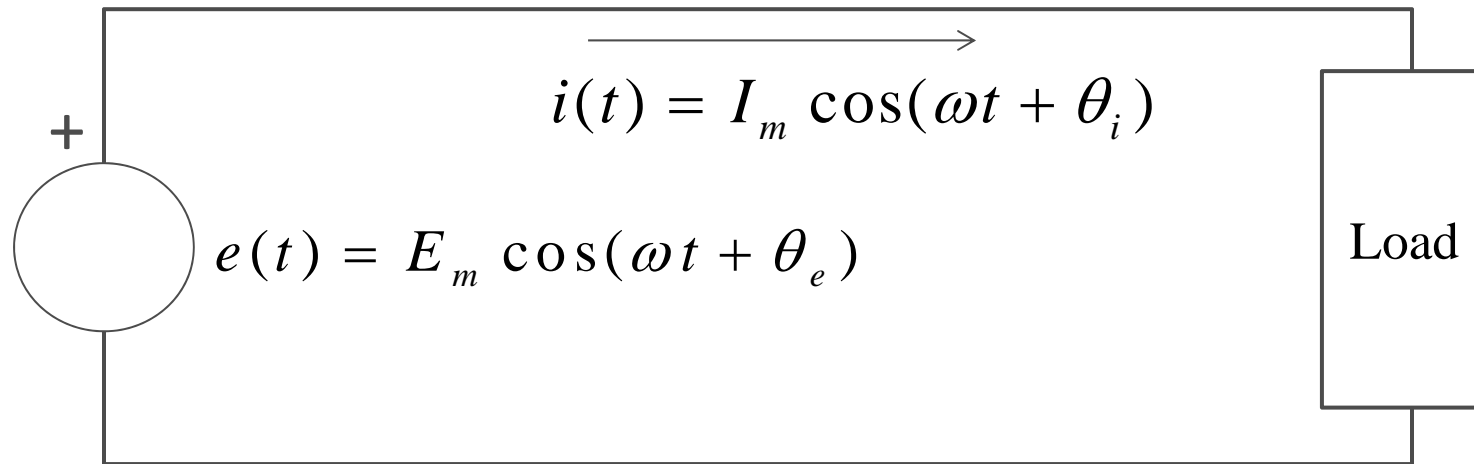
# 1-Phase AC System with Sinusoidal Voltage and Current



- $e, i$ : instantaneous voltage (V) and current (A)
- $E_m, I_m$ : peak values of the sinusoidal voltage (V) and current (A)
- $\omega = 2\pi f$  (rad/s): angular frequency, which is assumed constant here
- $\theta_e, \theta_i$ : constant phase angles (rad. or deg.) of voltage and current
- $E_m/\sqrt{2}, I_m/\sqrt{2}$ : RMS (root-mean-square, effective) values

$$\int_{t-T}^t [i(t)]^2 R dt = \frac{I_m^2 R T}{2} = I_{dc}^2 R T$$

Equal heating effects

$$\rightarrow I_{dc} = \frac{I_m}{\sqrt{2}} \triangleq \text{RMS value}$$



# Phasor Representation


$$e(t) = E_m \cos(\omega t + \theta_e) = \sqrt{2} |E| \cos(\omega t + \theta_e)$$

$$i(t) = I_m \cos(\omega t + \theta_i) = \sqrt{2} |I| \cos(\omega t + \theta_i)$$

Constant  $\omega$


$$E = \frac{E_m}{\sqrt{2}} \angle \theta_e = |E| \angle \theta_e = |E| e^{j\theta_e}$$

$$I = \frac{I_m}{\sqrt{2}} \angle \theta_i = |I| \angle \theta_i = |I| e^{j\theta_i}$$

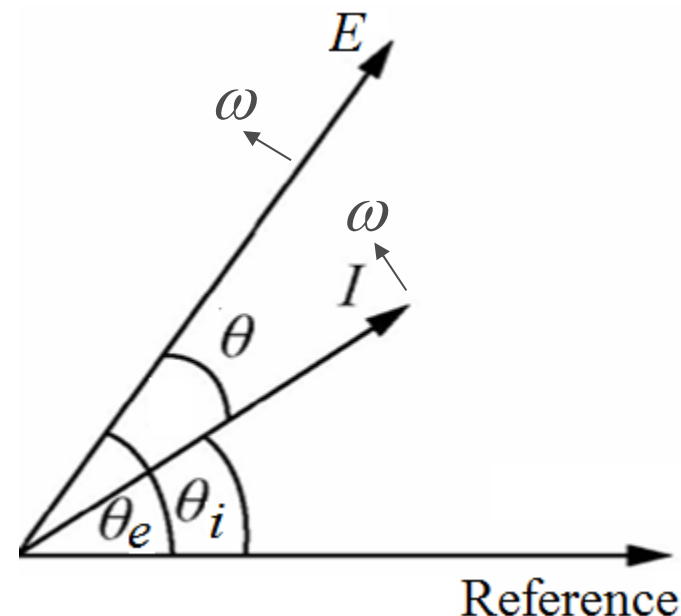

- $E$  and  $I$  are called RMS phasors of  $e(t)$  and  $i(t)$ ;  
 $E$  leads  $I$  by  $\theta = \theta_e - \theta_i$  or in other words,  $I$  leads  $E$  by  $2\pi - \theta$
- Phasor:
  - mapping a time-domain sinusoidal waveform (infinitely long in time) to a single complex number
  - carries the amplitude and phase angle information of a sinusoidal signal of a common frequency ( $\omega$ ) w.r.t. a chosen reference signal.

# Impedance

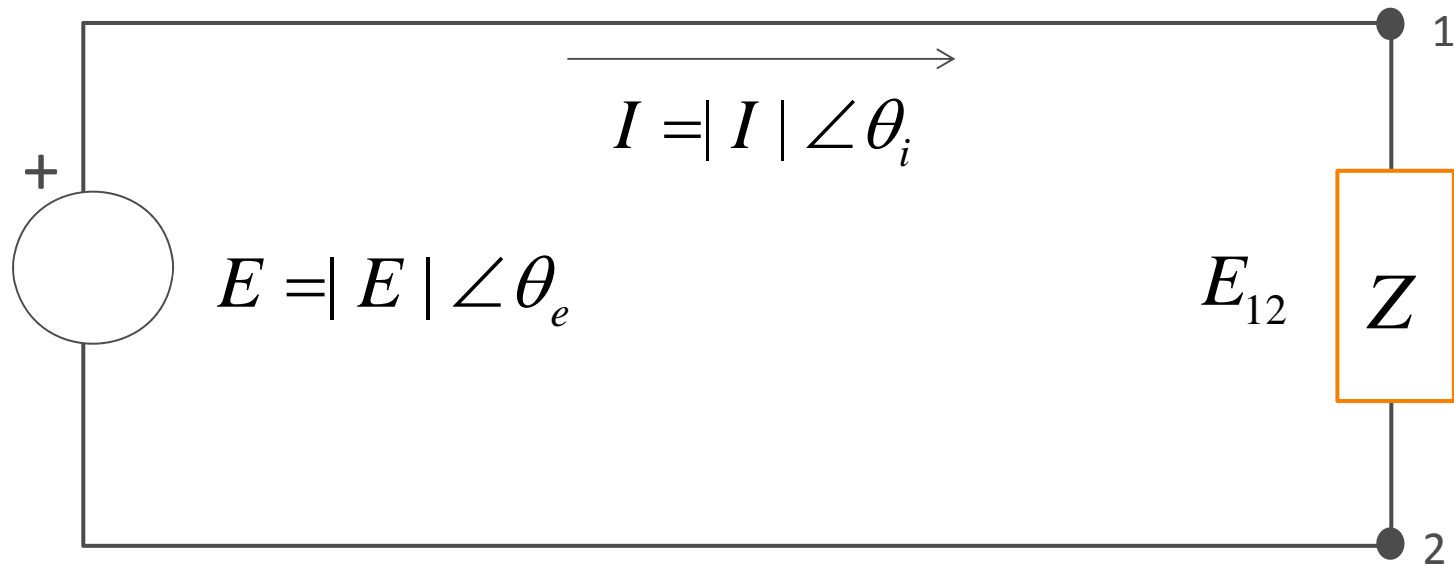

- Impedance is a complex number (in  $\Omega$ ) defined as

$$Z \stackrel{\text{def}}{=} \frac{E_{12}}{I} = \frac{E}{I} = \frac{|E| \angle \theta_e}{|I| \angle \theta_i} = |Z| \angle (\theta_e - \theta_i) = R + jX$$

$\theta_e - \theta_i \stackrel{\text{def}}{=} \theta$  (Impedance angle)

Impedance of branch 1-2 =  
 $\frac{\text{Voltage drop on 1-2}}{\text{Current flow into 1}}$

- Purely resistive:  $Z = |Z| = R$
- Purely inductive:  $Z = |Z| \angle 90^\circ = jX = jX_L = j\omega L$
- Purely capacitive:  $Z = |Z| \angle -90^\circ = jX = -jX_C = -j \frac{1}{\omega C}$

## Example 2-5

- Draw the phasor diagram of the voltage and current at a frequency of 60Hz. Calculate the time interval  $\Delta t$  between the positive peaks of  $E$  and  $I$

*Solution:*


$$\omega = 2\pi f = 377 \text{ (rad/s)} = 21600 \text{ (deg/s)}$$

$$|E| = 339/\sqrt{2} = 240 \text{ (V)}$$

$$|I| = 14.1/\sqrt{2} = 10 \text{ (A)}$$

Choose an arbitrary reference to draw phasors  $E$  and  $I$
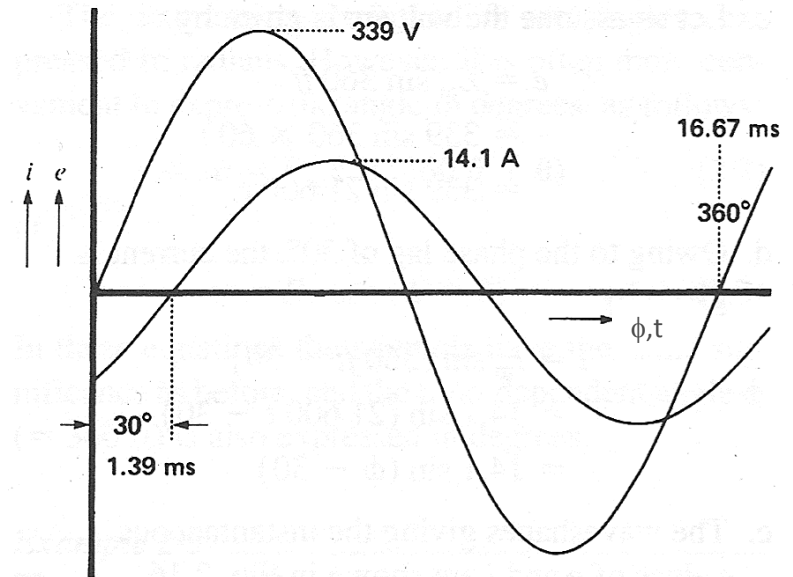
$$\Delta t = \theta/\omega = 30/21600 = 0.00139 \text{ (s)}$$



$$e(t) = 339 \cos(21600t - 90^\circ)$$

$$i(t) = 14.1 \cos(21600t - 120^\circ)$$

