
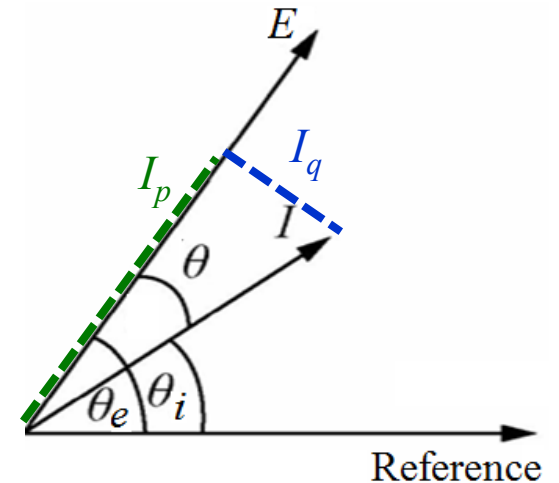


# Complex Power and Power Triangle


$$\begin{aligned}
 S &\stackrel{\text{def}}{=} P + jQ = |E||I|\cos\theta + j|E||I|\sin\theta = |E|I_p + j|E|I_q \\
 &= |E||I|\angle\theta = |S|\angle\theta = \sqrt{P^2 + Q^2}\angle\theta \\
 &= |E||I|\angle\theta_e - \theta_i = |E|\angle\theta_e |I|\angle-\theta_i = EI^*
 \end{aligned}$$

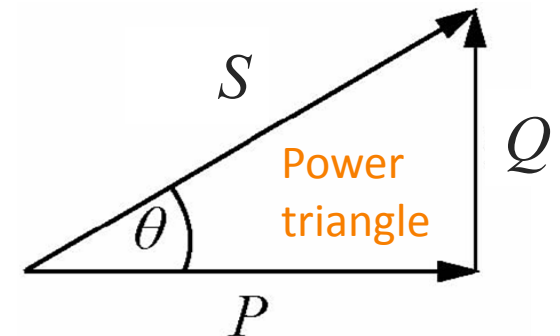

- $\theta = \tan^{-1}(Q/P)$ 
  - If  $\theta > 0$  ( $\theta_i < \theta_e$ , i.e. lagging PF), then  $Q > 0$ , which means **a reactive load** (inductive)
  - If  $\theta < 0$  ( $\theta_i > \theta_e$ , i.e. leading PF), then  $Q < 0$ , which means **a reactive source** (capacitive)
- $PF = \cos\theta = P/|S|$  (+/- sign of  $Q$  tells a lagging/leading PF)  
 $P = |S| \cdot \cos\theta = |S| \cdot PF$



- If the load impedance is  $Z = E/I$ , then  
 $S = ZII^* = Z|I|^2 = R|I|^2 + jX|I|^2 = P + jQ$   
 $P = R|I|^2$        $Q = X|I|^2$   
 $\theta$  is also called the load impedance angle

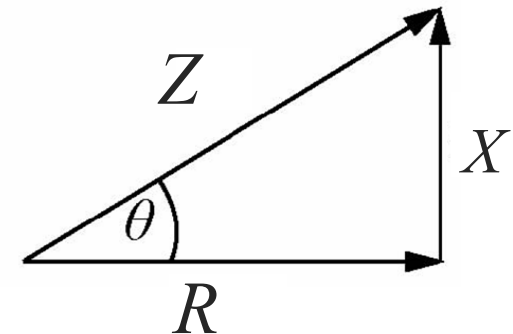

## Other Useful Formulas

$$S = EI^* = \frac{EE^*}{Z^*} = \frac{|E|^2}{Z^*}$$

$$= I^* Z = |I|^2 Z$$

$$Z = \frac{|E|^2}{S^*} = \frac{S}{|I|^2}$$

- If  $Z$  is purely resistive

$$P = \frac{|E|^2}{R}$$

- If  $Z$  is purely reactive

$$Q = \frac{|E|^2}{X} = \frac{|E|^2}{\omega L} \text{ or } \frac{|E|^2}{-1 / \omega C}$$

# Theorem of Conservation of Complex Power

- For a power network supplied by independent sources **all at the same frequency (all voltages and currents are assumed to be sinusoids)**, the sum of the complex power supplied by the independent sources equals the sum of the complex power received by all the other branches of the network

$$\Sigma(S_G \text{ of all actual sources}) = \Sigma(S_L \text{ of all the others})$$

- In other words, the total complex power supplied (received) by **all branches** is zero


$$\Sigma(S_G \text{ of all braches}) = 0 \text{ or } \Sigma(S_L \text{ of all braches}) = 0$$

- For a single source with elements in series or parallel, it is proved by Kirchhoff's voltage or current law (KVL/KCL)
- For a general case, it is proved by Tellegen's theorem.
- Application of the theorem: any part of the power network can be replaced by an equivalent independent source

- Two examples from A. Bergen and V. Vittal, Power System Analysis, Prentice Hall, 2000

### Example 2.4

For the circuit shown in Figure E2.4, find  $S_2$  in terms of  $S_1$ ,  $C$ , and  $V$ .

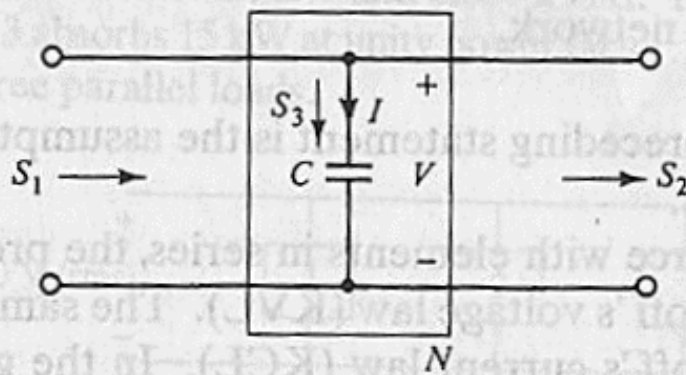

**Figure E2.4**

**Solution** Using the theorem of conservation of complex power, we have

$$S_1 - S_2 = S_3$$

where

$$S_3 = VI^* = VY^* V^* = -j\omega C|V|^2$$

Thus

$$S_2 = S_1 + j\omega C|V|^2$$


$$P_2 = P_1$$

$$Q_2 = Q_1 + \omega C|V|^2$$

We note that  $Q_2 > Q_1$ ; thus, it is reasonable and convenient to consider  $C$  as a source of reactive power!

**Example 2.5**

Consider the circuit shown in Figure E2.5. Assume that  $|V_2| = |V_1|$  and show that  $S_2 = -S_1^*$ .

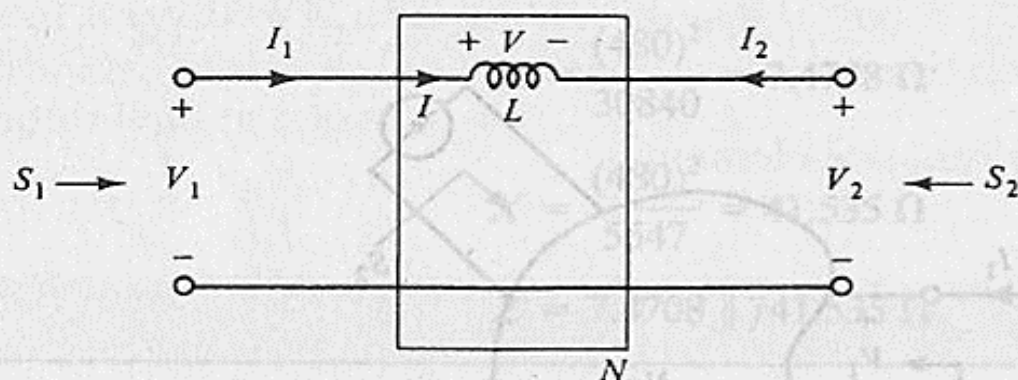**Figure E2.5**

**Solution** Using the theorem of complex power, the complex power into the inductor is

$$S_1 + S_2 = VI^* = j\omega L|I|^2$$

Thus

$$P_1 + P_2 = 0$$

$$Q_1 + Q_2 = \omega L|I|^2$$

Now using  $|V_2| = |V_1|$ , we find

$$\left. \begin{array}{l} S_1 = V_1 I^* \\ S_2 = -V_2 I^* \end{array} \right\} \Rightarrow |S_1| = |S_2| \Rightarrow P_1^2 + Q_1^2 = P_2^2 + Q_2^2$$

But since  $|P_2| = |P_1|$ , we get  $|Q_2| = |Q_1|$ . As a consequence,  $Q_1 = Q_2 = \frac{1}{2}\omega L|I|^2$ . We have finally

$$\left. \begin{array}{l} P_2 = -P_1 \\ Q_2 = Q_1 \end{array} \right\} \Rightarrow S_2 = -S_1^*$$

## Examples 7-2 & 7-3

## Example 2.2 on Saadat's book

$$V = 1200\angle 0^\circ \text{ V}, \quad Z_1 = 60 + j0\Omega,$$

$$Z_2 = 6 + j12\Omega, \quad Z_3 = 30 - j30\Omega$$

Find the power absorbed by each load and the total complex power

$$I_1 = \frac{V}{Z_1} = \frac{1200\angle 0^\circ}{60 + j0} = \frac{1200}{60} = 20 + j0 \text{ A}$$

$$I_2 = \frac{V}{Z_2} = \frac{1200\angle 0^\circ}{6 + j12} = \frac{200}{1 + j2} = \frac{200(1 - j2)}{5} = 40 - j80 \text{ A}$$



$$I_3 = \frac{V}{Z_3} = \frac{1200\angle 0^\circ}{30 - j30} = \frac{40}{1 - j} = \frac{40(1 + j)}{2} = 20 + j20 \text{ A}$$

$$S_1 = VI_1^* = 1200\angle 0^\circ(20 - j0) = 24,000 \text{ W} + j0 \text{ var}$$

$$S_2 = VI_2^* = 1200\angle 0^\circ(40 + j80) = 48,000 \text{ W} + j96,000 \text{ var}$$

$$S_3 = VI_3^* = 1200\angle 0^\circ(20 - j20) = 24,000 \text{ W} - j24,000 \text{ var}$$
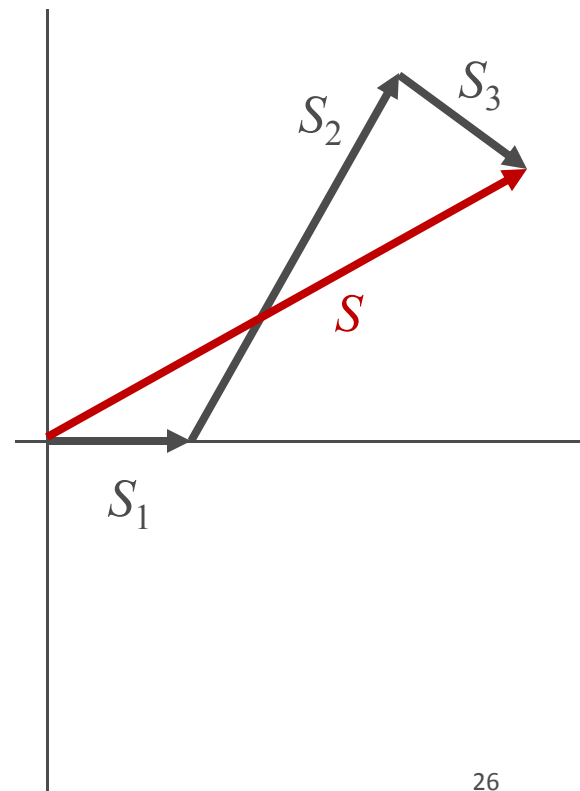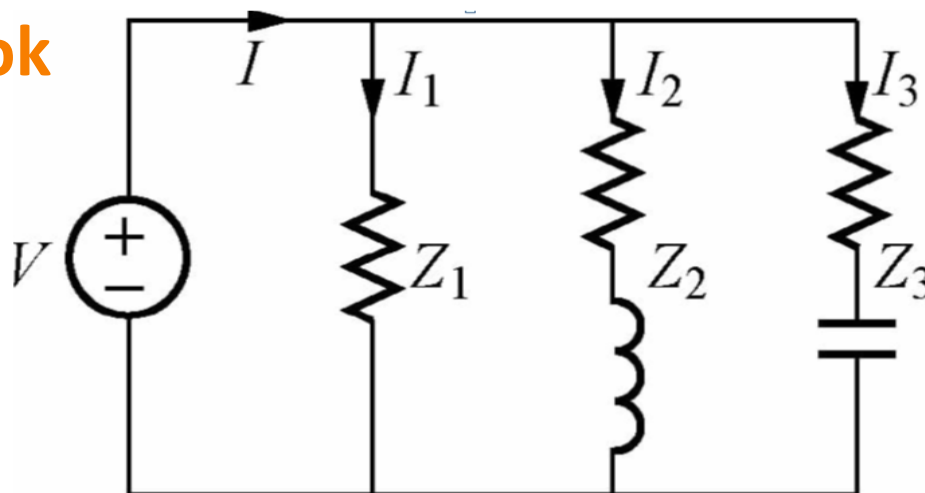
$$S = S_1 + S_2 + S_3 = 96,000 \text{ W} + j72,000 \text{ var}$$



- Other approaches

$$I = I_1 + I_2 + I_3 = (20 + j0) + (40 - j80) + (20 + j20) = 80 - j60 = 100 \angle -36.87^\circ \text{ A}$$

$$S = VI^* = (1200 \angle 0^\circ)(100 \angle 36.87^\circ) = 120,000 \angle 36.87^\circ \text{ VA} = 96,000 \text{ W} + j72,000 \text{ var}$$

or

$$Z_{//} = Z_1 // Z_2 // Z_3 = \frac{1}{1/Z_1 + 1/Z_2 + 1/Z_3} = 9.6 + j7.2 \Omega$$

$$S = \frac{|V|^2}{Z_{//}^*} = \frac{(1200)^2}{9.6 - j7.2} = 96,000 \text{ W} + j72,000 \text{ var}$$

$$S_1 = \frac{|V|^2}{Z_1^*} = \frac{(1200)^2}{60} = 24,000 \text{ W} + j0 \text{ var}$$

$$S_2 = \frac{|V|^2}{Z_2^*} = \frac{(1200)^2}{6 - j12} = 48,000 \text{ W} + j96,000 \text{ var}$$

$$S_3 = \frac{|V|^2}{Z_3^*} = \frac{(1200)^2}{30 + j30} = 24,000 \text{ W} - j24,000 \text{ var}$$