
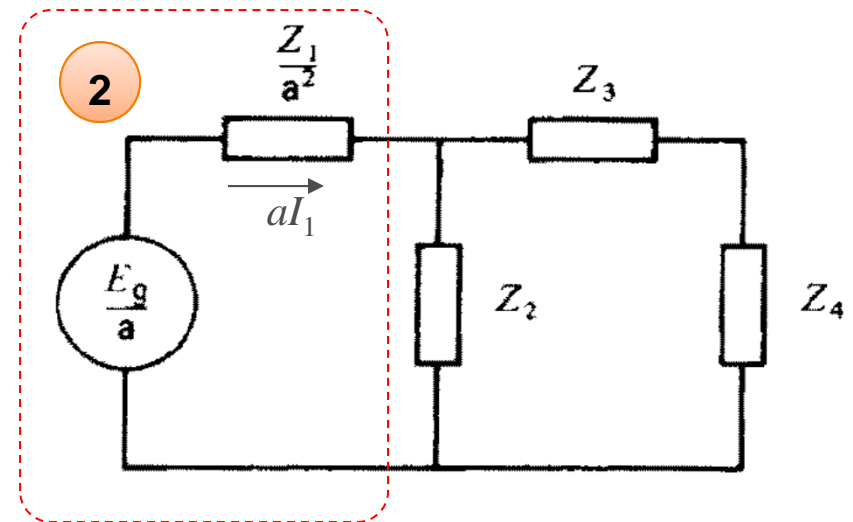
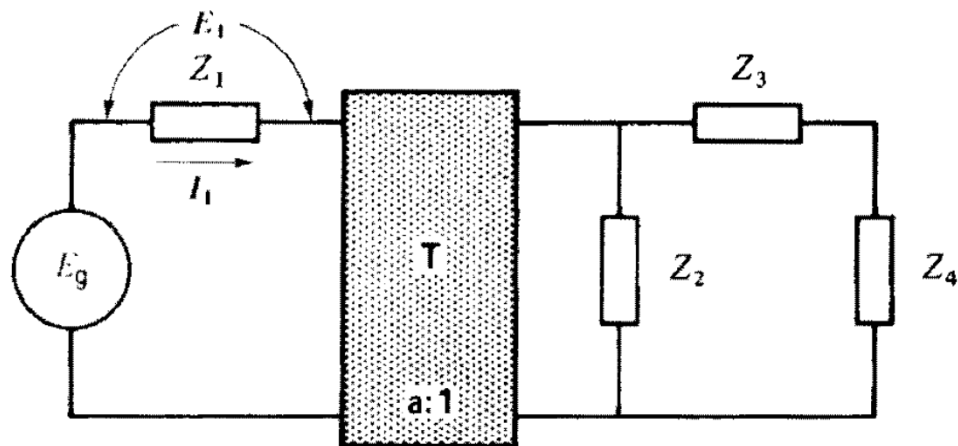


Shifting Impedances (P→S)

$$Z_p \longrightarrow \boxed{1/a^2} \longrightarrow Z_s$$


$$E_p \longrightarrow \boxed{1/a} \longrightarrow E_s$$

$$I_p \longrightarrow \boxed{a} \longrightarrow I_s$$

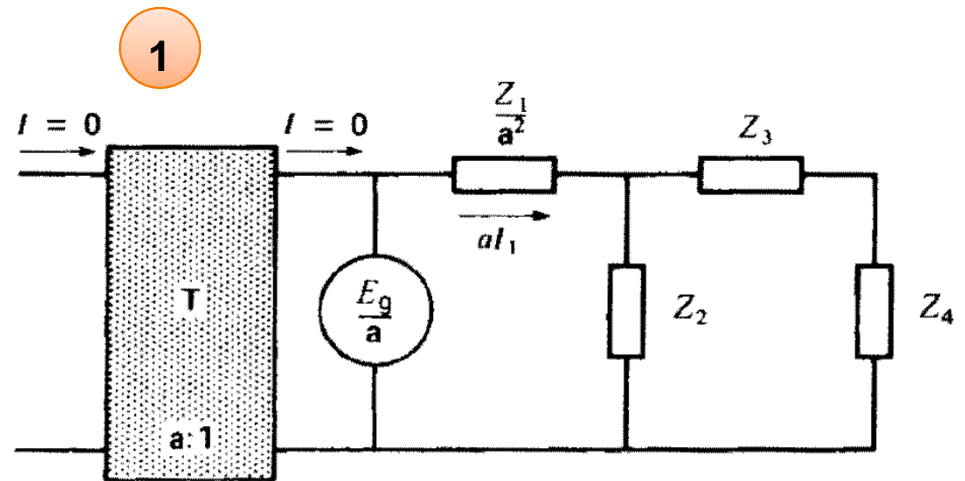

Examples 9-4&9-5

Considering an imperfect core

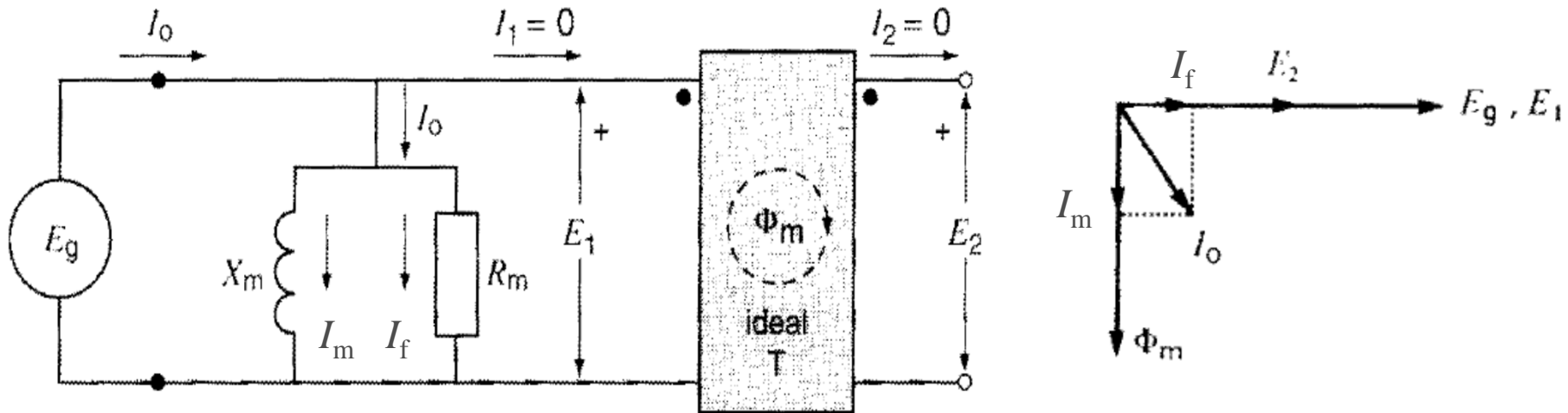

Under no-loading conditions: $I_1 = I_2 = 0$

- $P_m + jQ_m$ and I_o are the complex power and current outputs of source E_g . P_m is the iron loss (why?)
- R_m is a resistance causing the iron loss P_m and resulting heat

$$R_m = |E_1|^2 / P_m \quad I_f = E_1 / R_m$$

- X_m is the magnetizing reactance that measures permeability of the core. A smaller X_m means lower permeability and needs a higher magnetizing current I_m (i.e. bigger reactive power $Q_m = |E_1|^2 / X_m$) to set up mutual flux Φ_m

$$X_m = |E_1|^2 / Q_m \quad I_m = E_1 / jX_m$$

Considering loose coupling and resistances of windings

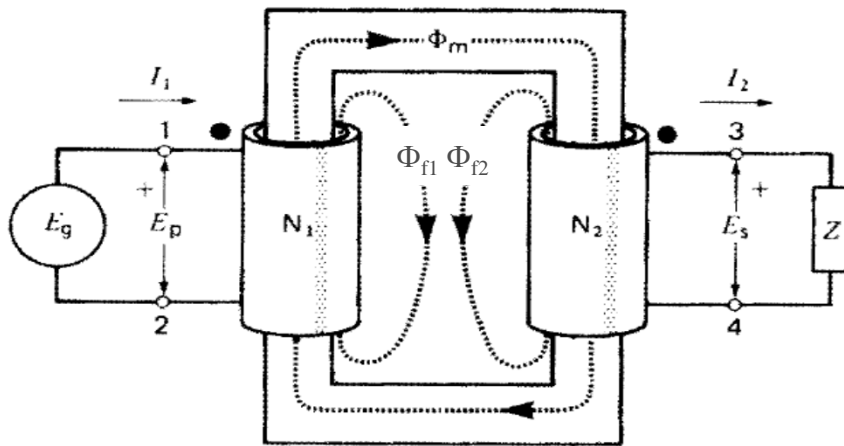


Figure 10.5
A transformer possesses two leakage fluxes and a mutual flux.

$$E_1 = 4.44fN_1\Phi_m \quad E_2 = 4.44fN_2\Phi_m$$

$$E_{f1} = 4.44fN_1\Phi_{f1} \quad E_{f2} = 4.44fN_2\Phi_{f2}$$

$$\text{KVL: } E_1 + E_{f1} = E_p = E_g \quad E_2 - E_{f2} = E_s$$

- Treat E_{f1} and E_{f2} as voltage drops on two winding impedances (including winding resistance and leakage reactance)

$$E_{f1} = (R_1 + jX_{f1}) I_1 \quad E_{f2} = (R_2 + jX_{f2}) I_2$$

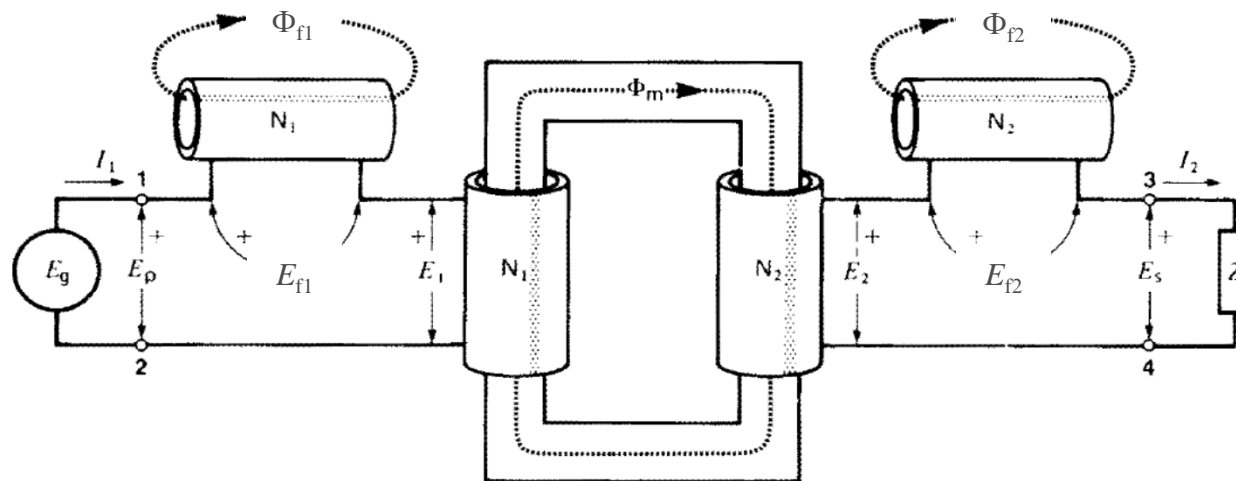


Figure 10.6
Separating the various induced voltages due to the mutual flux and the leakage fluxes.

Equivalent Circuit of a Practical Transformer

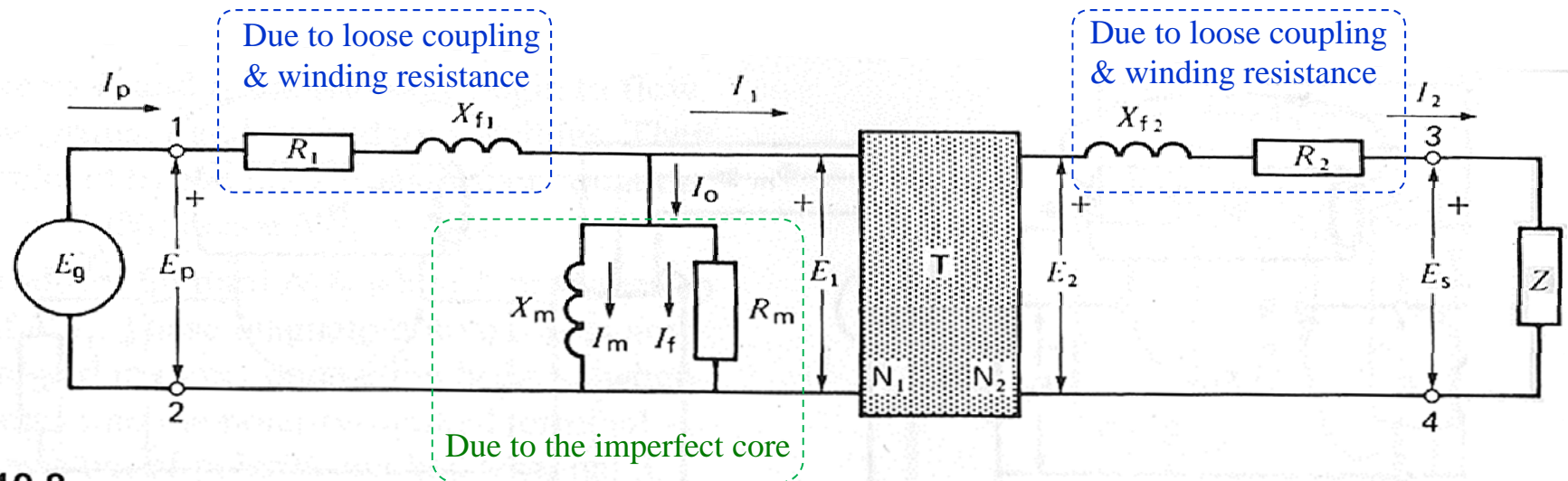


Figure 10.8

Complete equivalent circuit of a practical transformer. The shaded box T is an ideal transformer.

TABLE 10A ACTUAL TRANSFORMER VALUES

S_n	kVA	1	10	100	1000	400000
E_{np}	V	2400	2400	12470	69000	13800
E_{ns}	V	460	347	600	6900	424000
I_{np}	A	0.417	4.17	8.02	14.5	29000
I_{ns}	A	2.17	28.8	167	145	943
R_1	Ω	58.0	5.16	11.6	27.2	0.0003
R_2	Ω	1.9	0.095	0.024	0.25	0.354
X_{f1}	Ω	32	4.3	39	151	0.028
X_{f2}	Ω	1.16	0.09	0.09	1.5	27
X_m	Ω	200000	29000	150000	505000	460
R_m	Ω	400000	51000	220000	432000	317
I_o	A	0.0134	0.0952	0.101	0.210	52.9

No-load conditions

- $I_1 = I_2 = 0$
- Ignore R_1 , X_{f1} , R_2 and X_{f2}
- $E_p \approx E_1 = aE_2 = aE_s$

10%-100% load conditions

- $I_p \gg I_o$,
- Ignore I_o

Simplified Equivalent Circuits

- No-load conditions
($I_1=I_2=0$)
 - Ignoring winding leakage fluxes and losses

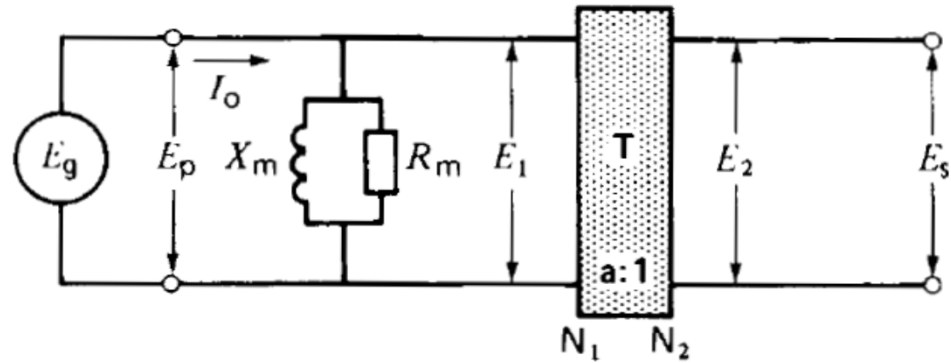


Figure 10.21
Simplified circuit at no-load.

- 10%-100% load conditions
(Ignoring I_o)
 - Ignoring core reluctance and losses


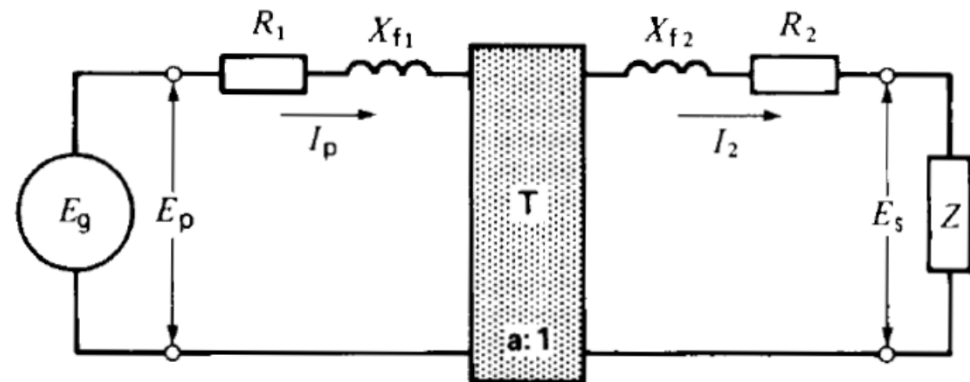
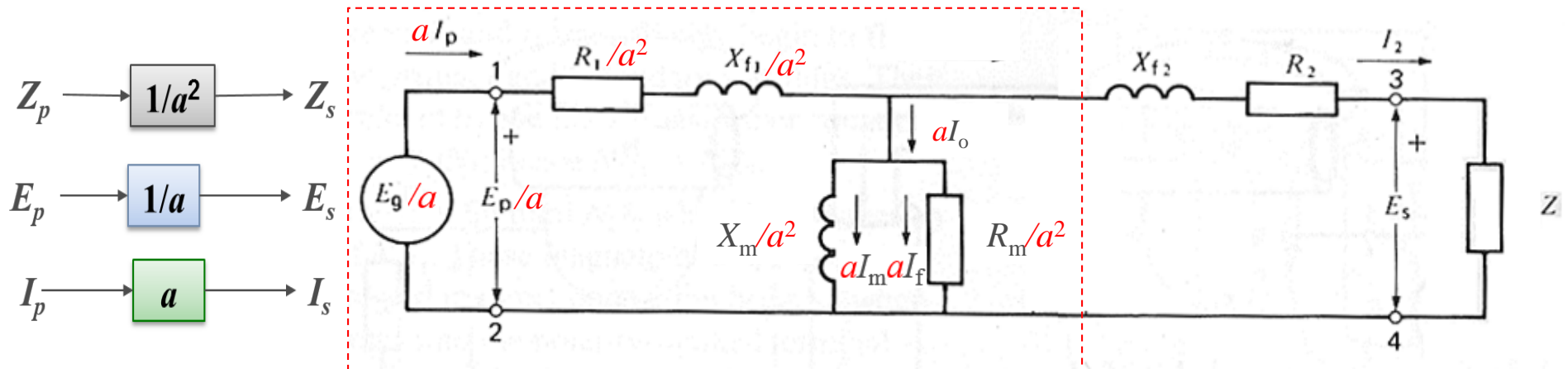
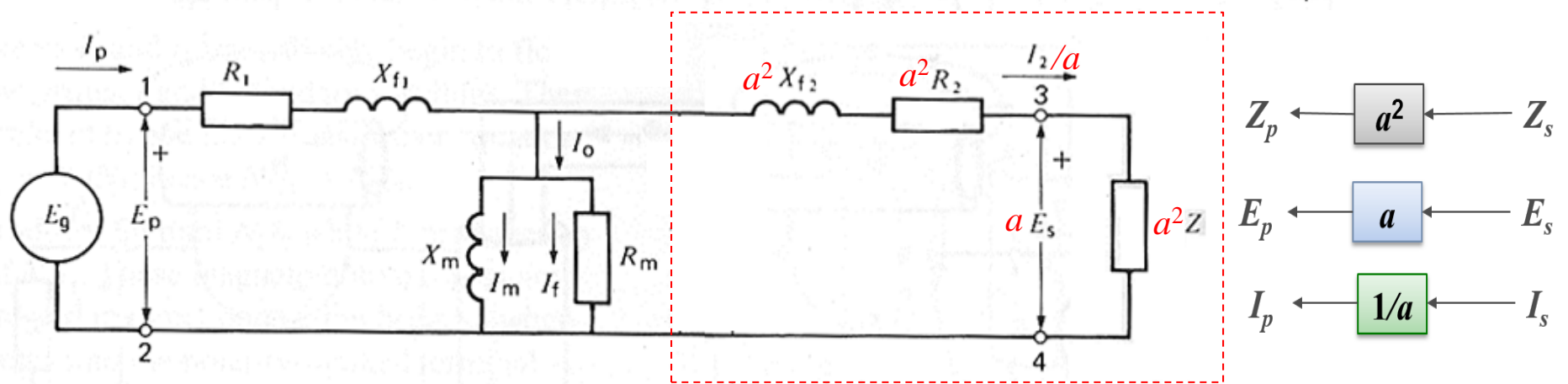


Figure 10.22
Simplified equivalent circuit of a transformer at full-load.

Equivalent Circuits Referred to One Side

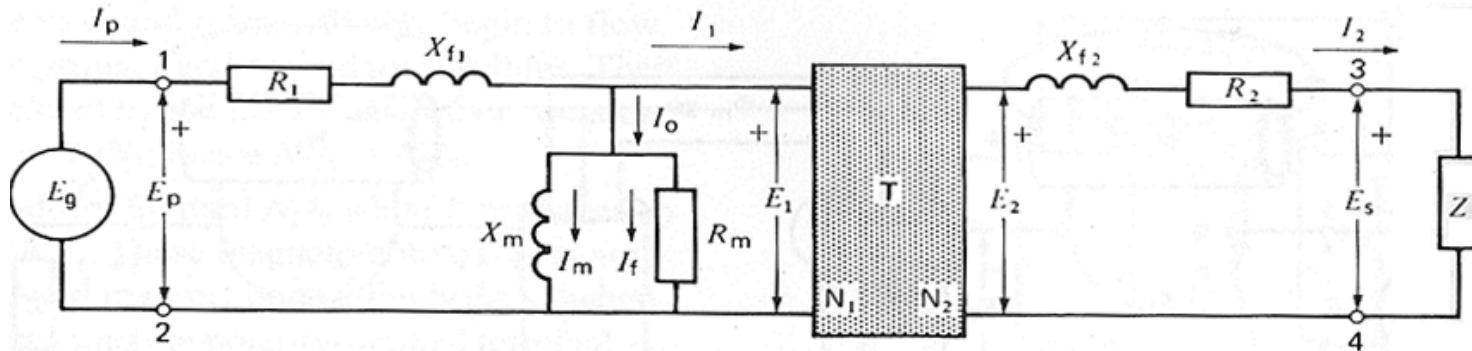

Simplified Equivalent Circuits Referred to One Side

- Under load conditions


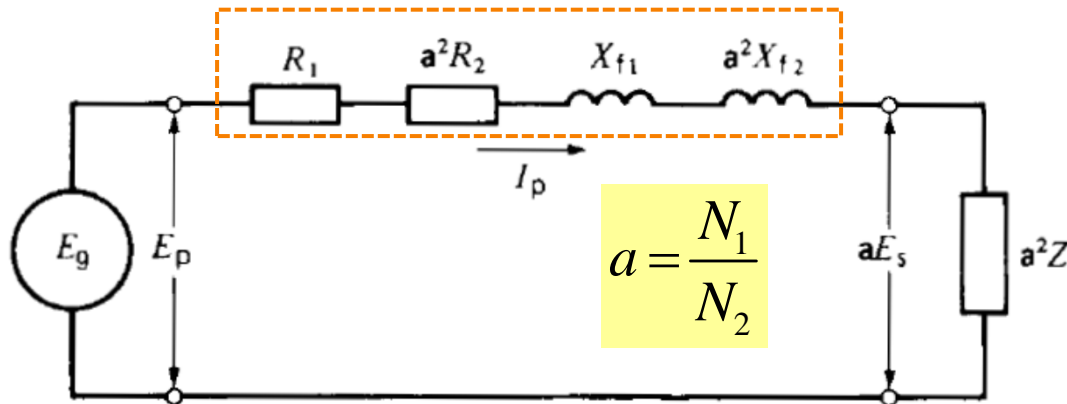


Figure 10.23

Equivalent circuit with impedances shifted to the primary side.
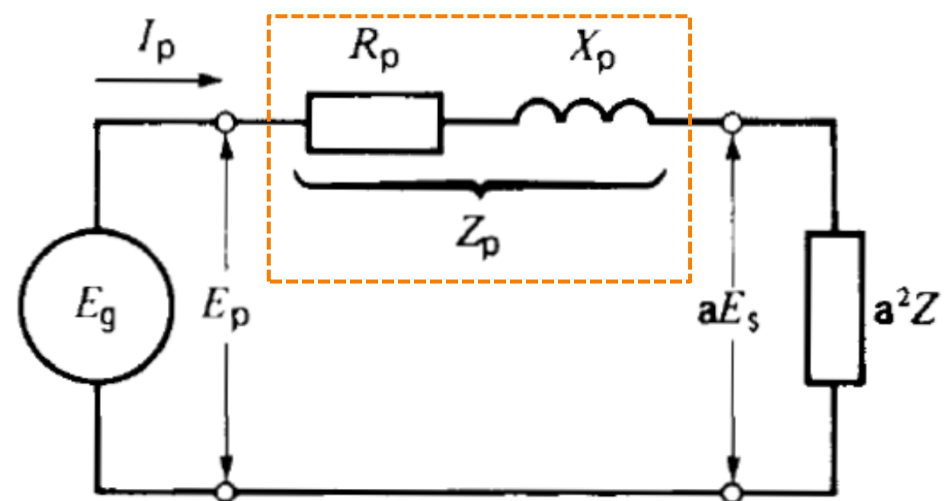
$$\begin{aligned} Z_p &= R_p + j X_p \\ &= R_1 + a^2 R_2 + j(X_{f1} + a^2 X_{f2}) \end{aligned}$$



Voltage Regulation

- With the primary voltage held constant at its rated value, the voltage regulation is % change of the secondary voltage from no-load to full load (rated)

$$\text{Voltage Regulation} = \frac{|E_{NL}| - |E_{FL}|}{|E_{FL}|} \times 100$$

E_{NL} : secondary voltage at no-load

E_{FL} : secondary voltage at full-load

- The voltage regulation depends on the power factor of the load on the secondary side
 - If the load is capacitive, the full-load voltage may exceed the no-load voltage, in which case the voltage regulation becomes negative

Measuring Transformer Impedances

- **Open-circuit (no-load) test**

- Neglect R_1 , X_{f1} , R_2 , X_{f2}
- Measure P_m (core loss), $|E_p|$, $|I_o|$ and $|E_s|$

$$R_m = \frac{|E_p|^2}{P_m} \quad |I_f| = \frac{|E_p|}{R_m}$$

$$|I_m| = \sqrt{|I_o|^2 - |I_f|^2}$$

$$X_m = \frac{|E_p|}{|I_m|}$$

$$a = \frac{N_1}{N_2} = \frac{|E_p|}{|E_s|}$$

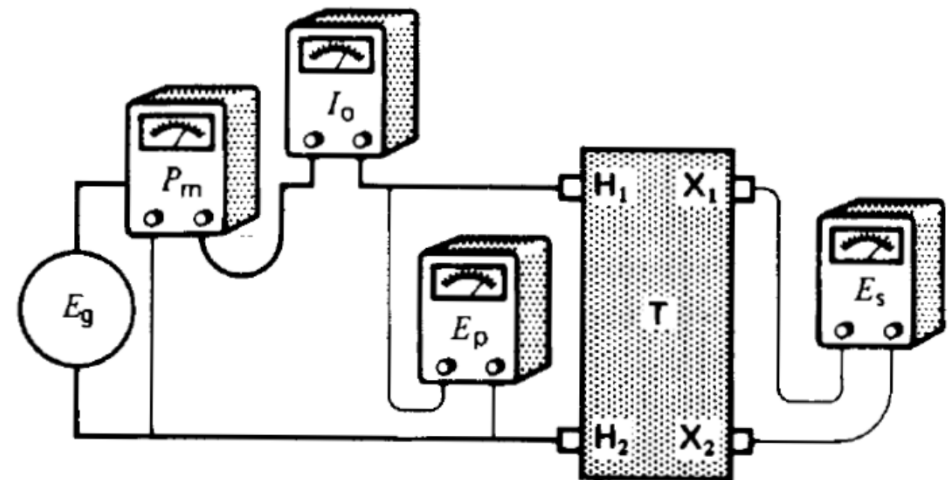
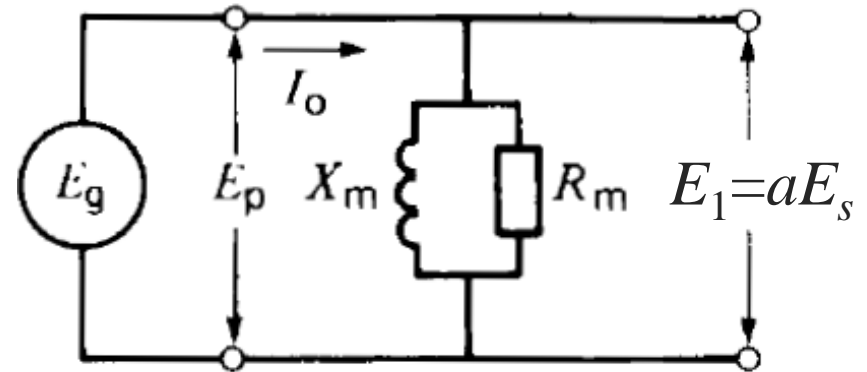


Figure 10.27

Open-circuit test and determination of R_m , X_m , and turns ratio.

• Short-circuit test

- Apply a low voltage E_{sc} to the primary side to create I_{sc} less than the nominal value to prevent overheating and rapid change in winding resistance
- Neglect R_m and X_m due to low core flux

$$|Z_p| = \frac{|E_{sc}|}{|I_{sc}|}$$

$$R_p = \frac{P_{sc}}{|I_{sc}|^2}$$

$$X_p = \sqrt{|Z_p|^2 - R_p^2}$$

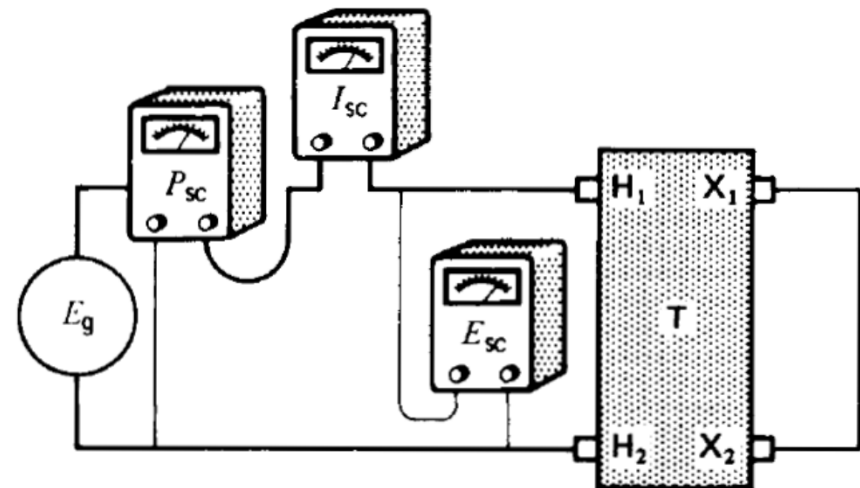
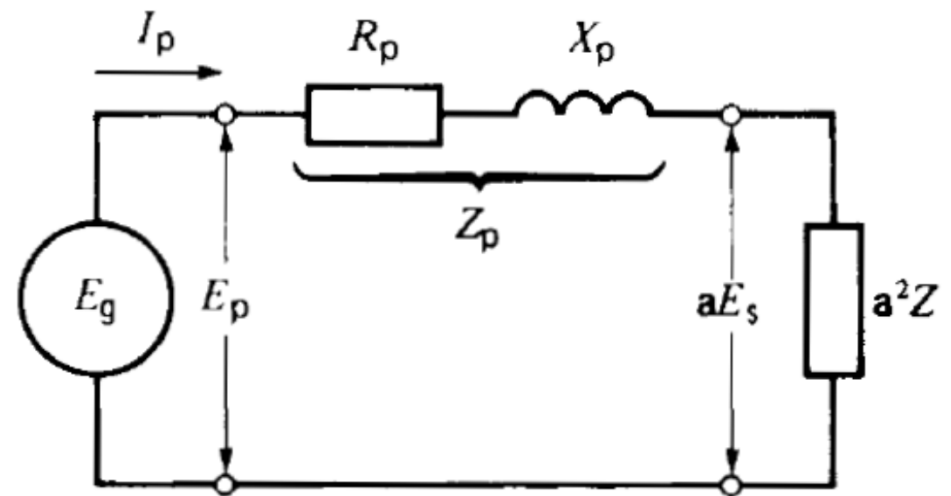


Figure 10.28

Short-circuit test to determine leakage reactance and winding resistance.

Construction of a power transformer

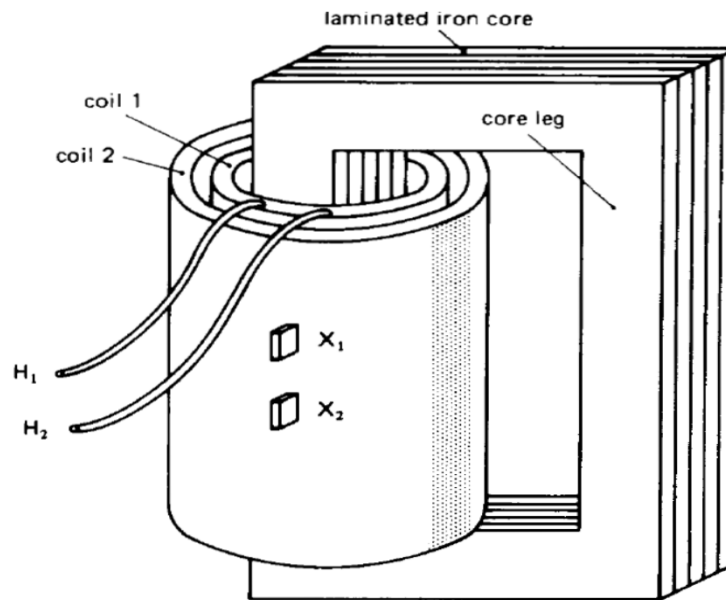



Figure 10.9a
Construction of a simple transformer.



- **Core:** made of iron for high permeability; laminated and high resistive to reduce iron losses
- **Windings:** the primary and secondary coils are wound closely on top of each other with careful insulation for tight coupling; the HV winding has more turns but uses a smaller size of conductor, so copper/aluminum of two windings are about the same

Standard terminal markings and polarity tests

additive polarity

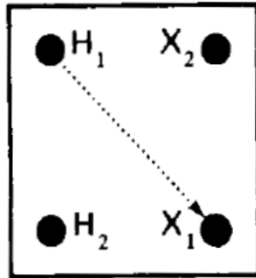

subtractive polarity

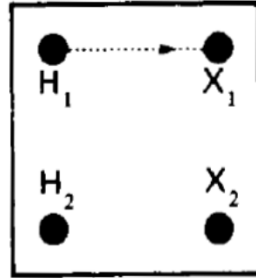


Figure 10.10

Additive and subtractive polarity depend upon the location of the H_1 - X_1 terminals.

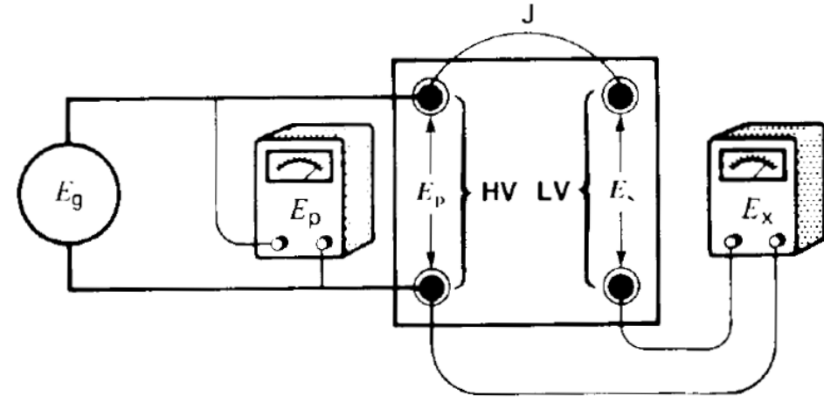


Figure 10.11

Determining the polarity of a transformer using an ac source.

- High-Voltage winding (H_1 & H_2) and Low-Voltage winding (X_1 & X_2)

$$E_{H1,H2}/E_{X1,X2} = E_H/E_X = N_H/N_X$$

- Polarity test:

1. Connect HV winding to a low voltage source E_g
2. Connect a jumper J between any two adjacent HV and LV terminals
3. Connect two voltmeters to as shown in Figure 10.11
4. The polarity is additive if $|E_x| > |E_p|$ or, otherwise, is subtractive.

The Per-Unit System

- Quantity in **Per-Unit** = **Actual** quantity / **Base or nominal** value of quantity
- Why per-unit notations?

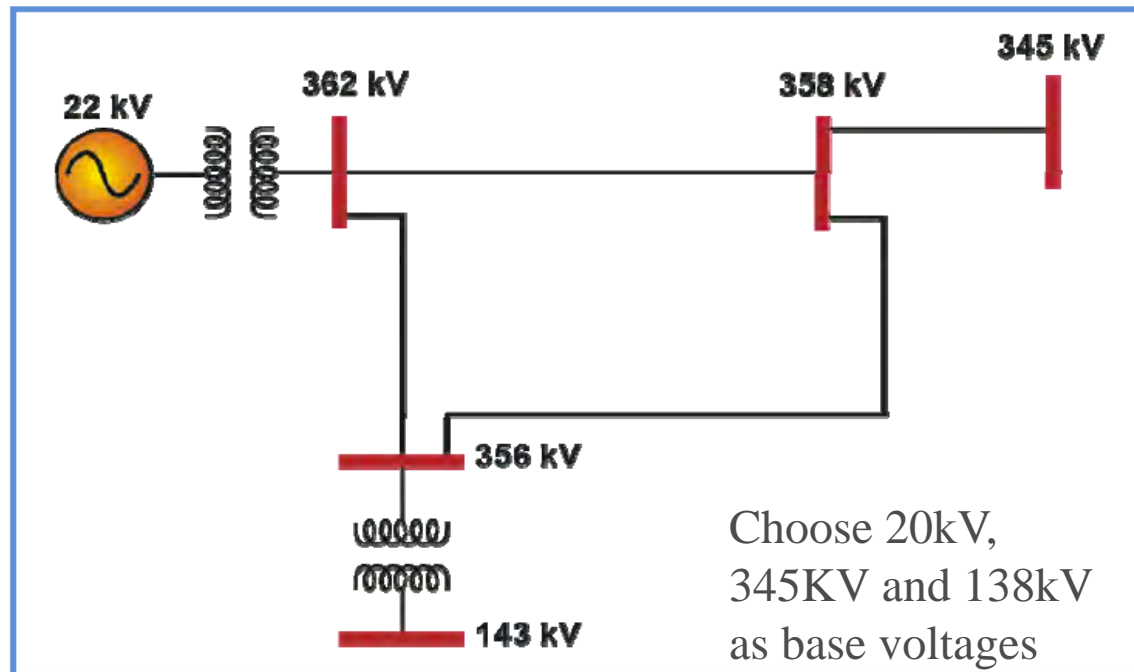


Figure 2-6. Example of the Usage of the Per-Unit System

- Neglecting different voltage levels of transformers, lines and generators
- Powers, voltages, currents and impedances are expressed as decimal fractions of respective base quantities

- Four base quantities are required to completely define a per-unit system

$$S_{pu} = \frac{S}{S_n} \quad E_{pu} = \frac{E}{E_n} \quad I_{pu} = \frac{I}{I_n} \quad Z_{pu} = \frac{Z}{Z_n}$$

- We need to select two independent base quantities of the four and calculate the other two, e.g. selecting S_n and E_n

$$I_n = \frac{S_n}{E_n} \quad Z_n = \frac{E_n}{I_n} = \frac{(E_n)^2}{S_n}$$

- For a transformer:

- Usually, S_n , E_{pn} , E_{sn} and the total impedance Z_p (in p.u. or %) referred to the primary side are given.

$$I_{np} = \frac{S_n}{E_{np}} \quad I_{ns} = \frac{S_n}{E_{ns}} \quad a = \frac{N_p}{N_s} = \frac{E_{np}}{E_{ns}}$$

$$Z_{np} = \frac{E_{np}}{I_{np}} = \frac{(E_{np})^2}{S_n} \quad (\Omega) \quad Z_{ns} = \frac{E_{ns}}{I_{ns}} = \frac{(E_{ns})^2}{S_n} \quad (\Omega)$$

$$Z_p(\Omega) = Z_p(\text{p.u.}) \times Z_{np}$$

Examples 10-5, 10-6, 10-7, 10-8 & 10-10