### ECE 325 – Electric Energy System Components 5- Transmission Lines

Instructor: Kai Sun Fall 2016



# Content

(Materials are from Chapter 25)

- Overview of power lines
- Equivalent circuit of a line
- Voltage regulation and power transmission of transmission lines

#### **Overview**

- Types of transmission lines
  - Overhead lines
  - Underground Cables (less than 1%)
- Properties
  - Series Resistance (stranding and skin effect)
  - Series Inductance (magnetic & electric fields; flux linkages within the conductor cross section and external flux linkages)
  - Shunt Capacitance (magnetic & electric fields; charge and discharge due to potential difference between conductors)
  - Shunt Conductance (due to leakage currents along insulators or corona discharge caused by ionization of air)
- Line-to-line voltage levels
  - 69kV, 115kV, 138kV and 161kV (sub-transmission)
  - 230kV, 345kV, and 500kV (EHV)
  - 765kV (UHV)

Corona discharge on insulator string of a 500 kV line (source: wikipedia.org)



#### **Overhead Transmission Lines**

Figure 2-83. Transmission Line Structures

Shield wires (ground wires) are ground conductors used to protect the transmission lines from lightning strikes



(Source: wikipedia.org and EPRI dynamic tutorial)

### **Overhead Transmission Lines**

- Many strands to reduce series resistance
- Materials
  - AAC (All Aluminum Conductor),
  - AAAC (All Aluminum Alloy Conductor)
  - ACSR (Aluminum Conductor Steel Reinforced)
  - ACAR (Aluminum Conductor Alloy Reinforced)
  - ACCC (Aluminum Conductor Composite Core)
- Why not copper?
  - Relative lower costs and higher strength-toweight ratios than copper
- Bundled conductors to reduce series reactance
  - Preferred for high voltages, e.g. 2-conductor bundles for 230kV, 3-4 for 345-500kV, and 6 for 765kV



ACSR (7 steel and 24 aluminum strands)



24/7 ACSR and modern ACCC conductors



A bundle of 4 conductor

### **Equivalent circuit of a transmission line**









- $R=r \times N$ ,  $X_L = x_L \times N$ ,  $X_C = x_C/N$ : With the increase of N (i.e. the length of the line), R and  $X_L$ increase but  $X_C$  decreases
- For HV lines, *R*<<*X*<sub>L</sub>



## **TABLE 25C**TYPICAL IMPEDANCE VALUES PERKILOMETER FOR 3-PHASE, 60 HZ LINES

Type of line	$x_{L}[\Omega]$	$x_{\rm C} [\Omega]$
aerial line	0.5	300 000
underground cable	0.1	3 000

#### Simplifying the equivalent circuit



$$R = r \times N$$
,  $X_L = x_L \times N$ ,  $X_C = x_C/N$   
HV lines:  $R << X_L$ 

Figure 25.17

Active and reactive powers of a transmission line.



Figure 25.18 Equivalent circuit of a short LV line.



Figure 25.19 Equivalent circuit of a long HV line.

#### Example 25-3



#### **Consider one phase:**

P=300/3=100MW

 $|E|=230/\sqrt{3}=133$ kV

|I|=100MW/133kV=750A

 $P_{\rm J} = |I|^2 R = 1.83 \,\rm{MW} = 0.0183 P$ 

 $Q_{\rm L} = |I|^2 X_{\rm L} = 14.1 \,{\rm Mvar}$ 

 $Q_{\rm C} = |E|^2 / X_{\rm C} = 3 \,\mathrm{Mvar} \ll Q_{\rm L}$ 

a. Find the equivalent circuit b. Calculate  $P_{\rm J}$  (loss),  $Q_{\rm L}$  and  $Q_{\rm C}$ 



Figure 25.16 Equivalent circuit of a 3-phase line.

