## Example 16-4

A 36 MVA, 20.8 kV, 3-phase alternator has  $X_{\rm S}$ =9 $\Omega$  and a nominal current of 1 kA. The no-load saturation curve gives the relationship between  $E_{\rm o}$  and exciting current  $I_{\rm X}$ . If the excitation is adjusted so that terminal voltage E remains fixed at 20.8 kV, calculate the exciting current  $I_{\rm X}$  required and draw the phasor diagram for conditions a-c:

### a. No-load

 $E_o = E = 20.8/1.73 = 12 \text{ kV}$   $I_X = 100 \text{ A}$ 

b. Resistive load of 36 MW

$$P=36/3=12 \text{ MW}$$
  

$$Z=|E|^{2}/S^{*}=E^{2}/P=12\text{kV}^{2}/12\text{MW}=12 \Omega$$
  

$$I=E/Z=12000/12=1000\text{A}$$
  

$$E_{o}=E+jX_{s}I=12000+j9\times1000=15\text{kV}\angle 36.9^{\circ}$$
  

$$I_{X}=200 \text{ A}$$

c. Capacitive load of 12 Mvar

$$Q=-12/3=-4$$
Mvar  
 $Z=|E|^2/S^*=E^2/(jQ)^*=-j12kV^2/4$ Mvar=-j36 Ω  
 $I=E/Z=12000/(-j36)=j333$ A  
 $E_0=E+jX_sI=12000+j9\times j333=9kV\angle 0^\circ$   
 $I_X=70$  A





# Synchronization of a generator

- Synchronous generators of a power system under normal operations are all synchronized
  - They all have the same frequency
- To connect a generator to a system (or a bigger generator)
  - 1. Adjust the **speed regulator** of the generator turbine so that the generator frequency is close to the system frequency
  - 2. Adjust the excitation of the generator so that generator voltage  $E_0$  is equal to the system voltage E
  - 3. Observe the phase angle difference between  $E_0$  and E by means a synchroscope
  - 4. Connect the generator at the moment the point crosses the 0 marker



### Synchronous generator on an infinite bus

- An infinite bus is a system so powerful that it has constant voltage *E* and frequency, e.g. 60Hz, no matter what apparatus is connected to it.
- For a generator on an infinite bus, only the exciting current  $I_X$  and the mechanical torque  $T_m$  exerted by the turbine vary
- If  $E_0 = E$  (having identical magnitudes and phases), then I=0, the generator delivers no power and it is said to **float** on the line
- If  $E_o \neq E$ ,  $E_x = E_o E$ ,  $I = (E_o E)/(jX_s)$ 
  - Complex power from  $E_{o}$

 $S_{o} = E_{o}I^{*} = E_{o}(E_{o} - E)^{*}/X_{s}^{*} = P_{o} + jQ_{o}$ 

- Complex power into the infinite bus  $S=EI^*=E(E_0-E)^*/X_s^*=P+jQ$ 

$$P_o = P = \frac{|E_o| \cdot |E|}{X_S} \sin \delta$$

$$Q_o = \frac{|E_o|^2}{X_s} - \frac{|E_o||E|}{X_s} \cos \delta$$
$$Q = \frac{|E_o||E|}{X_s} \cos \delta - \frac{|E|^2}{X_s}$$



# Effect of varying the exciting current



#### Figure 16.26b

Over-excited generator on an infinite bus.



#### Figure 16.26c

Under-excited generator on an infinite bus.

When  $E_0$  and E are in phase

- There is always  $P_0 = P = 0$
- If  $|E_o| > |E|$ , the generator is over-excited and supplies reactive power to the infinite bus (it looks like an inductor)
- If  $|E_o| < |E|$ , the generator is under-excited and absorbs reactive power from the infinite bus (it looks like a capacitor)

#### Effect of varying the mechanical torque $E_{\mathbf{o}}$ - E 5Ω E, 4 k V $T_m$ turbine / = 800 A +12 kV infinite bus $E_{o}$ E $T_e$ δ = **19.2°** 90 E 12 kV

- Starting from  $E_0 = E$  (the generator floats on the line) and keeping  $|E_0| = |E|$ 
  - Open the steam value of the turbine to increase the mechanical torque  $T_m$
  - The rotor will accelerate, and phasor  $E_0$  will lead phasor E by  $\delta > 0$
  - With the increase of  $\delta$ , power output of the generator  $P=|E|^2\sin\delta/X_s$  will increase, which exerts an increasing electric torque  $T_e=9.55P/n$
  - Once  $T_m = T_e$ , the rotor will stop accelerating,  $\delta$  will become constant and the generator will again run at synchronous speed
  - What is the direction of Q?
  - What is the angle of *I*?

$$Q = -Q_o = \frac{|E|^2}{X_s} (\cos \delta - 1)$$

(coming from both  $E_0$  and E)

(leading E and lagging  $E_o$  by the same angle)

## **Control of active power**



Figure 11.1 Generator supplying isolated load

- A synchronous generator has a governor to control its speed
- A sensitive governor may detect a speed change of 0.01% to modify the valve/gate opening of the turbine so as to maintain an almost constant speed
- A large power system has a computer program called Automatic Generation Control (AGC) to control the active power and frequency of the entire system
- Each synchronous generator has over- and under-speed protections responding to abnormal frequency

### How much frequency deviates in a power grid

- Under normal conditions, frequency in a large Interconnected power system (e.g. the Eastern Interconnection) varies approximately ±0.03Hz from the scheduled value
- Under abnormal events, e.g. loss of a large generator unit, frequency experiences larger deviations.





### **Transient reactance**

- For a sudden load current change such as a short-circuit, X<sub>s</sub> is replaced by a dynamic reactance X' whose value varies with time
  - X' drops to a much lower value X'<sub>d</sub> (called transient reactance, e.g. at  $0.15X_S$ )
  - The initial short-circuit current is much higher than the rated current

 $I_{SC} = E_{o} / X'_{d} >> E_{o} / X_{S}$ 

- After a time interval T (typically, <10s), X' basically goes back to  $X_S$
- A short-circuit must be interrupted in 3-6 cycles by circuit breakers
- Learn Example 16-8



### Figure 16.30

Variation of generator reactance following a shortcircuit.