
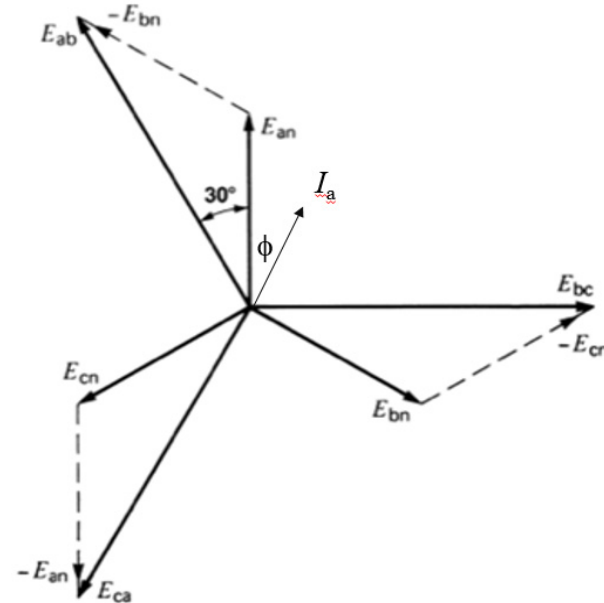


ECE 325, Fall 2016, Test 1

Problem 1 (35 points, 5 points each): Circle ALL correct statements (reasons are NOT required)



- For long distance power transmission, HVAC is always a more economical option than HVDC.
(At present, the cross-over point for HVDC to be competitive is around 500km for overhead lines or 50km for underground/submarine cables.)
- Natural gas is the 2nd largest energy resource of electricity generation for the overall US power grids.
- Both gas turbine plants and pumped-storage hydropower plants can be used as peak-generation plants
- The overall efficiency of any thermal power plant cannot exceed 50% *(The efficiency of a combined-cycle power plant may exceed 60%)*
- Usually, a nuclear power plant has a higher efficiency than a coal-fired power plant. *(lower)*
- The highest voltage level of AC power transmission systems in USA is 500kV *(765kV)*
- The 3-phase complex power of the wye-connected load equals $\sqrt{3}E_{ab}I_a^*$ *($\sqrt{3}E_{ab}I_a^* \cdot 1\angle -30^\circ$)*

Only b and c are correct (5 pts each).


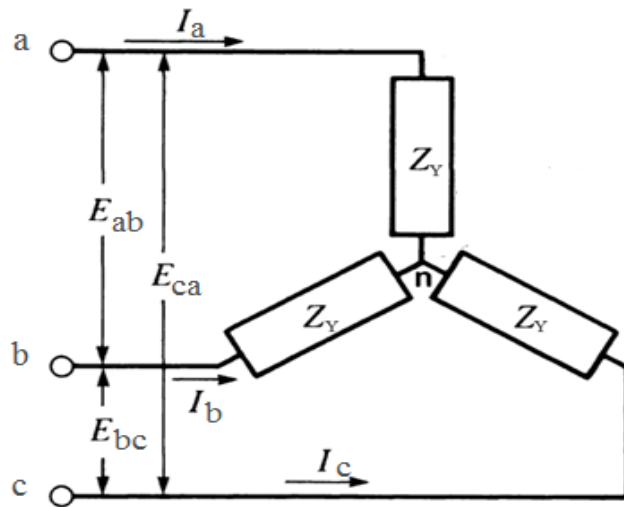


Problem 2 (10 points): A circuit connecting devices A and B has current I and voltage E as defined in the figure. Their instantaneous values, i and e , are given in the plot. Regarding the current operating condition of the circuit, circle the correct statements:

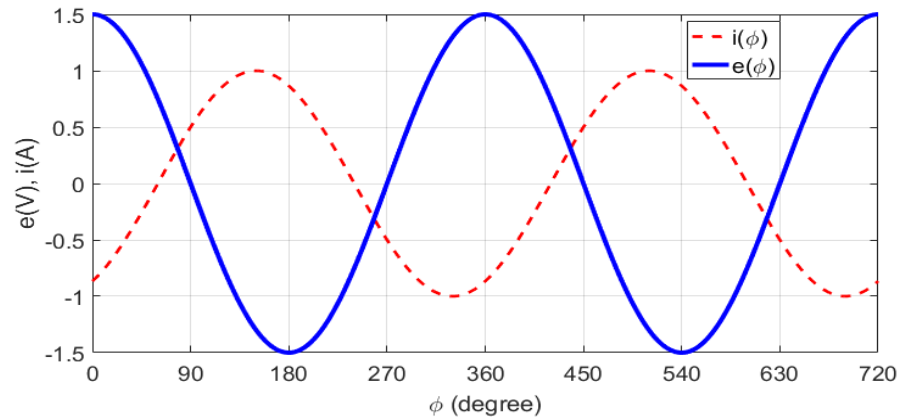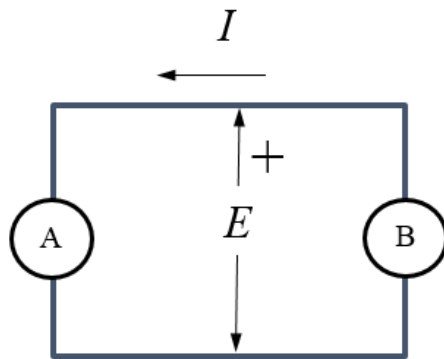- 1) Device A is the active source
- 2) Device B is the active source
- 3) Device A is the reactive load
- 4) Device B is the reactive load




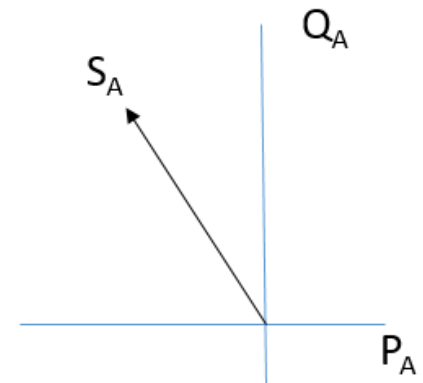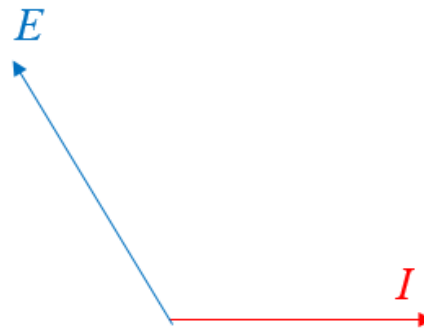5 pts for choosing 1), not 2)
 5 pts for choosing 3), not 4)



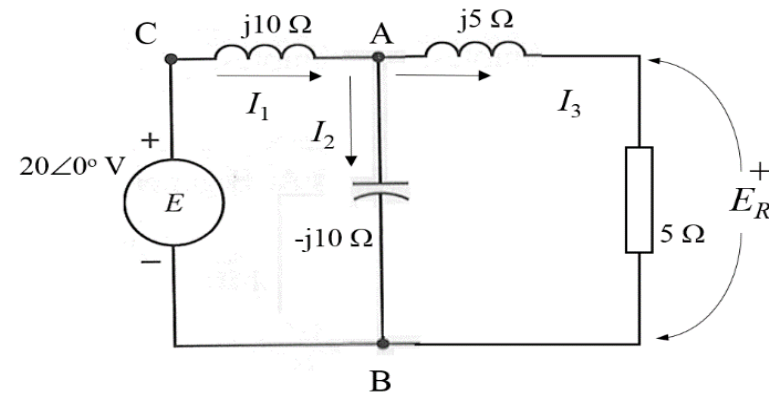Problem 3 (30 points): The circuit shown in the figure is powered by a 20V AC source. Calculate

- branch currents I_1 , I_2 and I_3 as defined in the figure
- the voltage E_R across the resistor
- the complex power supplied by the source E
- the reactive power supplied by the capacitor
- Draw the phasor diagram about E , E_R , I_1 , I_2 and I_3



a. (10 pts for Steps)

Method 1: $Z + 2$ KVL/KCL equations;

Method 2: 3 KVL/KCL equations

$$Z_1 = j10, \quad Z_2 = -j10, \quad Z_3 = 5 + j5$$

$$Z = Z_3 // Z_2 + Z_1 = (5 + j5) \times (-j10) / (5 + j5 - j10) + j10 = 10 + j10 \, \Omega$$

$$I_1 = E/Z = 20/(10 + j10) = 1 - j = 1.41 \angle -45^\circ \text{ A} \quad (1 \text{ pt} + 1 \text{ pt})$$

$$\text{KVL: } E - I_1 Z_1 - I_2 Z_2 = 0$$

$$I_2 = (E - I_1 Z_1) / Z_2 = 1 + j = 1.41 \angle 45^\circ \text{ A} \quad (1 \text{ pt} + 1 \text{ pt})$$

$$I_2 Z_2 - I_3 Z_3 = 0$$

$$I_3 = I_2 Z_2 / Z_3 = -j2 = 2 \angle -90^\circ \text{ A} \quad (1 \text{ pt} + 1 \text{ pt})$$

(Validated by KCL: $I_1 + I_2 + I_3 = 0$)

b. (1 pt for the equation)

$$E_R = I_3 R = 10 \angle -90^\circ \text{ V} \quad (1 \text{ pt} + 1 \text{ pt})$$

c. (1 pt for the equation)


$$S = E I_1^* = 20 \times (1 + j) = 20 \text{ W} + j20 \text{ var} \quad (1 \text{ pt} + 1 \text{ pt})$$

d. (1 pt for the equation)


$$S_C = |I_2|^2 Z_2 = 2 \times -j10 = -20j \text{ var}$$

Supply +20var (1 pt for “20” + 1 pt for “+”)

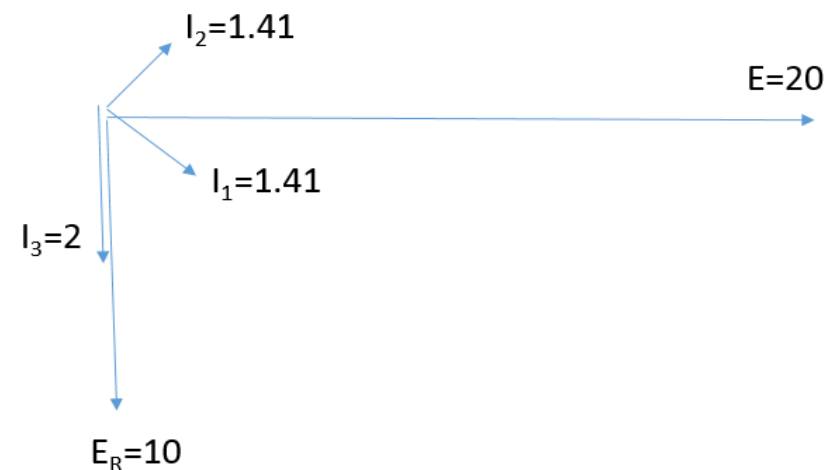e. Phasor diagram (5 pts: 1 pt per phasor)



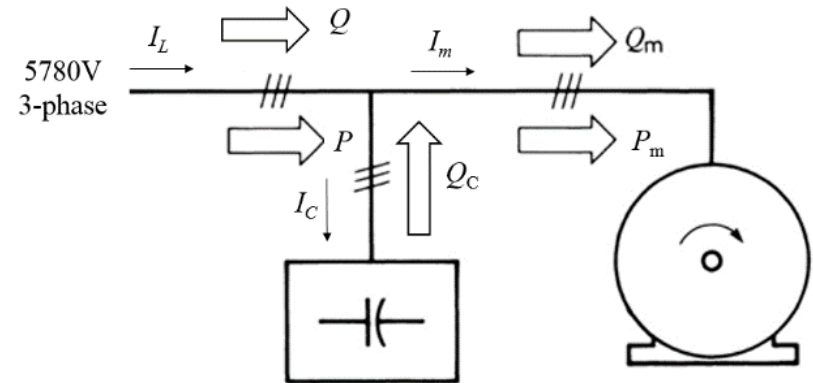Problem 4 (35 points): A wye-connected motor is connected to a 5780V (line-to-line voltage) 3-phase, 60Hz transmission line. A delta-connected capacitor bank rated at $Q_C=100\text{kvar}$ is also connected to the line to provide reactive power support. If the motor produces an output of 161kW at 93% efficiency and a power factor of 0.866 (lagging). I_L is the transmission line current, I_C is the line current drawn by the capacitor bank and I_m is the line current drawn by the motor. Calculate the following



- The reactive power Q_m absorbed by the motor
- The complex power $S=P+jQ$ supplied by the transmission line
- RMS values of I_L , I_C and I_m
- Draw a phasor diagram about I_L , I_m , I_C and line-to-neutral voltage E_{LN} of the transmission line for one phase

a. (6 pts for equations)

$$\phi_m = \cos^{-1}(0.866) = 30^\circ \quad 1 \text{ pt}$$

$$P_m = 161 / 0.93 = 173 \text{ kW} \quad 2 \text{ pt}$$

$$Q_m = P_m \tan(\phi_m) = 173 \times 1.73 = 100 \text{ kvar} \quad 1 \text{ pt}$$

b. (4 pts for equations)

$$S_m = 173 + j100 \text{ kVA}$$

$$S = S_m - jQ_C = 173 + j0 \text{ kVA} \quad 1 \text{ pt} + 1 \text{ pt}$$

c. (6 pts for equations)

$$|I_L| = |S| / (E_L \times 1.73) = 17.3 \text{ A} \quad 1 \text{ pt}$$

$$|I_m| = |S_m| / (E_L \times 1.73) = 20 \text{ A} \quad 1 \text{ pt}$$

$$|I_C| = |Q_C| / (E_L \times 1.73) = 10 \text{ A} \quad 1 \text{ pt}$$


d. (4 pts for equations)

$$E_{LN} = E_L / 1.73 = 3337 \text{ V} \quad 1 \text{ pt}$$

$$\phi = \tan^{-1}(Q/P) = 0^\circ \quad 1 \text{ pt}$$

Phasor diagram

4pts: 1 pt per phasor

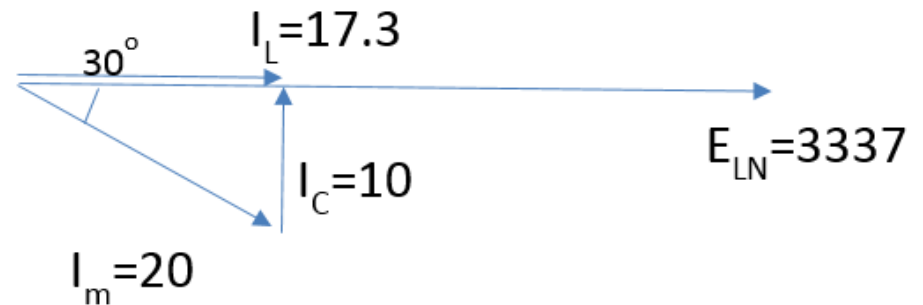

Problem 5 (10 points): A three-phase line having line-to-line voltage E_L is supporting both delta-connected resistances and wye-connected resistances through series reactors. All six resistances are identical and equal to R . All reactors have reactance X . Give the formulas on

- the magnitude of each line current
- the total three-phase complex power supplied by the line

a.

$$Z = R // \frac{R}{3} + jX = \frac{R}{4} + jX \quad 2 \text{ pts}$$

$$|I_L| = \left| \frac{E_L}{\sqrt{3}(\frac{R}{4} + jX)} \right| \quad 4 \text{ pts}$$

b.

$$S = \frac{3 |E_L / \sqrt{3}|^2}{Z^*} = \frac{|E_L|^2}{\frac{R}{4} - jX} \quad 4 \text{ pts}$$

