

CURRENT Fall 2016

Three-Phase Voltage-Source Converters

Jian Sun
CII 8015, jsun@rpi.edu



Outline


- Basic Operation & Applications
- Pulse-Width Modulation
- AC-Side Current Control
- DC-Link Voltage Regulation



Three-Phase VSC

2

Three-Phase VSC Circuit

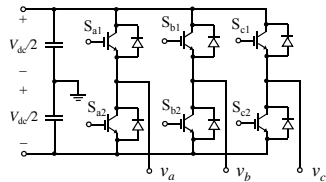

- A Versatile Interface between DC and Three-Phase AC
- Middle of DC Link is Usually Used as Reference Point
- Inductive Elements at AC Terminals Required
- Bidirectional Power Flow Capabilities



Three-Phase VSC

3

Applications in Power Systems


- Renewable Energy Integration into the Grid
 - Including Energy Storage
- High-Voltage DC Transmission
- Reactive Power Compensation
 - Including Harmonics as Active Power Filter
- Dynamic Voltage Restorer (DVR)
- Unified Power Flow Controller (UPFC)
- Other FACTS Devices



Three-Phase VSC

4

Carrier-Based PWM

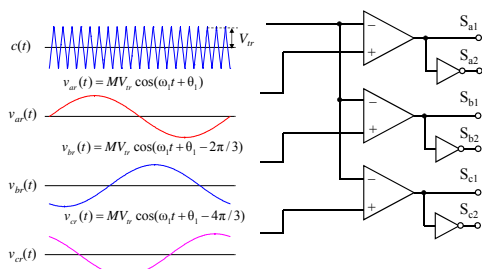


M : Modulation Index; Carrier Frequency $f_c = \omega_c/(2\pi)$, with an Initial Phase θ_c .



Three-Phase VSC

5

Phase and Line-Line Voltages

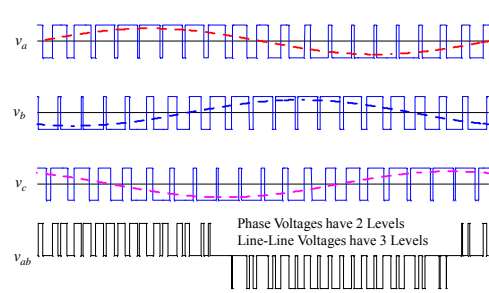

Three-Phase VSC

6

PWM Spectrum

$$v_{pm}(t) = M \cos(\omega_c t + \theta_c) + \sum_{m=1}^{\infty} \frac{4}{m\pi} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c)]$$

$M = V_f/V_m$; Modulation Index θ_i : Initial Phase Angle of Reference
 $\omega_f = 2\pi f_f$; Reference Frequency θ_c : Initial Phase Angle of Carrier
 $\omega_c = 2\pi f_c$; Carrier Frequency $J_n(x)$: Bessel Function of the 1st Kind

Three-Phase VSC 7

Spectral Composition

Fundamental (f_f)
Carrier (f_c) and Its Harmonics ($2f_c, 3f_c, \dots$)

$$v_{pm}(t) = M \cos(\omega_c t + \theta_c) + \sum_{m=1}^{\infty} \frac{4}{m\pi} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c)]$$

Sideband Components: $mf_c \pm f_f, mf_c \pm 2f_f, mf_c \pm 3f_f, \dots$

Alternative Form:

$$v_{pm}(t) = M \cos(\omega_c t + \theta_c) + \sum_{m=1}^{\infty} \sum_{n=0, \pm 1, \dots} \frac{4}{m\pi} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c)]$$

Three-Phase VSC 8

Phase Voltage Spectra

$$v_a(t) = \frac{V_d}{2} M \cos(\omega_c t + \theta_c) + \frac{2V_d}{\pi} \sum_{m=1}^{\infty} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c)]$$

$$v_b(t) = \frac{V_d}{2} M \cos(\omega_c t + \theta_c - \frac{2\pi}{3}) + \frac{2V_d}{\pi} \sum_{m=1}^{\infty} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c - \frac{2\pi}{3})]$$

$$v_c(t) = \frac{V_d}{2} M \cos(\omega_c t + \theta_c + \frac{4\pi}{3}) + \frac{2V_d}{\pi} \sum_{m=1}^{\infty} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c + \frac{4\pi}{3})]$$

Carrier and its harmonics are the same in all three phases; Sideband components are phase shifted by multiple times of that between the fundamental components.

Three-Phase VSC 9

Line-Line Voltage Spectra

$$v_{ab}(t) = \frac{\sqrt{3}V_d}{2} M \cos(\omega_c t + \theta_c + \frac{\pi}{6}) + \frac{2\sqrt{3}V_d}{\pi} \sum_{m=1}^{\infty} \sum_{n=0, \pm 1, \dots} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c) \pm \frac{\pi}{6}]$$

Sideband Components

Three-Phase VSC 10

AC Neutral Voltage

$$v_N = \frac{v_a + v_b + v_c}{3}$$

Assume Balanced AC with a Floating Neutral Point, N :

$$I_a(s) + I_b(s) + I_c(s) = 0 \implies i_a(t) + i_b(t) + i_c(t) = 0 \implies v_N(t) = \frac{v_a(t) + v_b(t) + v_c(t)}{3}$$

$$\frac{V_a(s) - V_N(s)}{Z(s)} + \frac{V_b(s) - V_N(s)}{Z(s)} + \frac{V_c(s) - V_N(s)}{Z(s)} = 0 \implies V_N(s) = \frac{V_a(s) + V_b(s) + V_c(s)}{3}$$

Three-Phase VSC 11

Common-Mode Voltage

$v_{cm} = \frac{v_a + v_b + v_c}{3}$

- Defined as the Common Component of Output Voltages
- The Same as the Load Neutral Voltage
- Also called Zero-Sequence Voltage

$$v_a(t) = \frac{V_d}{2} M \cos(\omega_c t + \theta_c) + \frac{2V_d}{\pi} \sum_{m=1}^{\infty} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c)]$$

Carrier and Its Harmonics

$$v_{ab}(t) = \frac{\sqrt{3}V_d}{2} M \cos(\omega_c t + \theta_c + \frac{\pi}{6}) + \frac{2\sqrt{3}V_d}{\pi} \sum_{m=1}^{\infty} \sum_{n=0, \pm 1, \dots} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c) + n(\omega_c t + \theta_c) \pm \frac{\pi}{6}]$$

Sideband Components Centered around the Carrier Frequency and its Harmonics

$$v_{cm}(t) = \frac{2V_d}{\pi} \sum_{m=1}^{\infty} \frac{1}{m} J_n\left(\frac{m\pi M}{2}\right) \sin\left(\frac{m+n}{2}\pi\right) \cos[m(\omega_c t + \theta_c)]$$

Carrier and Its Harmonics

Three-Phase VSC 12

Effects of CM Voltage

- Common-Mode (Ground) Current – EMI Problem
- Motor Bearing Current – Motor Reliability

Motor Stator Rotor

Motor Bearing Current

Possible Solutions:

- Common-Mode Voltage Filtering
- CM Voltage Reduction by Circuit Topology and PWM Techniques
- Ceramic Bearing (High Performance Systems e.g. Aerospace)

Three-Phase VSC 13

Maximum Output Voltage

- Maximum Output Voltage
 - Achieved when $M = 1$
 - $V_{a,max} = V_{dc} / 2$
- Overmodulation
 - Nonlinear Gain – Saturation
 - Increased Harmonics

Three-Phase VSC 14

3rd Harmonic Injection

- 3rd Harmonics (of the Fundamental) are of Zero-Sequence
 - Identical for All Three Phases: $3 \times 120^\circ = 360^\circ$
- Adding the Same 3rd-Order Harmonic to the References
 - Doesn't Affect Load Phase Voltages
 - Allows the Fundamental Amplitude to be Higher than the Carrier

Overmodulation Linear Operation

Three-Phase VSC 15

Triplen Harmonics Injection

All triplen harmonics are zero-sequence components, hence can be injected without affecting the load phase voltage. A special case is a triangular wave.

Phase a
Phase b
Phase c

Three-Phase VSC 16

Limits for Harmonics Injection

$$v_{a,ref}(t) = V_1 \sin(\omega_1 t) - v_{in}(t), \quad V_1 > 0.5V_{dc}$$




$v_{in}(t)$ must fall in the shadowed area in order to avoid distortion

Three-Phase VSC 17



Maximal Output Voltage

$$v_{ref}\left(\frac{iT_s}{6}\right) = V_1 \sin\left(\frac{\pi}{3}\right) = \frac{\sqrt{3}V_1}{2} \Rightarrow V_{1,max} = \frac{V_{dc}}{\sqrt{3}}$$

Three-Phase VSC 18

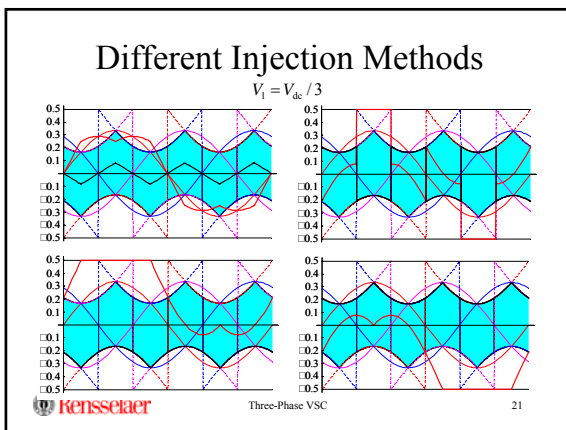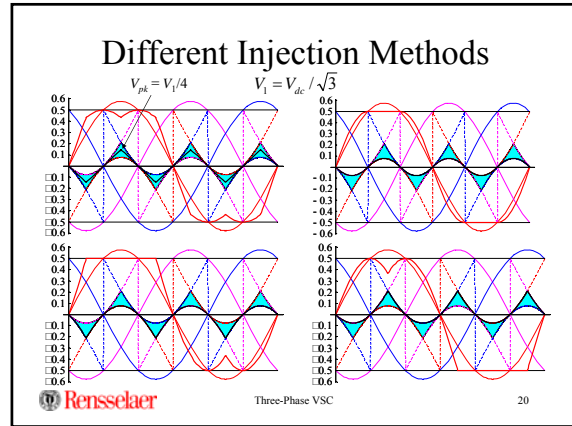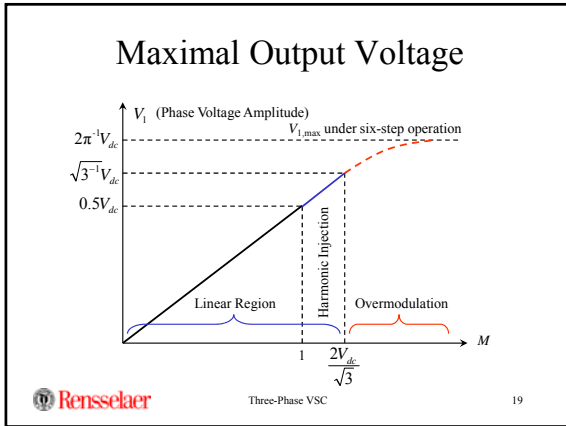

- ### Effects on Phase Voltages
- Phase Voltages Contain Additional Harmonics under Harmonic Injection
 - Injected Harmonics and Sideband Components
 - Identical in All Three Phases
 - Hence Cancel in Line-Line Voltages
 - These Harmonics Become Part of Common-Mode Voltage
 - Relatively Low Frequency and Magnitude Compared to the CM Voltage Generated by PWM
 - Phase Voltage Spectra can also be Obtained by Double Fourier Series Analysis
 - Closed-Form Results have been Reported in the Literature
 - Optimal Harmonic Injection
- Rensselaer Three-Phase VSC 22

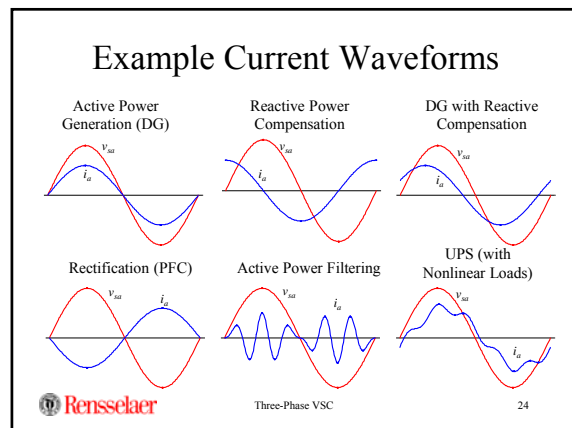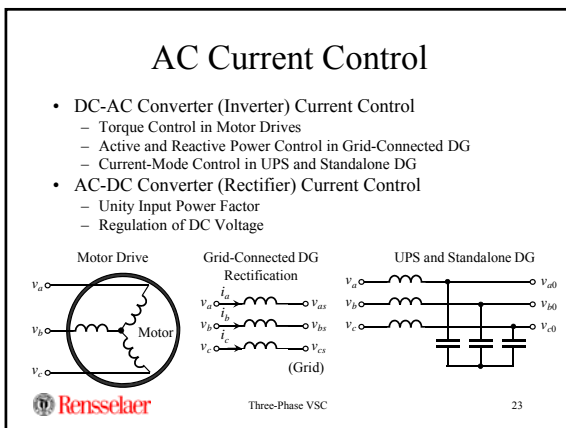

Current Control Principles

$\{V_{a1}, V_{ak}\}$

v_{Lk}

i_{Lk}

$$I_{L1} = \frac{V_{a1} - V_{a2}}{j2\pi f_1 L}$$

$$I_{Lk} = \frac{V_{ak} - V_{a1}}{j2\pi k f_1 L} = \frac{V_{ak}}{j2\pi k f_1 L}$$

Single Phase

Three Phase

Three-Phase VSC
25

Averaged Modeling

- $d_a, d_b,$ and d_c is the Duty Ratio of the Upper Switch in Phase a, b, and c, Respectively
- Averaging Removes Switching Ripple
 - Resulting Model is in General Valid at Frequencies Lower than Half the Switching (Carrier) Frequency

Three-Phase VSC
26

Basic Control Structure

- Objective: Control Phase Currents $i_a, i_b,$ and i_c to Follow Given References $\{i_{a,ref}, i_{b,ref}, i_{c,ref}\}$
- Assumption: Terminal Voltages $v_{sa}, v_{sb},$ and v_{sc} are Known
- Current Responses Governed by

$$L \frac{di_a}{dt} = v_a - v_{sa}, \quad L \frac{di_b}{dt} = v_b - v_{sb}, \quad L \frac{di_c}{dt} = v_c - v_{sc} \quad \Rightarrow \quad L \frac{d\mathbf{i}}{dt} = \mathbf{v} - \mathbf{v}_s$$

The modulator and the averaged model can be modeled together by a constant gain $V_{dc}/(2V_r)$.

Three-Phase VSC
27

Feedforward Control

Problem: Performance is Sensitive to Parameter Variations and Uncertainty

Three-Phase VSC
28

Linear Feedback Control

Control Structure

PI Regulator:

$$v_{ref} = K_p \Delta i + K_i \int \Delta i dt$$

- One Linear (PI) Regulator per Phase
- Simple, Robust
- Limited Performance
 - Existence of Control Error

$$V(s) = [I_{ref}(s) - I(s)] \left(K_p + \frac{K_i}{s} \right) \frac{V_{dc}}{2V_r}$$

$$I(s) = \frac{V(s) - V_i(s)}{Ls}$$


$$I(s) = \frac{I_{ref}(s) \left(K_p + \frac{K_i}{s} \right) \frac{V_{dc}}{2V_r} - V_i(s)}{Ls + \left(K_p + \frac{K_i}{s} \right) \frac{V_{dc}}{2V_r}}$$

Three-Phase VSC
29


Feedback + Feedforward

Three-Phase VSC
30

Nonlinear (Hysteretic) Control

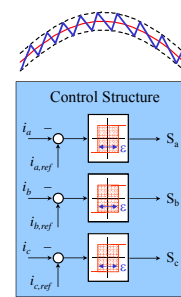


- Features
 - Direct Generation of Switch Gate Signals
 - No Need for PWM
 - Simple, Robust
 - Stable Operation, Fast Response
 - Variable Switching Frequencies
 - Not Suitable for Digital Control
- Possible Improvement
 - Variable Hysteretic Bands to Reduce Switching Frequency Variation
 - Space Vector-Based Hysteretic Control

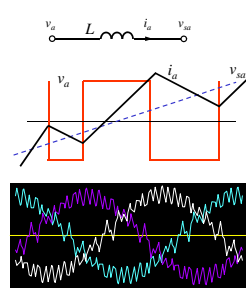

Three-Phase VSC
31

Practical Control Methods


- Control in DQ Reference Frame
 - Balanced Three-Phase References Become DC in DQ Frame
 - No Steady-State Tracking Error
- Resonant Feedback Compensation
 - Compensator has a Resonance at the Line Frequency
 - Improve Tracking of Inductor Current at the Line Frequency


Three-Phase VSC
32

Ripple Current and L Selection





- Inductor Currents Contain Ripple Components at the Switching Frequency
- Amplitude $\propto (L f_s)^{-1}$
 - Varies over a Line Cycle
- Effects of Current Ripple
 - Contribute to System Harmonics
 - Increase Converter Losses
- Inductor Design Considerations
 - Performance vs. Cost & Size


Three-Phase VSC
33


DC-Link Voltage Control

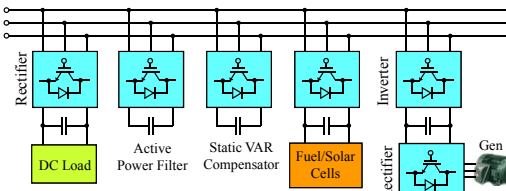- Applications Requiring Control of the DC-Link Voltage
 - Power Factor Corrected Rectifiers
 - Active Power Filters
 - Static VAR Compensators
 - Grid Interface for Fuel Cells, Solar, and Wind Power




Three-Phase VSC
34

DC-Link Voltage Model

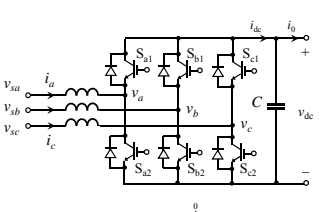

$$C \frac{dV_{dc}}{dt} = i_{dc} - i_o$$

$$\bar{i}_{dc} = d_a i_a + d_b i_b + d_c i_c$$


$$\bar{v}_a = \frac{d_a v_{dc}}{2} \cdot \frac{(1-d_a)v_{dc}}{2}$$

$$d_a = \frac{\bar{v}_a}{v_{dc}} + \frac{1}{2}$$

$$\bar{i}_{dc} = \frac{\bar{v}_a i_a + \bar{v}_b i_b + \bar{v}_c i_c}{v_{dc}} + \frac{i_a + i_b + i_c}{2} = \frac{\bar{v}_a i_a + \bar{v}_b i_b + \bar{v}_c i_c}{v_{dc}} + \bar{v}_o i_o$$

Power Balance: $\bar{i}_{dc} v_{dc} = \bar{v}_a i_a + \bar{v}_b i_b + \bar{v}_c i_c$

$$C \frac{dV_{dc}}{dt} = \frac{\bar{v}^T \bar{i}}{v_{dc}} - i_o$$


Three-Phase VSC
35

V_{dc} Response to Phase Currents


- Assume Balanced Sinusoidal Source Voltages
- Only Active Component of Phase Currents Affects Average of V_{dc}
- Reactive Component doesn't Affect V_{dc}
- Unbalanced Fundamental Components (Active or Reactive) Lead to 2nd Harmonic in V_{dc}
- Balanced $(6k \pm 1)^{th}$ Harmonic Currents Generates 6th Harmonic in V_{dc}

$$v_{sa}(t) = V_s \cos(\omega t), \quad v_{sb}(t) = V_s \cos(\omega t - 2\pi/3), \quad v_{sc}(t) = V_s \cos(\omega t - 4\pi/3)$$

$$\cos x \cos x + \cos\left(x - \frac{2\pi}{3}\right) \cos\left(x - \frac{2\pi}{3}\right) + \cos\left(x - \frac{4\pi}{3}\right) \cos\left(x - \frac{4\pi}{3}\right) = \frac{3}{2}$$

$$\sin x \cos x + \sin\left(x - \frac{2\pi}{3}\right) \cos\left(x - \frac{2\pi}{3}\right) + \sin\left(x - \frac{4\pi}{3}\right) \cos\left(x - \frac{4\pi}{3}\right) = 0$$

$$\sin 5x \cos x + \sin 5\left(x - \frac{2\pi}{3}\right) \cos\left(x - \frac{2\pi}{3}\right) + \sin 5\left(x - \frac{4\pi}{3}\right) \cos\left(x - \frac{4\pi}{3}\right) = \frac{3}{2} \cos 6x$$


Three-Phase VSC
36


Voltage Dynamics and Control

Assume Active Component of Phase Current $i_a = gv$

$$C \frac{d\bar{v}_{dc}}{dt} = \frac{\sqrt{3}i_a}{\bar{v}_{dc}} - i_o = \frac{3gV_{rms}^2}{\bar{v}_{dc}} - i_o$$

V_{rms} = Input Phase RMS Voltage

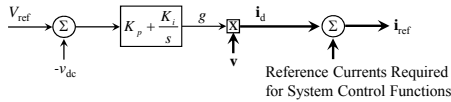- g is the Control Variable
 - Represents Voltage Compensator Output
- Dynamics Described by a Nonlinear Model
 - Linearization about a Steady-State Operation Point



Reading & HW Assignments

- Holmes and Lipo, Pulse Width Modulation for Power Converters, Chapters 5&6
- Consider A Three-Phase Solar Inverter Switched at 20 kHz and with a 350 V DC Input. The Inverter is Connected to a 120 V (Phase RMS) Grid through a 1 mH (per Phase) Inductor, and Supplies 10 kW Active Power to the Grid. Calculate
 - The Modulation Index M
 - The Amplitude of Phase Harmonic Current at 20 kHz, 20 kHz \pm 60 Hz, 20 kHz \pm 120 Hz, 20 kHz \pm 180 Hz; and 40 kHz, 40 kHz \pm 60 Hz, 40 kHz \pm 120 Hz, 40 kHz \pm 180 Hz