

User Note:

Run **View Show**
under the **Slide**
Show menu to
enable slide
selection.


Chapter 8 Basic RL and RC Circuits

- Fig. 8.1 A series RL circuit for which $i(t)$ is to be determined...
- Fig. 8.6 A plot of the exponential response versus time..
- Fig. 8.11 A parallel RC circuit for which $v(t)$ is to be determined...
- Fig. 8.21 (a) A voltage-step function is shown as the source...
- Fig. 8.19 (and Fig. 8.20) Two versions of the unit-step function...
- Fig. 8.23 A useful forcing function, the rectangular voltage pulse.
- Figs. 8.29 (and 8.30) Circuit from Example 8.4.
- Fig. 8.31 (and 8.32) Circuit from Example 8.5..
- Fig. 8.34 Circuit for Example 8.6.

Engineering Circuit Analysis Sixth Edition

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin

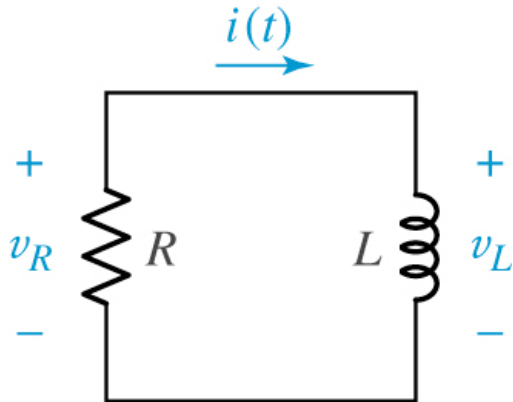Copyright © 2002 McGraw-Hill, Inc. All Rights Reserved.



A series RL circuit for which $i(t)$ is to be determined, subject to the initial condition that $i(0) = I_0$.

$$\text{KVL: } Ri(t) + L \frac{d}{dt}(i(t)) = 0$$


1st-order, linear, constant-coefficient, ordinary, homogeneous differential equation. The solution form is $i(t) = Ae^{\lambda t}$.

$$RAe^{\lambda t} + L\lambda Ae^{\lambda t} = 0 \Rightarrow R + \lambda L = 0 \Rightarrow \lambda = -R/L \Rightarrow i(t) = Ae^{-Rt/L}.$$

To find A we need a boundary condition. The most common boundary condition is $i(0) = I_0$. Then

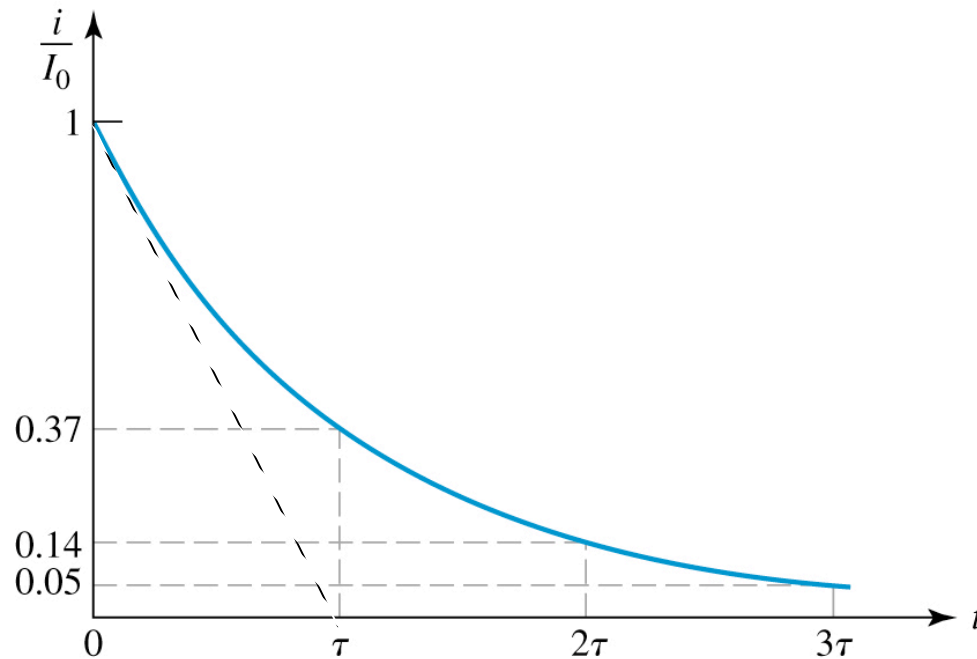
$$I_0 = A \Rightarrow i(t) = I_0 e^{-Rt/L}$$






A plot of the exponential response versus time.
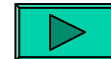
$$i(t) = I_0 e^{-Rt/L} = I_0 e^{-t/\tau} \text{ where } \tau = L / R$$




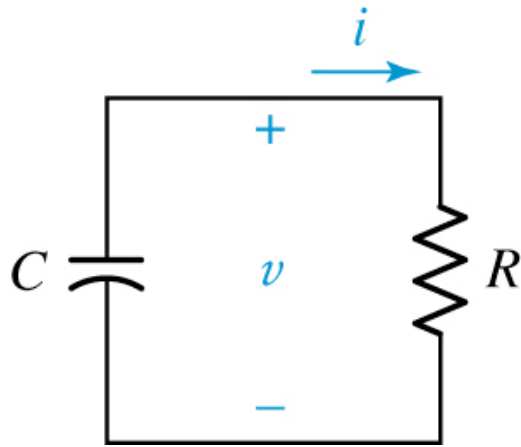



A parallel RC circuit for which $v(t)$ is to be determined, subject to the initial condition that $v(0) = V_0$.

$$\text{KCL: } C \frac{d}{dt} (v(t)) + \frac{v(t)}{R} = 0, \quad v(t) = Ae^{\lambda t} \Rightarrow CA\lambda e^{\lambda t} + \frac{Ae^{\lambda t}}{R} = 0$$


$$C\lambda + 1/R = 0 \Rightarrow \lambda = -1/RC \Rightarrow v(t) = Ae^{-t/RC}$$
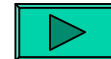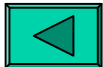
$$\text{If } v(0) = V_0, \text{ then } v(t) = V_0 e^{-t/RC} = V_0 e^{-t/\tau}, \text{ where } \tau = RC.$$




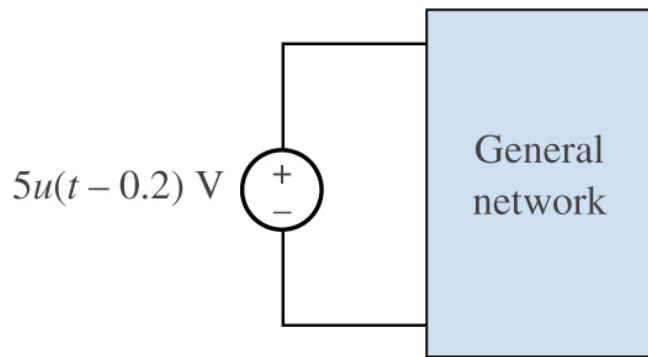

(a)

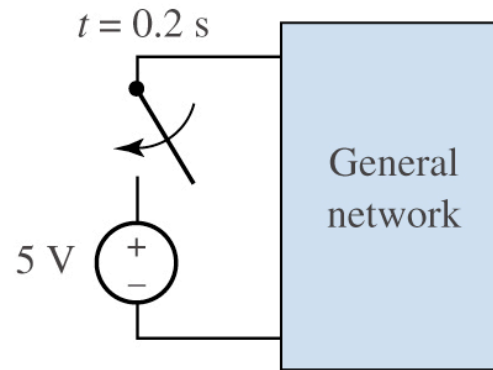



(b)

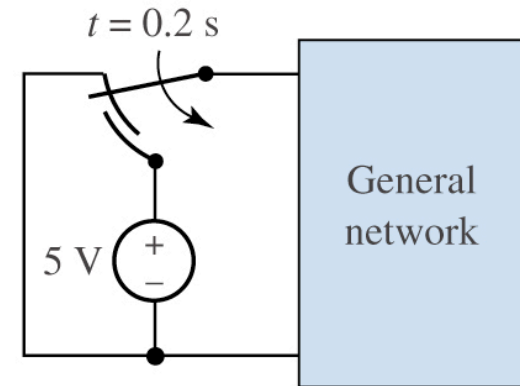


(c)

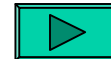(a) A voltage-step forcing function is shown as the source driving a general network. (b) A simple circuit which, although not the exact equivalent of part (a), may be used as its equivalent in many cases. (c) An exact equivalent of part (a).



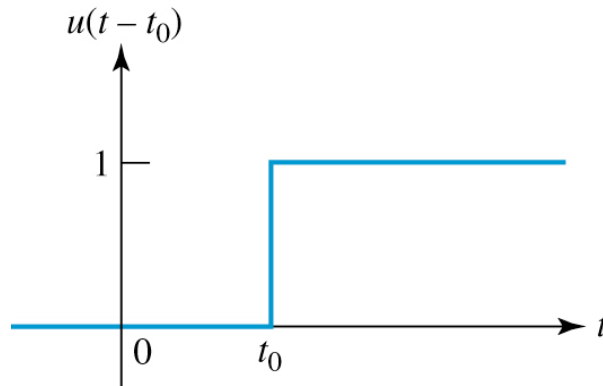


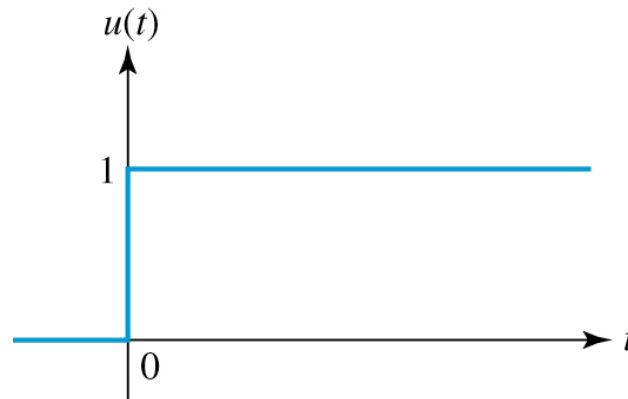The unit-step forcing function $u(t - t_0)$.



The unit-step forcing function $u(t)$.



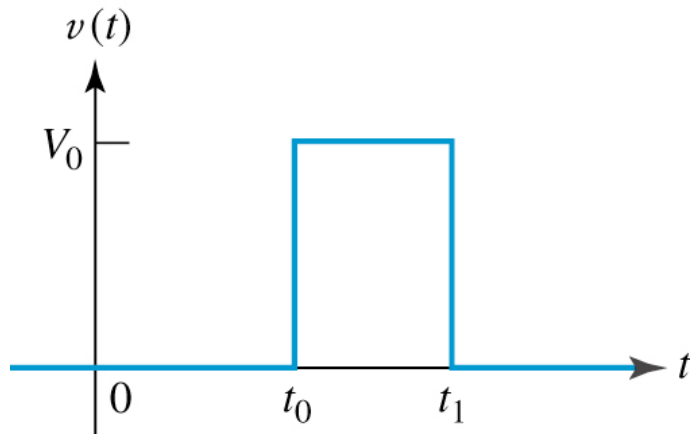


The rectangular pulse function

$$v(t - t_0) = \begin{cases} 0 & t < t_0 \\ V_0 & t_0 < t < t_1 \\ 0 & t > t_1 \end{cases}$$



Driven RL Circuit

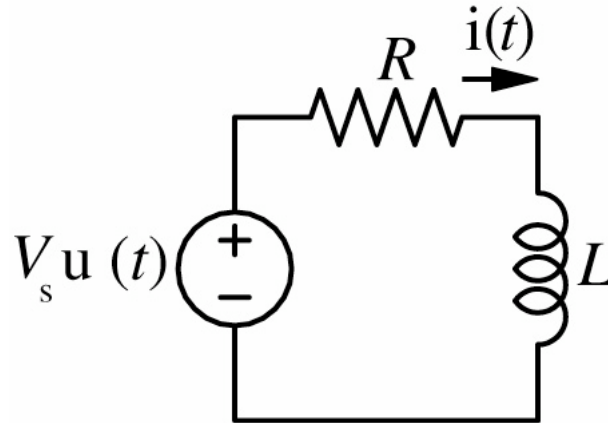

$$R i(t) + L \frac{d}{dt} (i(t)) = V_s u(t)$$


Solution form is $i(t) = A e^{-t/\tau} + I_f$, $t > 0$ where $I_f = i(\infty)$.

$$\tau = L / R, \quad I_f = V_s / R \Rightarrow i(t) = A e^{-Rt/L} + V_s / R$$

$$i(0^+) = i(0^-) = 0 = A + V_s / R \Rightarrow A = -V_s / R$$

$$i(t) = (V_s / R) (1 - e^{-Rt/L}), \quad t > 0$$

Driven RC Circuit

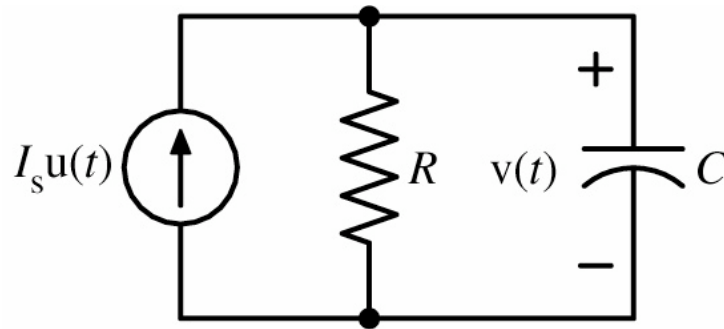


$$\frac{v(t)}{R} + C \frac{d}{dt}(v(t)) = I_s u(t)$$

Solution form is $v(t) = Ae^{-t/\tau} + V_f$, $t > 0$ where $V_f = v(\infty)$.


$$\tau = RC, \quad V_f = RI_s \Rightarrow v(t) = Ae^{-t/RC} + RI_s$$

$$v(0^+) = v(0^-) = 0 = A + RI_s \Rightarrow A = -RI_s$$
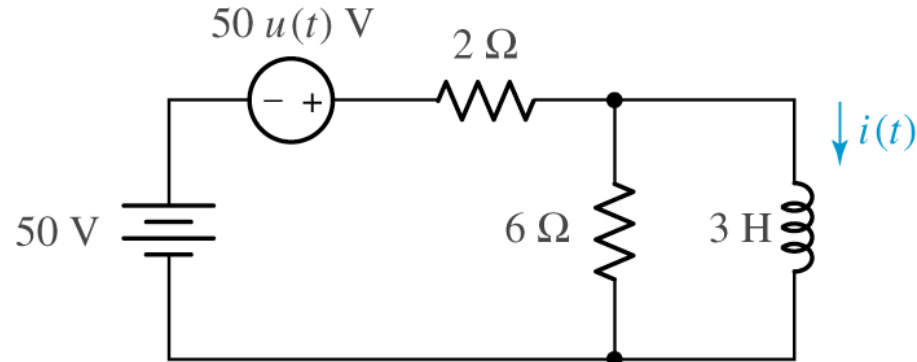
$$v(t) = RI_s (1 - e^{-t/RC}), \quad t > 0$$




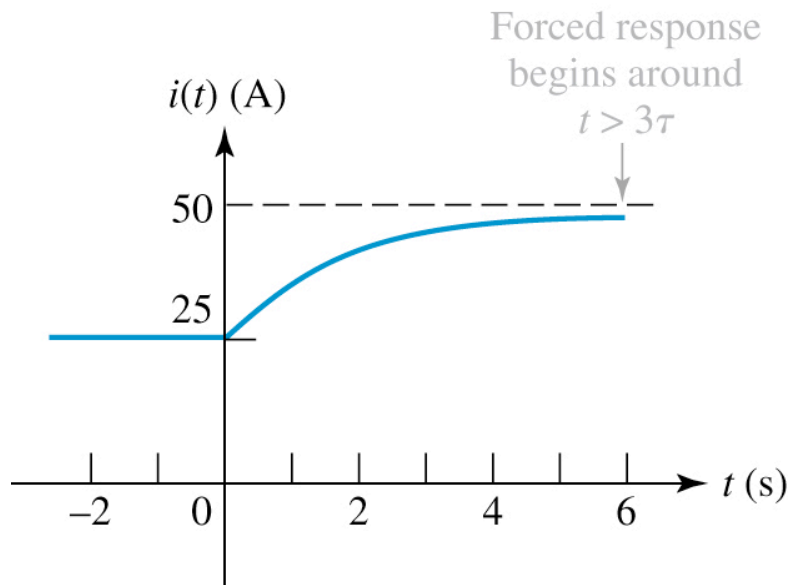Circuit for which a complete response $i(t)$ is desired.




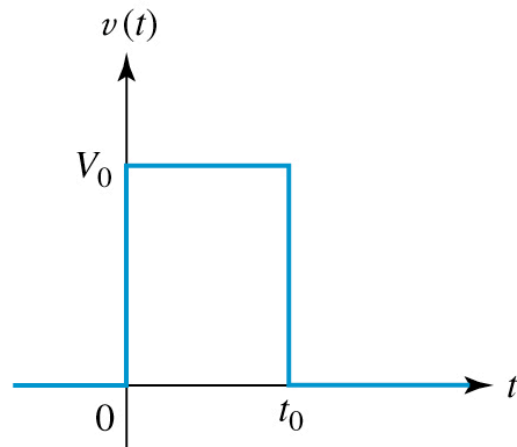The desired current response as a function of time.







(a)

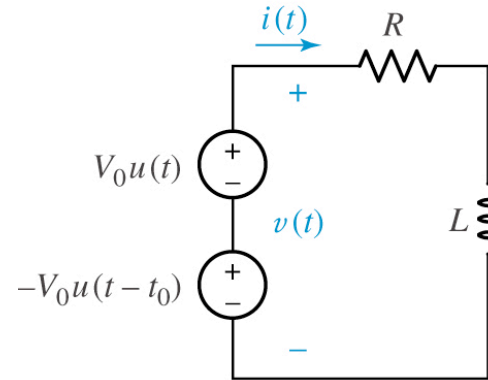

(b)


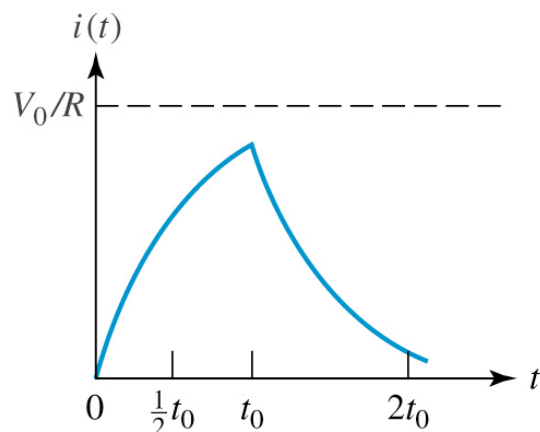


(c)



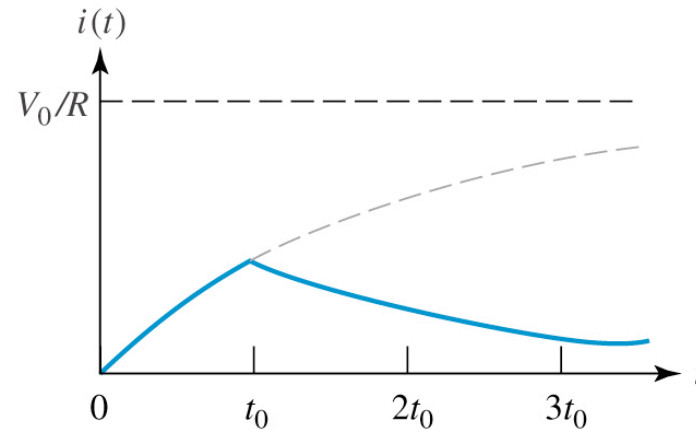


(d)

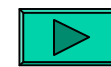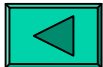(a) Pulse waveform; (b) Circuit driven by waveform (a); (c) $\tau = t_0/2$; (d) $\tau = 2t_0$.



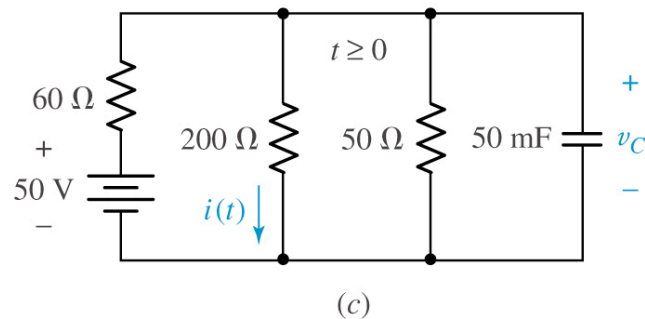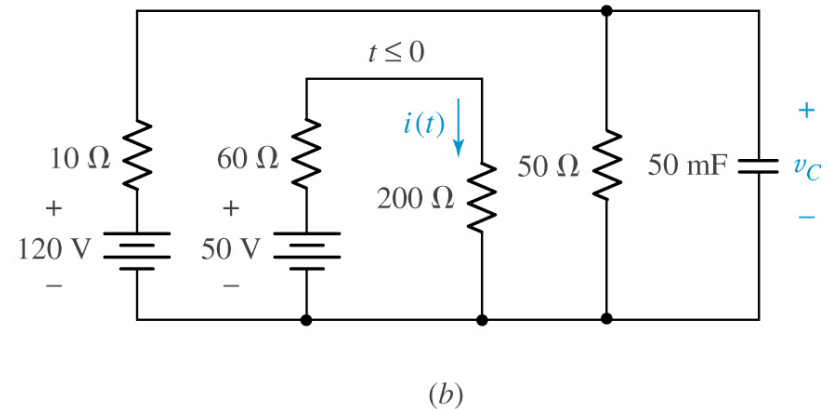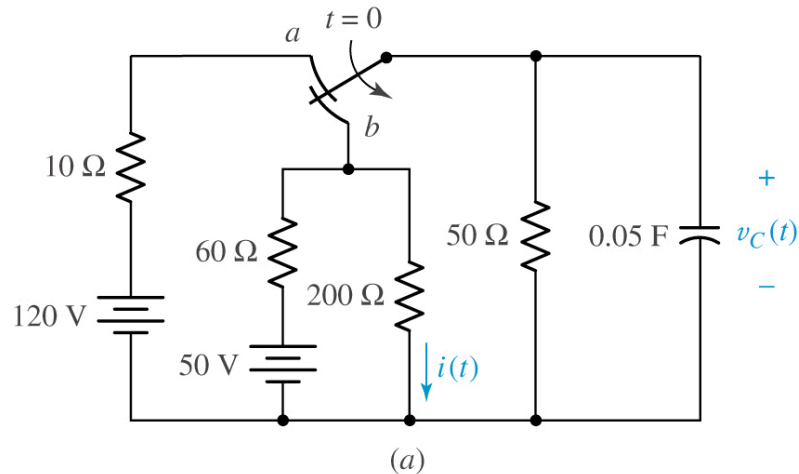Find the capacitor voltage $v_C(t)$ and the current $i(t)$ in the $200\text{-}\Omega$ resistor of the circuit shown in (a).



(a) Original circuit; (b) circuit valid for $t \leq 0$; (c) circuit for $t \geq 0$.

