

Answer to the Homework Problems:

Homework 1:

- 10.11 $8.84 \cos(100t-45^\circ)$
- 10.19 (a) $7.79 + j4.5$
(b) $6.74 - j0.023$
(c) $7.67 + j87.5$
(d) $3.15 + j2.5$
(e) $289.27 + j241.045$
- 10.26 (a) $11 \angle -90^\circ$
(b) $11 \angle 0^\circ$
(c) $11 \angle -90^\circ$
(a) $4.24 \angle 45^\circ$
- 10.40 (a) $23.24 \angle -12.9^\circ \Omega$
(b) $12.08 \angle -13.78^\circ \Omega$
(c) $11.14 \angle -1.54^\circ \Omega$
- 10.42 (a) $15 \angle -33.13^\circ \text{ V}$
(b) $15 \angle -73.13^\circ \text{ V}$
(c) $9 \angle -20^\circ \text{ V}$
(d) $20.13 \angle -43.44^\circ \text{ V}$
- 10.44 $i(t) = 2.98 \cos(100t - 46.48^\circ) \text{ A}$

Homework 2:

- 10.48 (a) $2.5 \cos 10 \text{ mA}$
(b) $1.5 \cos(10t - 42^\circ) \text{ mA}$
(c) $0.4843 \cos(10t - 16.48^\circ)$
- 10.51 $0.809 \angle -4.8^\circ$
- 10.54 $41.9 \angle 134.8^\circ \text{ V}$
- 10.62 $V_1 = 493.18 \angle -162.14^\circ \text{ V}, V_2 = 274.46 \angle -100.34^\circ \text{ V}$
- 10.64 $Z_{\text{thevenin}} = 4.77 \angle 34.32^\circ \text{ ohm}, V_{\text{th}} = 9.61 \angle 64.55^\circ \text{ V},$

- $I_1 = 1.6 \angle 57.92^\circ \text{ A}$
- 10.69 $24\cos^2(20t - 163^\circ) \text{ W}$
- 10.71 (b) I_s leads I_R by 83° ; I_C by -7° ; I_x by 146°

Homework 3:

- 11.5 $p_R(t) = 96 e^{-t/0.03} \text{ W}$
 $p_C(t) = -96 e^{-t/0.03} \text{ W}$
 $p_R(60\text{ms}) = 13 \text{ W}$
- 11.11 a) $P_1(t) = 0.73 + 1.16\cos(90t - 21^\circ) \text{ W}$
 b) $P_1(t) = 0.73 \text{ W}$
- 11.14 $P_R = 2129 \text{ W}$
 $P_{s1} = -230 \text{ W}, P_{s2} = -1899 \text{ W}$
 $P_L = 0 \text{ W}, P_C = 0 \text{ W}$
- 11.19 (a) $P_{4.8\Omega} = 69.6 \text{ W}, P_{8\Omega} = 36 \text{ W}$
 (b) $p_{j2A} = -9.6 \text{ W}, P_{1.6Ix} = -96 \text{ W}$
 (c) $Z_{th} = -8 + j3.2 \Omega$
- 11.25 $f_o = 0.167 \text{ Hz}, T = 6 \text{ s}$
 $I_{eff} = 1.291 \text{ A rms}$
 $f_o = 250 \text{ Hz}, T = 4 \text{ ms}$
 $I_{eff} = 1.443 \text{ A rms}$
- 11.26 (a) $i_{avg} = -3 \text{ mA}, i_{eff} = 5.196 \text{ mA rms}$
 (b) $f_{avg} = 0, f_{rms} = 0.333 * 10^{-3} \text{ rms}$
- 11.30 (a) $v_{avg} = 1 \text{ V}, v_{eff} = 1.225 \text{ V rms}$

Homework 4:

- 11.34 (a) Voltage lags current by 126°
 (b) Voltage leads current by 56.6°
 (c) Voltage lags current by 46.76°
 (d) Voltage lags current by 78.46°
- 11.36 a) $P_{load}(20\text{ms}) = 1.192 \text{ W}$
 b) $P_{1K\Omega} = 98 \text{ mW}, P_{load} = -333 \text{ mW}$

- c) AP_{load} (apparent power) = 1.92VA
d) $PF_{\text{source}} = 0.125$ leading 11.37 (a) $PF_{\text{source}} = 1$
(b) 0.9523 lagging (c) 0.9983 leading
- 11.37 (a) $PF_{\text{source}} = 1$
(b) 0.9523 lagging
(c) 0.9983 leading
- 11.41 (a) $AP=1.118$ KVA, $PF= 0.894$ lagging. $Q=500$ VAR
(b) $AP= 400$ VA, $PF= 1$, $Q=0$ VAR
(c) $AP= 150$ VA, $PF= 0.93$ leading, $Q= -53.75$ VAR
(d) $AP=75$ VA, $PF=.906$ lagging, $Q= 31.7$ VAR
- 11.45 360.85 μF
- 11.47 $S_{j30\Omega} = 88.4\angle 90^\circ$ VA $S_{10\Omega} = 20\angle 0^\circ$ VA
 $S_{15\Omega} = 3.54\angle 0^\circ$ VA $S_{-j25\Omega} = 5.9\angle -90^\circ$ VA
 $S_{\text{source}} = 85.85\angle 74.05^\circ$ VA
 $PF_{\text{source}} = 0.275$ lagging

Homework 5:

- 12.12 (a) $P_1 = 0.55$ W, $P_2 = 5.34$ W
(b) $P_{200\Omega} = 66$ W, $P_{50\Omega}=255.38$ W, $P_{10\Omega}=2.025$ W
(c) $PF = 0.954$
- 12.19 (a) $Z_P = 0.926 - 0.261j$
 $V_{an} = \frac{208}{\sqrt{3}}\angle -30^\circ$ V
 $V_{bn} = \frac{208}{\sqrt{3}}\angle -150^\circ$ V
 $V_{cn} = \frac{208}{\sqrt{3}}\angle 90^\circ$ V
(b) $V_{aA} = 208\angle 0^\circ$ V
 $V_{bB} = 208\angle -120^\circ$ V
 $V_{cC} = 208\angle 120^\circ$ V
(c) $I_{aA} = 216.19\angle 15.7^\circ$ A

$$I_{bB} = 216.19 \angle -104.3^\circ \text{ A}$$

$$I_{cC} = 216.19 \angle 135.7^\circ \text{ A}$$

$$(d) P = 129.84 \text{ kW}$$

$$12.21 \quad a) \quad \text{Power Factor} = 0.9688 \text{ leading}$$

$$b) \quad P = 22.76 \text{ kW}$$

$$c) \quad \text{Power Factor} = 0.9803 \text{ leading}, P = 18.36 \text{ kW}$$

$$12.31 \quad R = 0.66 \Omega$$


$$12.32 \quad I_{bB} = 36.08 \angle 95.54^\circ \text{ A}, V_{an} = (160/\sqrt{3}) \angle 240^\circ \text{ V}$$

$$12.34 \quad I_{aA} = 3.727 \text{ A}, I_{AB} = 2.152 \text{ A}, V_{an} = 176.91 \angle 20.73^\circ \text{ V}$$

Homework 6:

$$13.11 \quad V_2/V_1 = -2j\omega(4\omega^2 + (2+6j\omega)(1+4j\omega))$$

$$13.12 \quad (a)$$

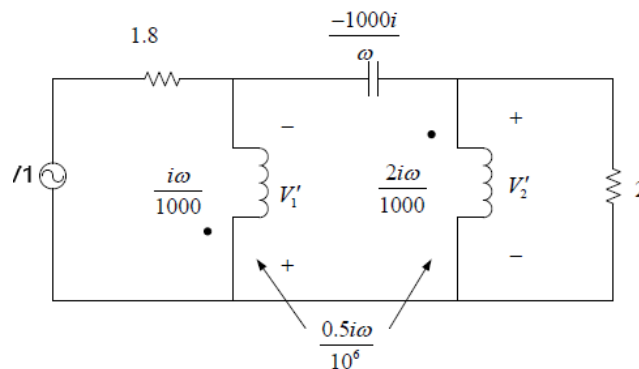

$$13.16 \quad v_{AG}(t) = -40 \sin t$$

$$13.18 \quad i_1(t) = 0.36 \sin(3t - 70.86^\circ)$$

$$i_2(t) = 0.126 \sin(3t + 176.82^\circ)$$

$$i_3(t) = 0.114 \sin(3t + 1.457^\circ)$$

$$13.21 \quad (a) \quad (4 - j5\omega)I_1 - j4\omega I_3 = 0$$

$$(6 + j5\omega)I_1 - j2\omega I_2 - 6I_3 = 0$$

$$-6I_1 - j4\omega I_2 + (11 + j6\omega)I_3 = 0$$

$$(b) \quad I_3 = -3.88 + j1.79$$

Homework 7:

- 13.31 155 nH, -25 nH, 38 nH
13.38 $v_o = -4.1 \cos 1000t - 4.5 \sin 1000t$
13.40 (a) $I_2 = 24/\sqrt{2} \angle 77^\circ$ A, $V_2 = 24 \angle 32^\circ$ V
(b) $I_2 = \text{infinity}$, $V_2 = 24 \angle 32^\circ$
(c) $I_2 = 8 \angle 98^\circ$ A, $V_2 = 12 \angle 118^\circ$ V
13.42 8.88 mW and 467 mW
13.45 $V_1 = -0.75$ V $V_2 = -45/26$ V
Power dissipated by 100 Ω , 4 Ω , 2 Ω and 2.7 k Ω are 15mW, 16.9mW, 0.562mW and 2.24mW, respectively
13.54 (b) $V_2 = -0.9973 \angle -15^\circ$ V, $P_{8\Omega} = 62.16$ mW

Homework 8:

- 14.2 (a) -1
(b) $0.2 \angle 110^\circ$
(c) $-0.5617 - j5.0769$
(d) $17.84 e^{-j(56.26^\circ + 2t)}$
14.11 (a) $\text{Re}[19 e^{5t + j84}]$
(b) $\text{Re}[19 e^{j84}]$
(c) $\text{Re}[19 e^{j84} e^{(-4 + j)t}]$
14.20 (a) $185.35 \angle -47.58^\circ$
(b) $185.35 e^{-3t} \cos(4t - 47.58^\circ)$ V
14.49 (a) $V(t) = 5i(t) + 5 \int i(t) dt$
(b) $I(s) = \frac{2}{5} \frac{1}{s+1}$
(c) $i(t) = \frac{2}{5} e^{-t} u(t)$
15.9 $V_s = 0.2s^*(2/(s+2) + 0.1)/(0.2s+1000)$
 $v(t) = 0.1\delta(t) - (498 e^{-5000t} - 0.0008e^{-2t}) u(t)$
15.11 $I_1(t) = (2.9 e^{-0.67t} - 0.6e^{-1.5t} - 2e^t)u(t)$
 $I_2(t) = e^{-1.5t}u(t)$
 $I_3(t) = (1.33 - 0.33 e^{-1.5t})u(t)$

15.19 $i_1(t) = 936 \cos 2t - 270 \sin 2t$

Homework 9:

16.4 (a) 0.5

(b) 62.7 and 159.5 rad/s

16.10 $B = 210.8 \text{ rad/s}$

(a) 47.42 Ω

(b) 25.8 $\angle 57^\circ \Omega$

(c) 44.7 $\angle -20^\circ \Omega$

(d) 4.3 $\angle 85^\circ \Omega$

16.15 (a) 750k Ω

(b) $i(t) = 3.92 \cos (4.25 * 10^6 t - 89.99^\circ)$

16.31 Sketch the plots

16.40 Design problem (many possible solutions)

16.41 Design problem (many possible solutions)

Homework 10:

17.11
$$Y = \begin{bmatrix} 11 * 10^{-4} & -10^{-4} \\ -10^{-4} & 1/8000 + 1/10000 \end{bmatrix}$$

17.33
$$Z = \begin{bmatrix} 125 & 25 \\ 25 & 75 \end{bmatrix}$$

17.41
$$h1 = \begin{bmatrix} 50 \text{ ohms} & 1 \\ -1 & 40\text{ms} \end{bmatrix}$$

$$h2 = \begin{bmatrix} 1.67 \text{ ohms} & 0.67 \\ -0.67 & 13.3\text{ms} \end{bmatrix}$$

17.53 (a)
$$\begin{bmatrix} 16.8 & 1.87 * 10^4 \\ 0.004 & 4.2 \end{bmatrix}$$

$$(b) \begin{bmatrix} 6.67 & 1.14 * 10^4 \\ 8.26 * 10^{-3} & 1.43 \end{bmatrix}$$