



Power Electronics for Grid Applications

Fred Wang, UTK/ORNL

fred.wang@utk.edu

March 8, 2024




Northeastern



Rensselaer



TUSKEGEE

Traditional Power Grid Equipment

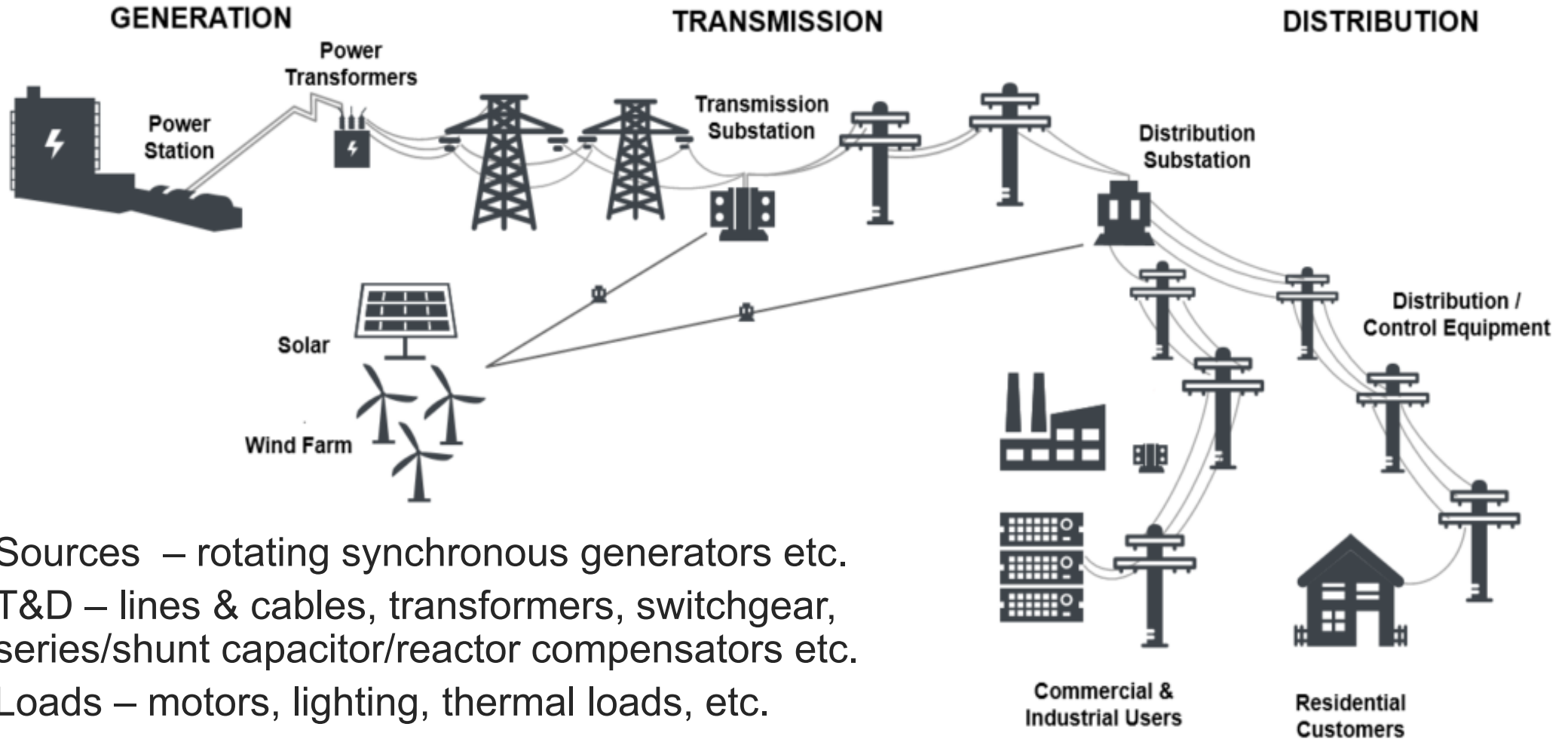

- Sources – rotating synchronous generators etc.
- T&D – lines & cables, transformers, switchgear, series/shunt capacitor/reactor compensators etc.
- Loads – motors, lighting, thermal loads, etc.
- Limited power electronics

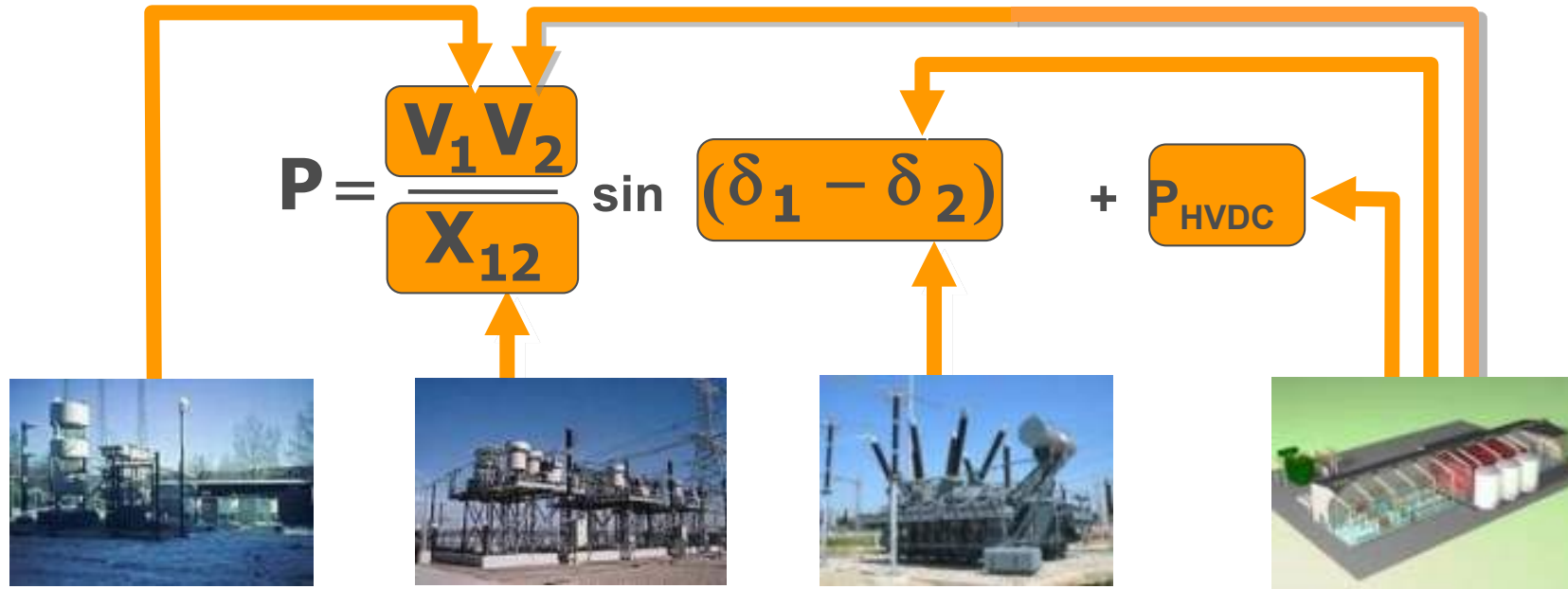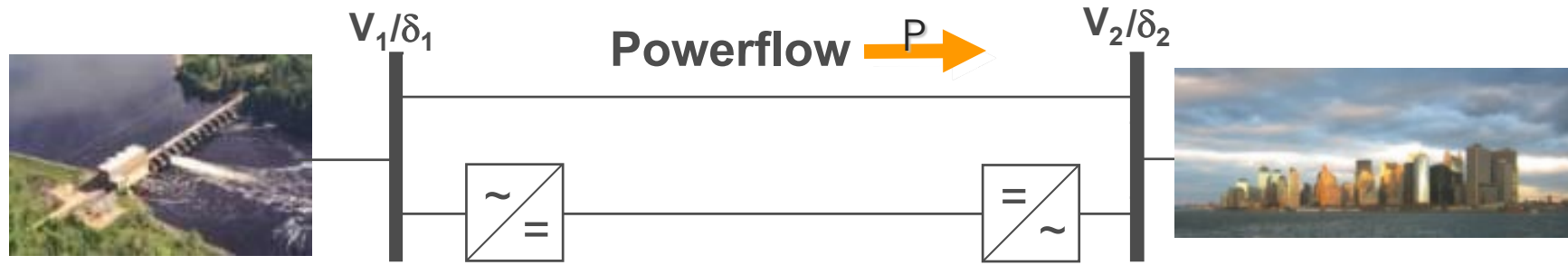Power Transfer in Grid - From “AC vs DC” to “AC and DC”



Shunt Compensation


Series Compensation

Phase Shifting Transformers


HVDC

Power Electronics for AC Transmission – Flexible AC Transmission Systems (FACTS)

- Series connected compensators

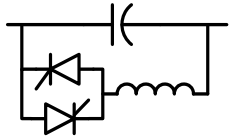


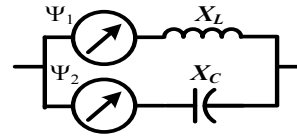Thyristor-controlled series compensator (TCSC)




Ψ_1 and Ψ_2 are phase-shift elements

Interphase power controller (IPC)

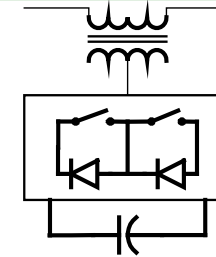


Static synchronous compensator (STATCOM)


- Shunt connected compensators

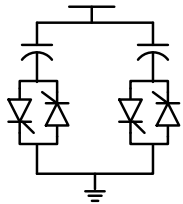


Thyristor-switched capacitor (TSC)

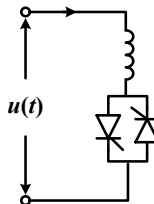

Thyristor-switched reactor (TSC)

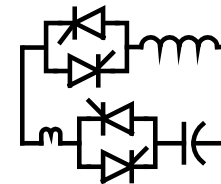


Static var compensator (SVC)

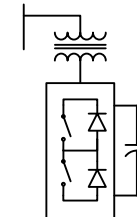


Static synchronous compensator (STATCOM)

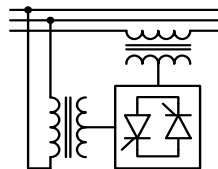- Series and shunt connected compensators



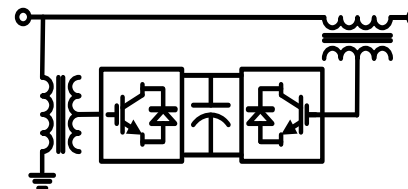Thyristor-controlled phase shifting transformer (TCPST)




Unified power flow controller (UPFC)


Conventional FACTS mostly based on Si thyristor technology, with limited performance and capabilities

Power Electronics for AC Distribution – Custom Power


- Power flow control and interruption

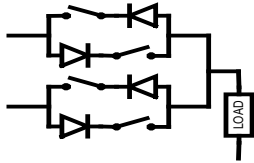

Solid-state transfer switch (SSTS)

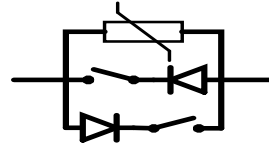


Solid-state circuit breaker (SSCB)

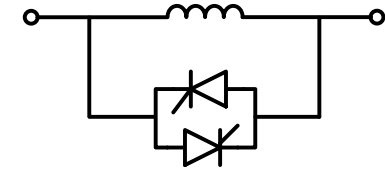


Solid-state fault current limiter (SSFCL)

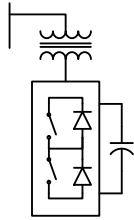
- Power system conditioning and compensation



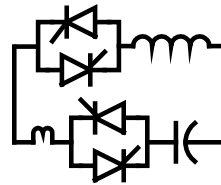
Distribution static synchronous compensator (DSTATCOM)



Static var compensator (SVC)

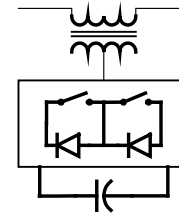


Dynamic voltage restorer (DVR)

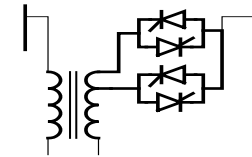


Thyristor-controlled voltage regulator (TCVR)

- Power quality enhancement

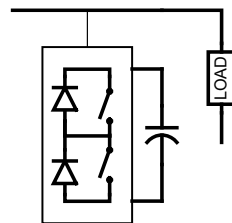


Active power filter (APF)

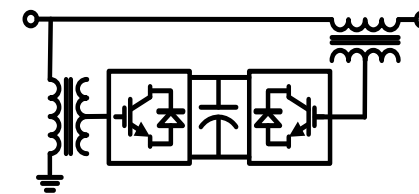


Unified power quality conditioner (UPQC)

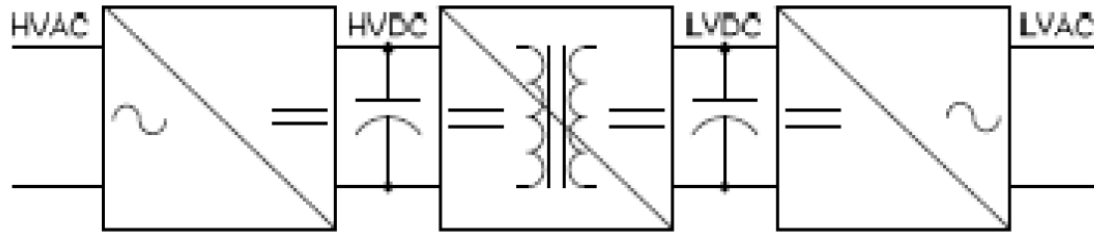
Power Electronics for T&D – More Recent Development




Solid-state transformer

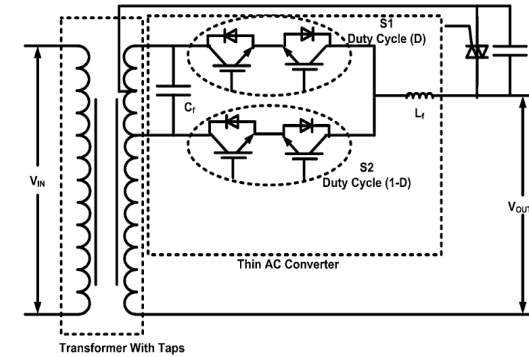

Controllable network transformer

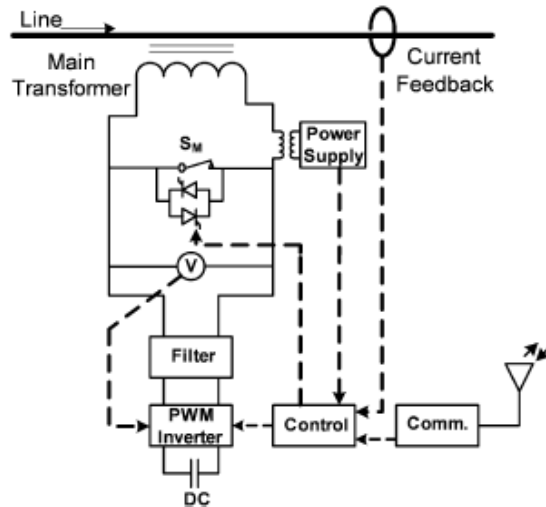


Distributed static series compensator

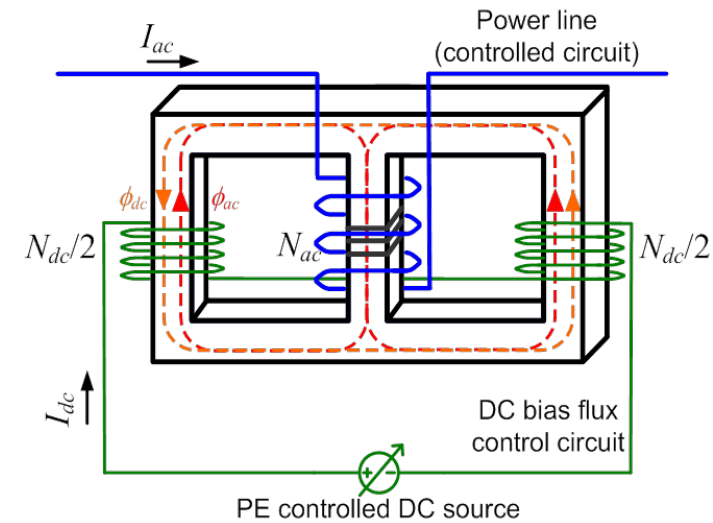


Continuously variable series reactor (CVSR)

Grid Power Electronics – Sources and Loads

- Renewable energy source interface

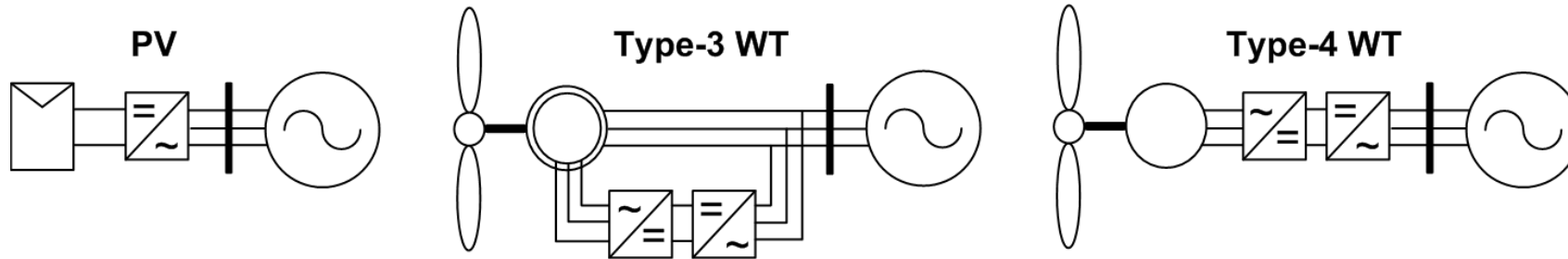


- Energy storage systems

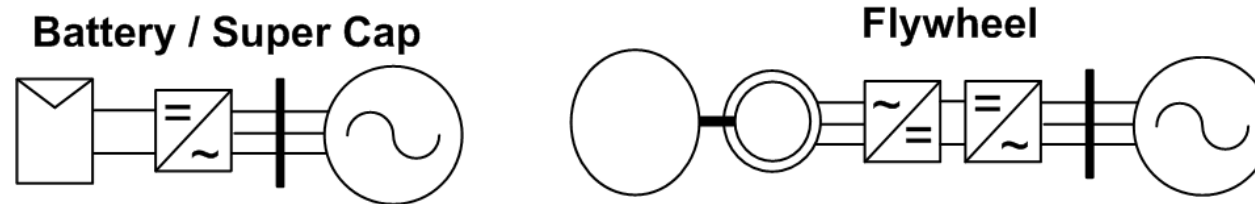


- Power electronic loads: data center, EV charging station, large motor drive

Microgrids

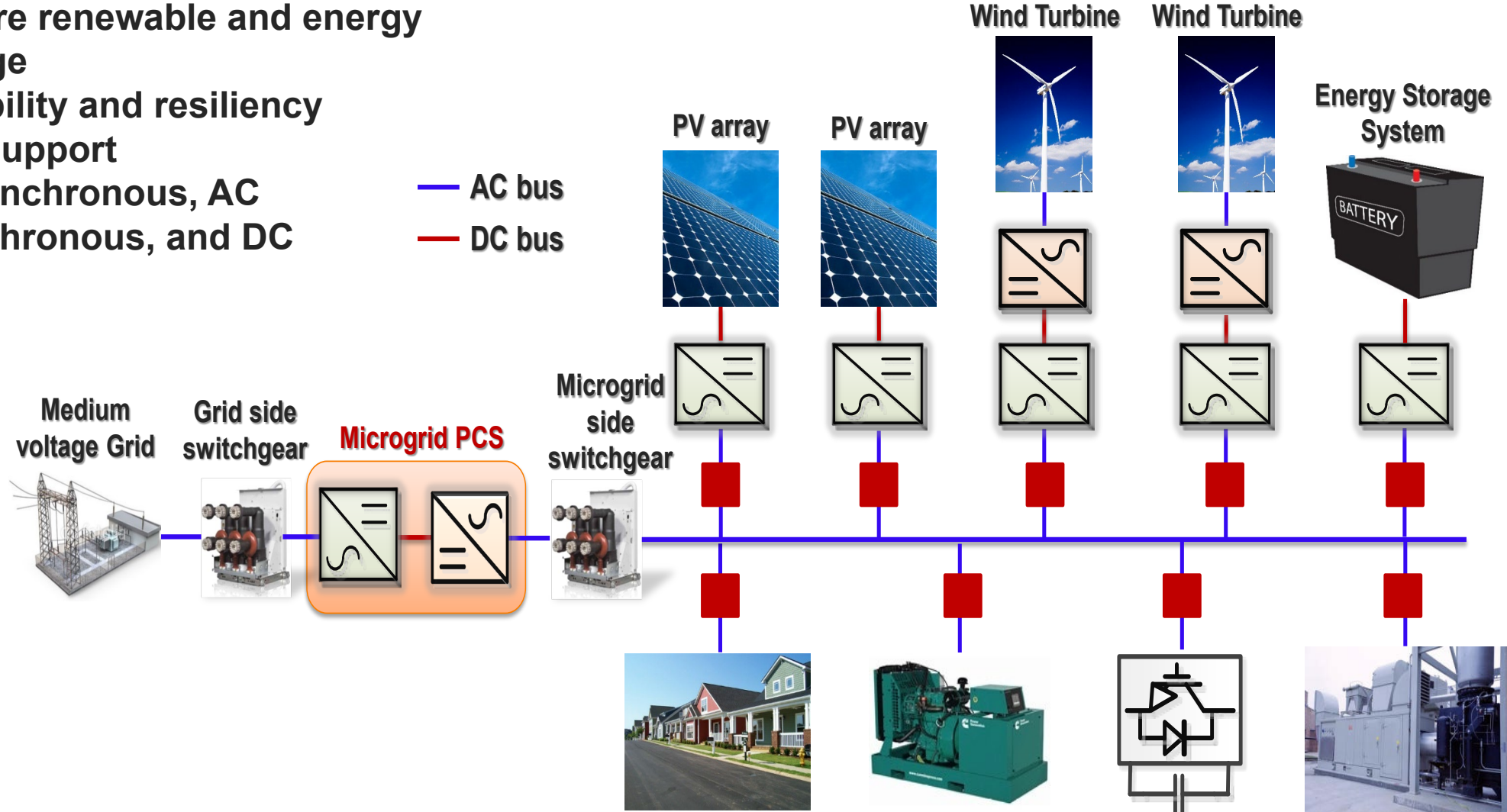- Feature renewable and energy storage
- Reliability and resiliency
- Grid support
- AC synchronous, AC asynchronous, and DC




AC and DC Transmission Principles

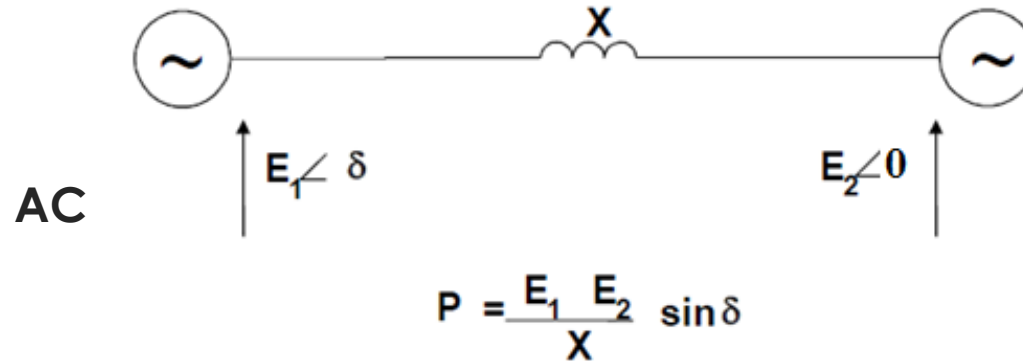

Compared with AC, the main features of DC transmissions:


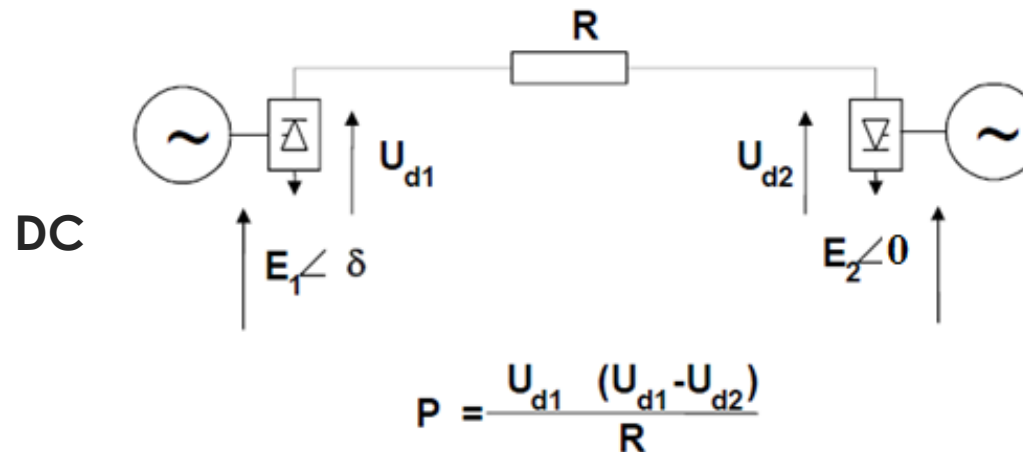
- Long distance
- Asynchronous interconnection
- Controllability



DC does require AC/DC converters and other associated equipment

- Filters and var compensators
- Communications
- Special transformers






HVDC vs. HVAC Cost

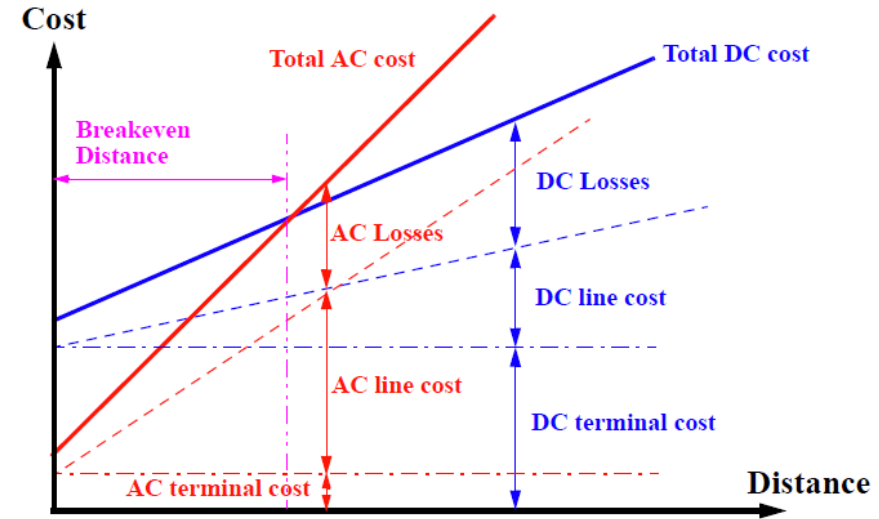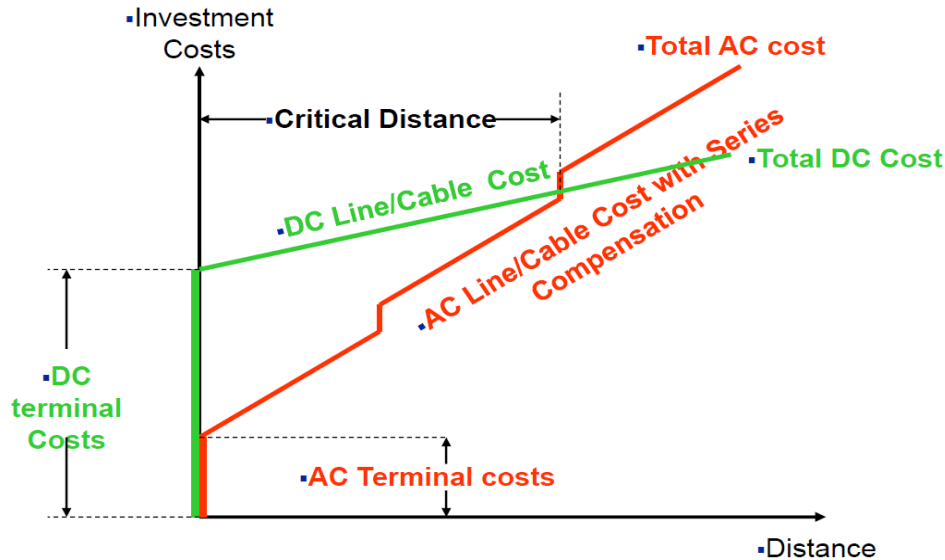

- There is a breakeven or critical distance beyond which the DC scheme will be more economical
- The breakeven distance depends on many factors. For overhead lines in the range of several hundred of miles (300 to 500); for cables, in the range of tens of miles (30 to 60 miles)

HVDC Converter – Principle of Load Commutated Converter (LCC)


Thyristor or SCR

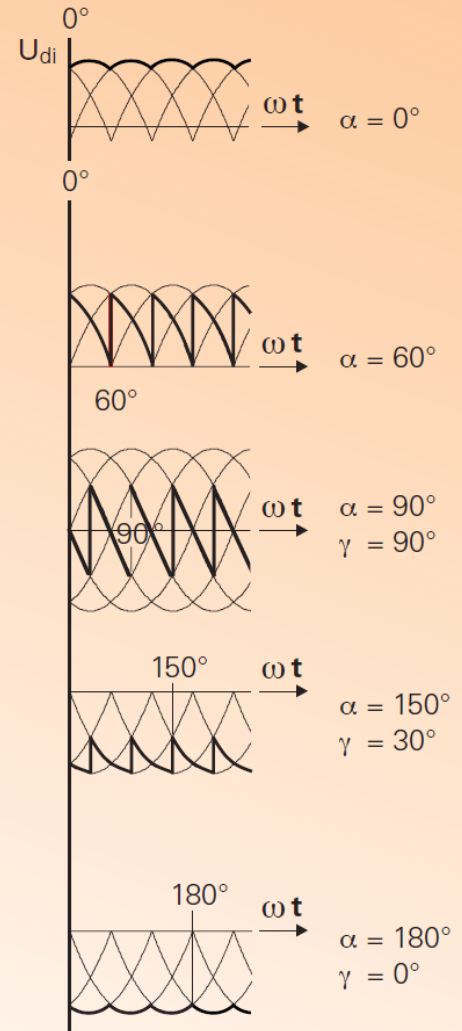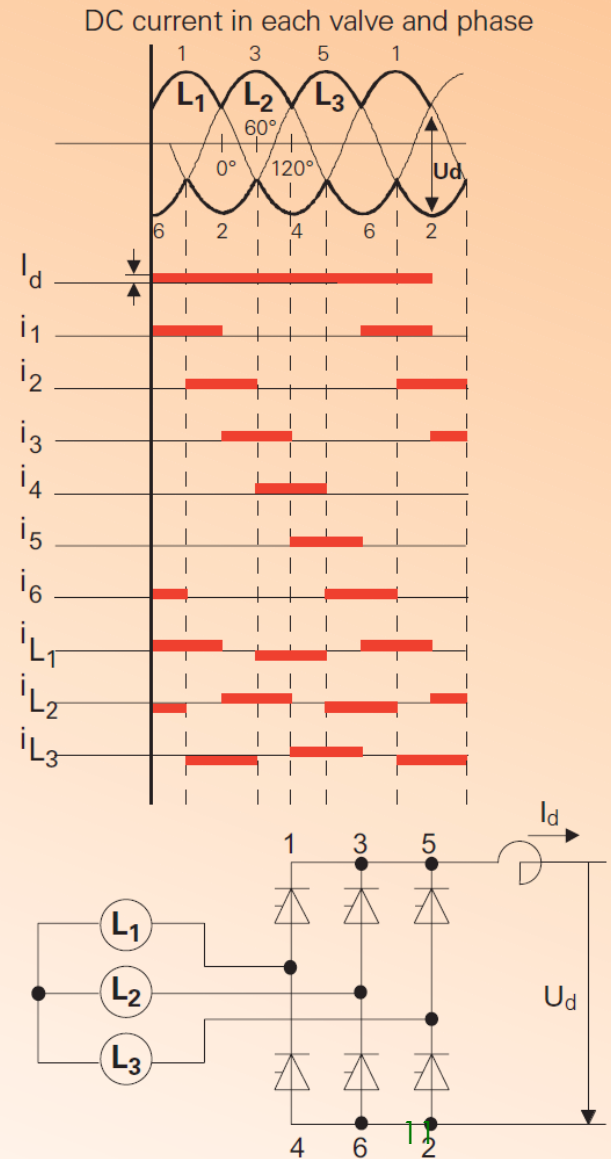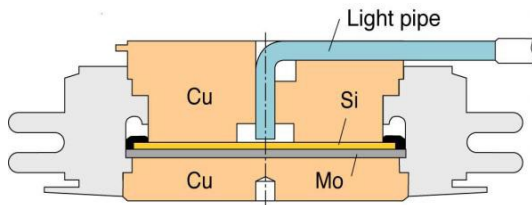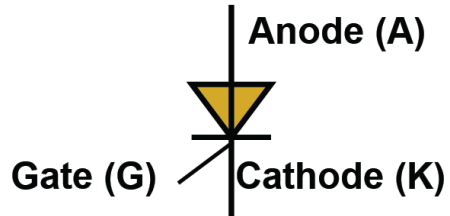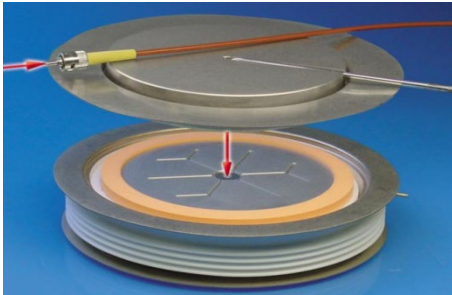



Six Pulse LCC Converter Bridge and Its Operation

HVDC Converter – Principles of Voltage Source Converter (VSC)


VSC – Voltage Source Converter

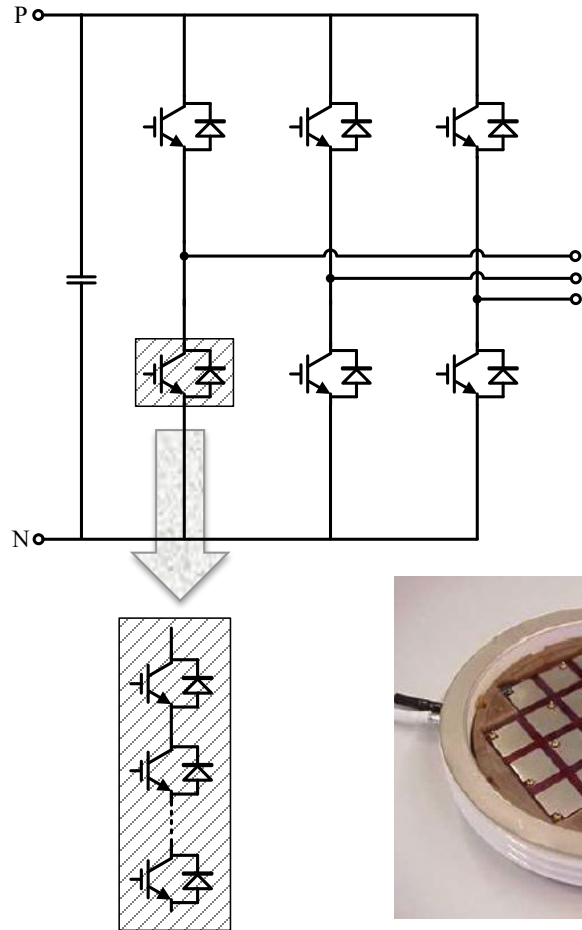

Pulse Width Modulation (PWM) Control

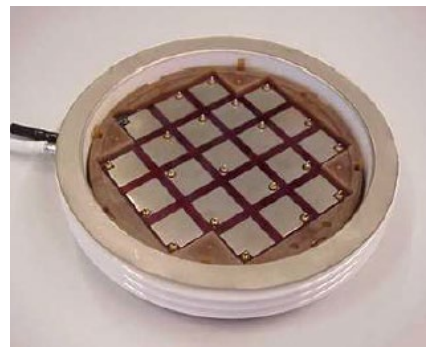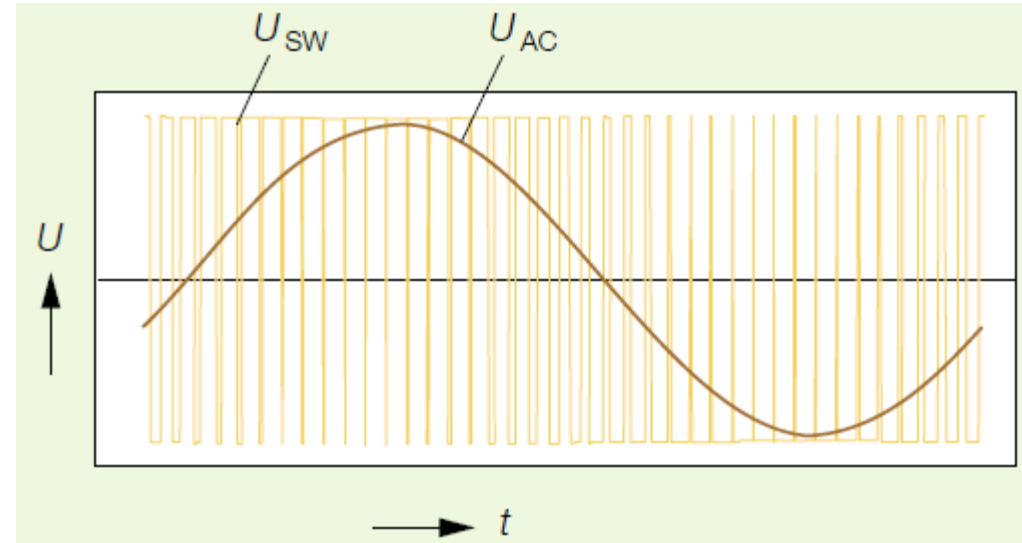

IGBT

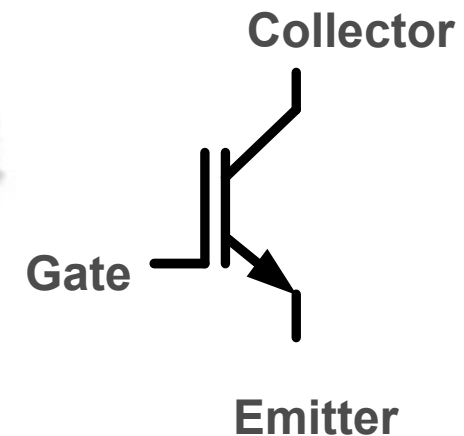

HVDC Technology Development

**Mercury Arc Valve
HVDC (Phased out)**



1954

Pros: Low losses
Cons: Reliability
Maintenance
Environment


**Thyristor Valve
HVDC Classic**



1970

Pros: Reliable
Scalable
Cons: Footprint

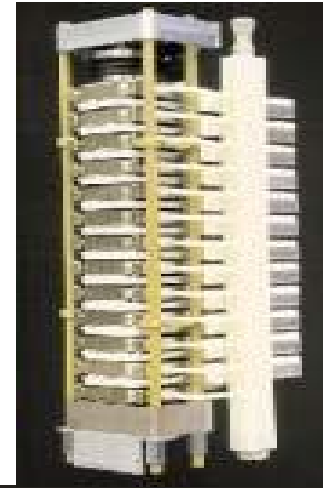**IGBT (Transistor)
HVDC Light (VSC HVDC)**




1980

2000


Year

Pros: Controllability
Footprint
DC Grids
Cons: Losses

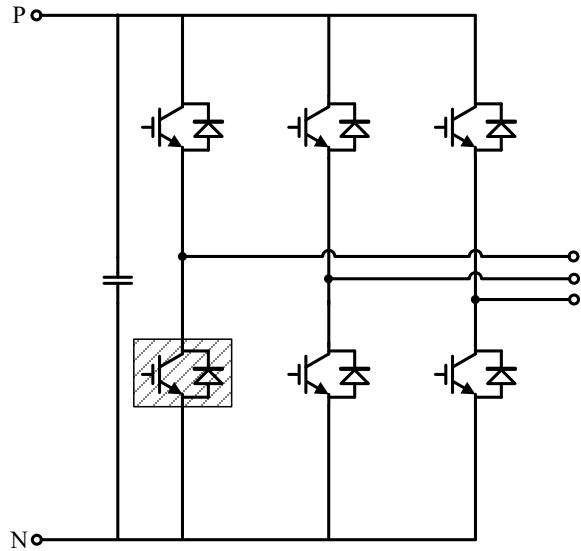
HVDC Technology Evolution: Voltage Source Converter (VSC) Topologies



Two-level

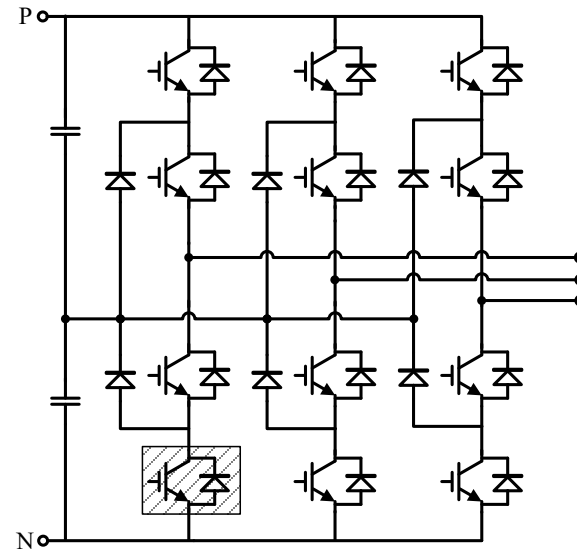



Three-level (NPC)

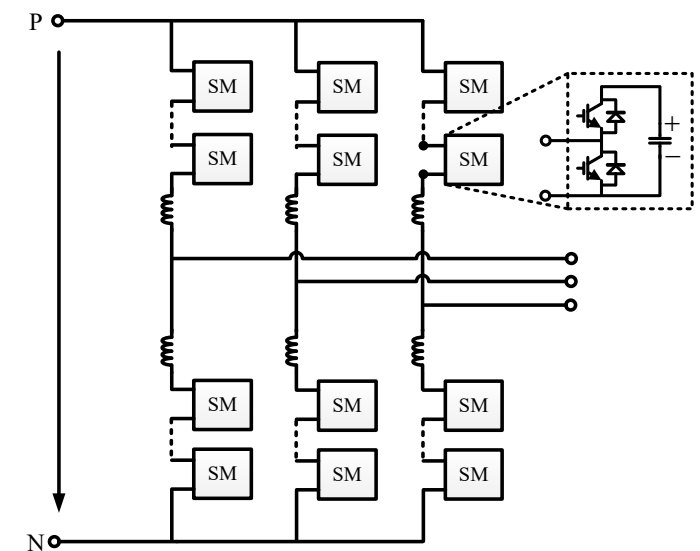

Modular multi-level converter (MMC)


- VSC based on switching devices (IGBT/IGCT), with better performance than thyristor based LCC, and significantly reduced converter station footprint and less right-of-way
- MMC latest generation of VSC topology: low loss, and no series devices

MMC VSC vs. Conventional VSC

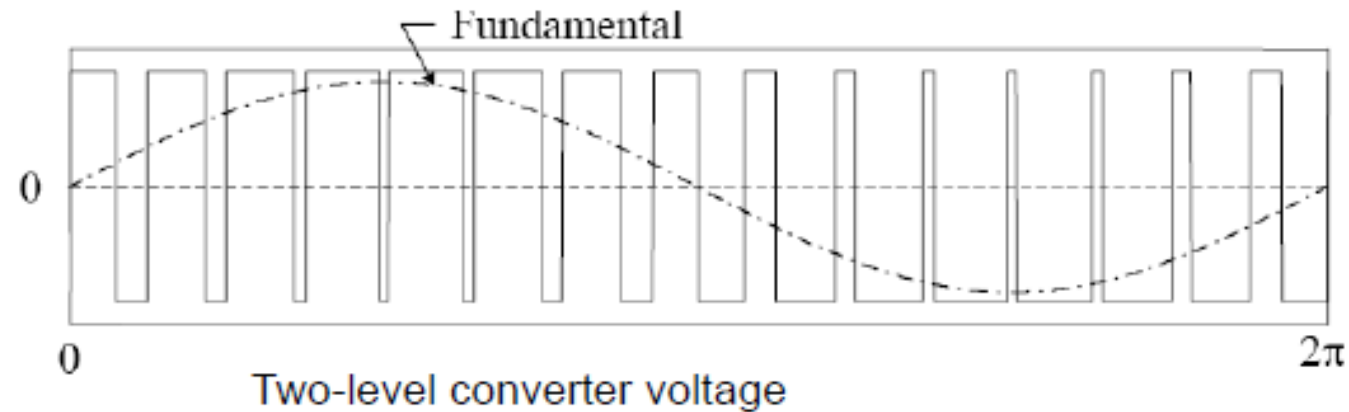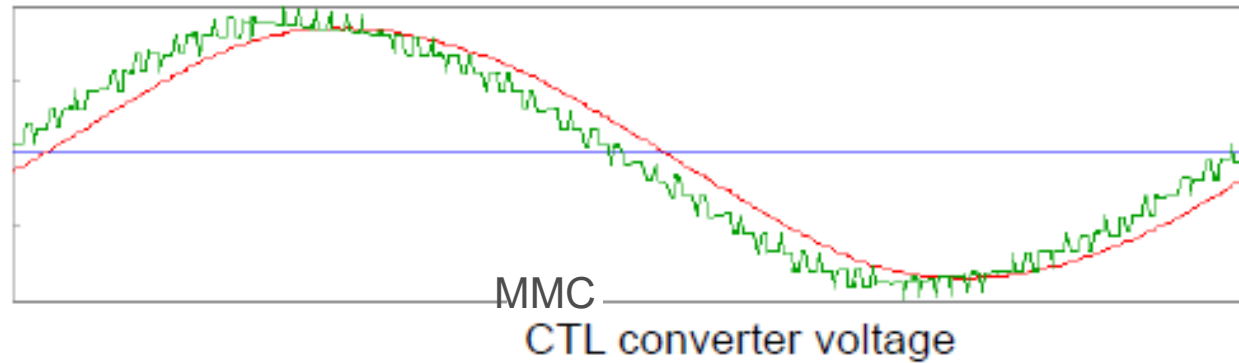



Technology Evolution – VSC Efficiency

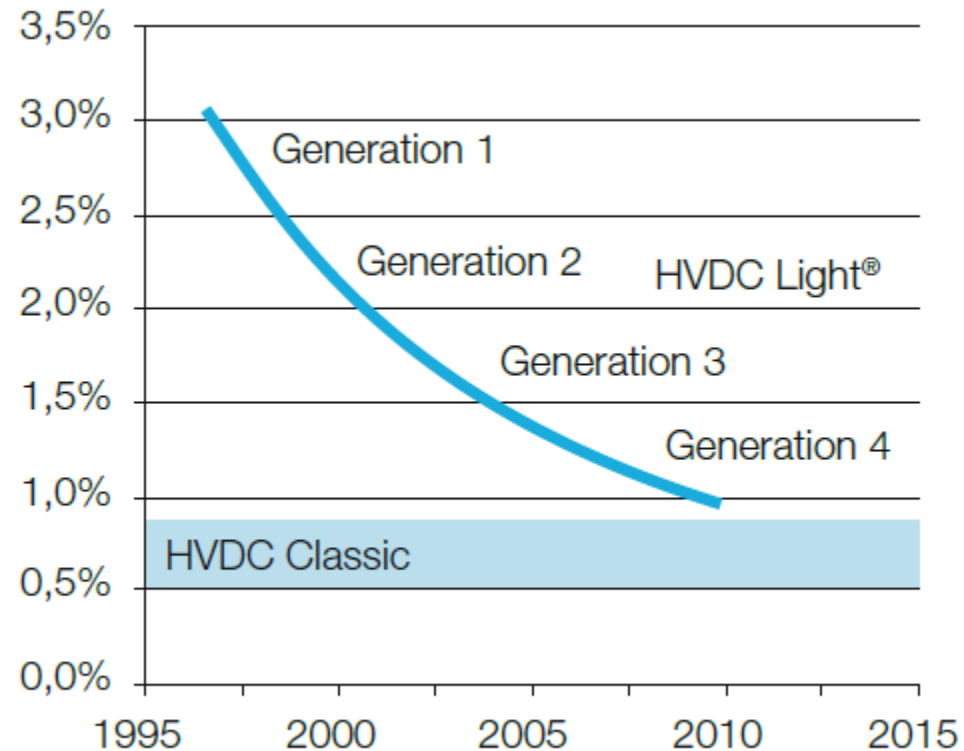- Generations 1-3 adopt the two-level converter and 3-level converter
- Generation 4 adopts MMC, and the converter efficiency is comparable to LCC HVDC




HVDC System Types


- Point-to-point transmission

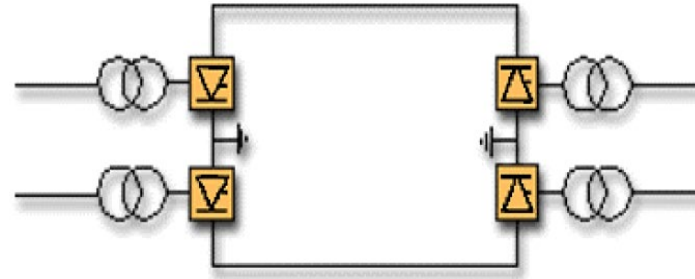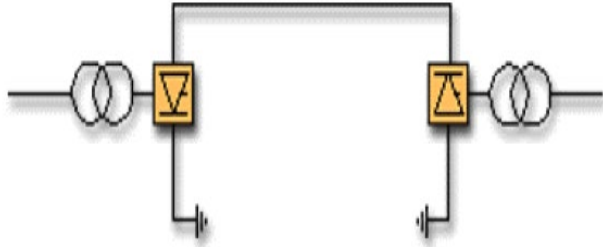

- Back-to-back system

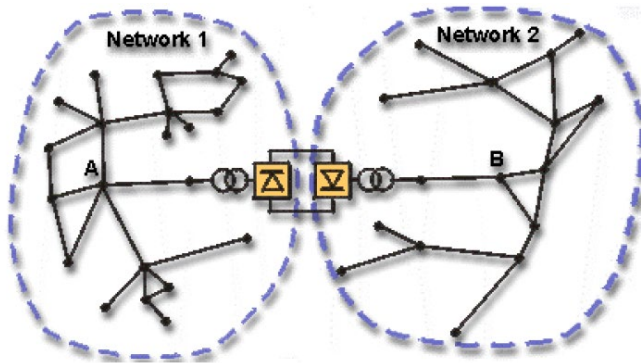

- Multi-terminal system

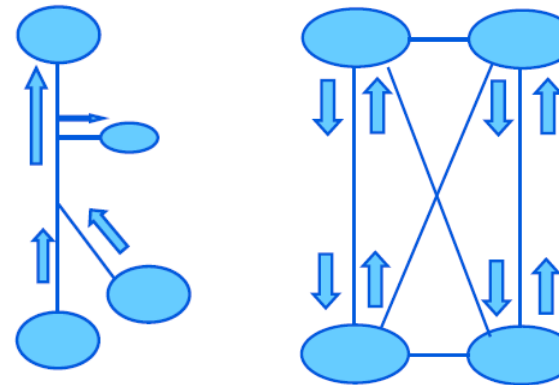


HVDC more economical for long-distance transmission; HVDC can decouple dynamics of AC systems, benefiting system stability and protection

Summary of HVDC Benefits

- Long distance bulk power transmission
- Asynchronous interconnections
- Lower cost for cable transmission (subsea, offshore)
- AC system support
 - Controllability (including damping, f support, power flow and voltage control)
 - Limitation of faults
 - Low short-circuit current contribution
- Better use of right-of-way
- Environmental benefits (corona, noise, etc.)

Better Use of Right-of-Way

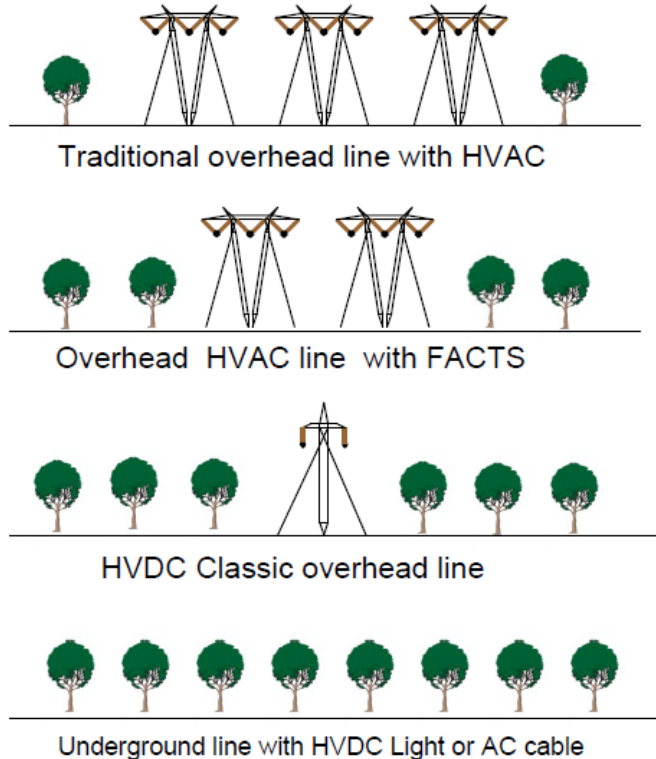Different technologies: Same power transmitted



Based on information from ABB

Several aspects on this point:



- For the same power transmitted, HVDC requires less right-of-way
- For the same right-of-the-way, HVDC can transfer more power
- With the same lines, HVDC can have lower loss

Disadvantages and Issues with HVDC

- High cost and complex converters
- Converters generate harmonics
- LCC HVDC require large var compensation and filters
- Challenges on grounding electrodes and converter transformers
- Difficulty of breaking DC current (DC breaker)


VSC HVDC Protection – Challenge

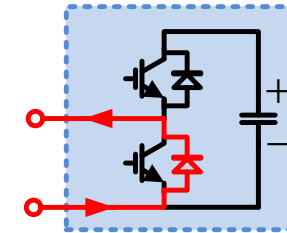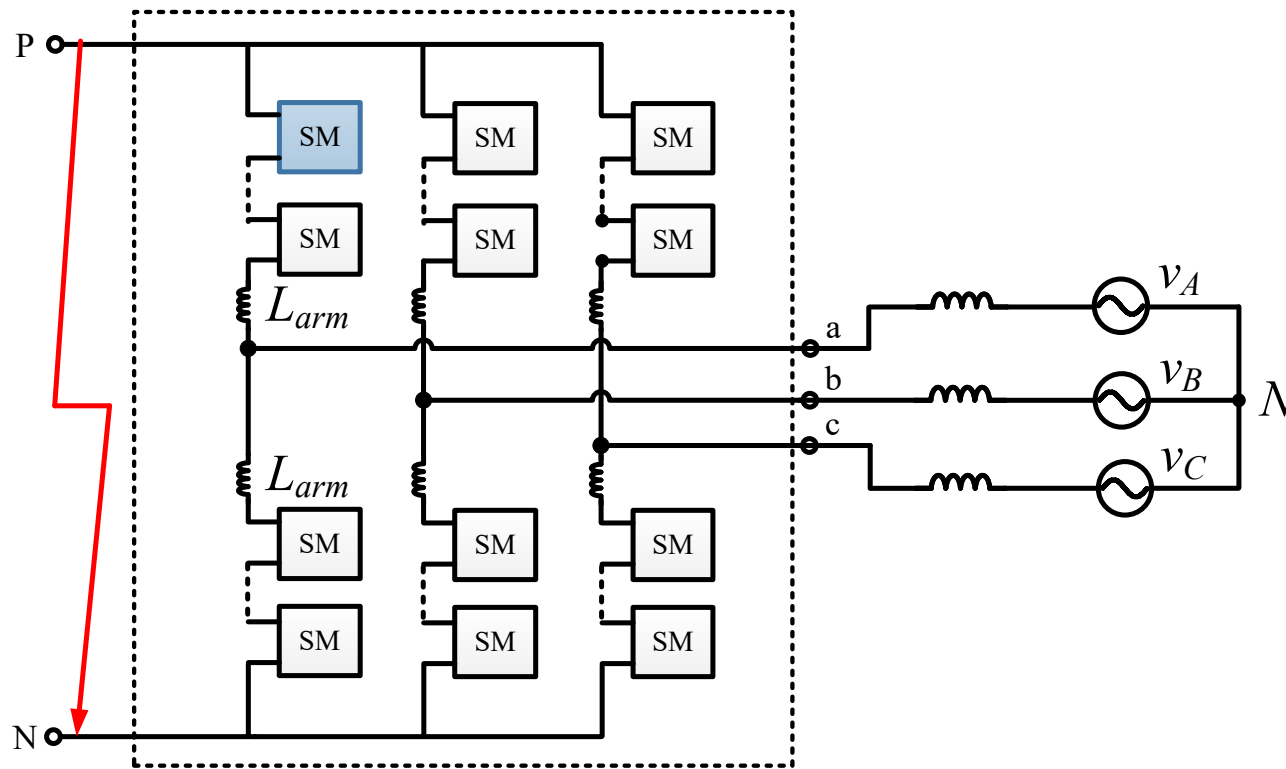- VSC is vulnerable to DC side short circuit fault, as the fault current can still flow through the diode after IGBT switches turned off
- DC current is difficult to clear without zero-crossing





VSC HVDC DC Fault Protection – Solution

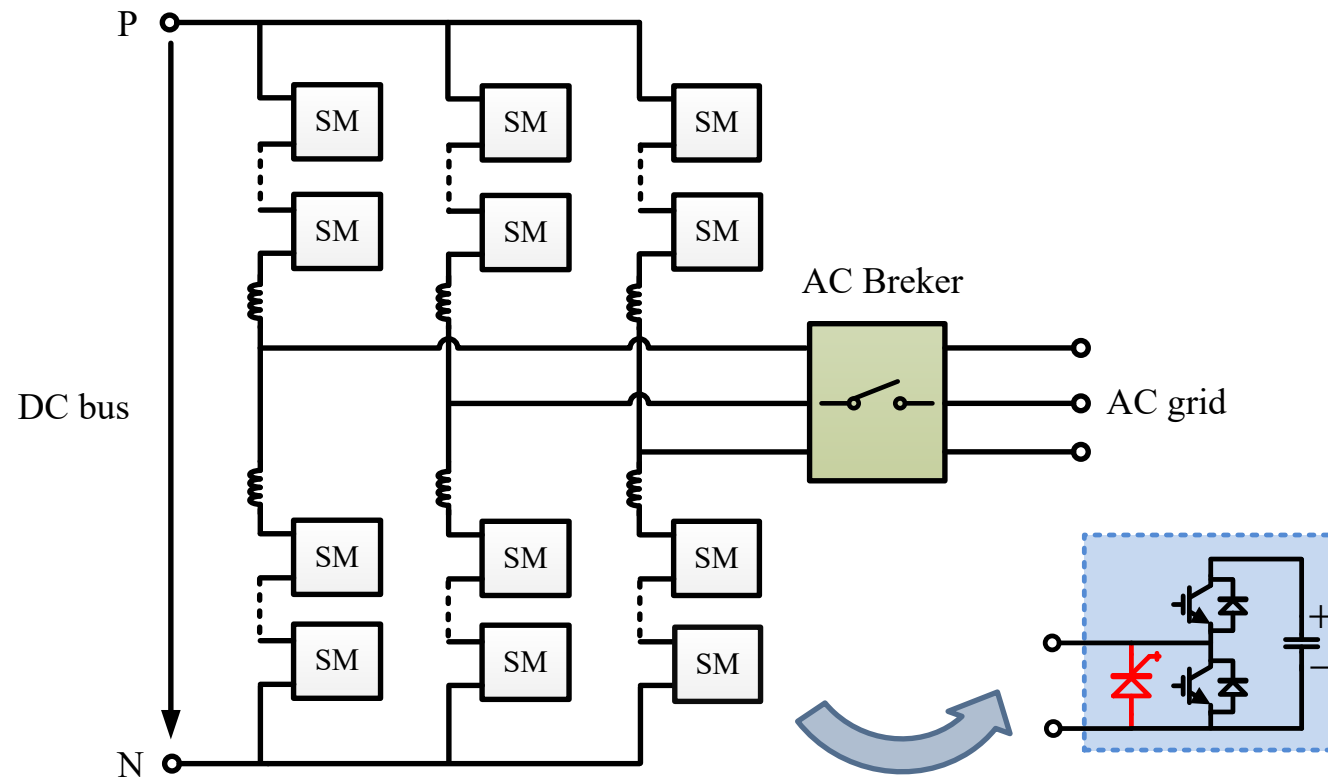- State of art solution: AC breaker + bypass thyristor (if necessary)
- 100 ms to clear the fault, and 2 s to restart the system




VSC HVDC DC Fault Protection – Solution

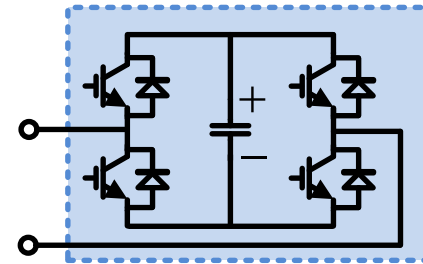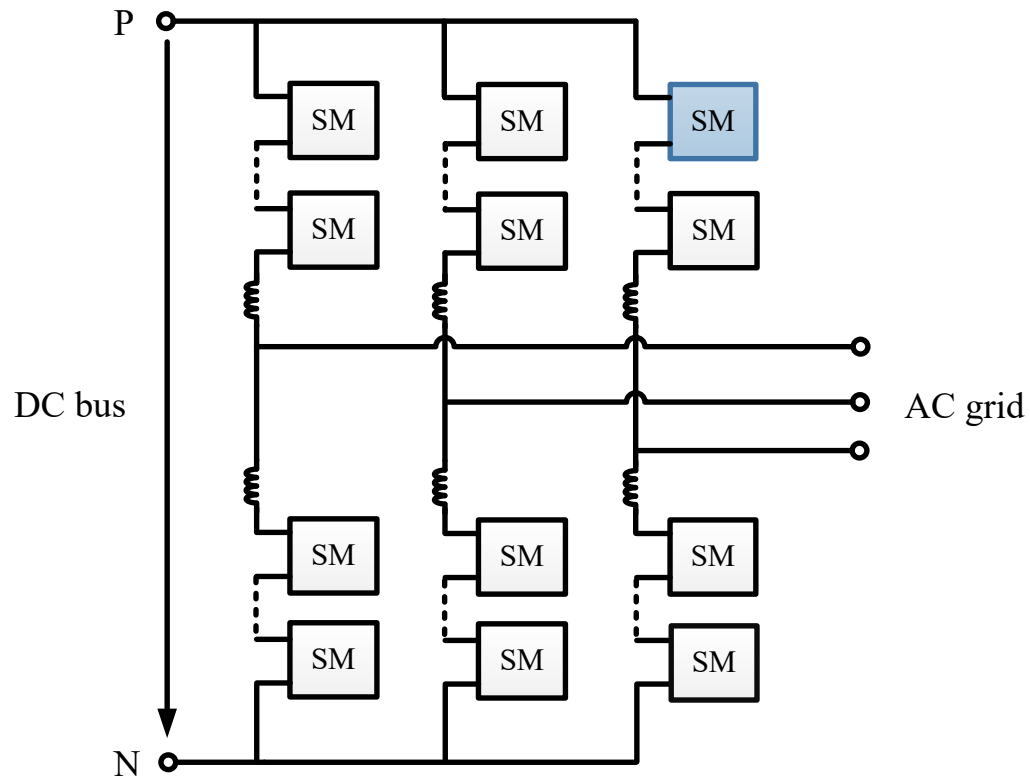- Fast fault clearance solution (<5 ms)
 - ❖ Siemens method: MMC with fault blocking sub-module




OR

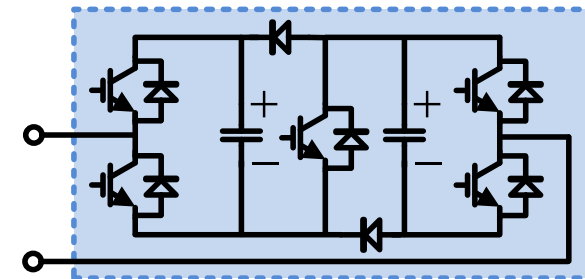


VSC HVDC DC Fault Protection – Solution

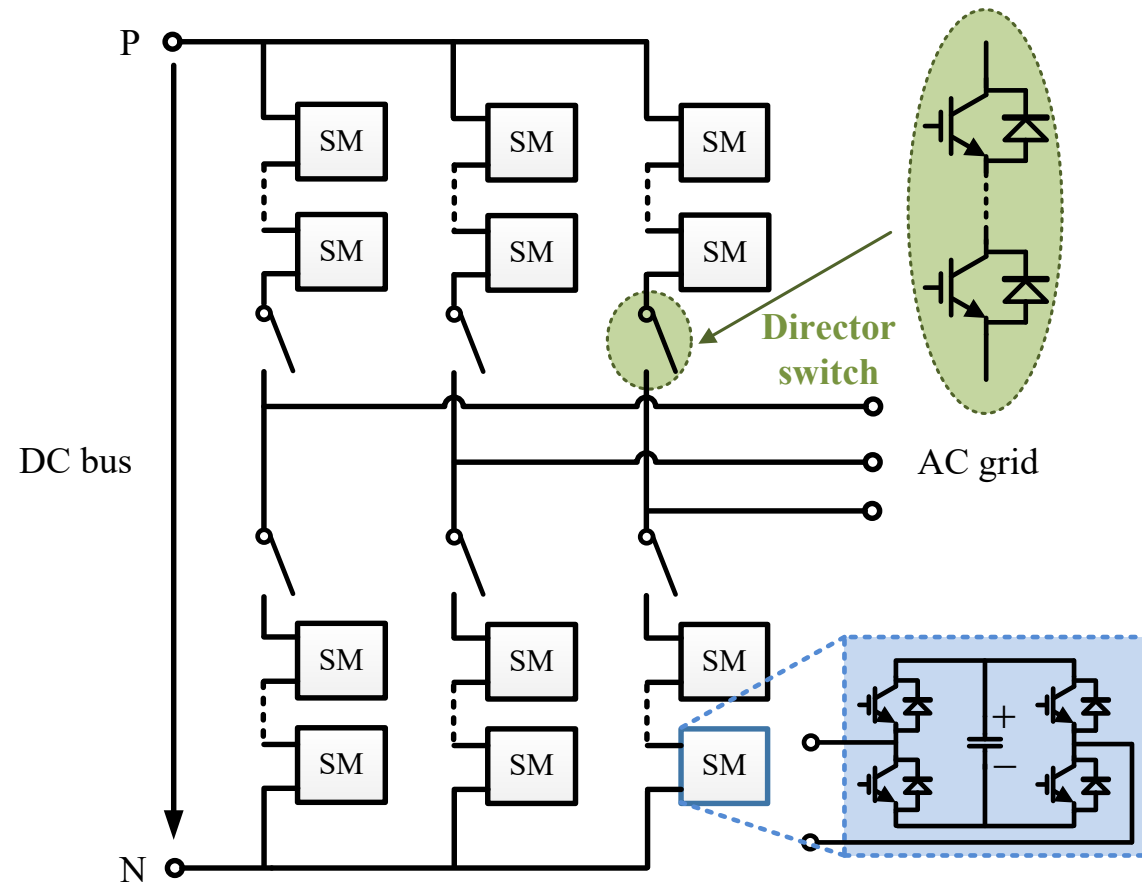- Fast fault clearance solution (<5 ms)
 - ❖ GE/Alstom method: hybrid MMC




VSC HVDC DC Fault Protection – Solution

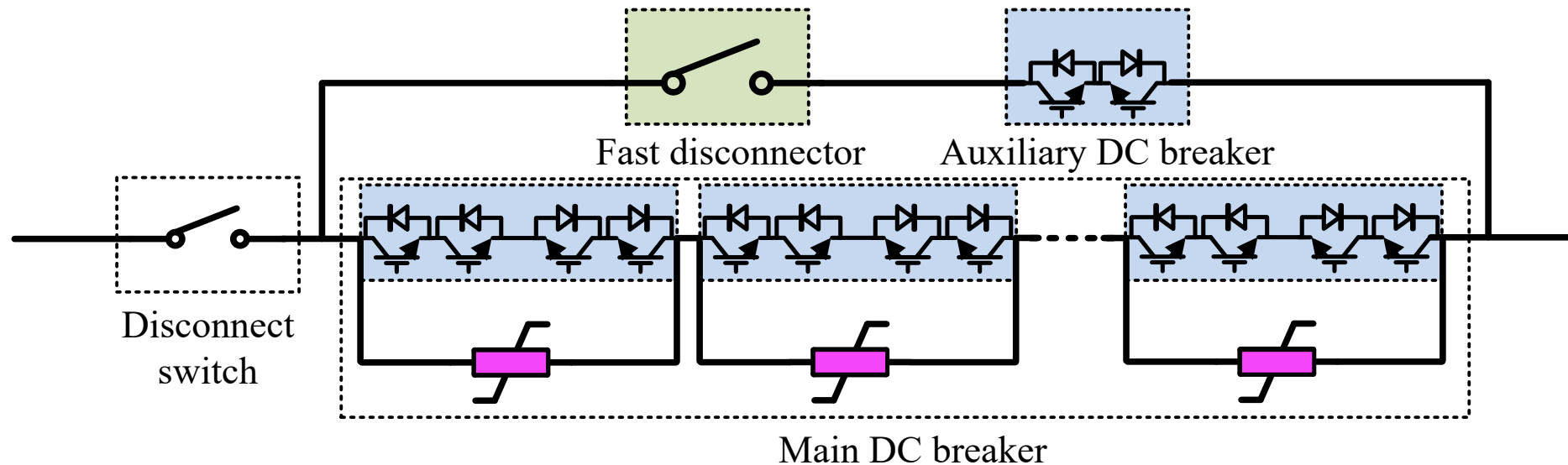- Fast fault clearance solution (<5 ms)
 - ❖ Hitachi/ABB method: Hybrid DC breaker




Hybrid AC/DC System

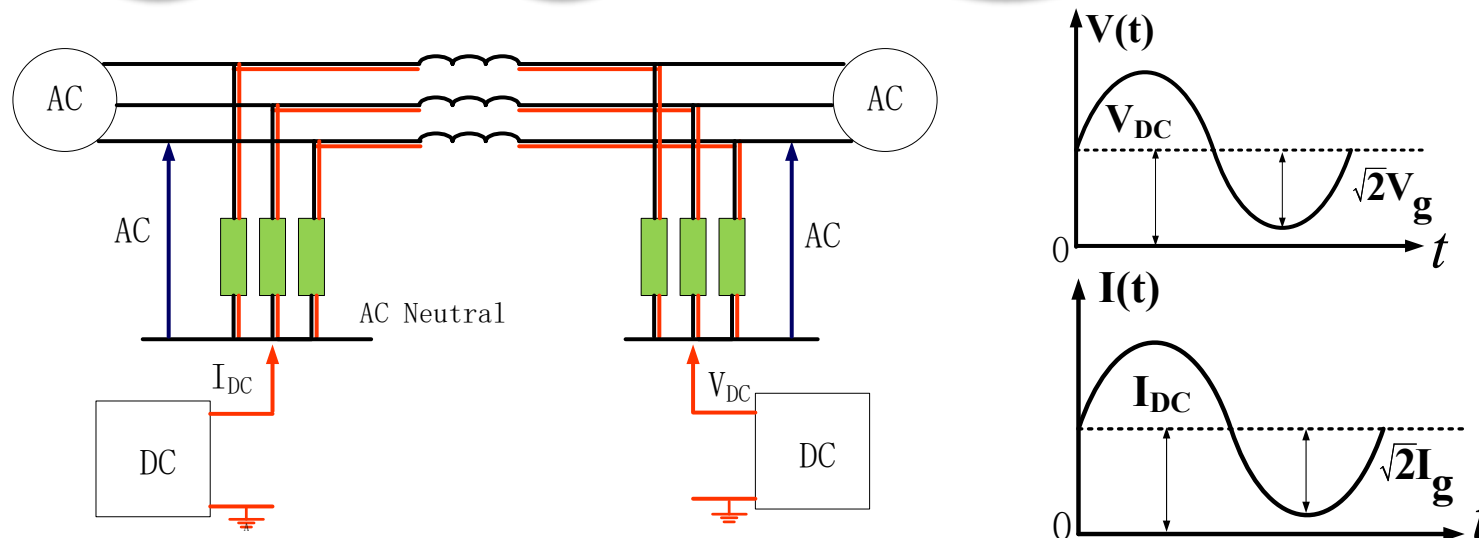Objective: Upgrade existing AC lines to hybrid AC and DC lines, to expand the power transmission capability




Basic Concept of Hybrid AC/DC System

System topology:

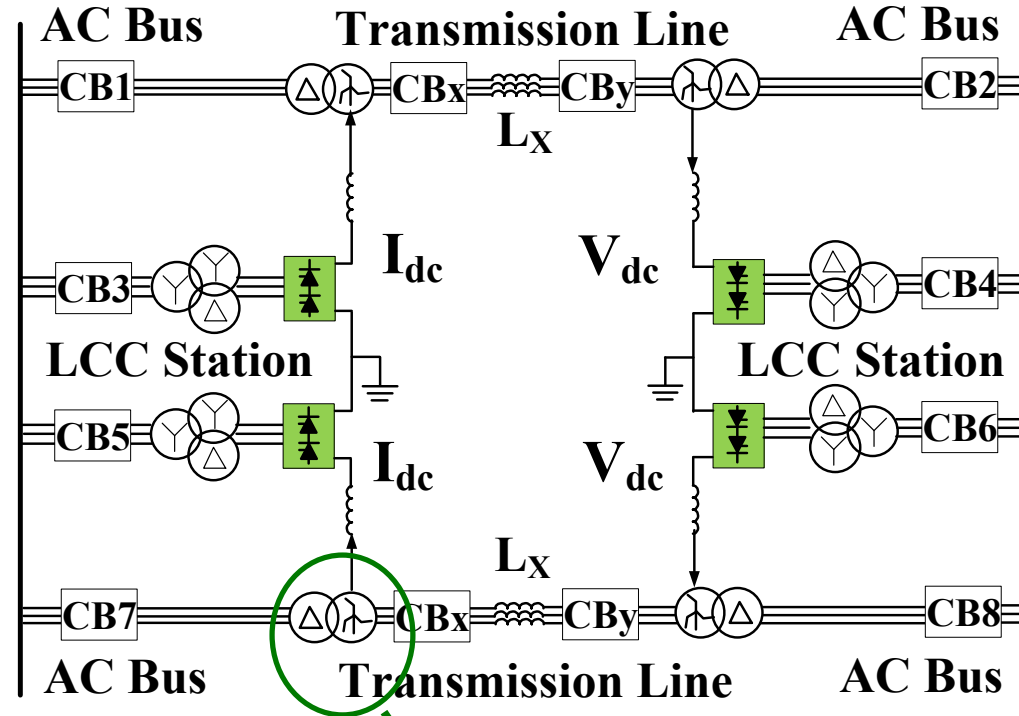



DC injection link: zigzag transformer

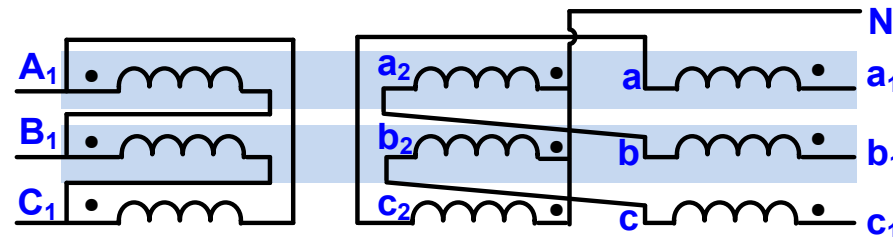

Benefits and Issues

Benefits:

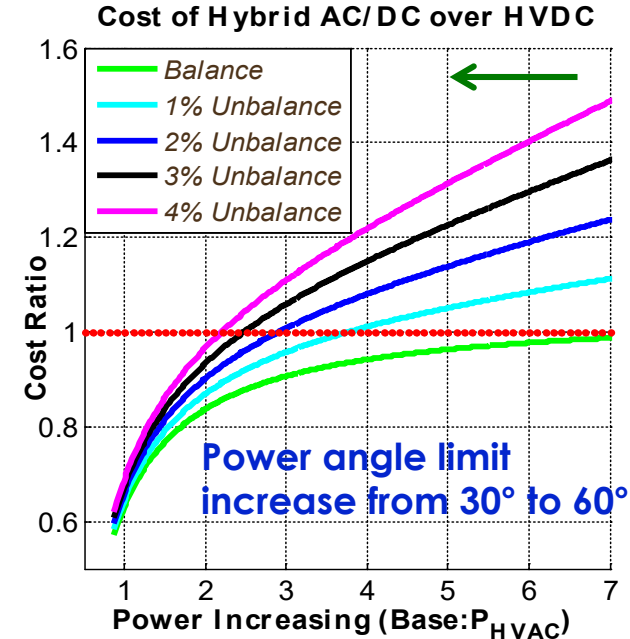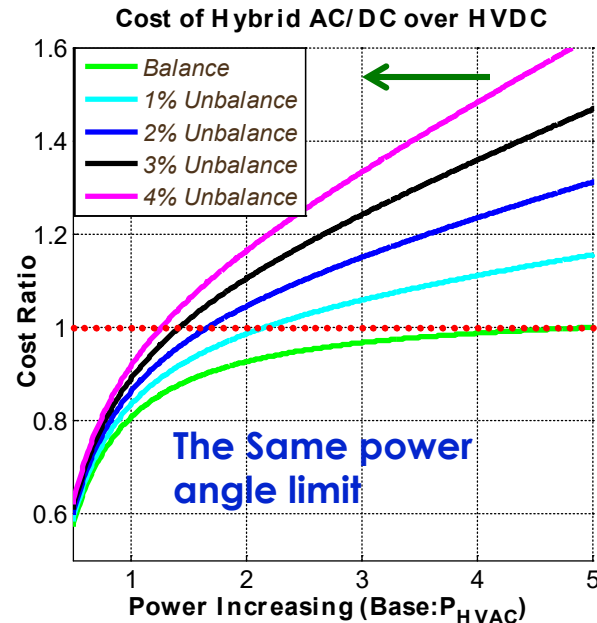- A lower cost solution for increased power transfer and improved stability







Issues:

- **Zigzag transformer may be saturated with unbalanced AC line resistance, due to the uncanceled DC flux within zigzag windings.**
- Neutral point of zigzag transformer needs extra insulation to withstand dc bias voltage

Method 1: Design Tolerance Margin

Method 1: DC tolerance design


- Can tolerate a certain unbalance range ($\pm\beta$)
- To tolerate more unbalance will cause more power loss and/or VAR loss
- Effective AC flux density is reduced, lead to higher cost

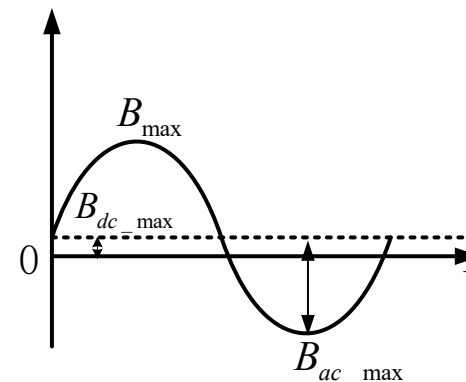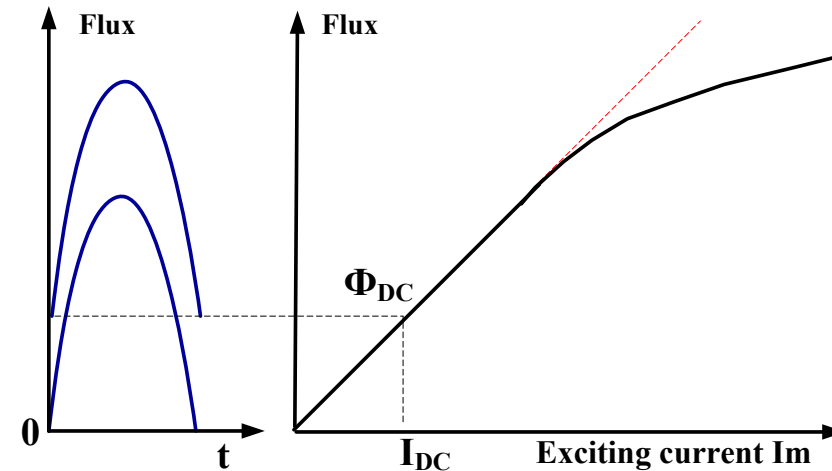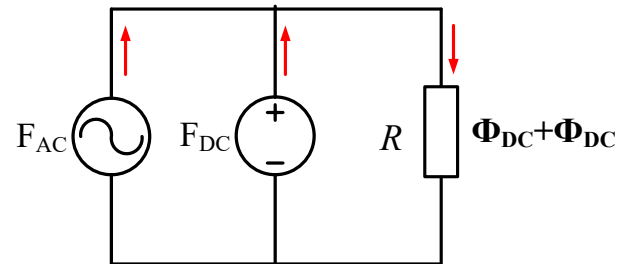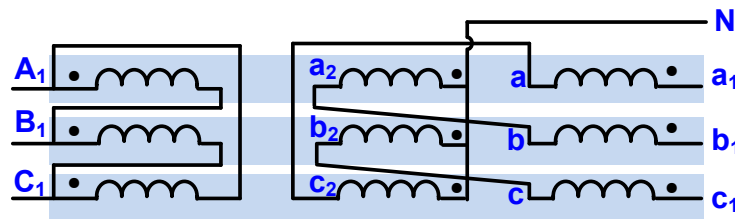

Method 2: Adjust Transformer Turns

Method 2: DC flux cancelation design by adjusting turns

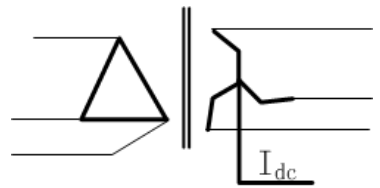- Less power or VAR loss compared to method1 for the same rating
- Cost closest to normal AC transformer.
- Introduces a certain extra voltage unbalance
- Sensitive to real-time unbalance




$$N_{z1}I_{a_DC} - N_{z2}I_{b_DC} = 0$$

$$\frac{N_{z1}}{N_{z2}} = \frac{I_{b_DC}}{I_{a_DC}}$$

For a general design: use tap changers for each winding

Impacts on method 2

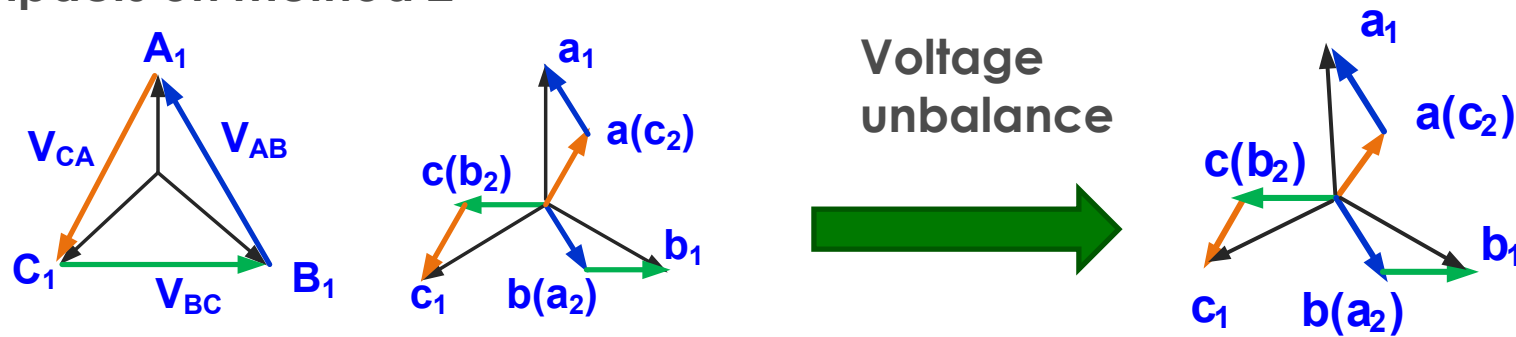


Method3: Active Unbalance Mitigation

Method 3: Hybrid line balance control

- Immunity to unbalance
- Low voltage rating, no insulation issue
- Active impedance with low loss
- With extra converter cost, but low compared to main HVDC converters

Hybrid line impedance conditioner:

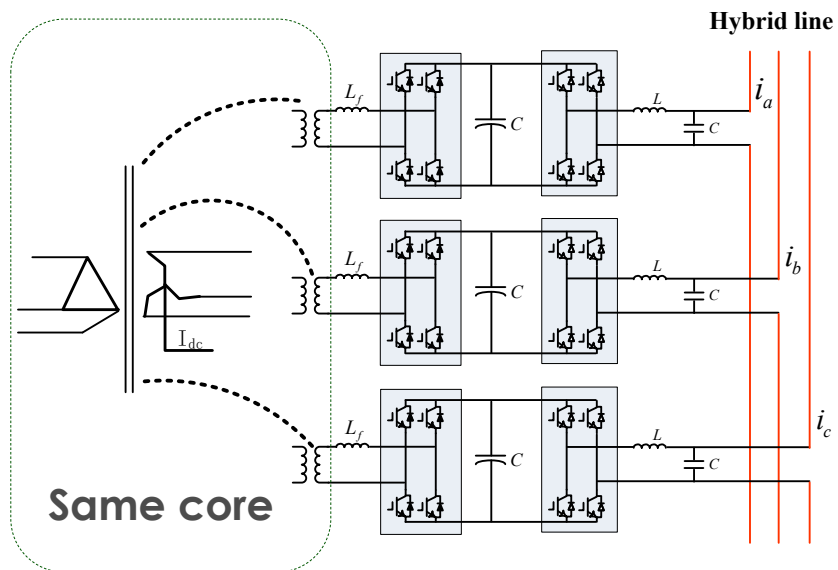

Adjust the line resistance by phase.



Can be enabled or bypassed

$$\Delta R = \frac{V_{AC/DC}}{I_{AC/DC}} \approx \frac{\Delta V_{DC}}{I_{DC}/3}$$

Bidirectional Active Hybrid Line Impedance Conditioners
(Two conditioners are active, at the most)

Method3: Impedance Conditioner Design and Simulation


System Parameters	
Line Length	650km
Impedance	0.035Ohm/km+ 0.9337mH/km
Unbalance	5%
Line voltage (phase)	AC: 115 kV; DC 180 kV
Line current	AC: 612A, DC: 1000A
Transmission Power	729 MW (189 AC and 540 DC)
Inverter AC voltage	3.183kV(peak)
DC link voltage	3.617kV
DC link Capacitance	3300uF
Rectifier AC voltage	3.183 kV(peak)
Zigzag transformer windings	balance design + conditioner winding (170/138/138/3)

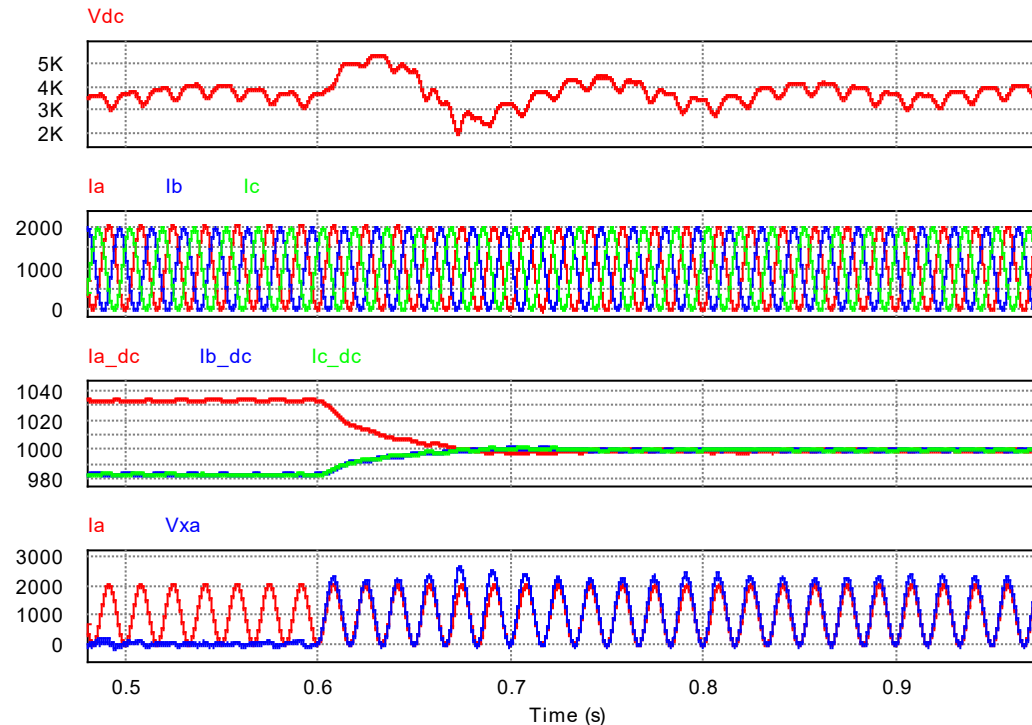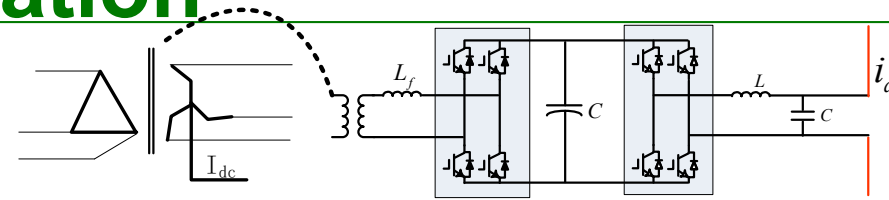

Conditioner enabled at 0.6s. Control reference goes from zero to the desired impedance.


Scaled Hybrid AC/DC System Prototype

Prototype:

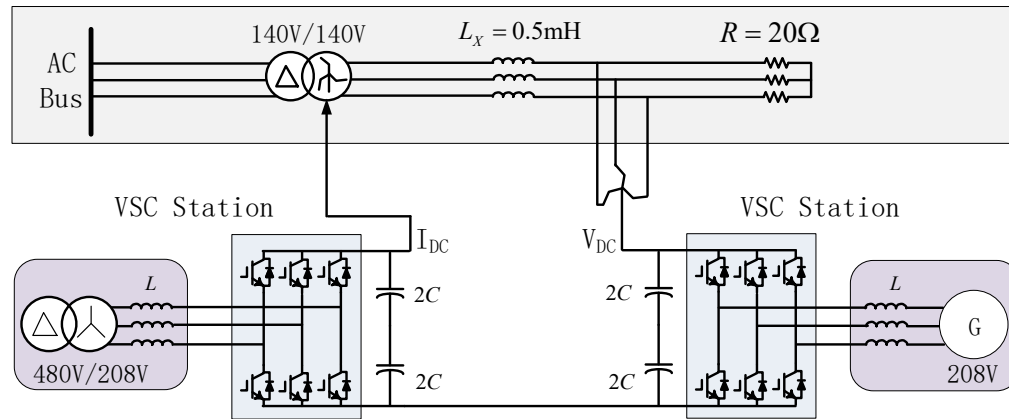

Scaled Hybrid AC/DC System Experiments

Before DC injection:

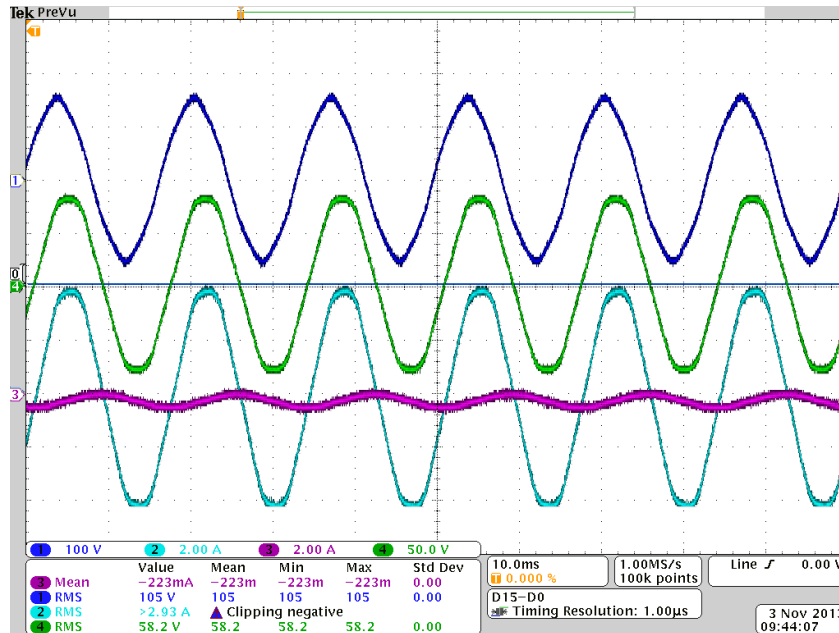


v_{AB} (100V/div)
 i_a (2A/div)
 i_{a_zig2} (2A/div)
 v_{an} (250V/div)

BTB AC grid voltage: 80V

Rectifier: $V_{DC_ref} = 150V$, $Q_{ref} = 0var$

After DC injection:


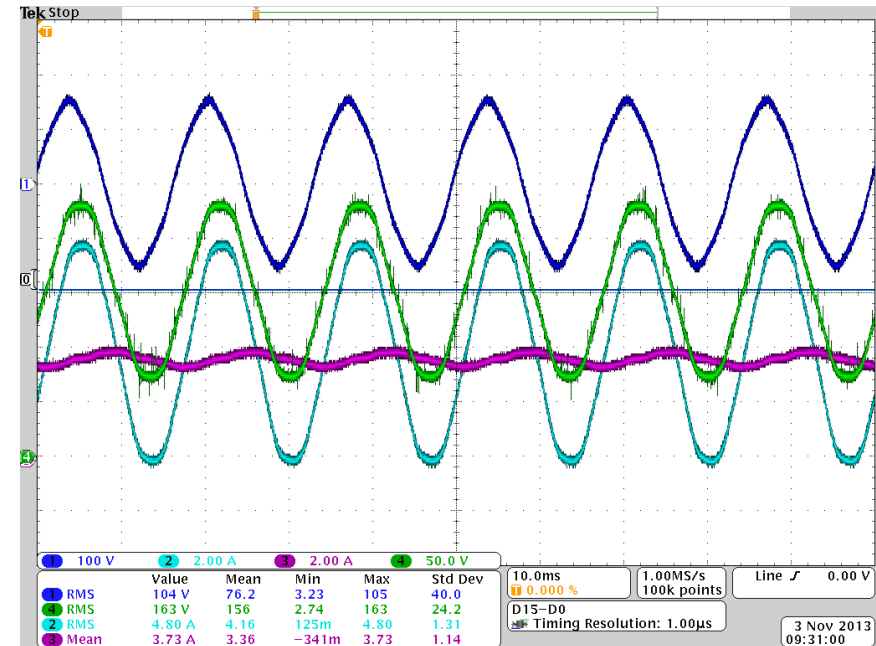


v_{AB} (100V/div)
 i_a (2A/div)
 i_{a_zig2} (500mA/div)
 v_{an} (250V/div)

AC line voltage: 104V

Inverter: $I_{DC} = 12A$, $Q_{ref} = 0var$

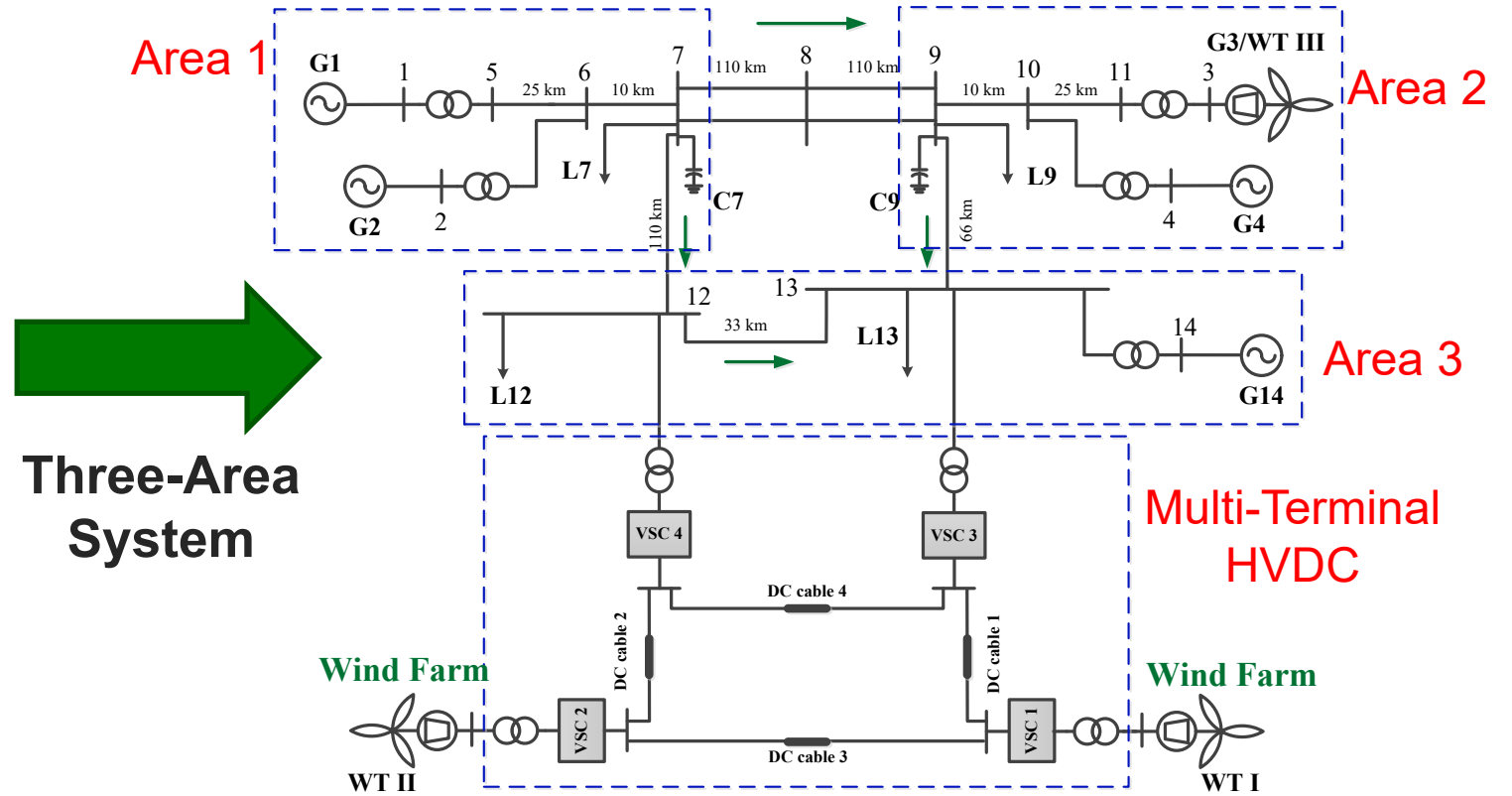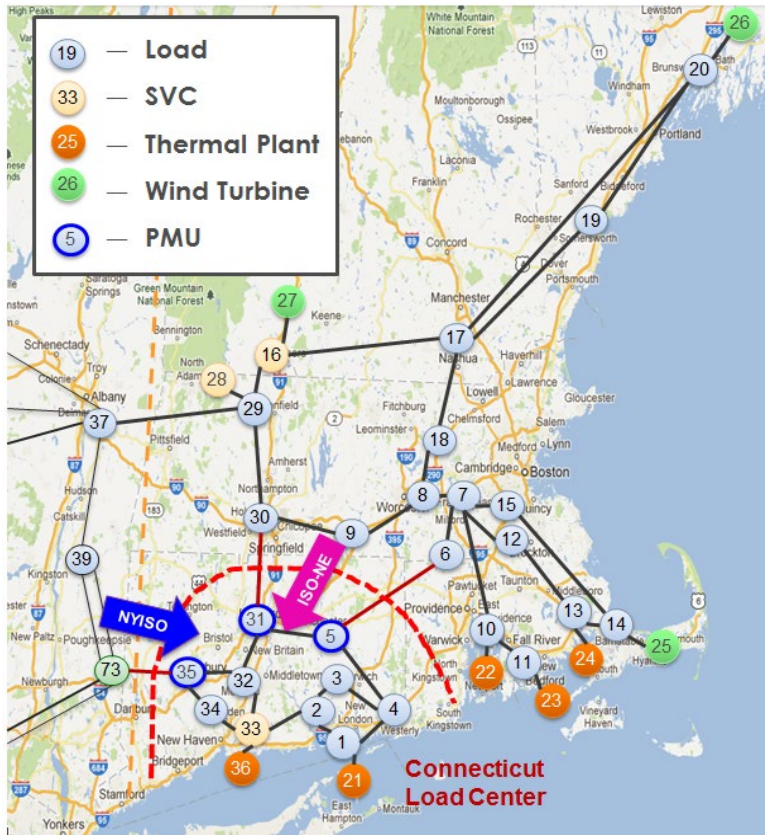
HTB 3-Area Structure – NPCCC Representation




Three-Area System

- Emulate various grid scenarios with interconnected clusters of scaled-down generators, loads, and energy storage.

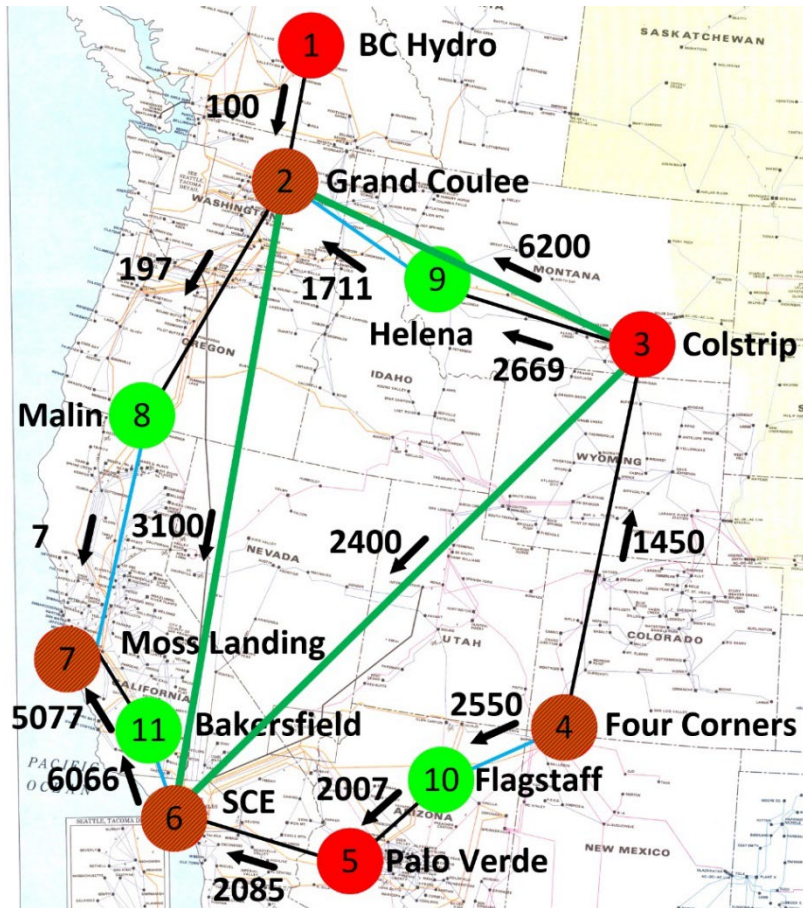HTB 4-Area Structure – WECC Representation




Four-Area System

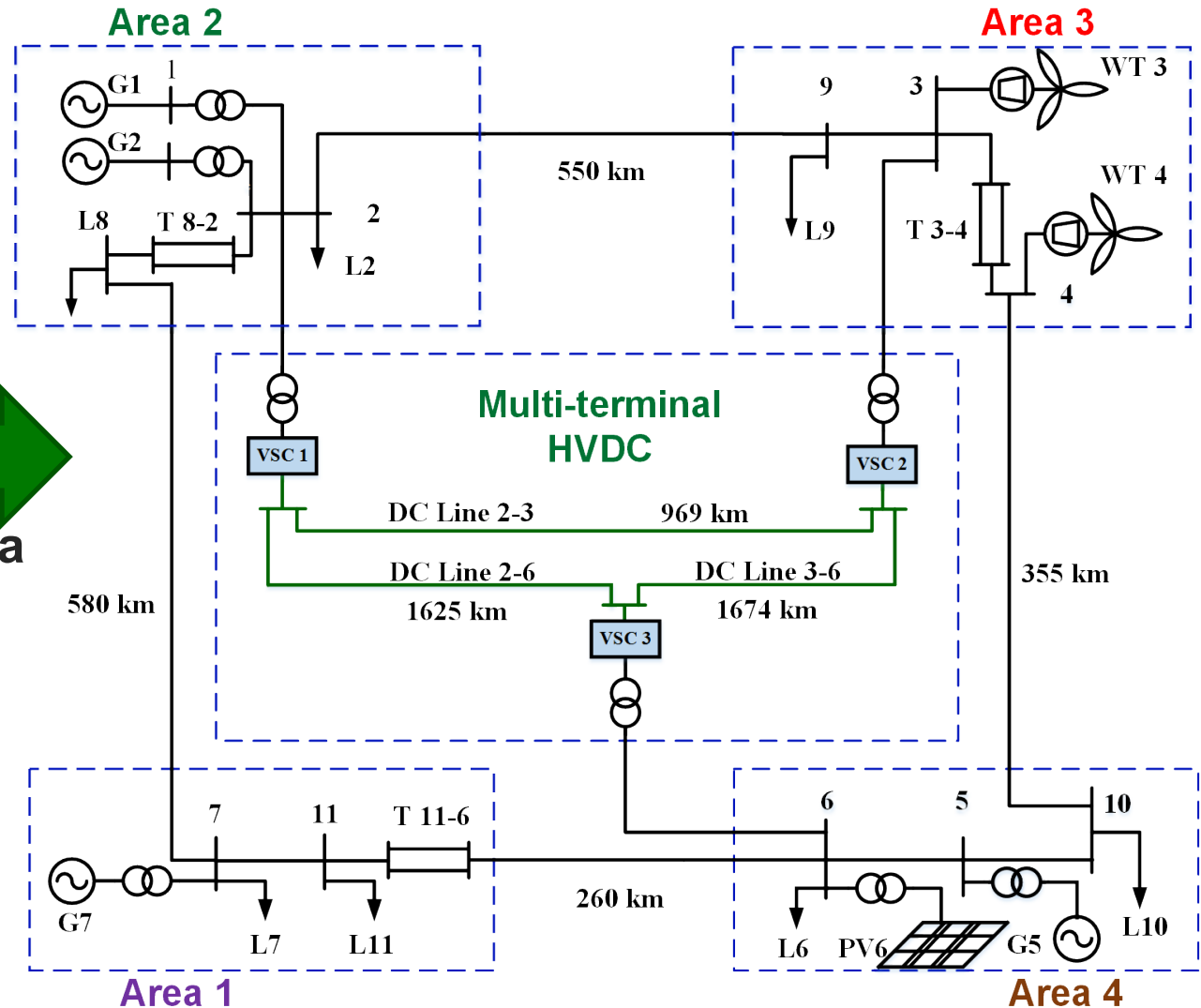

Multi-Terminal HVDC Testbed

Objective: Build a hardware platform for MT-HVDC system operation/control/protection development and demonstration

System Structure

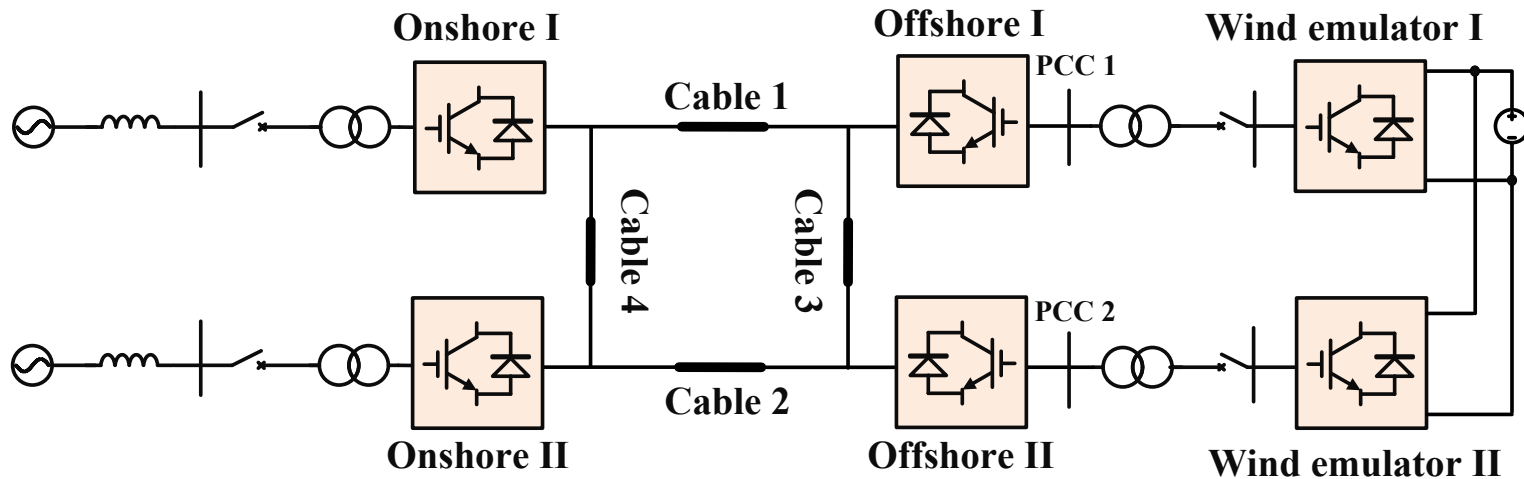

Testbed Capability on Scenario Emulation:

- System start-up
- Station online re-commission
- Wind farm power variation
- Station outage
- Transmission line trip
- Station online mode transition

MTDC Testbed Hardware



Acknowledgements



Other government and industry sponsors are also acknowledged.

Thank You!