

**ECE 300**  
**Spring Semester, 2003**  
**HW Set #7**

**Due: March 10, 2003**  
wlg

Name \_\_\_\_\_  
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Problems with plots count 15 points. Problems without plots count 10 points.

**Following are to be worked by standard differential equation methods:**

6.3  $v_c(t) = 6e^{-2.5t}$  V  $t > 0$

6.5  $i_o(t) = (2/3)e^{-5t}$  A  $t > 0$

6.7 Use MATLAB (with simulink) to plot your answer:  $v_o(t) = 4.36(1 - e^{-1.83t})$  V  $t > 0$

6.10 Use MATLAB to plot your answer:  $i_L(0^-) = (4/3)$ ,  $i_L(t) = (4/3)e^{-9t}$  A,  $t > 0$

6.12 Use MATLAB (with simulink) to plot your answer:  $v_c(t) = 6e^{-3.75t}$  V  $t > 0$ ;  $v_c(0^-) = 6$  V

6.18 Use MATLAB to make your plot:  $v_o(t) = -9.6e^{-9.6t}$  V  $t > 0$ ;  $v_o(0^-) = 0$

6.21  $i_o(t) = 0.5e^{-3.33t}$  mA  $t > 0$ ;  $i_o(0^-) = 1$  mA

**Following are to be worked by the step-by-step method:**

6.28  $i_o(t) = 2e^{-t/2.4}$  mA  $t > 0$ ;  $i_o(0^-) = 2$  mA

6.34  $i_L(0^-) = 1$  mA;  $v_o(t) = 1.85e^{-5.54t}$  V  $t > 0$

6.37  $v_c(0^-) = 4$  V;  $i_o(t) = [3 - (1/3)e^{-t/0.6}]$  mA  $t > 0$

6.47  $v_o(t) = -6e^{-4t}$  V  $t > 0$

6.51 Use MATLAB (with simulink) to plot your answer:

$$i_o(t) = \frac{e^2}{e^3} - \frac{8}{3}e^{-\frac{15}{8}t} \text{ mA} \quad t > 0$$