

1.12

$$P_1 = 4 \times 2 = 8 \text{ W}$$

$$P_2 = -8 \times 2 = -16 \text{ W}$$

1.17

$$P_{36V} = 36 \times (-4) = -144 \text{ W}$$

$$P_1 = 12(4) = 48 \text{ W}$$

$$P_2 = 24(2) = 48 \text{ W}$$

$$P_{D_3} = 4(-2) = -8 \text{ W}$$

$$P_3 = 28(2) = 56 \text{ W}$$

2.7

$$P_3 = I \cdot V = (3 + 3)(12) = 72 \text{ W}$$

2.10

$$I_1 + I_2 = I_4 \quad 3 \text{ mA} + I_2 = 6 \text{ mA}$$

$$\therefore I_2 = 3 \text{ mA}$$

$$\text{By KCL } I_1 = I_4 = 6 \text{ mA}$$

2.17

$$\text{KVL } -9 + V_x + 2V_x = 0$$

$$V_x = 3 \text{ V}$$

2.24

The current in clockwise direction is

$$I = \frac{12 - 4}{4 \text{ k}} = 2 \text{ mA}$$

$$V_{bd} = 2 \text{ mA} (1 \text{ k}) + 4 = 6 \text{ V}$$

2.28

Assuming a clockwise current KVL $\Rightarrow \frac{V_x}{2} + 20 \text{ kI}$

$$V_x = 40 \text{ I} \quad \therefore -\frac{40 \text{ kI}}{2} + 20 \text{ kI} + 40 \text{ kI} + 5 = 0$$

$$V_1 = V_x + 5 = 40 \text{ kI} + 5 = 0 \text{ V} \quad I = 0.125 \text{ mA}$$

2.29

Assuming a-clockwise current

Pg 2/2

$$\text{KVL} \quad -12 + 30kI + 2V_x + V_x = 0$$

$$V_x = 10kI$$


$$\therefore -12 + 30kI + 20kI + 10kI = 0$$

$$I = 200\mu\text{A}$$

$$P_{30k} = I^2 R = (200 \times 10^{-6})^2 30k \\ = 1.2\text{mW}$$

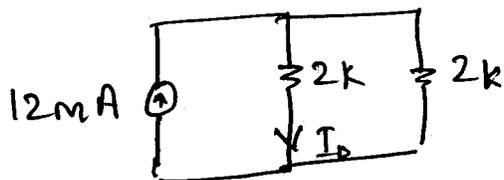2.30

Combining the 6k and 3k resistors yields this network.



$$I_0 = 12\text{mA} \left(\frac{2k}{2k+2k} \right) \\ = 6\text{mA}$$

2.35

Applying KCL

$$\frac{V_1}{2k} - 6\text{mA} + \frac{I_x}{2} + \frac{V_1}{4k} = 0 \quad I_x = \frac{V_1}{2k}$$

$$\therefore \frac{V_1}{2k} + \frac{V_1}{4k} + \frac{V_1}{4k} = 6\text{mA}$$

$$V_1 = 6\text{V}$$

$$I_L = \frac{6}{4k} = 1.5\text{mA}$$