

ECE 300  
Spring Semester, 2004  
HW Set #2

Desk  
Name LODY  
Print (last, first) LODY

Due: January 29, 2004

wlg

PM Section

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 5 points.

Work the following problem from the text.

2.43  $R_{AB} = 3 \text{ kohms}$

2.50  $I_A = 3 \text{ mA}$

2.57  $I_0 = 0.75 \text{ mA}$

2.61  $V_S = 41 \text{ V}$

2.76  $I_0 = 3 \text{ A}$

2.78  $V_0 = 10 \text{ V}$

2.83  $I_0 = -20 \text{ mA}$

2FE-3  $V_0 = 36 \text{ V}$

✓ 3.4  $V_0 = -7.28 \text{ V}$

✓ 3.10  $V_1 = 2 \text{ mA}$

✓ 3.13  $I_0 = -1 \text{ mA}$

✓ 3.19  $I_0 = -1.59 \text{ mA}$


✓ 3.22  $V_0 = -7.71 \text{ V}$

✓ 3.31  $V_0 = 9 \text{ V}$


3.37  $V_0 = (4/3) \text{ V} \quad 15 \text{ V}$

2.43 wlg


Find  $R_{AB}$

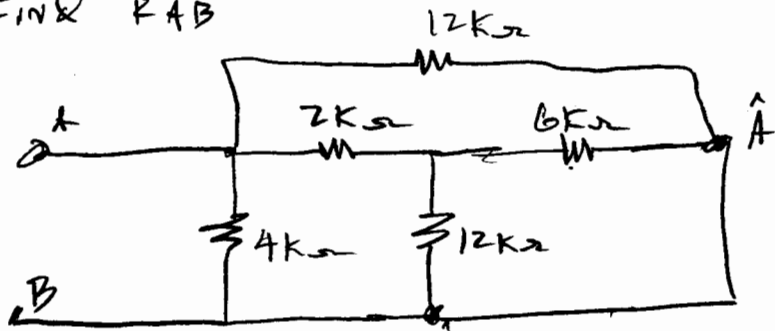

Look point A to B.

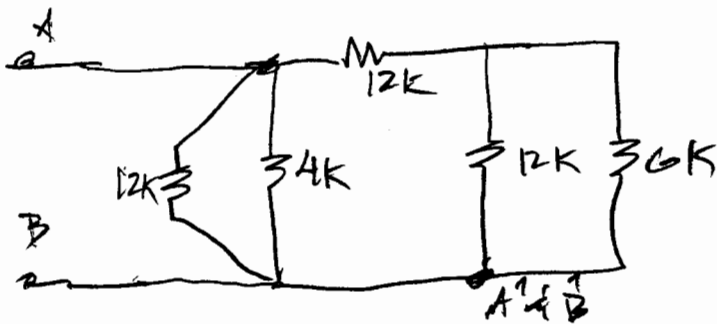

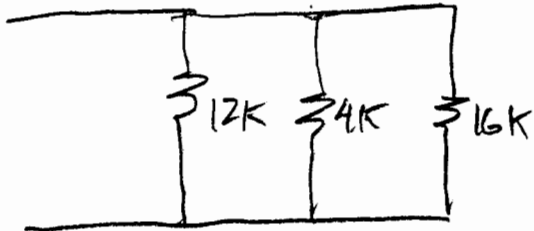
$$6 \parallel 12 = \frac{6 \times 12}{18} = 4k$$




$$4k \parallel 16k = \frac{4 \times 16}{20}$$

2.50 wlg

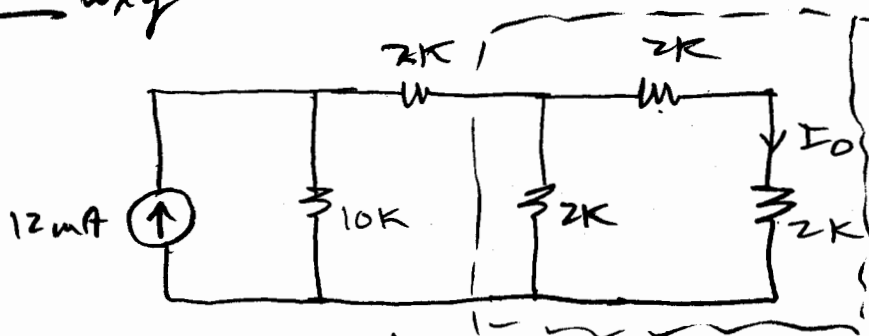


Using current splitting
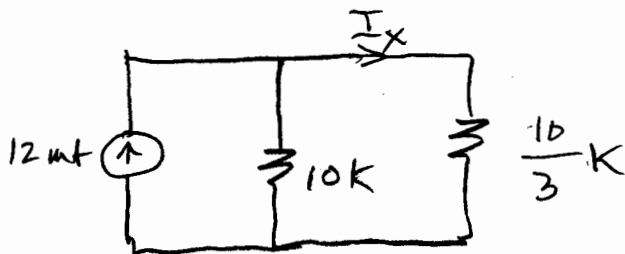
$$2K \parallel 4K = \frac{8K}{6} = \frac{4}{3}K$$



$$I_x = \frac{(12mA) 10K}{10 + \frac{10}{3}} = \frac{3 \times 12 \times 10}{40}$$


$$I_x = 9mA$$

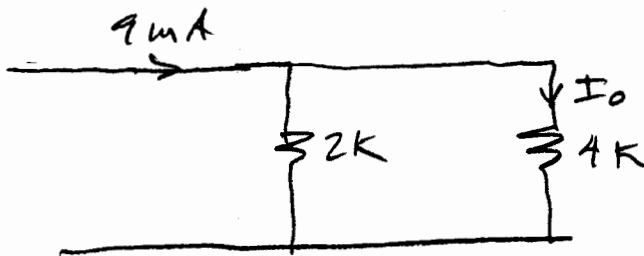



$$I_0 = \frac{9mA \times 2K}{6K} = 3mA$$

$$I_0 = 3mA$$

2.43 wlg

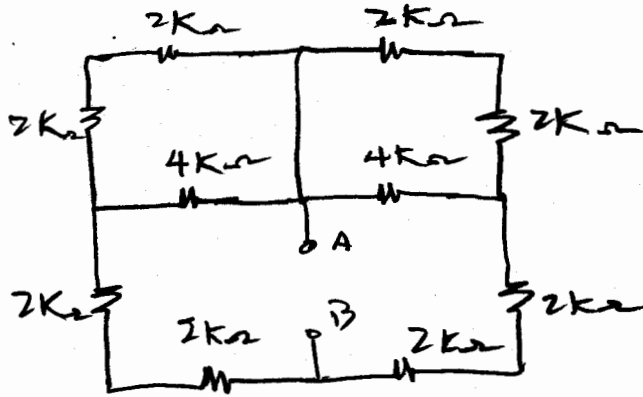


becomes

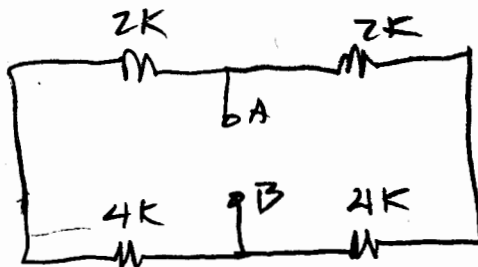
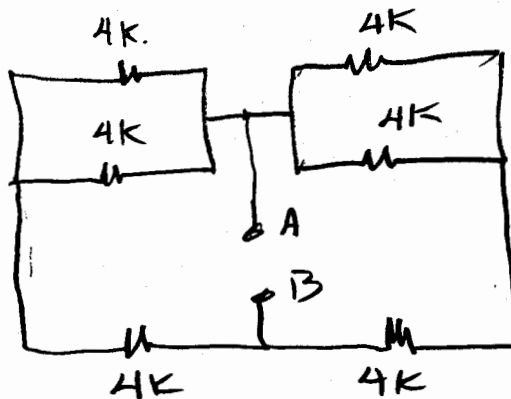


$$R_{AB} = 6k \parallel 6k = 3k$$

2.57 w/g

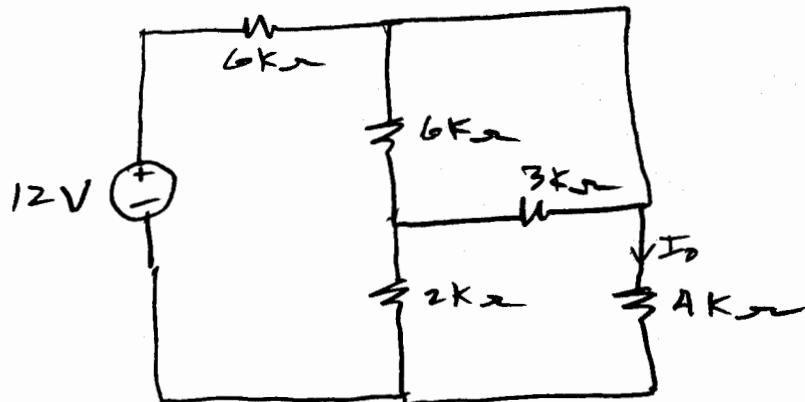

Becomes

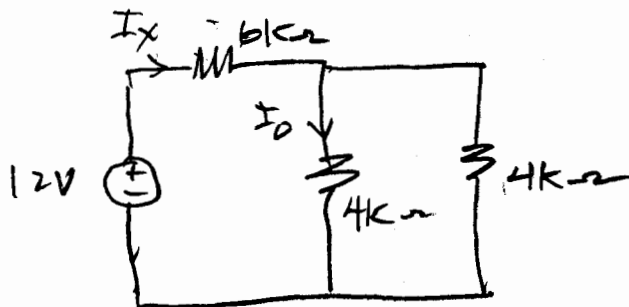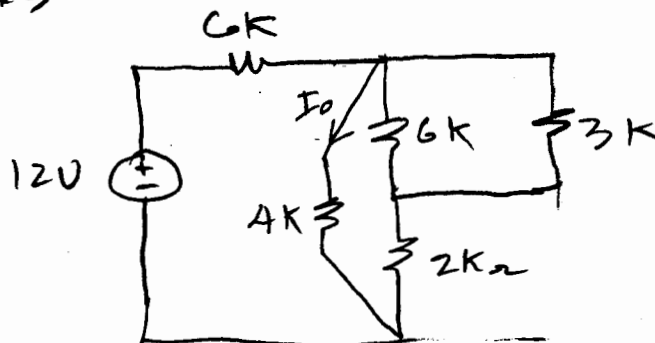


$$I_x = \frac{12}{6+2} = \frac{12}{8} = \frac{3}{2} = 1.5 \text{ A}$$

$$I_0 = \frac{I_x \times 4k}{8k} = 0.75 \text{ A}$$

$$I_0 = 0.75 \text{ A}$$

2.61 wlg

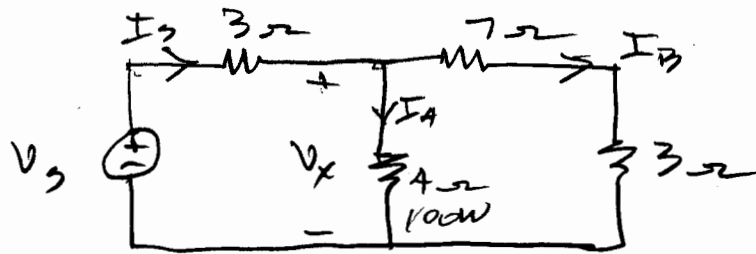

Power absorbed by  $4\Omega$  resistor is  $100\text{W}$ . Find  $V_s$

$$P = 100\text{W} = I_A^2 \times 4$$

$$I_A = 5\text{A}$$

$$V_x = 5 \times 4 = 20\text{V}$$

$$I_B = \frac{20}{10} = 2\text{A}$$

$$I_s = I_A + I_B = 7\text{A}$$


$$V_s = 3 \times 7 + V_x$$

$$= 21 + 20$$


$$V_s = 41\text{V}$$

2.76 wly

$R \times R + R \times R +$

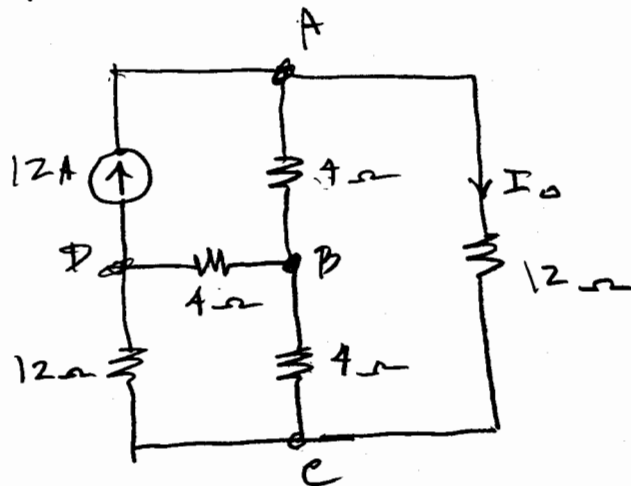


Find  $I_0$

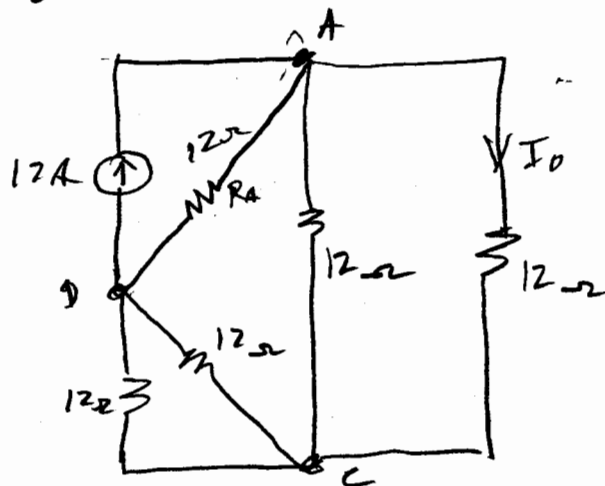

Since all arms of the Y are equal;

$$R_A = 3R_Y$$


$$R_A = 3 \times 4 = 12\Omega$$

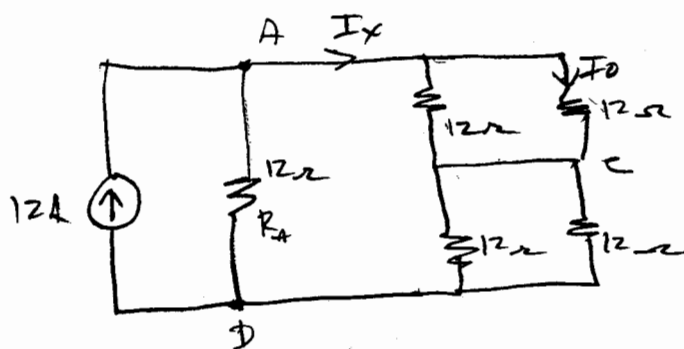

$$I_x = 6 \text{ A} \quad (\text{inspection})$$

$$I_0 = \frac{I_x}{2} = 3 \text{ A}$$

2.78 wly

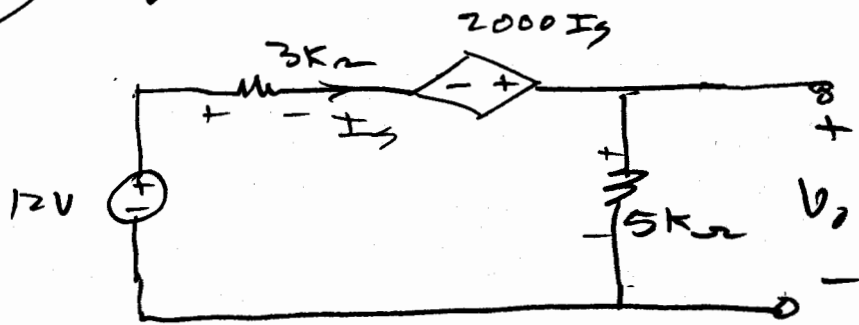

FIND  $V_o$

KVL

$$-12 + (3K)I_s + 2000I_s + 5K I_s = 0$$


$$(6K) I_s = 12$$

$$I_s = 2 \text{ mA}$$

$$V_o = I_s \times 5K$$

$$V_o = 10 \text{ V}$$

2.83 wly

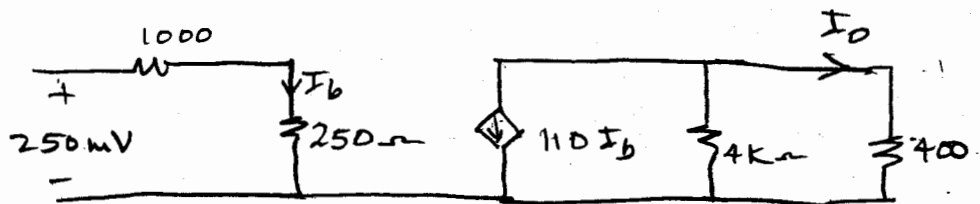

$$I_o = \frac{(-110 I_b)(4K)}{4.4K} = -100 I_b$$


$$I_b = \frac{0.25}{1250} = .2 \text{ mA}$$

$$I_o = -100 \times .2 \times 10^{-3}$$



$$I_o = -20 \text{ mA}$$



2FE-3 wlg Find  $V_0$

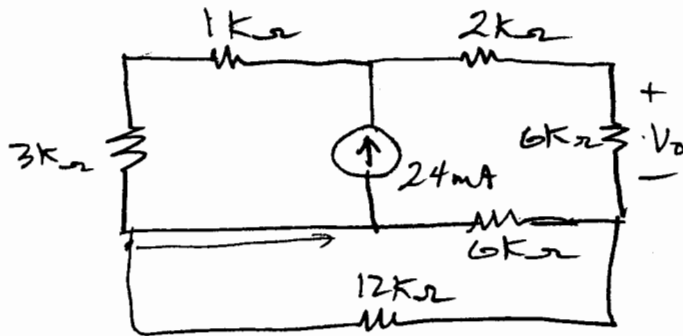

$$6 \parallel 12 = \frac{72}{18} = 4$$

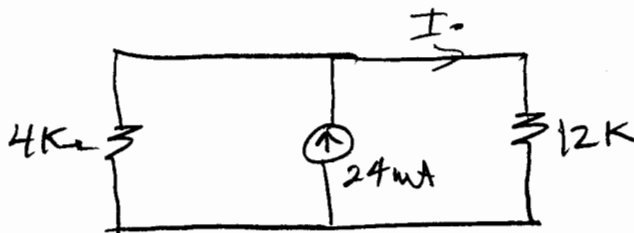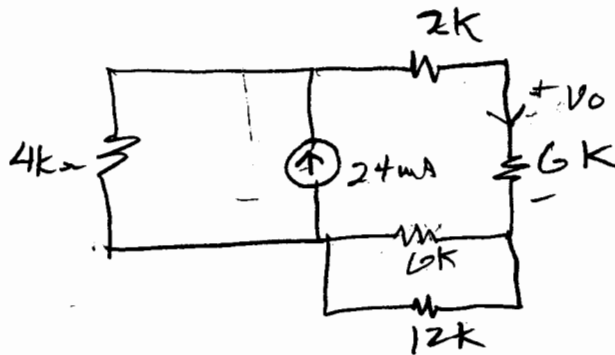


$$I_0 = \frac{(24\text{mA})(4\text{K})}{16\text{K}} = 6\text{mA}$$

$$V_0 = (6\text{K})(I_0) = (6\text{K})(6\text{mA})$$

$$V_0 = 36\text{V}$$

3.14 wly

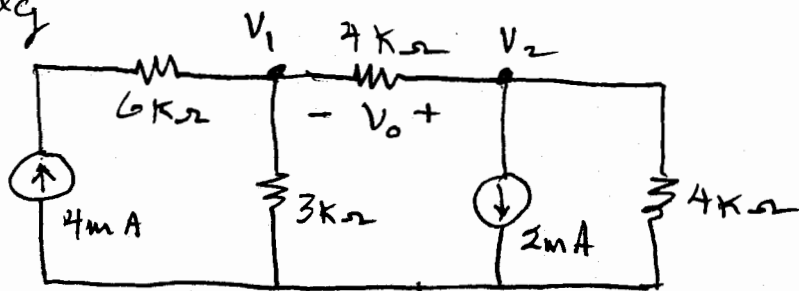

Use nodal analysis to find  $V_o$ .

At  $V_1$

$$-\frac{4A}{1K} + \frac{V_1}{3K} + \frac{V_1 - V_2}{4K} = 0$$

$$4V_1 + 3V_1 - 3V_2 = 48$$

OR

$$\boxed{7V_1 - 3V_2 = 48}$$

At  $V_2$

$$\frac{V_2 - V_1}{4K} + \frac{2A}{1K} + \frac{V_2}{4K} = 0$$

$$V_2 - V_1 + V_2 = -8$$

$$\boxed{-V_1 + 2V_2 = -8}$$


$$\begin{bmatrix} 7 & -3 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 48 \\ -8 \end{bmatrix}$$

$$V_1 = 6.55 \text{ V} \quad ; \quad V_2 = -0.727$$

$$V_o = V_2 - V_1 = -0.727 - 6.55$$

$$\boxed{V_o = -7.28 \text{ V}} \quad \text{Ans}$$

3.10 wkg

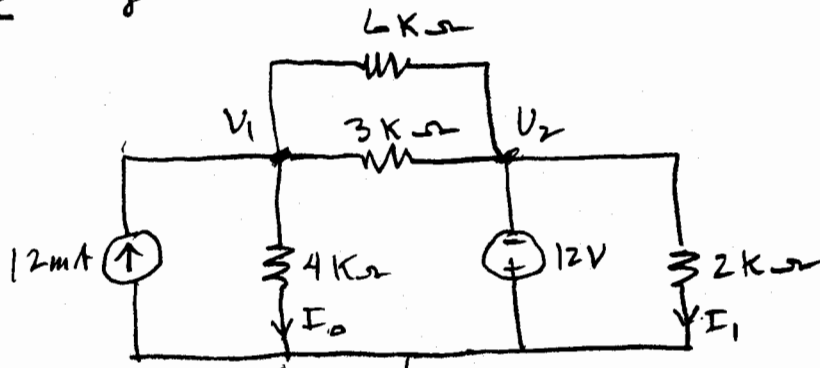

Find  $I_0$  &  $I_1$  using nodal analysis.

Solution:

Assign  $V_1$  &  $V_2$  as shown. Write nodal equations then solve for  $V_1$  &  $V_2$ . Use  $V_1$  and  $V_2$  to find  $I_0$  &  $I_1$ .

At  $V_1$

$$12\text{cd} \quad -\frac{12}{1\text{k}} + \frac{V_1}{4\text{k}} + \frac{V_1 - V_2}{3\text{k}} + \frac{V_1 - V_2}{6\text{k}} = 0 \quad (1)$$

$$-144 + 3V_1 + 4V_1 - 4V_2 + 2V_1 - 2V_2 = 0$$

$$\boxed{9V_1 - 6V_2 = 144} \quad (2)$$

At  $V_2$

$$V_2 = -12\text{V} \quad \text{by inspection:}$$

∴ from (2)

$$9V_1 + 72 = 144$$

$$V_1 = 8\text{V}$$


So

$$I_0 = \frac{V_1}{4\text{k}} = \frac{8}{4\text{k}} = 2\text{mA}$$

$$\boxed{I_0 = 2\text{mA}} \quad \text{Ans}$$


$$\boxed{I_1 = \frac{-12}{2\text{k}} = -6\text{mA}} \quad \text{Ans}$$

3.13 wlg

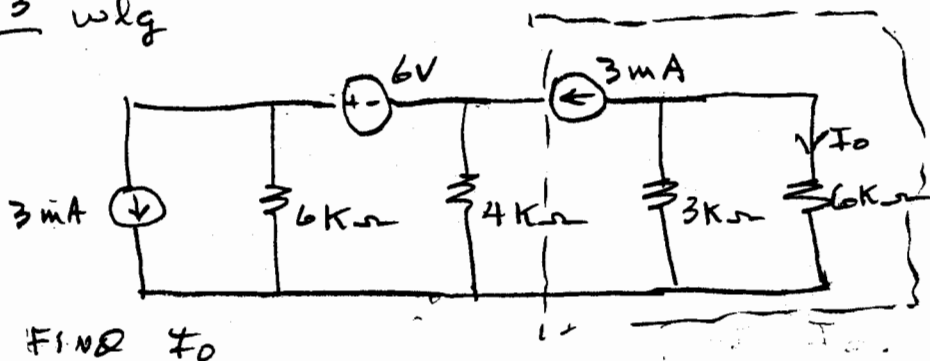

FIND  $I_0$

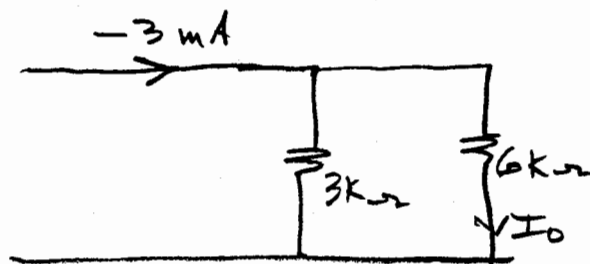Solution: The author set this problem up to catch you off guard. You don't need to do nodal analysis. The dashed portion is all we need to consider. We have;




By current splitting;

$$I_0 = \frac{(-3\text{mA}) \times 3\text{K}}{3\text{K} + 6\text{K}}$$

$$I_0 = -1\text{mA} \quad \text{ANS}$$

3.19 wlg

Find  $I_0$  in the circuit below.

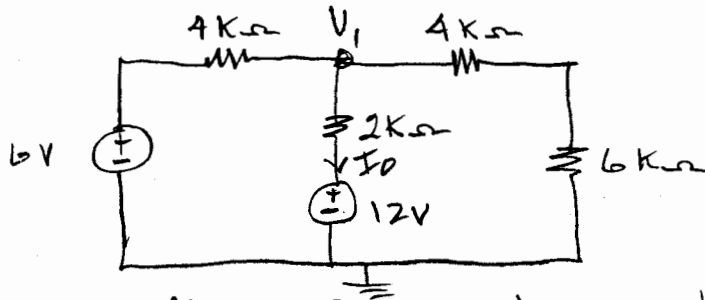

The author does not say to work by nodal analysis. I will however because it is straightforward. Assign node voltage  $V_1$  as shown.

At  $V_1$

$$\frac{V_1 - 6}{4K} + \frac{V_1 - 12}{2K} + \frac{V_1}{10K} = 0$$

202d

$$5V_1 - 30 + 10V_1 - 120 + 12V_1 = 0$$

$$17V_1 = 150$$

$$V_1 = 8.82$$


$$I_0 = \frac{V_1 - 12}{2K} = \frac{8.82 - 12}{2K}$$

$$I_0 = -1.59$$

ANS

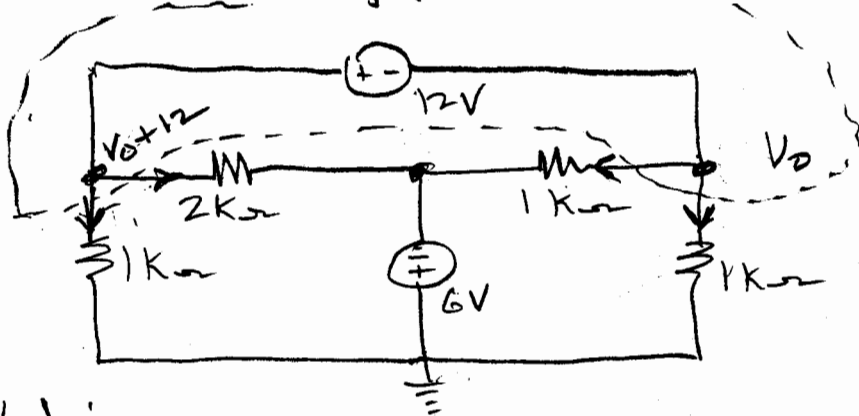3.22 wkg

Find  $V_o$  in the ckt below using nodal analysis.



Solution

We have a "supernode" to consider, this is indicated with dashed lines. Four currents leave the supernode as shown with arrows. The node on the left can be written as  $V_o + 12$ .

For the supernode;

$$\frac{V_o}{1K} + \frac{V_o + 6}{1K} + \frac{V_o + 12 + 6}{2K} + \frac{V_o + 12}{1K} = 0$$


$$2V_o + 2V_o + 12 + V_o + 18 + 2V_o + 24 = 0$$

$$7V_o = -54$$

$$V_o = -7.71 \text{ V}$$

3.31 wkg

Find  $V_o$  using nodal analysis

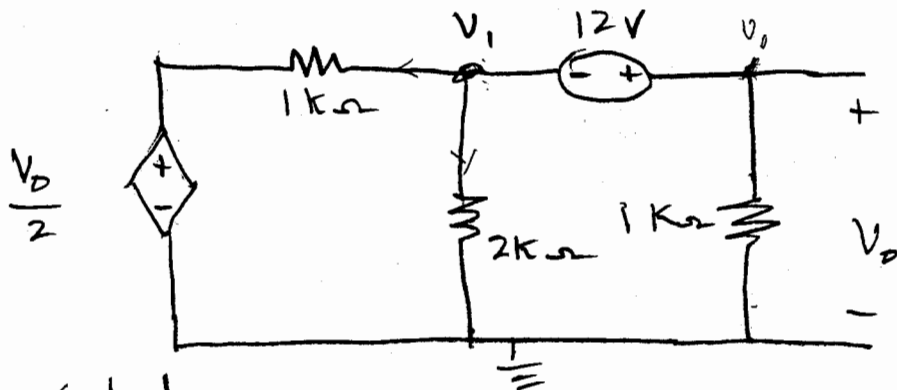

Solution:

Assign  $V_1$  as shown. Write KCL at  $V_1$ .

$$\frac{(V_1 - 0.5V_o)}{1K} + \frac{V_1}{2K} + \frac{V_1 + 12}{1K} = 0$$

$$2V_1 - V_o + V_1 + 2V_1 + 24 = 0$$

$$5V_1 - V_o = -24 \quad (1)$$

but  $V_1 + 12 - V_o = 0$

$$V_o = V_1 + 12 \quad (2)$$

substitute (2) into (1)

$$5V_1 - (V_1 + 12) = -24$$


$$4V_1 = -12$$

$$V_1 = -3V$$

then

$$V_o = 9V$$

3.37 w/z

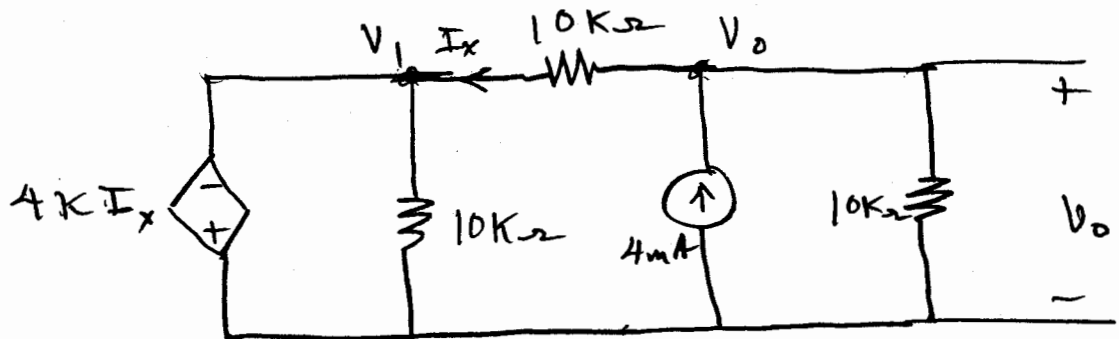

Find  $V_o$  using nodal analysis:

At  $V_1$

$$V_1 = -4K I_x \quad (1)$$

At  $V_o$

$$\frac{V_o - V_1}{10K} - \frac{4A}{1K} + \frac{V_o}{10K} = 0$$

so,

$$V_o - V_1 - 40 + V_o = 0$$

$$2V_o = 40 + V_1 \quad (2)$$

Now

$$I_x = \frac{V_o + 4K I_x}{10K} \quad (3)$$

and from (3)

$$I_x = \frac{V_o}{6K}$$

From (1)

$$V_1 = -4K \left( \frac{V_o}{6K} \right) = -\frac{2}{3} V_o$$

Into (2)

$$2V_o = 40 - \frac{2}{3} V_o$$

Giving

$$\boxed{V_o = 15V}$$



3.37 w/g

Another way of working

$$V_1 + 4K I_x = 0 \quad (1)$$

$$V_1 - 2V_0 = -40 \quad (2)$$

$$V_0 - 6K I_x = 0 \quad (3)$$

From (1), (2), and (3)

$$\begin{matrix} & V_1 & V_0 & I_x \\ \begin{bmatrix} 1 & 0 & 4K \\ 1 & -2 & 0 \\ 0 & 1 & -6K \end{bmatrix} & \begin{bmatrix} V_1 \\ V_0 \\ I_x \end{bmatrix} & = & \begin{bmatrix} 0 \\ -40 \\ 0 \end{bmatrix} \end{matrix}$$

$$V_1 = -10, \quad V_0 = 15, \quad I_x = 0.0025 \text{ A}$$