

Desk Copy

ECE 300
Spring Semester, 2004
HW Set #3
PM Section


February 5, 2004
wlg

Name Green
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 5 points.

- ✓ 3.38 $I_x = 1 \text{ mA}$, $V_o = 4 \text{ V}$
- ✓ 3.39 $V_o = 32.25 \text{ V}$
- ✓ 3.40 $V_o = 4 \text{ V}$
- ✓ 3.43 $V_o = (4/3) \text{ V}$
- ✓ 3.47 $I_o = 7 \text{ mA}$
- ✓ 3.51 $V_o = 2 \text{ V}$
- ✓ 3.54 $I_o = 2 \text{ mA}$
- ✓ 3.65 $V_o = 6 \text{ V}$
- ✓ 3.71 $V_o = -10 \text{ V}$
- ✓ 3.74 $V_o = -11.2 \text{ V}$
- ✓ 3FE-1 $V_o = (10/3) \text{ V}$
- ✓ 3FE-3 $I_x = 12 \text{ A}$

3.38 w/g

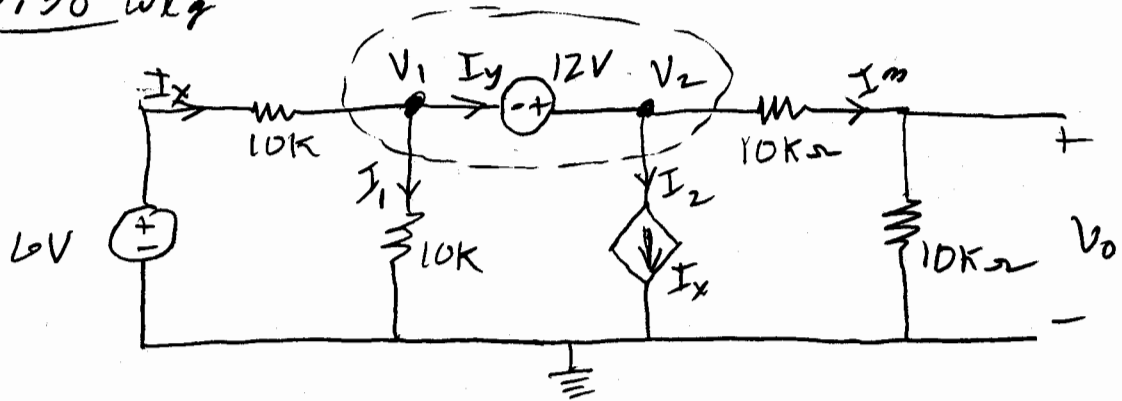

At V_1 :

$$\frac{V_1 - 6}{10k} + \frac{V_1}{10k} + I_x + \frac{V_2}{20k} = 0$$

$$I_x = \frac{6 - V_1}{10k}$$

$$\frac{V_1 - 6}{10k} + \frac{V_1}{10k} + \frac{6 - V_1}{10k} + \frac{V_2}{20k} = 0$$

$$2V_1 - 12 + 2V_1 + 12 - 2V_1 + V_2 = 0$$

$$2V_1 + V_2 = 0$$

Constraint:

$$V_1 - V_2 = -12$$

so

$$V_1 = -4V$$

$$V_2 = 8V$$

$$V_0 = \frac{10V_2}{10+10} = 4V$$

$$I_x = \frac{6 - V_1}{10k} = \frac{6 + 4}{10k} = 1mA$$

$$I_1 = \frac{V_1}{10k} = \frac{-4}{10k} = -0.4mA$$

2.78

(2)

cont.

$$I_2 = I_x = 1 \text{ mA}$$

$$I_3 = \frac{V_2}{20\text{k}} = \frac{8}{20\text{k}} = 0.4 \text{ mA}$$

~~A₁~~

V₁

$$I_x = I_y + I_1$$

$$I_y = I_x - I_1 = 1 \text{ mA} - (-.4 \text{ mA})$$

$$\boxed{I_y = 1.4 \text{ mA}}$$


~~A₂~~ V₂

$$I_y = I_2 + I_3$$

$$1.4 \text{ mA} = 1 \text{ mA} + 0.4 \text{ mA}$$

check

3.39 Use nodal analysis to find V_o .

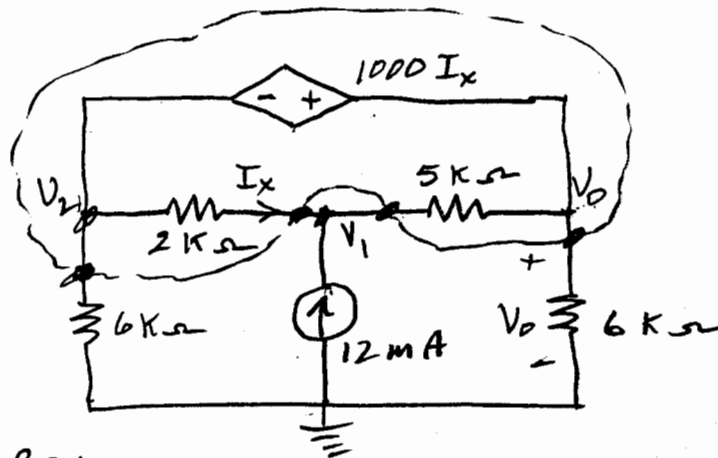

At super node:

$$\frac{V_o}{6k} + \frac{V_o - V_1}{5k} + \frac{V_2 - V_1}{2k} + \frac{V_2}{6k} = 0$$

$$5V_o + 6V_o - 6V_1 + 15V_2 - 15V_1 + 5V_2 = 0$$

$$11V_o - 21V_1 + 20V_2 = 0$$

Constraint Eq:

$$V_2 + 1k I_x - V_o = 0$$

$$\text{but } I_x = \frac{V_2 - V_1}{2k}$$

$$V_2 + 1k \left[\frac{V_2 - V_1}{2k} \right] - V_o = 0$$

$$2V_2 + V_2 - V_1 - 2V_o = 0$$

$$-2V_o - V_1 + 3V_2 = 0$$

Now go to node V_1

3.39 cont

2

At V_1 :

$$\frac{V_2 - V_1}{2k} + \frac{12A}{k} + \frac{V_0 - V_1}{5k} = 0$$

$$5V_2 - 5V_1 + 120 + 2V_0 - 2V_1 = 0$$

$$2V_0 - 7V_1 + 5V_2 = -120$$


$$\begin{bmatrix} 11 & -21 & 20 \\ -2 & -1 & 3 \\ 2 & -7 & 5 \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -120 \end{bmatrix}$$

$$V_0 = 32.3 \text{ V}$$

$$V_1 = 54.8 \text{ V}$$

$$V_2 = 39.8 \text{ V}$$

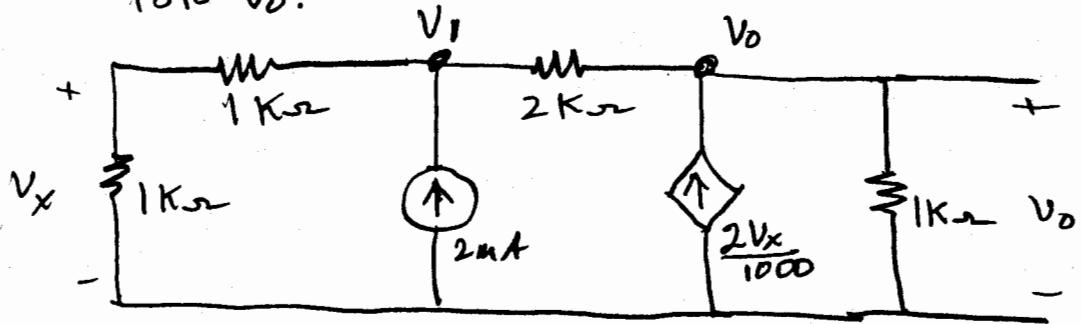3.40 wlg: Use nodal analysis to solve for V_o .



At V_1

$$\frac{V_1}{2K} + \frac{V_1 - V_o}{2K} = \frac{2}{K}$$

$$V_1 + V_1 - V_o = 4$$

$$\boxed{-V_o + 2V_1 = 4}$$

At V_o

$$\frac{V_o - V_1}{2K} + \frac{V_o}{1K} = \frac{2V_x}{1K} = 2 \left[\frac{V_1 \times 1K}{2K} \right] = V_1$$

$$V_o - V_1 + 2V_o = 2V_1$$

$$3V_o - 3V_1 = 0$$

$$\boxed{V_o - V_1 = 0}$$


$$\begin{bmatrix} -1 & 2 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_o \\ V_1 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix}$$

$$V_o = 4V$$

$$V_1 = 4V$$

3.43 wly

Find V_0 using mesh analysis

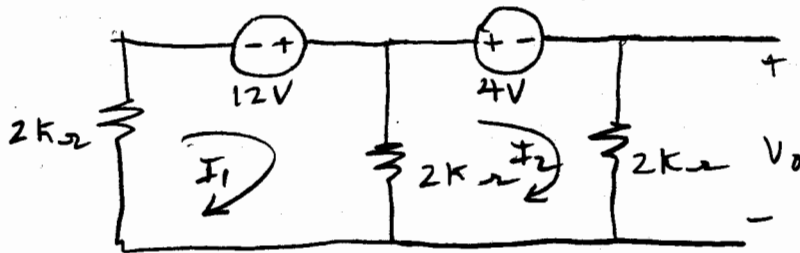

$$2kI_1 + 12 + 2kI_1 - 2I_2 = 0$$

$$4kI_1 - 2kI_2 = 12$$

$$2k(I_2 - I_1) + 4 + 2kI_2 = 0$$

$$-2kI_1 + 4kI_2 = -4$$

$$\begin{bmatrix} 4k & -2k \\ -2k & 4k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -4 \end{bmatrix}$$



$$I_1 = 0.333 \text{ mA}$$

$$I_2 = 0.667 \text{ mA}$$

$$V_0 = (2k)I_2$$

$$V_0 = 1.33 \text{ V}$$

3.47 wrq: Use loop analysis to find I_0

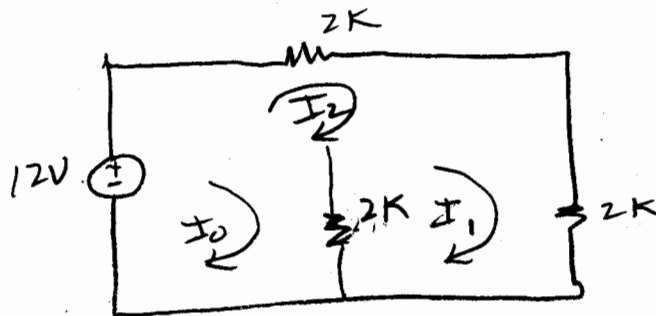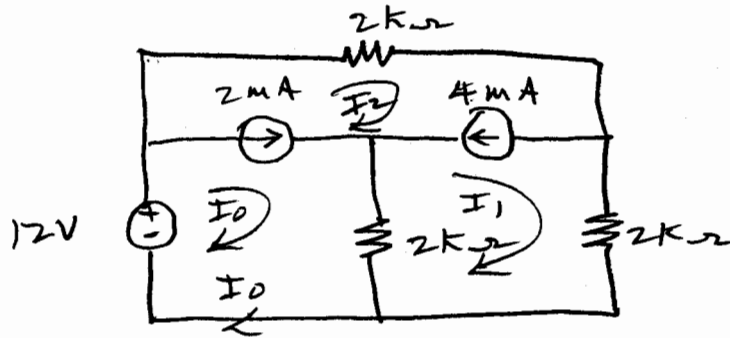

$$-12 + 2kI_2 + 2kI_1 = 0$$

$$0I_0 + 2kI_1 + 2kI_2 = 12$$

$$I_0 - I_2 = 2mA$$

$$I_0 + 0I_1 - I_2 = 2mA$$

$$I_2 - I_1 = 4mA$$

$$0I_0 - I_1 + I_2 = 4mA$$



$$\begin{bmatrix} 0 & 2k & 2k \\ 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 2mA \\ 4mA \end{bmatrix}$$

$$I_0 = 7mA$$

$$I_1 = 1mA$$

$$I_2 = 5mA$$

3.51 wlg Find V_0 using mesh analysis

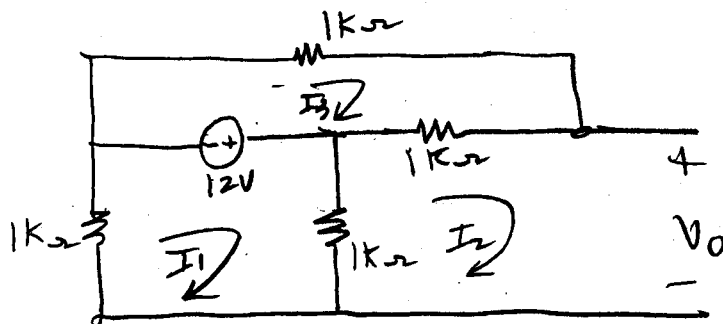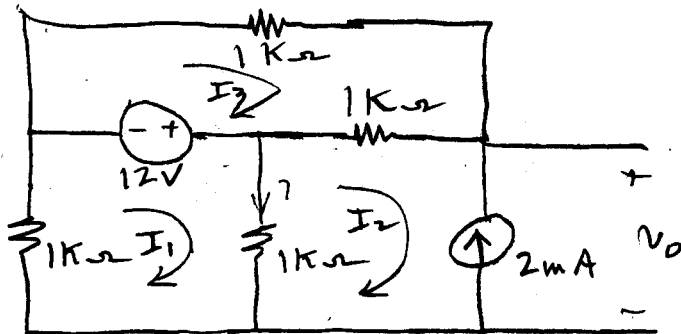

$$1kI_1 - 12 + (I_1 - I_2)1k = 0$$

$$2kI_1 - 1kI_2 + 0I_3 = 12$$

$$12 + 1kI_3 + 1kI_3 - 1kI_2 = 0$$

$$0I_1 - 1kI_2 + 2kI_3 = -12$$

$$-I_2 = -2mA$$

$$0I_1 + I_2 + 0I_3 = -2mA$$

$$\begin{bmatrix} 2k & -1k & 0 \\ 0 & -1k & 2k \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -12 \\ -2mA \end{bmatrix}$$

3.51 wly cont.

$$I_1 = 5 \text{ mA}$$

$$I_2 = -2 \text{ mA}$$

$$I_3 = -7 \text{ mA}$$


$$V_0 + (1\text{K})I_3 + (1\text{K})I_1 = 0$$

$$V_0 = -1\text{K}(I_1 + I_3)$$

$$V_0 = -1\text{K}(5\text{mA} - 7\text{mA})$$

$$V_0 = 2\text{V}$$

3.54 wlg

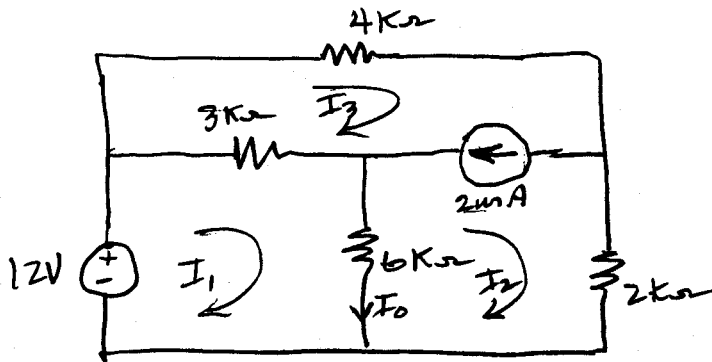

$$3K(I_1 - I_3) + 6K(I_1 - I_2) = 12$$

$$\boxed{9KI_1 - 6KI_2 - 3KI_3 = 12} \quad \checkmark$$

$$(4K)I_3 + (2K)I_2 = 12$$

$$\boxed{0I_1 + 2KI_2 + 4KI_3 = 12} \quad \checkmark$$

$$I_3 - I_2 = 2mA \quad \checkmark$$

$$0I_1 - I_2 + I_3 = 2mA$$

$$\begin{bmatrix} 9K & -6K & -3K \\ 0 & 2K & 4K \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 12 \\ .002 \end{bmatrix}$$

$$I_1 = 2.667$$


$$I_2 = 0.667$$

$$I_3 = 2.667$$

$$I_0 = I_1 - I_2 = 2.667 - 0.667$$

$$\boxed{I_0 = 2mA}$$

3.65 wlg

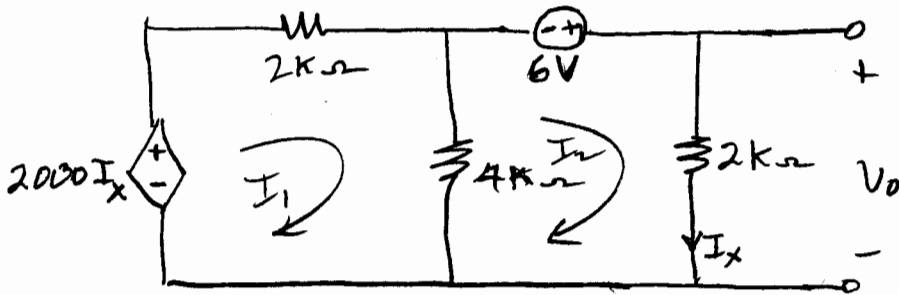

$$6kI_1 - 4kI_2 = 2000I_x = 2000I_2$$

$$6kI_1 - 6kI_2 = 0$$

$$-4kI_1 + 6kI_2 = 6$$

$$\begin{bmatrix} 6k & -6k \\ -4k & 6k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 6 \end{bmatrix}$$


$$I_1 = 3 \text{ mA}$$

$$I_2 = 3 \text{ mA}$$

$$V_0 = I_2 \times 2k = (3 \text{ mA})(2k)$$

$$V_0 = 6 \text{ V}$$

3.71 w/g

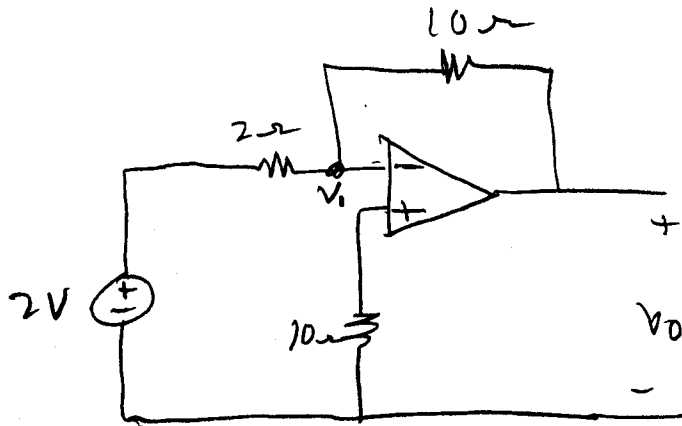

At V_i :


$$\frac{2 - V_i}{2} = \frac{V_i - V_o}{10}$$

but $V_i = 0$

$$1 = -\frac{V_o}{10}$$

$$V_o = -10V$$

3.74 wly

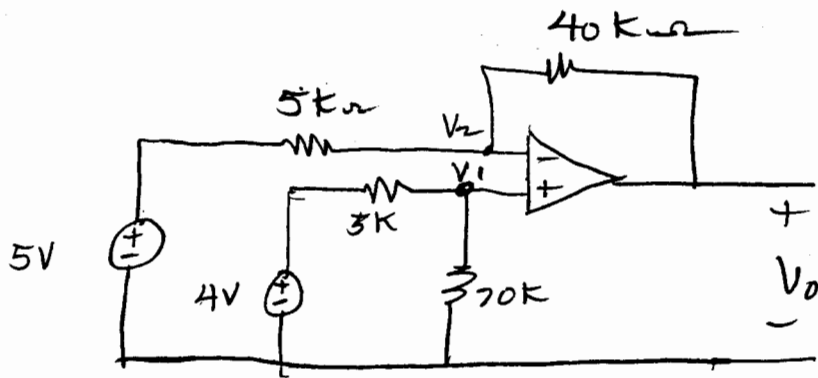

$$V_1 = \frac{4 \times 20K}{5K + 20K} = \frac{80}{25} = V_2 = 3.2$$

$$\frac{5 - V_2}{5K} = \frac{V_2 - V_0}{40K}$$


$$\frac{5 - 3.2}{5K} = \frac{3.2 - V_0}{40K}$$

$$(1.6) 40K = 16K - 5KV_0$$

$$5V_0 = -72 + 16 = -56$$

$$V_0 = -11.2$$

3FE-1

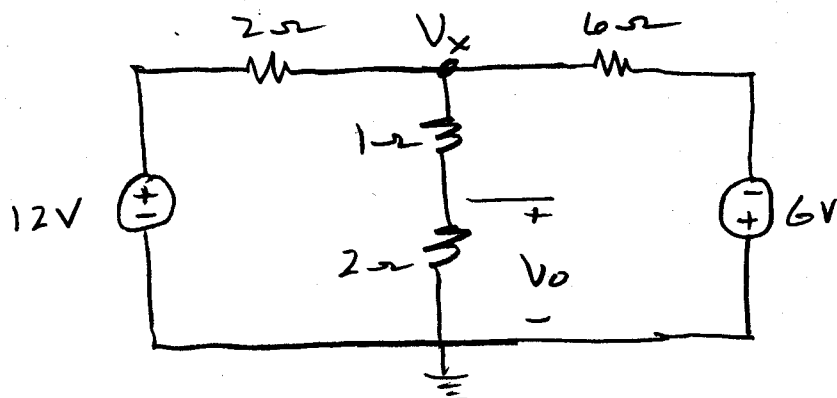

Find V_0 :

I will use nodal analysis to find V_x

$$\frac{V_x - 12}{2} + \frac{V_x + 6}{6} + \frac{V_x}{3} = 0$$

$$3V_x - 36 + V_x + 6 + 2V_x = 0$$

$$6V_x = 30$$

$$V_x = 5 \text{ V}$$


Use voltage division

$$V_0 = \frac{V_x \times 2}{1 + 2}$$

$$V_0 = \frac{5 \times 2}{3}$$

$$V_0 = \frac{10}{3} \text{ V}$$

3FE-3

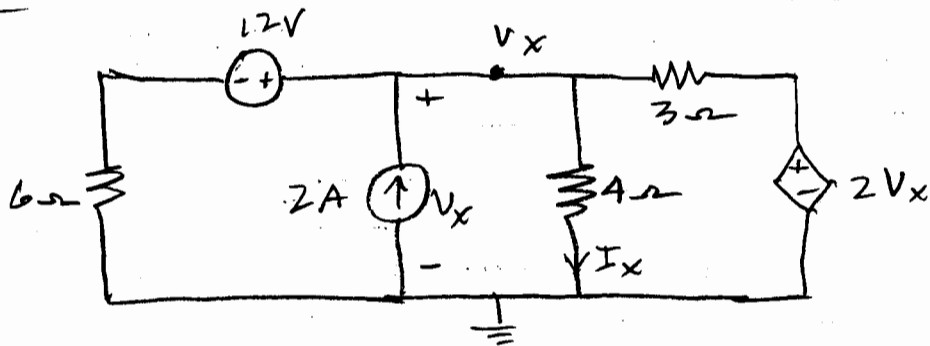

use nodal analysis to find V_x 's

$$\frac{V_x - 12}{6} + \frac{V_x}{4} + \frac{V_x - 2V_x}{3} = 2A$$

$$2V_x - 24 + 3V_x + 4V_x - 8V_x = 24$$

$$V_x = 48$$

$$I_x = \frac{V_x}{4} = \frac{48}{4}$$

$$I_x = 12A$$