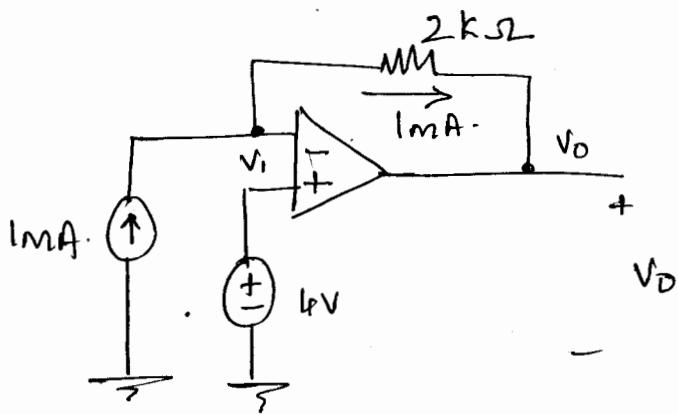


(1)



$$\text{Voltage at } V_1 = 4 \text{ V}$$

We know that 1mA is flowing through the  $2k\Omega$  resistor in the direction shown.


$$\frac{V_1 - V_0}{2k\Omega} = 1 \text{ mA}$$

$$\frac{4 - V_0}{2k\Omega} = 1 \text{ mA}$$

$$\text{Solving we get } V_0 = 2 \text{ V.}$$

$$\boxed{V_0 = 2 \text{ V}}$$

(2)

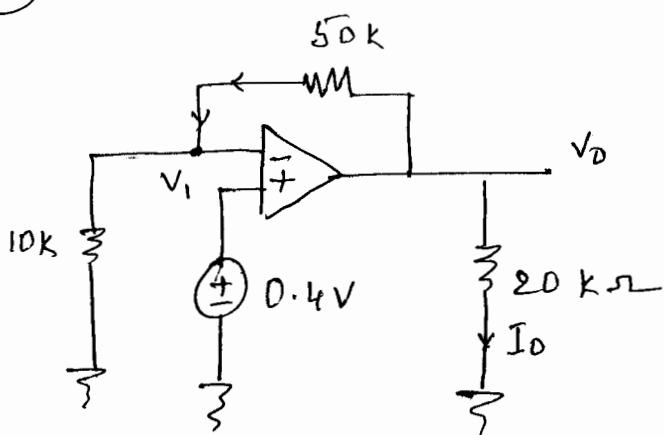

$$\frac{V_0 - V_1}{50k} = \frac{V_1}{10k} \quad V_1 = 0.4 \text{ V}$$

Solving we get


$$V_0 = 2.4 \text{ V}$$

$$I_0 = \frac{2.4}{20k} = 1.2 \times 10^{-4} \text{ A.}$$

$$\boxed{I_0 = 120 \mu\text{A}}$$

(1)

(3)

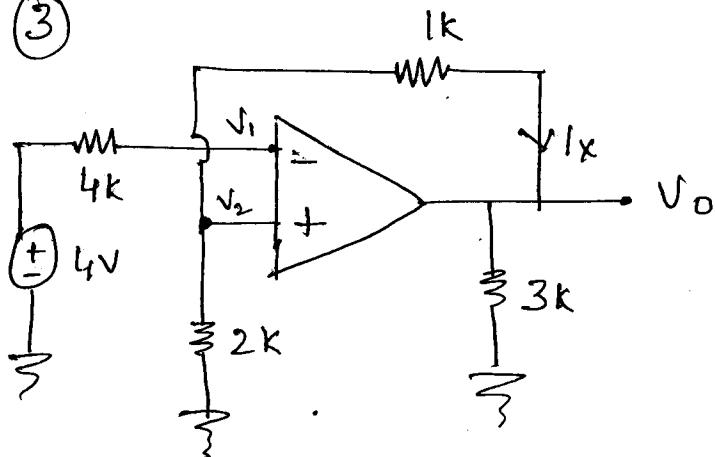

$V_1 = 4V$  as no current goes into the inverting terminal

$$V_1 = 4V = V_2$$

Nodal analysis at  $V_2$

$$\frac{V_2 - V_0}{1k} + \frac{V_2}{2k} = 0 \quad V_2 = 4V$$

solving.

$$\boxed{V_0 = 6V}$$

$$-I_x = \frac{V_0 - V_2}{1k} = \frac{6-4}{1} = \frac{2}{1k} = 2mA$$



$$-I_x = 2mA$$

$$\boxed{I_x = -2mA}$$

(2)

4.1D


$I_o$  with current source alone

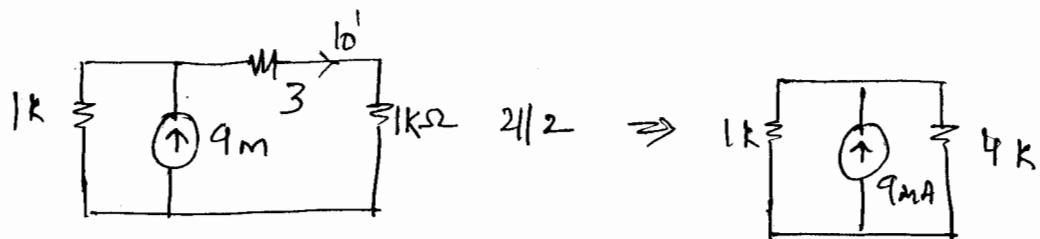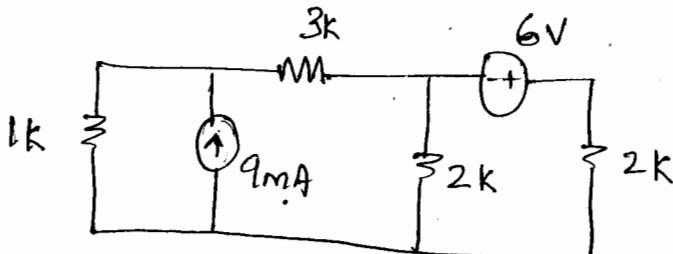

using current division

$$I_{o1} = 1.8 \text{ mA}$$

with voltage source alone

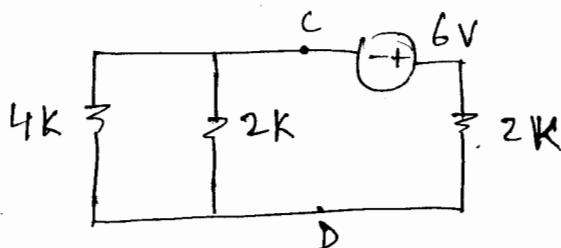

$$R_{CD} = (1k + 3k) \parallel 2k = 1.33 \text{ k}$$

$$V_{CD} = -6 \left[ \frac{R_{CD}}{R_{CD} + 2k} \right] = -2.4 \text{ V}$$

$$I_{ov} = -\frac{V_{CD}}{4k} = 0.6 \text{ mA}$$

$$I_o = I_{oi} + I_{ov}$$




=

$$2.4 \text{ mA}$$

$I_o = 2.4 \text{ mA}$

(3)

4.2b

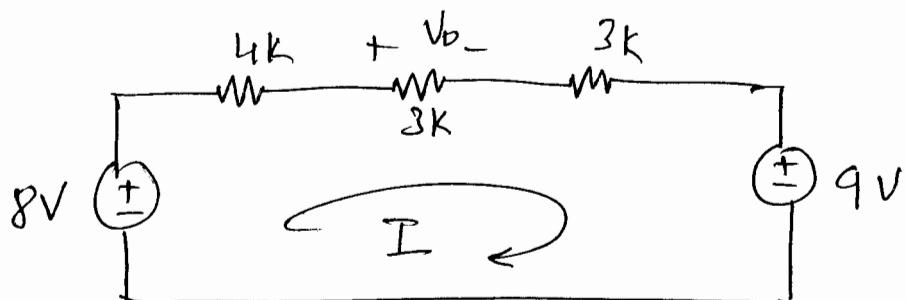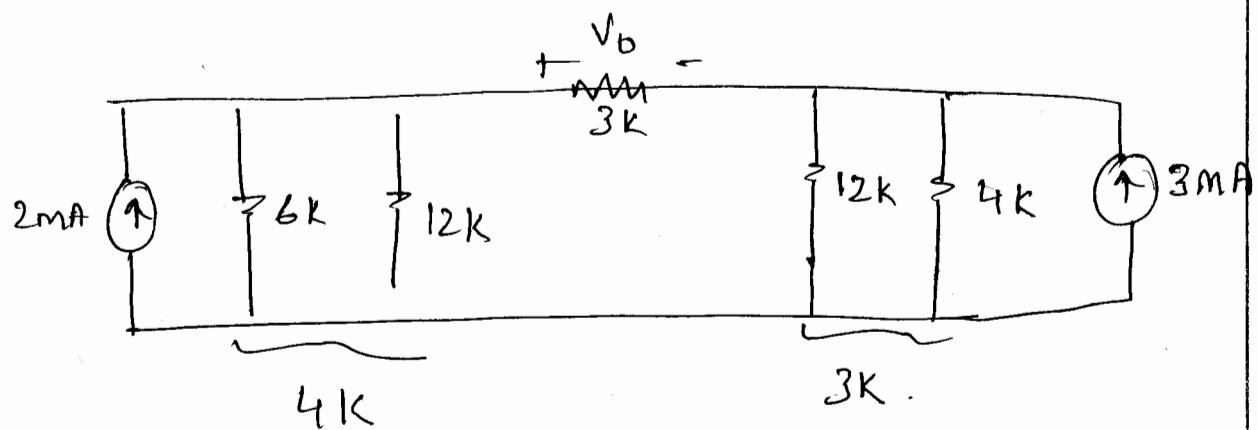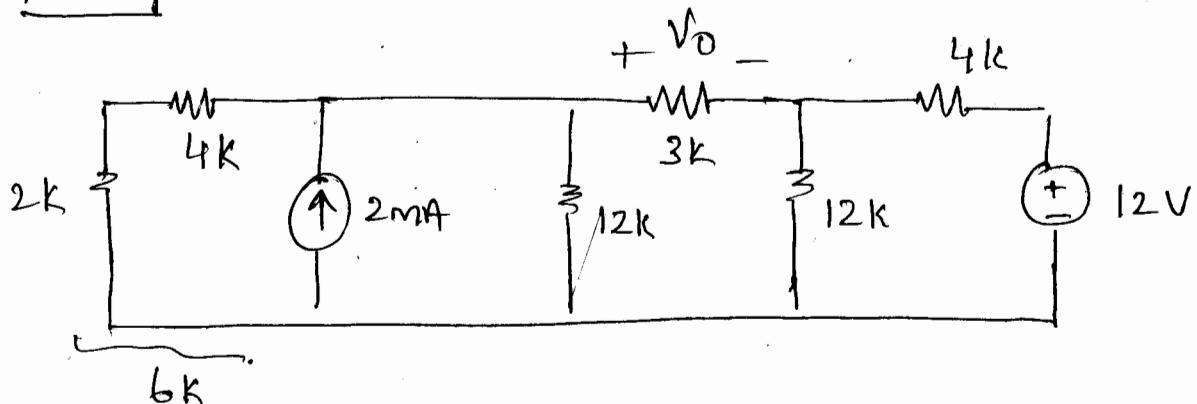



$$-8 + I(4k + 3k + 3k) + 9 = 0$$

$$I = -0.1 \text{ mA}$$

$$V_D = I(8k) = -0.3 \text{ V}$$

$$\boxed{V_D = -0.3 \text{ V}}$$



### NO 4.33

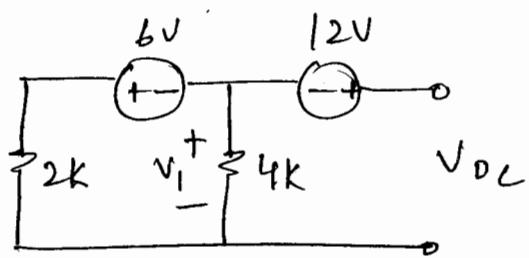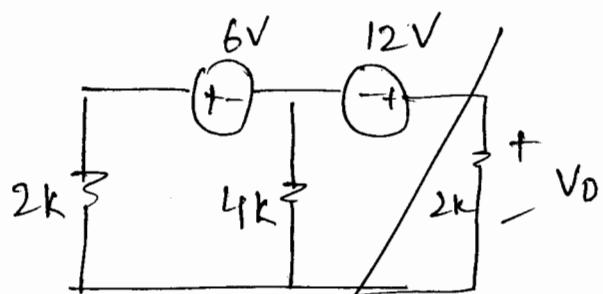


$$V_1 = -6 \left[ \frac{4k}{4k+2k} \right]$$

$$V_1 = -4V$$

$$V_{DC} = 12 + V_1 = 8V$$

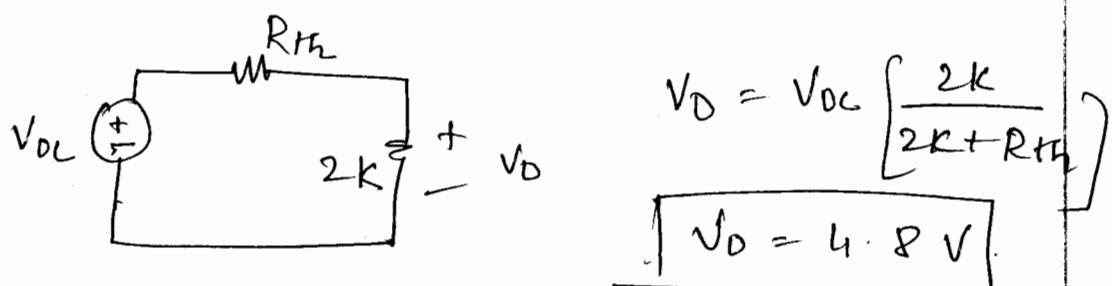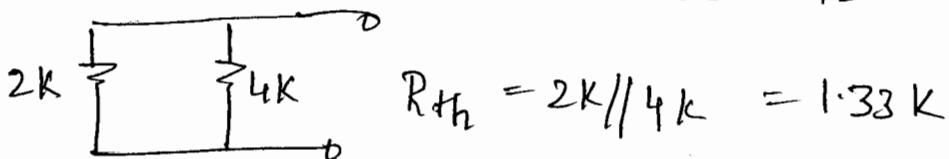

### NO 4.40

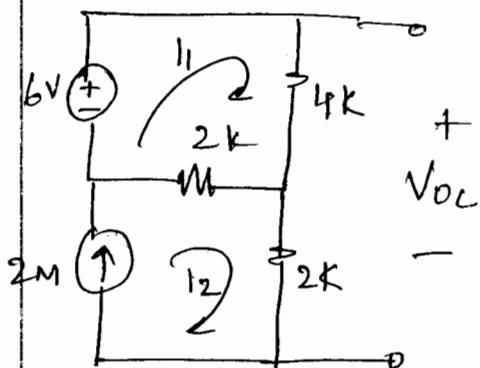


$$I_2 = 2mA.$$

$$-6 + 4kI_1 + 2k(I_1 - 2mA) = 0$$

$$I_1 = \frac{10}{6k} = 1.66mA.$$

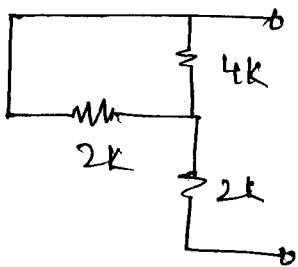
$$\begin{aligned} V_{DC} &= 4kI_1 + 2kI_2 \\ &= 10.66V \end{aligned}$$



$$R_{th} = 2k + (2k \parallel 4k)$$

$$= \frac{10}{3} k$$

$$= 3.33k$$

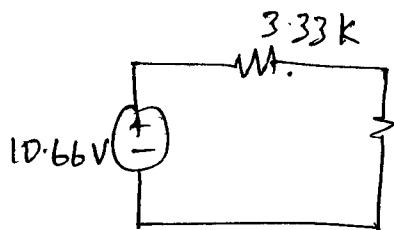


$$V_o = \frac{48}{7} = 6.85V$$

$$\boxed{V_o = 6.85V}$$


14.66

To find  $R_{th}$

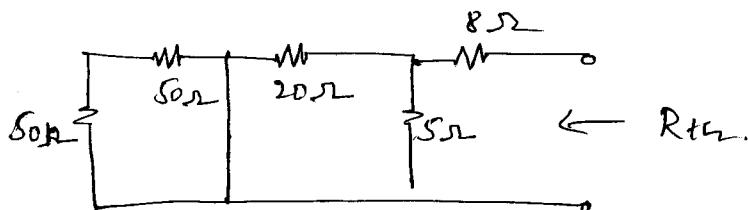


$$R_{th} = 20 \parallel 5 + 8 = 12 \Omega$$

To find  $V_{th}$ .

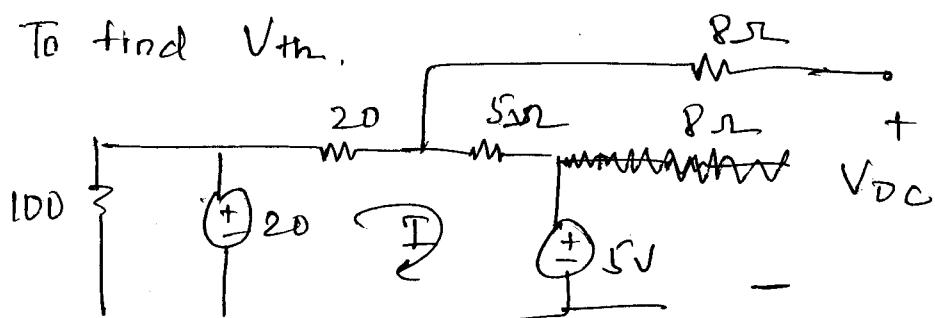

$$I = \frac{20 - 5}{25 \Omega} = 0.6 A.$$

$$V_{DC} = 20 - (0.6 \times 20) = 8V$$

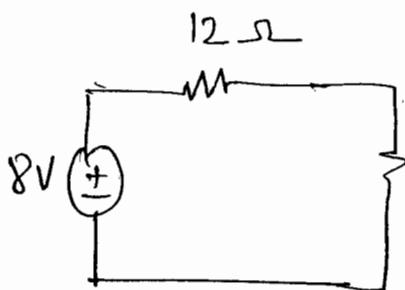

12Ω


$$I_0 = \frac{8V}{24\Omega} = 0.33A$$

$$V_{Th} = 8V$$

$$R_{Th} = 12\Omega$$

$$I_0 = 0.33A$$

4.5D

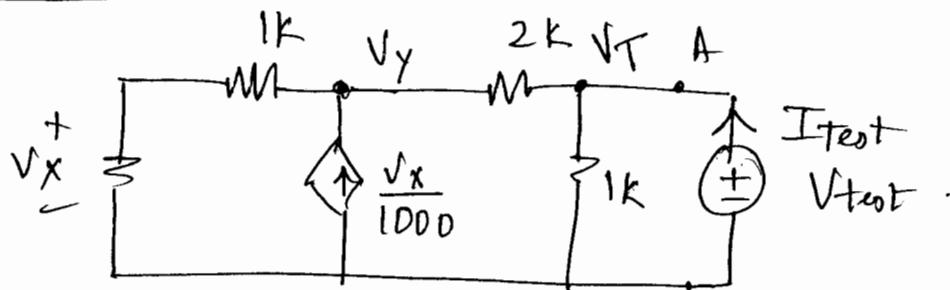

Apply a test source  $V_{test}$

$$\text{we get } \frac{V_{test}}{I_{test}} = R_{Th}$$

$$V_x = V_y \left[ \frac{1k}{1k+1k} \right] = V_x = V_y/2$$

$$\text{At } V_y : \frac{V_x}{1k} = \frac{V_y}{2k} + \frac{V_{test} - V_y}{2k}$$

$$\text{At } V_T : \Rightarrow V_y = V_{test}. \quad \boxed{V_{test} = 0 = V_y}$$

$$I_{test} = \frac{V_{test}}{1k} + \frac{V_{test} - V_y}{2k}$$


we know  $V_y = V_{out}$

$$I_{test} = \frac{V_{test}}{1k}$$


$$\frac{V_{test}}{I_{test}} = 1k = R_{AB}$$

$V_{th} = 0 \quad R_{th} = 1k$

4.62

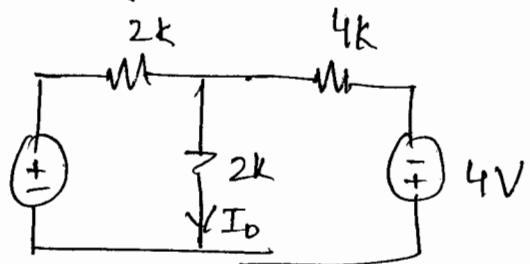



Finding  $I_{sc}$ .

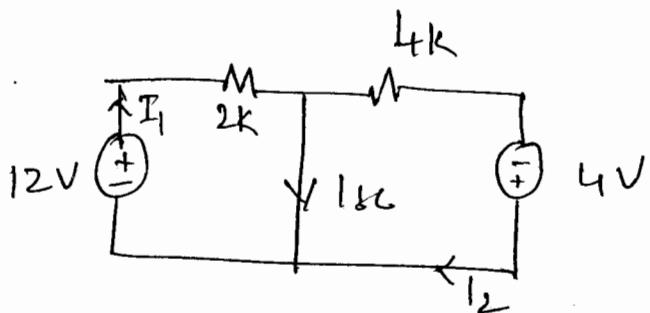

$$I_1 = \frac{12}{2k} = 6mA$$

$$I_2 = \frac{4}{4k} = 1mA$$


$$I_{sc} = I_1 - I_2 = 5mA$$

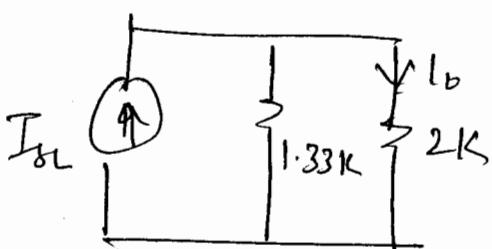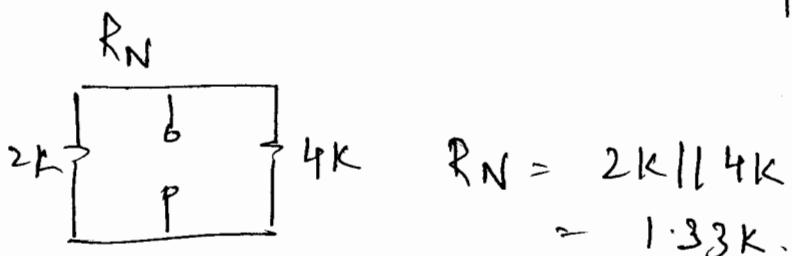


$$I_o = I_{sc} \left[ \frac{R_{out}}{R_{out} + 2k} \right]$$

$I_o = 2mA$

4.65

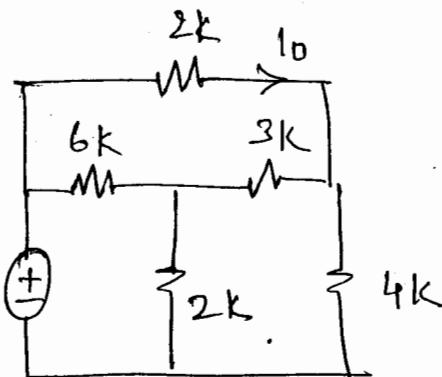

Find  $I_{sc}$

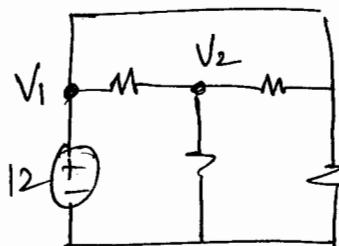


$$V_1 = 12V$$

$$\frac{V_1 - V_2}{6k} + \frac{V_1 - V_2}{3k} = \frac{V_2}{2k}$$


$$V_2 = 6V$$
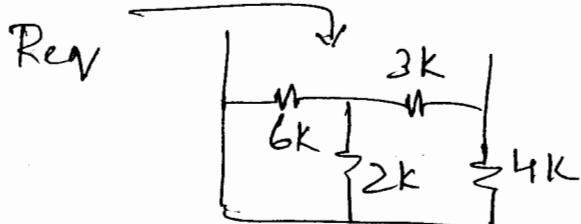
$$I_{sc} = \frac{V_1 - V_2}{3k} + \frac{V_1}{4k} = 5mA$$



$$R_{eq} = 4k \parallel [3k + (2k \parallel 6k)]$$


$$= 2.12k$$

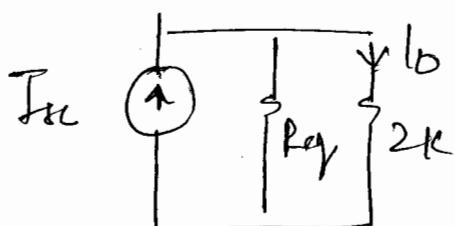

$$I_o = I_{sc} \left[ \frac{R_{eq}}{R_{eq} + 2k} \right]$$

$$I_o = 2.57mA$$

4.69

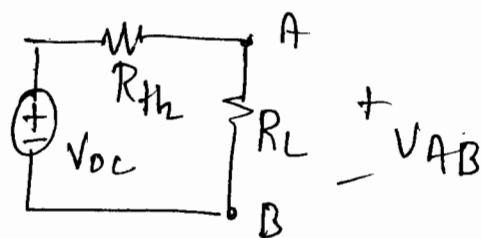

$$V_{AB} = V_{DC} \left[ \frac{R_L}{R_L + R_{Th}} \right]$$

$$\Rightarrow V_{DC} = V_{AB} \left[ 1 + \frac{R_{Th}}{R_L} \right]$$

If  $R_L = 8\text{k}$   $V_{AB} = 16\text{V}$   $\Rightarrow V_{DC} = 16 \left[ 1 + \frac{R_{Th}}{8\text{k}} \right]$

$R_L = 2\text{k}$   $V_{AB} = 8\text{V}$   $\Rightarrow V_{DC} = 8 \left[ 1 + \frac{R_{Th}}{2\text{k}} \right]$


Solving the simultaneous linear equations

$$R_{Th} = 4\text{k}\Omega \quad V_{DC} = 24\text{V}$$

If  $R_L = 20\text{k}\Omega$   $V_{AB} = 24 \left( \frac{20}{20+4} \right)$

$$\boxed{V_{AB} = 20\text{V}}$$

4FEI

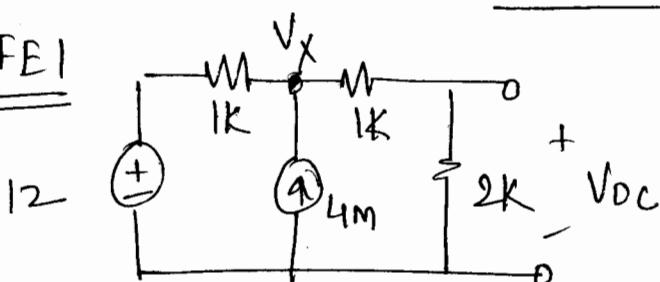


$$\frac{V_X - 12}{1\text{k}} + \frac{V_X}{3\text{k}} - 4\text{mA} = 0$$

$$V_X = 12\text{V}$$


$$V_{DC} = V_X \left( \frac{2\text{k}}{2\text{k} + 1\text{k}} \right)$$

$$V_{DC} = 8\text{V}$$

(10)

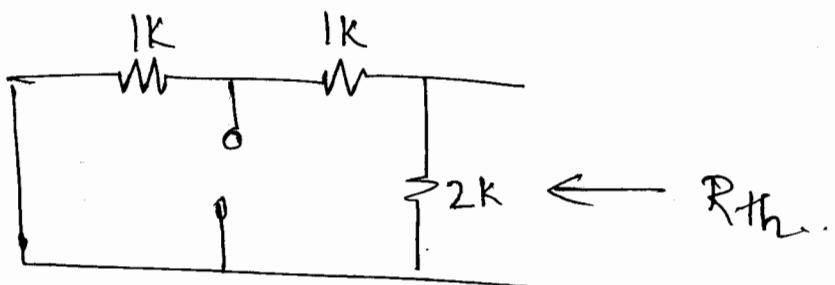

$$R_{th} = 2k \parallel 2k = 1k\Omega$$

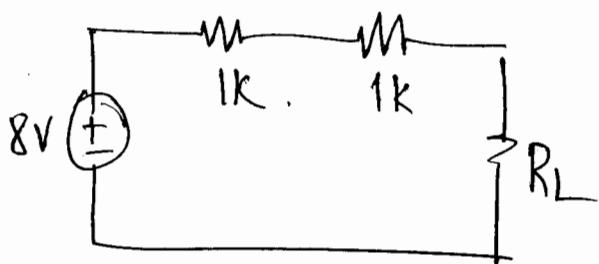

$R_L = 2k$  for max P.T.

$$\left(\frac{8}{4k}\right)^2 (2k) = 8mW$$

$$\boxed{P_{max} = 8mW}$$