

Desk copy

ECE 300
Spring Semester, 2004
HW Set #6

March 2, 2004
wlg

Name Green
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

6.57 easy problem: (c) $v_1(t) = [k_1 e^{-t} \cos 2t + k_2 e^{-t} \sin 2t] V u(t)$

6.61 $v(t) = [10e^{-4t} \cos 2t - 40e^{-t} \sin 2t] V u(t)$

6.63 $v(t) = [12 - 13.75e^{-1127t} + 1.75e^{8873t}] V u(t)$


6.64 $v_o(t) = [16.67[e^{-200000t} - e^{-800000t}]] V u(t)$

6.67 $I(t) = (4.57e^{-8t} - 0.57e^{-t}) A u(t)$

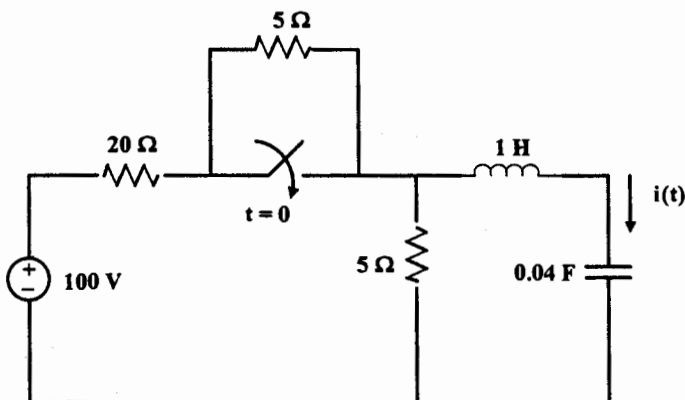6.71 Characteristic equation: $s^2 + 4 \times 10^6 s + 3 \times 10^{12} = 0$

$v_o(t) = 19.2[e^{-1000000t} - e^{-3000000t}] V u(t)$

6x1 Find $i(t)$ for the circuit below. Answer: $i(t) = 0.727e^{-2t} \sin(4.58t) A u(t)$



Wolq

6.57 $V(t)$ of a network is given as

$$\frac{d^2 V_1(t)}{dt^2} + 2 \frac{dV_1(t)}{dt} + 5V_1(t) = 0$$

(a) characteristic equation:

$$s^2 + 2s + 5 = 0$$

(b) the circuit natural frequencies.
(only one natural frequency)

Compare:

$$s^2 + 2s + 5 = 0$$

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

 ω_n is the natural frequency.

$$\omega_n^2 = 5$$

$$\omega_n = \sqrt{5} = 2.24 \text{ rad/sec}$$

$$\zeta = \frac{2}{2\omega_n} = 0.45$$

(c) the expression for $V_1(t)$.

Since the equation does not have a forcing function we need only $x_c(t)$. First write the root of the C.E.


$$s = -1 \pm j2$$

$$V_1(t) = e^{-\zeta\omega_n t} \left(A \cos(\omega_n \sqrt{1-\zeta^2} t) + B \sin(\omega_n \sqrt{1-\zeta^2} t) \right)$$

$$V_1(t) = e^{-t} [A \cos(2t) + B \sin(2t)] V_u(t)$$

wlg

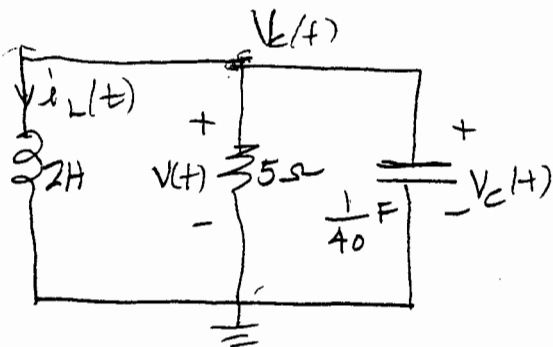6.61 For the following circuit $i_L(0^-) = 1\text{ A}$,
 $V_C(0^-) = 10\text{ V}$. Determine $v(t)$.



$$\frac{V_C(t)}{R} + C \frac{dV_C}{dt} + i_L(t) = 0 \quad (1)$$

$$\frac{dV_C(0^+)}{dt} = -\frac{i_L(0^+)}{C} - \frac{V_C(0^+)}{RC} = -40 - 80 = -120$$

so: $V_C(0^+) = 10\text{ V}$, $\dot{V}_C(0^+) = -120\text{ V/s}$

with

$$i_L = \frac{1}{L} \int_0^t V_C(t) dt + i_L(0^+)$$

substituting into (1)

$$\frac{V_C(t)}{R} + C \frac{dV_C}{dt} + \frac{1}{L} \int_0^t V_C(t) dt + 1 = 0 \quad (2)$$

Take the derivative of (2)

$$C \frac{d^2 V_C}{dt^2} + \frac{1}{R} \frac{dV_C}{dt} + \frac{V_C(t)}{L} = 0$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{dV_C}{dt} + \frac{V_C(t)}{L} = 0 \quad (3)$$

wkg

6.61 continued

Putting parameter values into (3) gives;

$$\frac{d^2 V_c(t)}{dt^2} + 8 \frac{dV_c(t)}{dt} + 20 V_c(t) = 0$$

compare with standard form;

$$s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$s^2 + 8s + 20 = 0$$

$$\omega_n = \sqrt{20} = 4.47 \text{ rad/sec}$$

$$2\zeta\omega_n = 8 \quad \zeta\omega_n = 4$$

$$\zeta = \frac{4}{\omega_n} = \frac{4}{\sqrt{20}} = 0.894 \text{ (underdamped)}$$

$$V_c(t) = e^{-\zeta\omega_n t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)]$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2} = \sqrt{20} (\sqrt{1 - 0.894^2})$$

$$\omega_d = 2.0 \text{ rad/sec}$$

$$V_c(t) = V(t) = e^{-4t} [K_1 \cos(2t) + K_2 \sin(2t)] \quad (4)$$

$$V(0^+) = 10V = K_1$$

$$\frac{dV(0^+)}{dt} = -200 = e^{-4t} [-2K_1 \sin(2t) + 2K_2 \cos(2t)] - 4e^{-4t} [K_1 \cos(2t) + K_2 \sin(2t)] \quad (5)$$

wlg

6.61 continued

Evaluate (5) at $t=0$

$$-120 = 2K_2 - 4K_1 \quad (6)$$

$$= 2K_1 + K_2 = -60$$

$$\text{and } K_1 = 10$$


$$K_2 = -60 + 20 = -40$$

$$V(t) = e^{-4t} [10 \cos(2t) - 40 \sin(2t)]$$

wlg

6.63. Find $V_c(t)$ for $t > 0$; $V_c(0^-) = 0 = V_c(0^+)$

$$i_L(0^-) = i_L(0^+) = 0$$

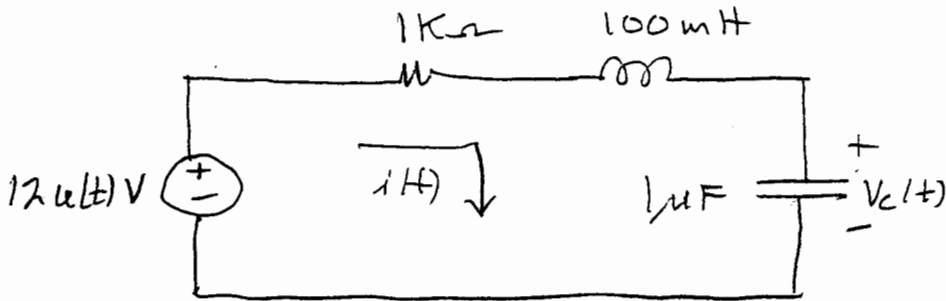

$$Ri(t) + L \frac{di}{dt} + V_c(t) = 12 \quad (1)$$

but

$$i(t) = C \frac{dV_c}{dt} \quad (2)$$

(2) into (1);

$$RC \frac{dV_c}{dt} + LC \frac{d^2 V_c}{dt^2} + V_c(t) = 0$$

$$\frac{d^2 V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{V_c(t)}{LC} = \frac{12}{LC} \quad (3)$$

$$\frac{d^2 V_c}{dt^2} + 10,000 \frac{dV_c}{dt} + 10,000,000 V_c(t) = 120,000,000$$

$$V_c = V_f + V_n$$

$$V_f = 12 \text{ V}$$

char. Eq.

$$s^2 + 10,000s + 10,000,000 = 0$$

wlg

2

6.63 continued

Roots of characteristic equation are:

$$\left. \begin{aligned} s_1 &= -1127 \\ s_2 &= -8873 \end{aligned} \right\} \text{overdamped}$$

$$v_c(t) = \left[12 + k_1 e^{-1127t} + k_2 e^{-8873t} \right] u(t) \text{ V} \quad (4)$$

$$\boxed{v_c(0^+) = 0}$$

and from (2), with $i(0^+) = 0 \rightarrow \boxed{\dot{v}_c(0^+) = 0}$

Back to (4), evaluated at $t=0$:

$$0 = 12 + k_1 + k_2$$

$$\boxed{k_1 + k_2 = -12}$$

Take the derivative of (4)

$$\dot{v}_c(t) = -1127k_1 e^{-t} - 8873k_2 e^{-t} \quad \Big|_{t=0}$$

$$0 = -1127k_1 - 8873k_2$$

$$\begin{bmatrix} 1 & 1 \\ -1127 & -8873 \end{bmatrix} \begin{bmatrix} k_1 \\ k_2 \end{bmatrix} = \begin{bmatrix} -12 \\ 0 \end{bmatrix}$$

$$k_1 = -13.8$$


$$k_2 = 1.75$$

∴ Back to (4)

$$\boxed{v_c(t) = \left[12 - 13.8 e^{-1127t} + 1.75 e^{-8873t} \right] u(t) \text{ V}}$$

QED

wlg

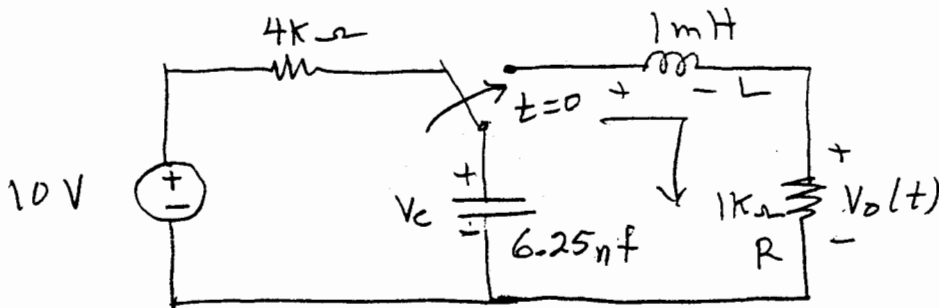6.64 Find $V_o(t)$ for $t > 0$. Plot using MATLAB

$$V_c(0^+) = 10V, \quad i(0^+) = 0, \quad V_o(0) = 0$$

We can write

$$-\frac{1}{C} \int_0^t i dt - 10 + L \frac{di}{dt} + Ri(t) = 0 \quad (1)$$

Take the derivative of (1)

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i(t)}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i(t)}{LC} = 0 \quad (2)$$

Since $V_o(t) = Ri(t)$ this means we can multiply (2) by R and have have $V_o(t)$

Thus,

$$\frac{d^2 V_o}{dt^2} + \frac{R}{L} \frac{dV_o}{dt} + \frac{V_o(t)}{LC} = 0 \quad (3)$$

Substituting in numbers gives

$$\ddot{V}_o(t) + 1 \times 10^6 \dot{V}_o(t) + 16 \times 10^{10} V_o(t) = 0 \quad (4)$$

$$s^2 + 1 \times 10^6 s + 16 \times 10^{10} = 0 \quad (5)$$

whg

2

6.64 continued

Roots of the characteristic equation are;

$$s_1 = -200,000, \quad s_2 = -800,000$$

$$V_o(t) = K_1 e^{-200,000t} + K_2 e^{-800,000t} \quad (6)$$

Now

$$V_o(0^+) = 10$$

and

$$\dot{V}_o(0^+) \text{ we need. } \rightarrow \dot{V}_o(0^+) = R \frac{di(0^+)}{dt}$$

Go to Eq (1)

$$\frac{di(0^+)}{dt} = -\frac{Ri(0^+) + 10}{L}$$

so

$$R \frac{di(0^+)}{dt} = \dot{V}_o(0^+) = +\frac{10R}{L} = +10,000,000$$

From Eq (6) evaluated at $t=0$;

$$\boxed{10 = K_1 + K_2} \quad (7)$$

Take the derivative of Eq (6), evaluated at $t=0$.


$$\dot{V}_o(0^+) = -200,000 K_1 - 800,000 K_2 = +10,000,000$$

$$\boxed{-2K_1 - 8K_2 = +100} \quad (8)$$

From (7) & (8) $K_1 = 16.67, K_2 = -16.67$

$$V_o(t) = 16.67 \left[e^{-200,000t} - 16.67 e^{-800,000t} \right] \text{ u(t) V}$$

w/

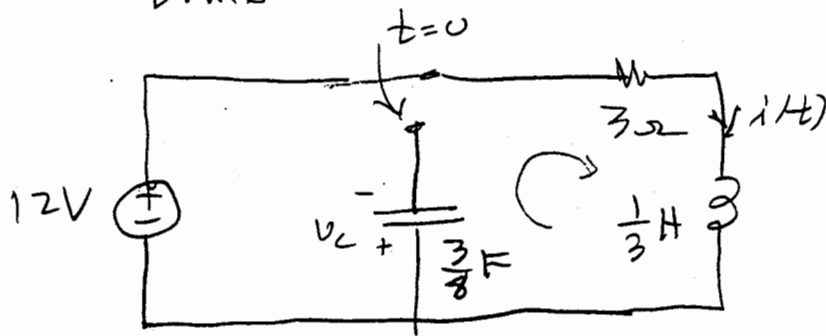6.67 Find $i(t)$, switch closed for a long time

$$\frac{1}{\frac{1}{3} \times \frac{3}{8}} = 8$$

$$i(0^-) = i(0^+) = 4 \text{ A} \quad (1)$$

$$\frac{1}{C} \int i dt + v_C(0) + R i(t) + L \frac{di}{dt} = 0 \quad (2)$$

From (1)

$$\frac{d^2 i(0^+)}{dt^2} = -\frac{R}{L} i(0^+) = -\frac{3 \times 10 \times 4}{1/3} = -36 \quad (3)$$

Taking the derivative of (2)

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad (4)$$

Putting in numbers

$$\frac{d^2 i}{dt^2} + 9 \frac{di}{dt} + 8 i(t) = 0$$

$$s^2 + 9s + 8 = 0$$

$$(s+8)(s+1) = 0 \quad (5)$$

Overdamped

why

6.67 continued

2

$$i(t) = k_1 e^{-8t} + k_2 e^{-t} \quad (6)$$

$$i(0^+) = 4 = \left[k_1 e^{-8t} + k_2 e^{-t} \right] \Big|_{t=0}$$

$$\text{so } \boxed{-k_1 + k_2 = 4}$$

Take the derivative of Eq (6)

$$\frac{di}{dt} = -8k_1 e^{-8t} - k_2 e^{-t} \quad (7)$$

Evaluate Eq (7) at $t=0$

$$\boxed{-36} = -8k_1 - k_2 \quad \text{From Eq (3)}$$

$$k_1 + k_2 = 4$$

$$-8k_1 - k_2 = -36$$

$$k_1 = 4.57$$

$$k_2 = -0.57$$


Back to Equation (6)

$$i(t) = \boxed{[4.57 e^{-8t} - 0.57 e^{-t}] u(t) \text{ A}}$$

Wkg

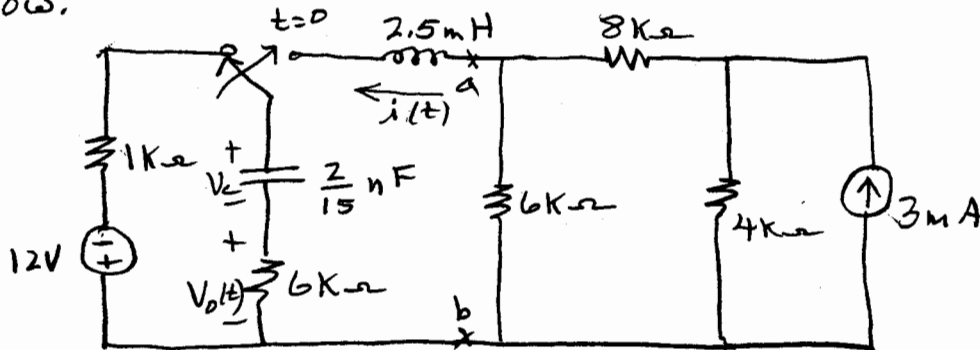6.7

Find $V_o(t)$ for $t > 0$ in the circuit below.




The capacitor is charged to $V_c = -12V$ prior to $t=0$. Just after $t=0$, that is, $t=0^+$, the capacitor voltage is $V_c(0^+) = -12V$.

The inductor current, $i(t)$, does not change instantaneously so $i(0^+) = 0$.

Using Thevenin's Theorem, the circuit to the right of terminals a-b is reduced as shown in the following diagram.

$i_L(0^+) = 0$

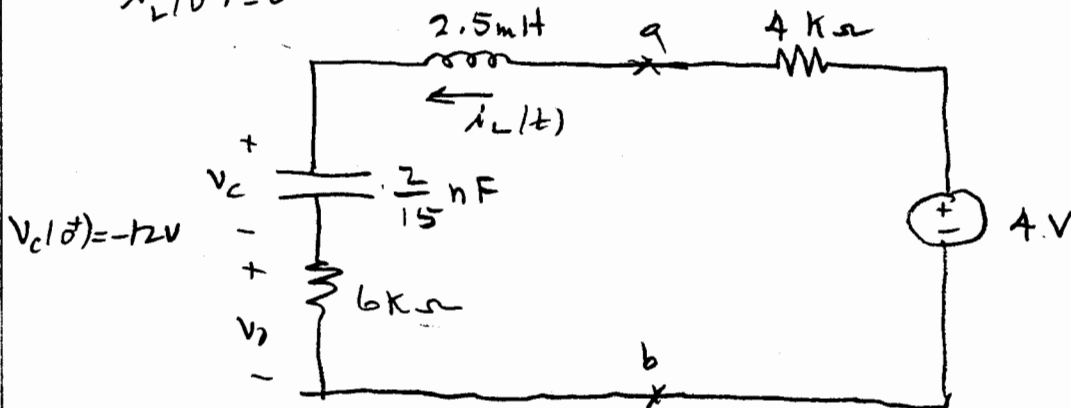

Applying KVL around the circuit gives the following equation:

wlq

6.7 cont.

2

$$R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt - 12 = 4 \quad (1)$$

$$R = 10 \text{ k}\Omega$$

$$L = 2.5 \text{ mH}$$

$$C = \frac{2}{15} \text{ nF}$$

Differentiating (1) gives,

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i(t)}{C} = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i(t)}{LC} = 0 \quad (2)$$

OR

$$\frac{d^2i}{dt^2} + 4 \times 10^6 \frac{di}{dt} + 3 \times 10^{12} i = 0 \quad (3)$$

Characteristic equation is

$$s^2 + 4 \times 10^6 s + 3 \times 10^{12} = 0 \quad (4)$$

$$(s + 1 \times 10^6)(s + 3 \times 10^6) = 0$$

$$i(t) = K_1 e^{-1 \times 10^6 t} + K_2 e^{-3 \times 10^6 t} \quad (5)$$

There is no steady state term as such.

wky

3

6.71 continued

We know $i(0^+) = 0$; from (1) we have

$$Ri(0^+) + L \frac{di(0^+)}{dt} = 16$$

$$\text{OR } \frac{di(0^+)}{dt} = \frac{16}{L} = \frac{16}{2.5} \times 10^3 = 6.4 \times 10^3$$

$$V_o(0^+) = 0; \quad V_o(t) = 6 \times 10^3 \times \frac{di(0^+)}{dt} = 38.4 \times 10^6 \quad (6)$$

From (5)

$$i(t) = \left[k_1 e^{-1 \times 10^6 t} + k_2 e^{-3 \times 10^6 t} \right]$$

and (7)

$$V_o(t) = 6 \times 10^3 i(t)$$

$$V_o(t) = k_3 e^{-1 \times 10^6 t} + k_4 e^{-3 \times 10^6 t} \quad (8)$$

$$V(0^+) = 0 = k_3 + k_4$$

$$\frac{dV(0^+)}{dt} = 38.4 \times 10^6 = -1 \times 10^6 k_3 - 3 \times 10^6 k_4$$

$$k_3 + k_4 = 0$$

$$k_1 = 19.2$$

$$-k_3 - 3k_3 = 38.4$$


$$k_2 = -19.2$$

$$V_o(t) = 19.2 \left[e^{-1 \times 10^6 t} - e^{-3 \times 10^6 t} \right] V, u(t)$$


wlg

①

b x 1 FIND $i(t)$ for the circuit below.

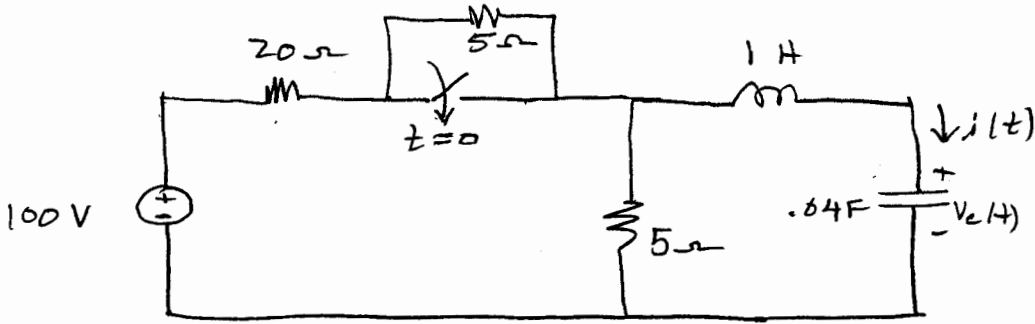


FOR $t < 0$

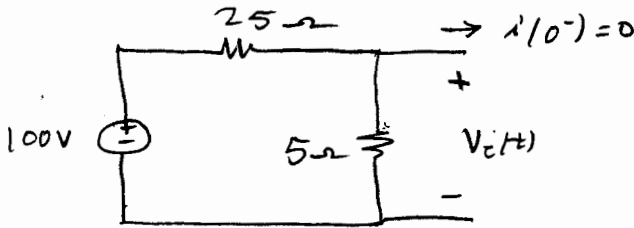


$$V_c(0^-) = \frac{100 \times 5}{30} = \frac{50}{3} \text{ V} = 16.67 \text{ V} \quad (A)$$

$t > 0$

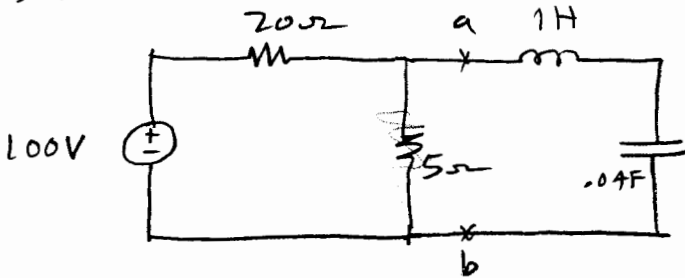

FIND THE THÉVENIN TO THE LEFT OF a-b

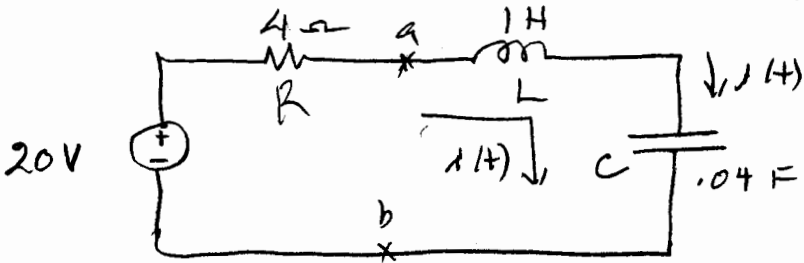

WRT R KVL:

$$R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt + V_C(0) = 20 \quad (1)$$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i(t)}{C} = 0 \quad (2)$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i(t)}{LC} = 0 \quad (3)$$

From (1), with $V(0) = 16.67$ (from (A))

$$\frac{di(0)}{dt} = \frac{20 - 16.67}{L = 1H} = 3.33 \quad (4)$$

From (3), the char. Eq. is

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad (5)$$

Putting in numbers;

$$s^2 + 4s + 25 = 0 \quad \checkmark$$

$$(s + 2 + j4.58)(s + 2 - j4.58) = 0$$

$$i(t) = e^{-2t} [K_1 \cos(4.58t) + K_2 \sin(4.58t)] \quad (6)$$

$$i(0) = 0 = K_1 + 0 \times K_2$$

$$\boxed{K_1 = 0}$$

$$\left. \frac{di}{dt} \right|_{t=0} = e^{-2t} [4.58 K_2 \cos(4.58t)] - 2e^{-2t} K_2 \sin 4.58t$$

From (4)

$$3.33 = 4.58 K_2 \quad (7)$$

wlq

3

Ex 1 continued

From (7)

$$k_2 = \frac{3.33}{4.58} = 0.727$$

i.

$$i(t) = 0.727 e^{-2t} \sin(4.58t) \text{ A}$$

QED