

ECE 300
Spring Semester, 2004
HW Set #7

Desk Copy

March 23, 2004

wlg

Name GREEN
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

7.6 (a) $i(t) = 8\cos(377t + 68)$ A, (b) $i(t) = 4\sin(377t + 154)$ A = $4\cos(377t + 64)$ A

7.14 $Z_{AB} = 4.79\angle-7.33$ Ω

7.18 $C = 431$ μ F

7.21 $v(t) = 5.17\cos(377t + 45)$ V

7.26 $I_L = 1\angle-54.3$ A; $I_C = 0.01\angle125.7$ A

7.43 $Z = 0.78\angle130.9$ Ω

7.47 $V_o = 3.09\angle-23.8$ V

7.51 $V_o = 9\angle51.3$ V


7.52 $V_o = 5.55\angle86.8$ V

7.68 ~~$V_o = 2.61\angle125.8$ V (from answer book; not verified, yet)~~

$V_o = 0.485 \angle 104^\circ$ V

wk 5

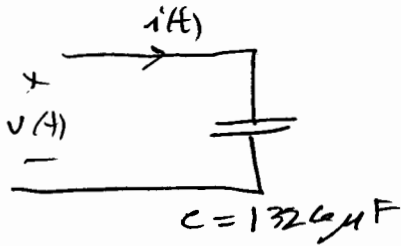
7.6 Determine $i(t)$ in the following circuit for the given $v(t)$ and capacitance



(a) $v(t) = 16 \cos(377t - 22^\circ) \text{ V}$

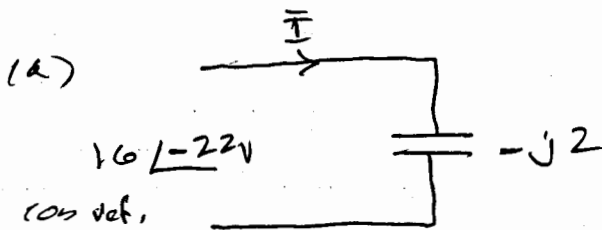(b) $v(t) = 8 \sin(377t + 64^\circ) \text{ V}$

$$\frac{1}{\omega C} = \frac{1}{3.77 \times 10^2 \times 0.1326 \times 10^{-2}} = 2$$



$$\underline{I} = \frac{16 \angle -22^\circ}{2 \angle -90^\circ} = 8 \angle 68^\circ$$

$$\boxed{i(t) = 8 \cos(377t + 68^\circ) \text{ A}}$$


Also, note that

$$i(t) = C \frac{dv}{dt} = 0.1326 \times 10^{-2} \times 16 \times 377 \sin(377t - 22^\circ)$$

$$i(t) = -8 \sin(377t - 22^\circ) = 8 \cos(377t + 68^\circ)$$

$$\boxed{i(t) = 8 \cos(377t + 68^\circ) \text{ A}}$$

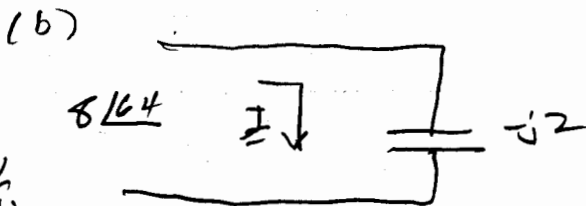Same answer as obtained by phasor method.




$$\underline{I} = \frac{8 \angle 64^\circ}{2 \angle -90^\circ} = 4 \angle 154^\circ$$

$$\boxed{i(t) = 4 \sin(377t + 154^\circ) \text{ A}}$$

w8g

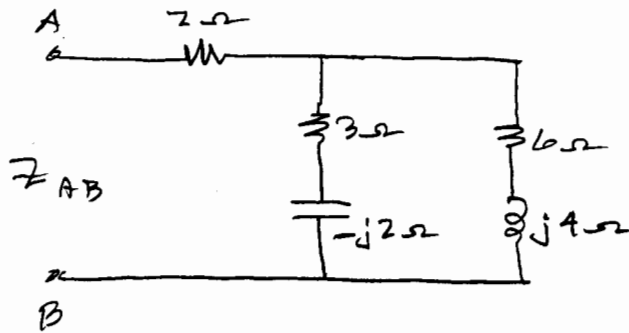7.14 FIND the impedance seen looking into terminals A-B.



$$Z_{AB} = 2 + \frac{(3-j2)(6+j4)}{(3-j2) + (6+j4)}$$

$$Z_{AB} = 2 + 2.82 \angle -12.53^\circ$$

$$Z_{AB} = 4.79 \angle -7.33^\circ \Omega$$


polar form

$$Z_{AB} = (6.75 - j0.611) \Omega$$

rectangular form

wl2

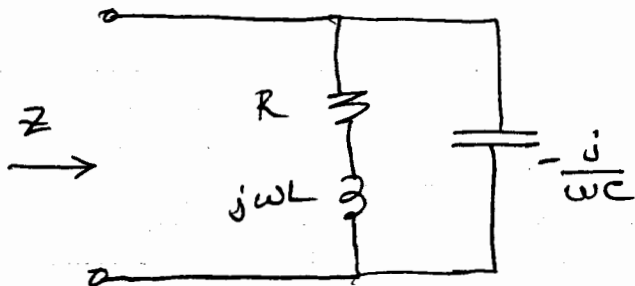7.18 At $\omega = 10$, the impedance seen looking into the terminals is purely real. Determine C .



$$Z = \frac{(R + j\omega L) \left(-\frac{j}{\omega C}\right)}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{-j(R + j\omega L)}{\omega RC + j(\omega^2 LC - 1)}$$

$$Z = \frac{\omega L - jR}{\omega RC + j(\omega^2 LC - 1)} \times \frac{[\omega RC - j(\omega^2 LC - 1)]}{[\omega RC - j(\omega^2 LC - 1)]}$$

$$Z = \frac{\cancel{\omega^2 RLC} - j\omega L(\omega^2 LC - 1) - j\omega R^2 C - \cancel{\omega^2 RLC} + R}{\omega^2 R^2 C^2 + (\omega^2 LC - 1)^2}$$

$$= \frac{jR - j[\omega L(\omega^2 LC - 1) + \omega R^2 C]}{D}$$

Make $\omega L(\omega^2 LC - 1) + \omega R^2 C = 0$

$$\omega^2 L^2 C - L + R^2 C = 0$$


$$C(\omega^2 L^2 + R^2) = L$$

$$C = \frac{L}{\omega^2 L^2 + R^2} = \frac{10 \times 10^{-3}}{[377^2 \times (0.01)^2 + 9]}$$


$$C = 431 \mu F$$

wk2

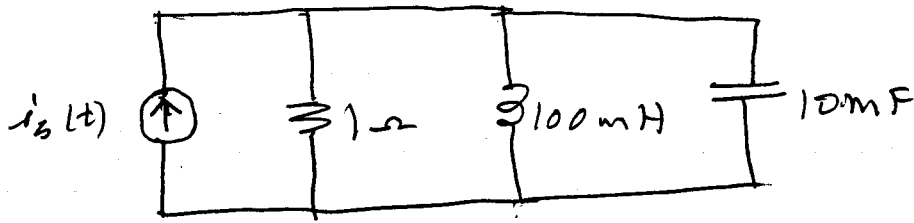7.21 Draw the frequency-domain circuit and calculate $v(t)$ for the following:


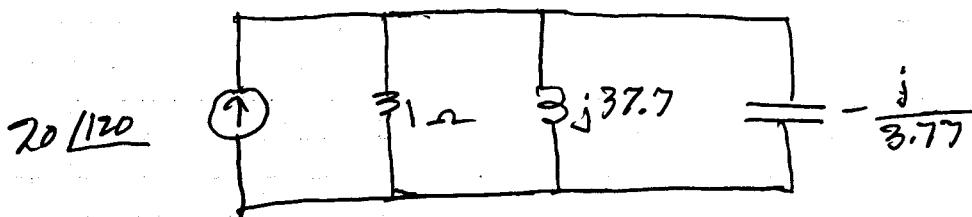
$$i_s(t) = 20 \cos(377t + 120^\circ) \text{ A} \rightarrow \omega = 377$$



$$Y = 1 + \frac{1}{j37.7} - \frac{j37.7}{j} = 1 - \frac{j}{37.7} + j3.77$$

$$V = \frac{I}{Y} = \frac{20 \angle 120}{1 + j3.74}$$

$$V = 5.17 \angle 45 \text{ V}$$

$$v(t) = 5.17 \cos(377t + 45^\circ) \text{ V}$$

wrg

7.26 For the circuit below, determine \hat{I}_L and \hat{I}_C . Show, both analytically and graphically (phasors) that

$$\hat{I} = \hat{I}_L + \hat{I}_C$$



$$Z = 1 + \frac{(10 \angle 90)(1000 \angle -90)}{990 \angle -90} \Omega$$

$$Z = 10.15 \angle 84.3$$

$$\hat{I} = \frac{10 \angle 30}{10.15 \angle 84.3} = 0.99 \angle -54.3$$


$$\hat{I}_L = \frac{\hat{I} \times (1000 \angle -90)}{990 \angle -90} = 0.99 \angle -54.3 \times \frac{1000}{990}$$

$$\hat{I}_L = 1 \angle -54.3 \text{ A}$$

$$\hat{I}_C = \frac{\hat{I} \times j10}{990 \angle -90} = \frac{0.99 \angle -54.3 \times 10 \angle 90}{990 \angle -90}$$

$$\hat{I}_C = 0.01 \angle 125.7 \text{ A}$$

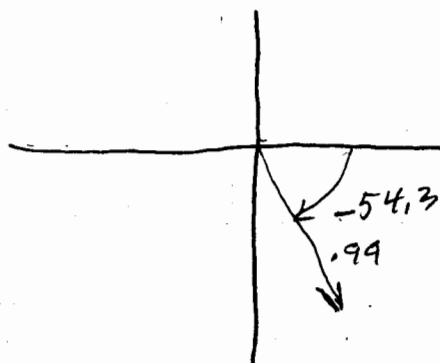
$$\hat{I} = 1 \angle -54.3 + 0.01 \angle 125.7 = 0.99 \angle -54.3 \text{ A}$$



Not good to illustrate phasors.

wlg

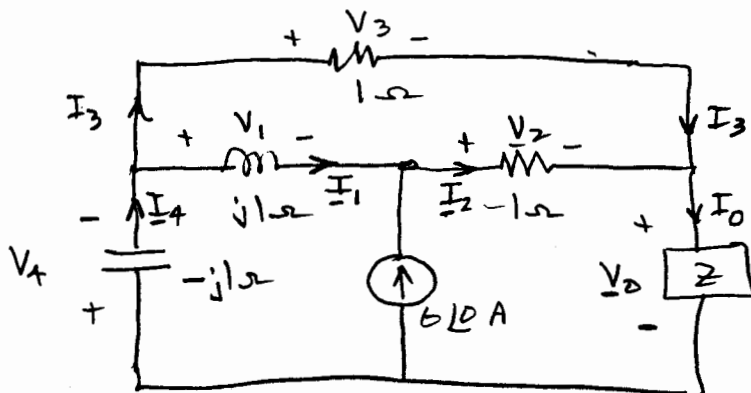7A3 In the following diagram $V_1 = 2 \angle 45^\circ \text{ V}$
Find Z .



$$\underline{I}_1 = \frac{V_1}{j1} = \frac{2 \angle 45^\circ}{j1} = 2 \angle -45^\circ \text{ A}$$

$$\underline{I}_2 = 6 + \underline{I}_1 = 6 + 2 \angle -45^\circ = 7.414 - j1.414 \text{ A}$$

$$\underline{V}_2 = \underline{I}_2 \times 1 = 7.414 - j1.414 \text{ V}$$

$$\underline{V}_3 = \underline{V}_1 + \underline{V}_2 = 2 \angle 45^\circ + (7.414 - j1.414) = 8.83 \text{ V}$$

$$\underline{I}_3 = \frac{V_3}{1} = 8.83 \text{ A}$$

$$\underline{I}_4 = \underline{I}_1 + \underline{I}_3 = 2 \angle -45^\circ + 8.83 = (10.242 - j1.414) \text{ V}$$

$$\underline{V}_4 = (-j) \underline{I}_4 = (-1.414 - j10.242) \text{ V}$$

$$V_0 + V_4 + V_3 = 0$$

$$V_0 = -(V_3 + V_4) = -8.83 + (1.414 + j10.242)$$

$$V_0 = (-7.416 + j10.242) \text{ V}$$


$$I_0 = I_2 + I_3 = 7.414 - j1.414 + 8.83 = (16.24 - j1.414) \text{ A}$$

$$Z = \frac{V_0}{I_0} = \frac{(-7.416 + j10.242)}{(16.24 - j1.414)}$$

$$Z = 0.78 \angle 130.9^\circ \Omega$$

7.47

Find V_o

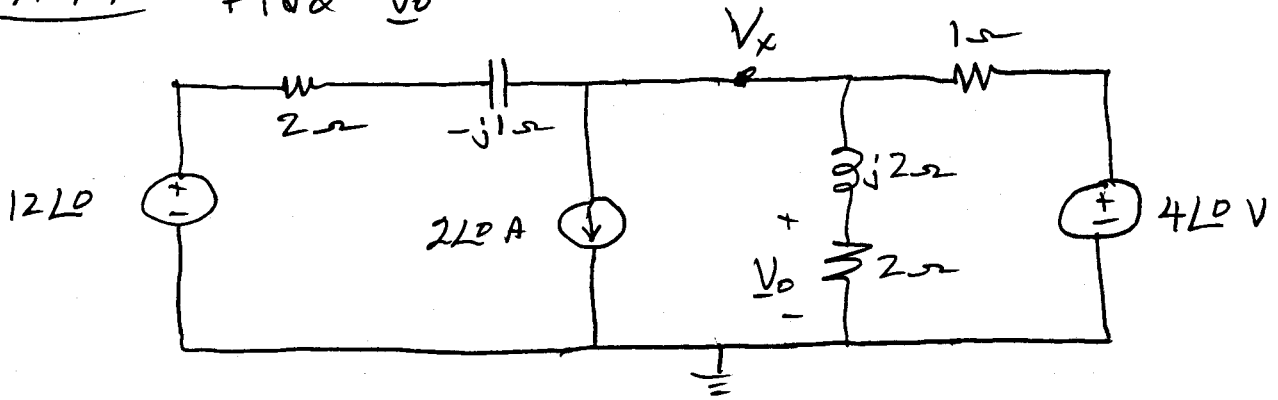

Find V_x then

$$V_o = \frac{2V_x}{2+j2} \quad (1)$$

$$\frac{V_x}{2+j2} + \frac{V_x - 4}{1} + \frac{V_x - 12}{2-j} = -2$$

$$(0.25 - j0.25)V_x + V_x - 4 + (0.4 + j0.2)V_x - 12(0.4 + j0.2) = -2$$

$$(1.65 - j0.05)V_x = 4 - 2 + 12(0.4 + j0.2)$$

$$= 6.8 + j2.4$$


$$V_x = \frac{6.8 + j2.4}{1.65 - j0.05} = 4.37 \angle 21.18$$

$$V_o = \frac{2 \times 4.37 \angle 21.18}{2 + j2} = 3.09 \angle -23.8$$

$$V_o = 3.09 \angle -23.8 \text{ V}$$

wly

7.51 Use mesh analysis to find V_0

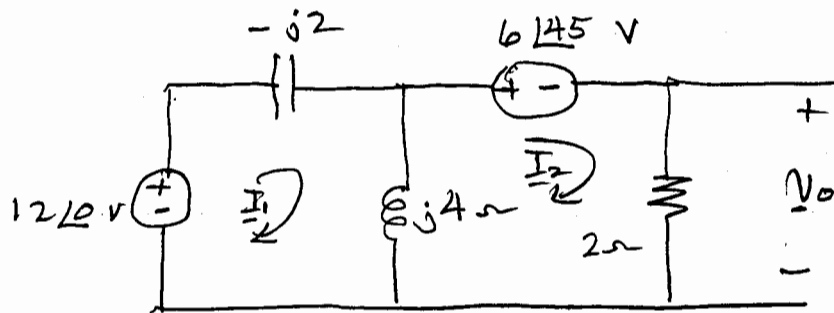

$$\begin{bmatrix} j2 & -j4 \\ -j4 & 2+j4 \end{bmatrix} \begin{bmatrix} \underline{I}_1 \\ \underline{I}_2 \end{bmatrix} = \begin{bmatrix} 12 \\ -6\angle 45 \end{bmatrix}$$

$$\underline{I}_1 = 5.7 \angle 10.6^\circ \text{ A}$$


$$\underline{I}_2 = 4.5 \angle 51.3^\circ \text{ A}$$

$$\underline{V}_0 = 2 \times \underline{I}_2$$

$$\underline{V}_0 = 9 \angle 51.3^\circ \text{ V}$$

wlg

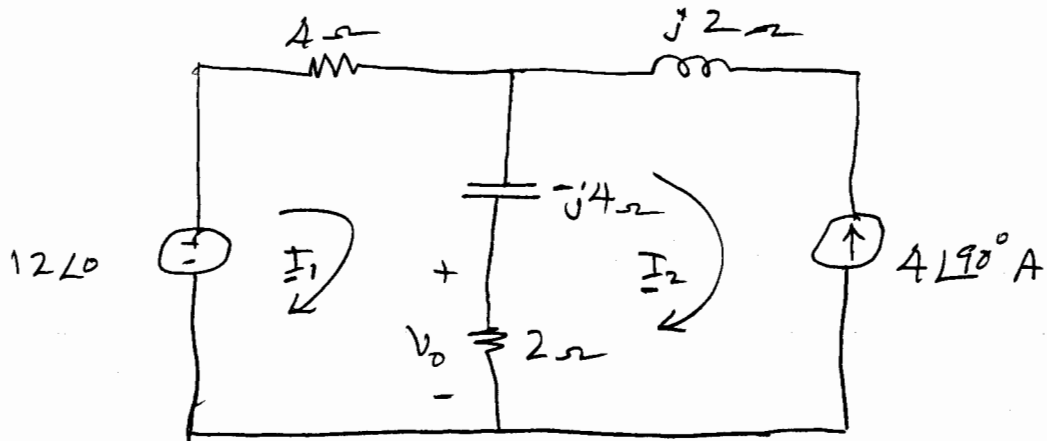7.52 Find V_o in the circuit below using mesh analysis.



$$(6 - j4) \underline{I}_1 - (2 - j4) \underline{I}_2 = 12$$

$$0 \underline{I}_1 - \underline{I}_2 = 4 \angle 90^\circ$$

$$\underline{I}_1 = 1.24 \angle -82.9^\circ \text{ A}$$

$$\underline{I}_2 = 4 \angle -90^\circ \text{ A}$$


$$\underline{V}_o = 2 [\underline{I}_1 - \underline{I}_2]$$

$$= 2 \left[(1.24 \angle -82.9^\circ) + (-4 \angle -90^\circ) \right]$$


$$\underline{V}_o = 5.55 \angle 86.8^\circ \text{ V}$$

wkg
7.68

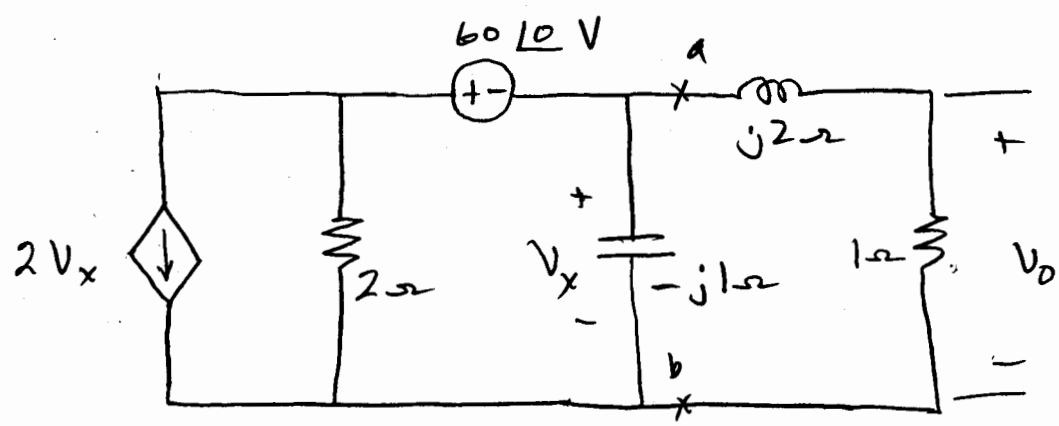Find V_o in the following network using Thevenin's theorem.



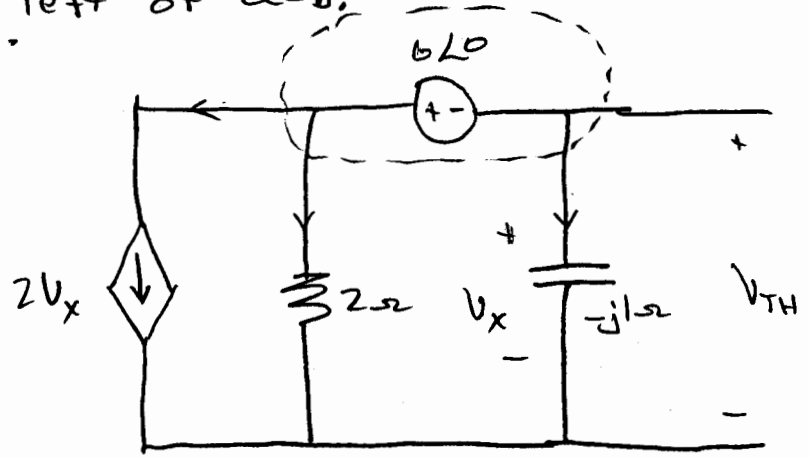Find the Thevenin equivalent circuit to the left of a-b.



At the supernode;

$$\frac{V_x + 6}{2} + 2V_x + \frac{V_x}{j} = 0$$

$$0.5V_x + 3 + 2V_x + jV_x = 0$$

$$(2.5 + j)V_x = -3$$

$$V_x = \frac{-3}{(2.5 + j)} = 1.114 \angle 158.2^\circ \text{ V}$$

$$V_{TH} = 1.114 \angle 158.2 \text{ V}$$


continued

wsg


(2)

7.68

Now find I_{sc}

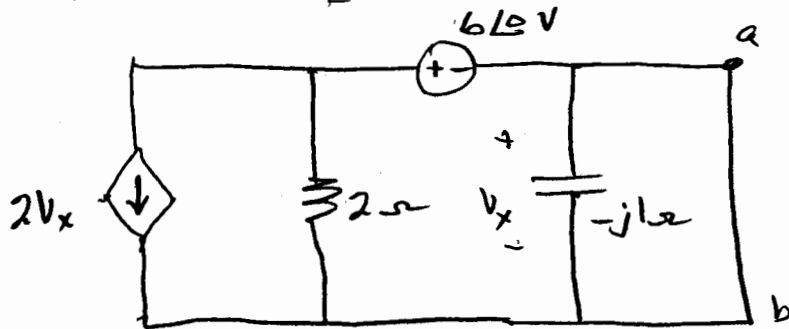


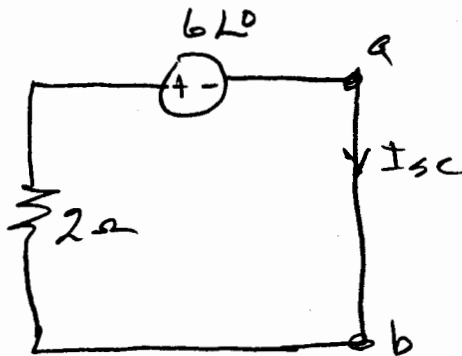When you short a-b this makes $V_x = 0$ which disables the $2V_x$ current source, leaving



$$I_{sc} = -\frac{6}{2} = -3$$
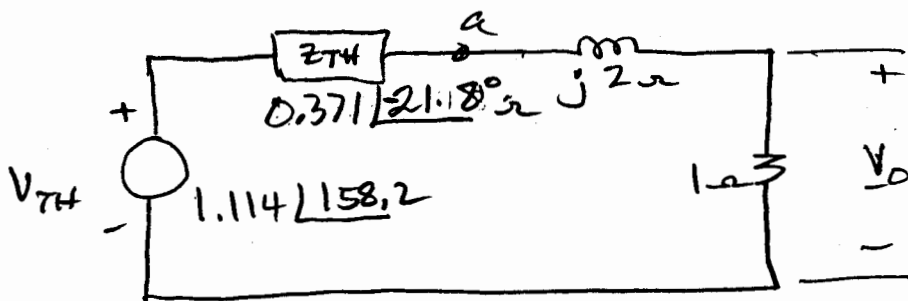
$$Z_{TH} = \frac{V_{OS}}{I_{sc}} = \frac{1.114 \angle 158.2}{-3} = 0.371 \angle -21.8$$



$$V_0 = \frac{(1.114 \angle 158.2)(1)}{((1 + j2) + (0.371 \angle -21.8))} = 0.485 \angle 104^\circ \text{ V}$$

$$V_0 = 0.485 \angle 104^\circ \text{ V}$$