


Home work 6 of # 9

wls

8.4 Given the following network

(a) write the d.e. for $V_a(t)$ and $V_b(t)$.

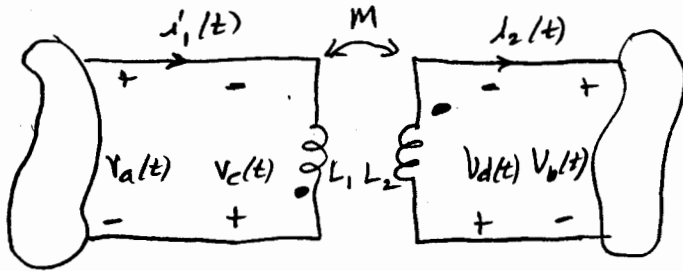(b) write the d.e. for $V_c(t)$ and $V_d(t)$.



$$(a) \quad V_a(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_b(t) = -L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$


(b)

$$V_c(t) = -V_a(t) = -L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_d(t) = -V_b(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

wlg
8.12

Find V_o in the network below.

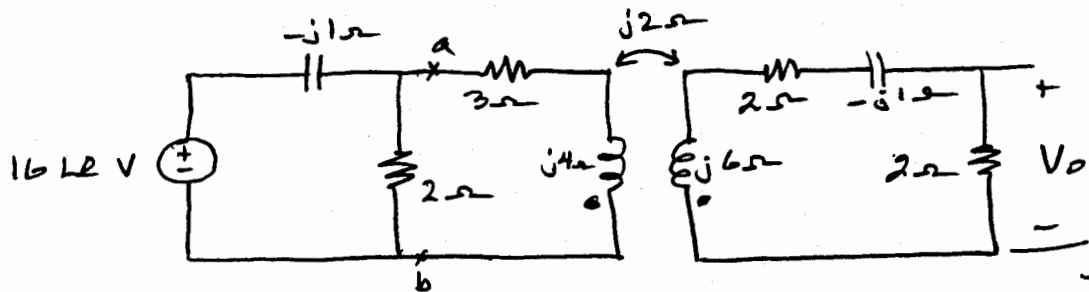


Make a Thevenin to the left of a-b

$$V_{TH} = \frac{16 + 2}{2 - j1} = 14.3 \angle 26.6^\circ \text{ V}$$

$$Z_{TH} = \frac{2(1 \angle -90)}{2 - j1} = 0.89 \angle -63.4^\circ = 0.4 - j0.8$$

So we have

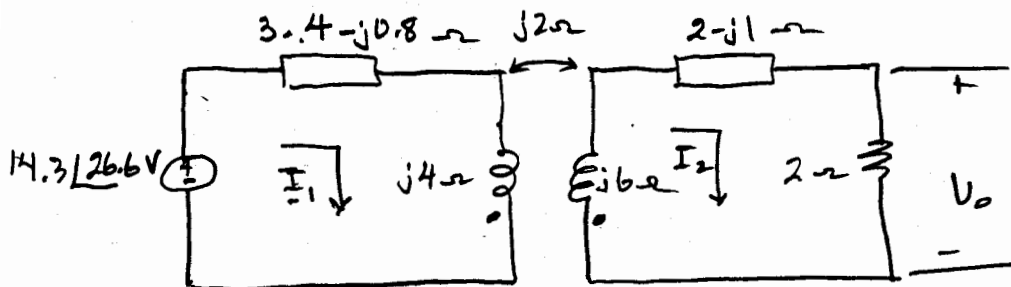

$$(3.4 + j3.2)I_1 - j2I_2 = 14.3 \angle 26.6$$

$$-j2I_1 + (4 + j5)I_2 = 0$$


$$I_1 = 3.03 - j0.47 \quad I_2 = 0.833 + j0.474 = 0.958 \angle 29.6^\circ \text{ A}$$

$$V_o = 2 (0.958 \angle 29.6)$$

$$V_o = 1.92 \angle 29.6^\circ \text{ V}$$

wkg

8.24 Find V_o in the following circuit

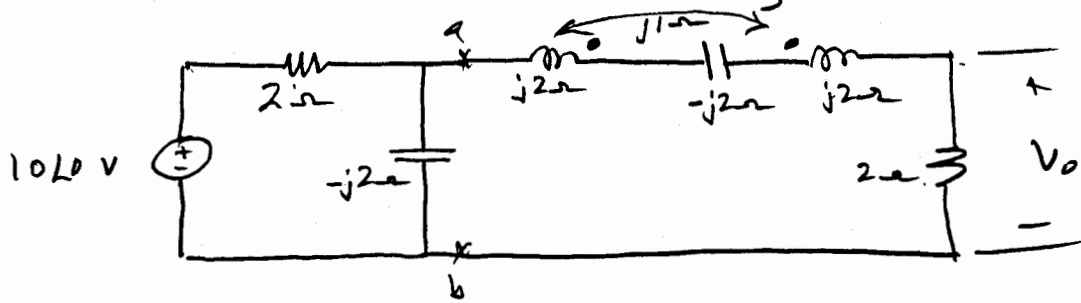


Apply Thevenin to the left of a-b

$$V_{TH} = \frac{10 \times 2 \angle -90}{2 - j2} = 5 - j5 = 7.07 \angle -45^\circ \text{ V}$$

$$Z_{TH} = \frac{2(2 \angle -90)}{2 - j2} = 1 - j1$$

Redraw the circuit:

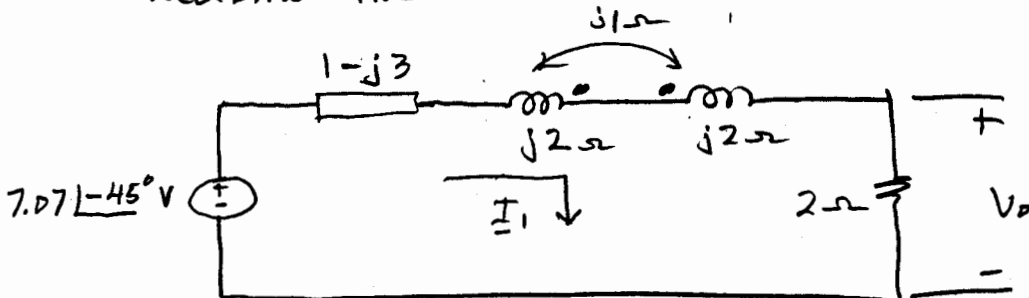

$$(3 - j3) I_1 + j4 I_1 - j1 I_1 - j1 I_1 = 7.07 \angle -45^\circ$$

$$(3 - j1) I_1 = 7.07 \angle -45^\circ$$

$$I_1 = 2 - j1 = 2.24 \angle -26.6^\circ \text{ A}$$


$$V_o = 2 I_1 = 4.48 \angle -26.6^\circ \text{ V}$$

$$V_o = 4.48 \angle -26.6^\circ \text{ V}$$

wkg

8.30

Find I_0 in the circuit below.

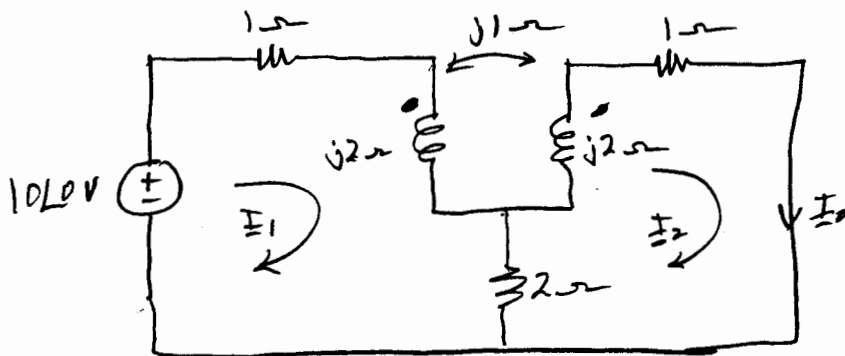

$$(1+j2+2)I_1 - 2I_2 - j1I_2 = 10L0$$

$$(3+j2)I_1 + (-2-j1)I_2 = 10L0$$

$$(-2-j)I_1 + (3+j2)I_2 = 0$$

$$\begin{bmatrix} 3+j2 & -2-j \\ -2-j & 3+j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$


$$I_1 = 3.24 - j2.94$$

$$I_2 = I_0 = 1.77 - j2.05 = 2.7 \angle -49.4^\circ \text{ A}$$

$$I_0 = 2.7 \angle -49.4^\circ \text{ A}$$

wkg
8.35

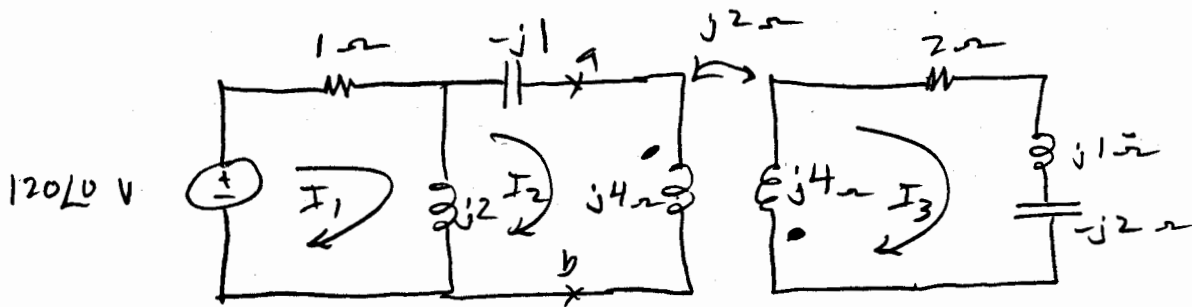Determine the impedance seen by the source in the network below.



Mesh #1

$$(1+j2)I_1 - j2I_2 = 120\angle 0$$

Mesh #2

$$-j2I_1 + j5I_2 + j2I_3 = 0$$

Mesh #3

$$j2I_2 + (2+j3)I_3 = 0$$

$$\begin{bmatrix} I_1 & I_2 & I_3 \\ 1+j2 & -j2 & 0 \\ -j2 & j5 & j2 \\ 0 & j2 & 2+j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

Need I_1 : $I_1 = 57.4 - j52.2$


$$Z_{in} = \frac{120}{I_1} = \frac{120}{57.4 - j52.2}$$

$$Z_{in} = 1.55 \angle 42.3^\circ \Omega$$

wlg

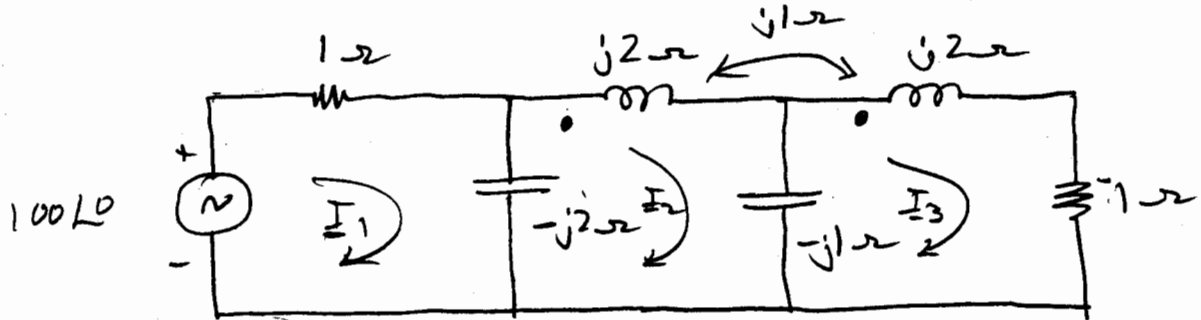8.38

Determine the input impedance of the network below.



We assume a $100\angle 0$ V source

mesh #1

$$(1-j2)I_1 + j2I_2 = 100$$

mesh #2

$$j2I_1 + (-j3+j2)I_2 + j1I_3 + j1I_3 = 0$$

mesh #3

$$j1I_2 + (-j1+j2+1)I_3 + j1I_2$$

$$\begin{bmatrix} I_1 & I_2 & I_3 \\ 1-j2 & j2 & 0 \\ j2 & -j1 & j2 \\ 0 & j2 & 1+j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \\ 0 \end{bmatrix}$$


we get $I_1 = 42.86 + j28.6$

$$Z_{in} = \frac{100}{42.86 + j28.6} = 1.94 \angle -33.7^\circ \Omega$$


$$Z_{in} = 1.94 \angle -33.7^\circ \Omega$$

wkg

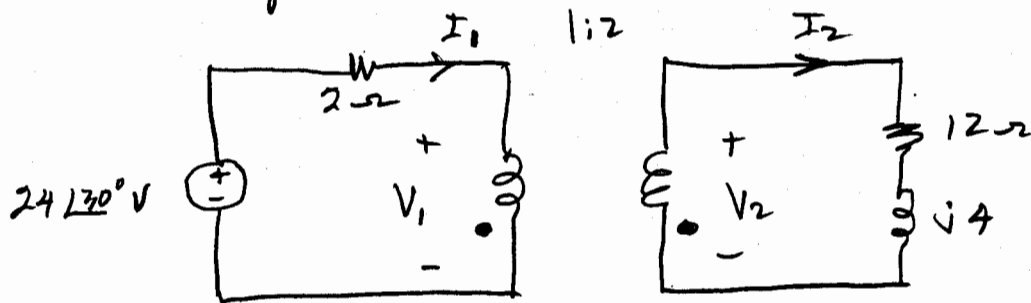8.46 Find all currents and voltages in the following network.



Reflecting secondary to primary

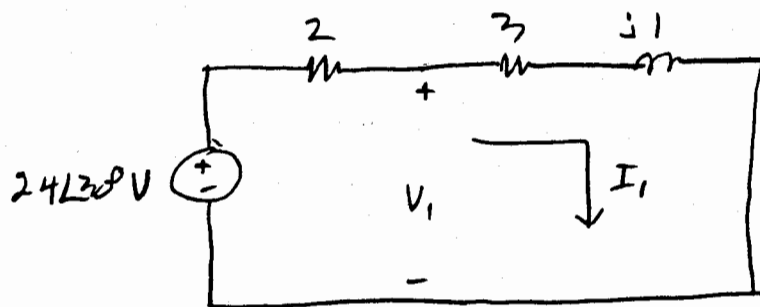

$$I_1 = \frac{24 \angle 30^\circ}{5 + j1} = 4.7 \angle 18.7^\circ \text{ A check}$$

$$I_2 = \frac{I_1}{2} = 2.23 \angle 18.7^\circ \text{ A check}$$

$$V_1 = 24 \angle 30^\circ - 2(4.7 \angle 18.7^\circ)$$

$$V_1 = 14.9 \angle 37.1^\circ \text{ V}$$


$$V_2 = 2 \times V_1$$

$$V_2 = 30 \angle 37.1^\circ \text{ V}$$

wkg

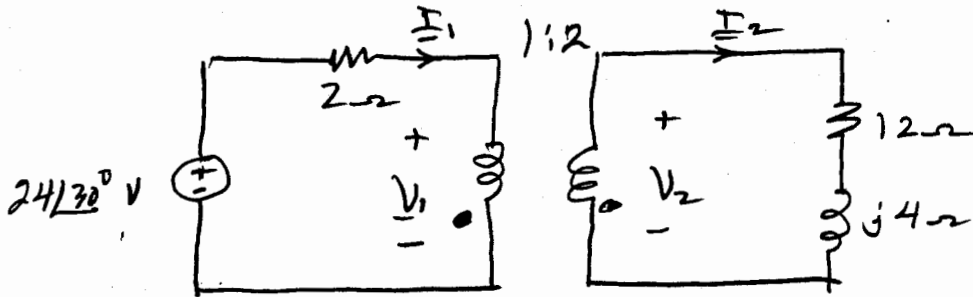8.46

Find all currents and voltages in the following network



Standard Mesh equation solution.

$$2I_1 + V_1 = 24\angle 30^\circ$$

$$(12 + j4)I_2 - V_2 = 0$$

$$\frac{V_2}{V_1} = 2 \rightarrow 2V_1 - V_2 = 0$$

$$\frac{I_1}{I_2} = 2 \quad I_1 - 2I_2 = 0$$

$$\begin{bmatrix} V_1 & V_2 & I_1 & I_2 \\ 1 & 0 & 2 & 0 \\ 0 & -1 & 0 & 12 + j4 \\ 2 & -1 & 0 & 0 \\ 0 & 0 & 1 & -2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 24\angle 30^\circ \\ 0 \\ 0 \\ 0 \end{bmatrix}$$


$$V_1 = 11.87 + j8.98 = 14.88\angle 37^\circ \text{ V}$$

$$V_2 = 23.7 + j17.97 = 29.7\angle 37.1^\circ \text{ V}$$

$$I_1 = 4.46 + j1.51 = 4.7\angle 18.7^\circ \text{ A}$$

$$I_2 = 2.23 + j0.75 = 2.35\angle 18.6^\circ \text{ A}$$

wlg
8.50

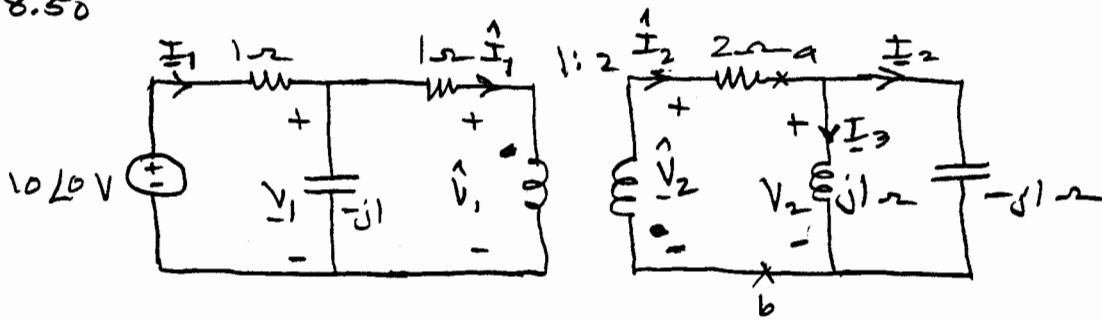

To the right of a-b we have $j1 \parallel -j1 = \infty$,
 so it looks like an open circuit.
 This means $\hat{I}_2 = 0$. Therefore $\hat{I}_1 = 0$.

Then

$$\underline{\hat{V}_1} = \frac{10 \times (-j1)}{1 - j1} = \underline{7.07 \angle -45^\circ} \text{ A}$$

$$\underline{\hat{I}_1} = \frac{10 \angle 0}{1 - j1} = \underline{7.07 \angle 45^\circ} \text{ A}$$

since $\hat{I}_1 = 0$, $\hat{V}_1 = V_1$

With the dot marking given,

$$\hat{V}_2 = -2 \hat{V}_1 = -14.14 \angle -45^\circ \text{ V}$$

$$\underline{\hat{V}_2} = \underline{14.14 \angle 135^\circ} \text{ V} = \underline{V_2}$$

With $\hat{I}_2 = 0$, $V_2 = \hat{V}_2$, then

$$\underline{\hat{I}_2} = \frac{V_2}{-j1} = \frac{14.14 \angle 135^\circ}{1 \angle -90^\circ} = \underline{14.14 \angle -135^\circ} \text{ A}$$

Note;

$$\underline{\hat{I}_3} = \frac{V_2}{j1} = \frac{14.14 \angle 135^\circ}{1 \angle 90^\circ} = \underline{14.14 \angle 45^\circ}$$


We see $\underline{\hat{I}_2} + \underline{\hat{I}_3} = 0$ as it should.

We have an ideal tank circuit.

"Perpetual motion"


wlg

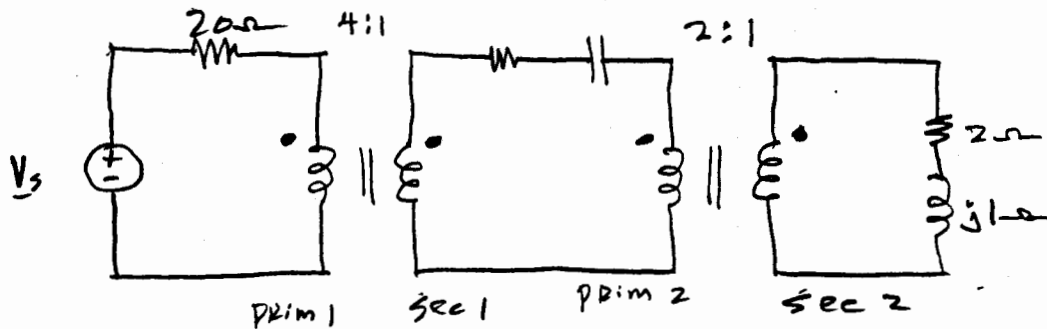8.54 Determine the input impedance seen by the source in the network below.




Step 1:

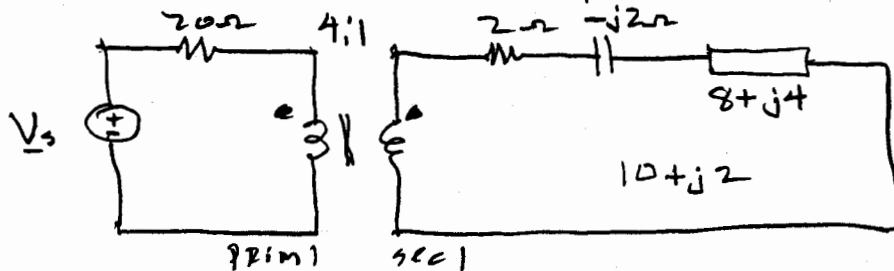Reflect sec 2 to prim 2 $2^2(2+j1) = 8+j4$



$$4^2(10+j2) = 16(10+j2) = 160 + j32$$

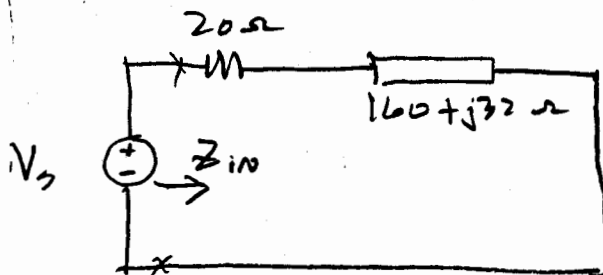


$$Z_{in} = 20 + 160 + j32$$

$$Z_{in} = 180 + j32 \Omega$$

3FE-2

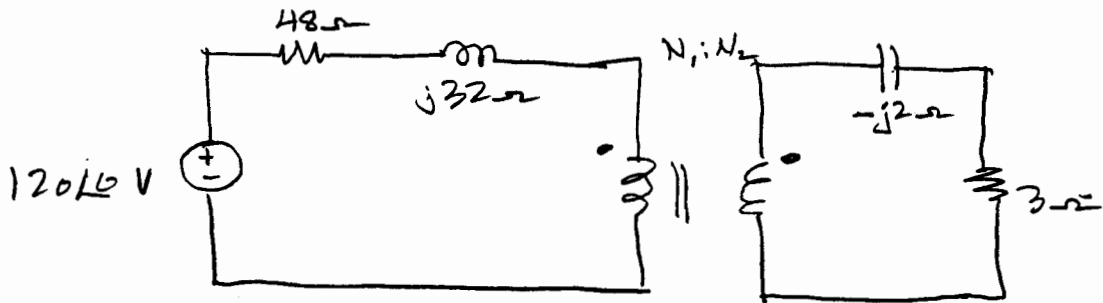Select $N_2:N_1$ for maximum power transfer. Calculate this power.




Want $n = \frac{N_2}{N_1}$ such that

$$\frac{3 - j2}{n^2} = (48 + j32)^* = 48 - j32$$

$$n^2 = \frac{1}{16}$$

$$\frac{1}{n} = \frac{N_1}{N_2} = \sqrt{16} = 4$$

$$\frac{N_1}{N_2} = 4$$

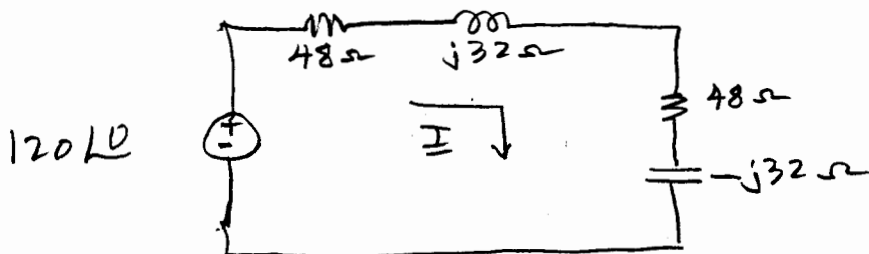


$$I = \frac{120}{96}$$

$$P_{48} = \left(\frac{120}{96}\right)^2 \frac{48}{2} = 37.5 \text{ W}$$

$$P_{48} = 37.5 \text{ W}$$


wlg

3FE-3

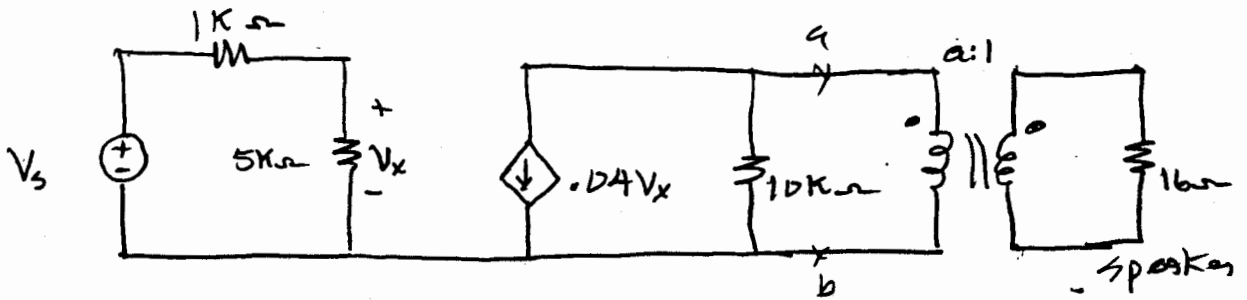

Select "a" so that the output impedance of the transistor amplifier matches the reflected resistance of the speaker.

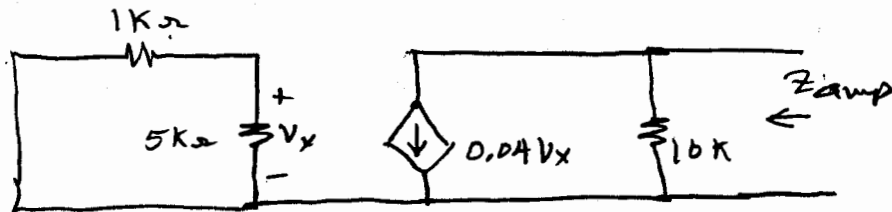Look into a-b with independent voltages replaced with shorts:



With $V_s = 0$, $V_x = 0$. This makes the dependent current source $0.04V_x = 0$ (open). Thus

$$Z_{amp} = 10 \text{ k}\Omega.$$

Want

$$a^2 \times 16 = 10 \text{ k}$$

$$a^2 = 625$$

$$a = 25$$