

ECE 300
Short Test #1
Spring 2004

Name Solutions.
Print (last, first)

AM

Each problem counts 10%. Do your work on the exam sheet.

(1) Given the circuit in Figure 1.

- (a) How much power is supplied by the 30 V source?
- (b) How much power is supplied by the 10 V source?
- (c) How much power do the two resistors in the circuit absorb?

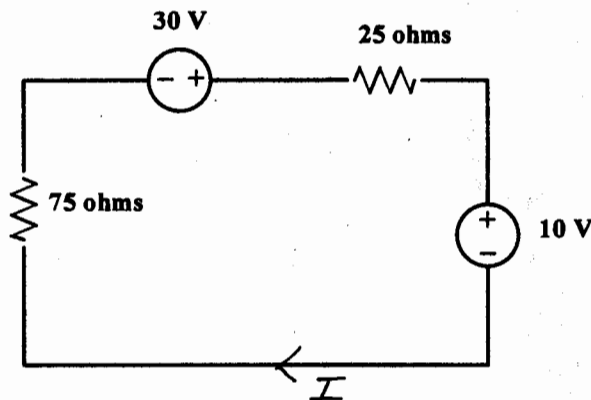


Figure 1: Circuit for problem 1.

$$I = \frac{30 - 10}{75 + 25} = 0.2 \text{ A}$$

$$\text{Power supplied by the 30V source} = VI = 30 \times 0.2 = 6 \text{ W}$$

$$\text{Power supplied by the 10V source} = -10 \times 0.2 = -2 \text{ W}$$

+2W absorbed

The two resistors absorb

$$75 \times (0.2)^2 + 25 \times (0.2)^2$$

$$= 4 \text{ W}$$

- (2) An ohmmeter is connected to terminals A-B in the circuit below. What value of resistance will the meter read in ohms?



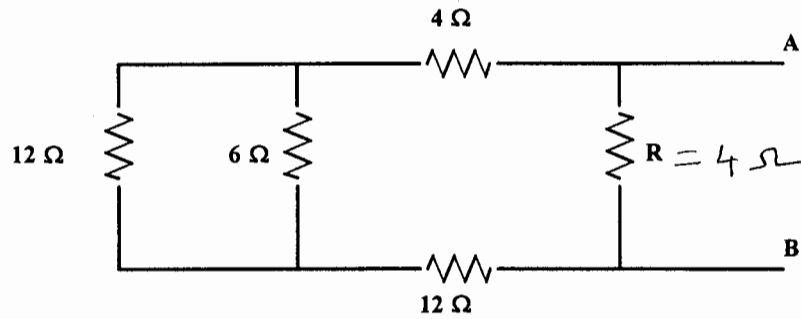


Figure 2: Circuit for problem 2.
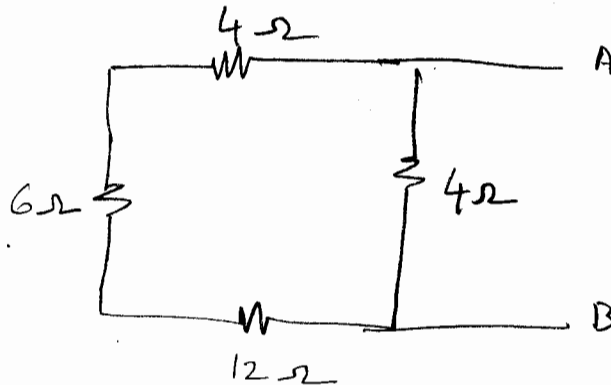
$$12\ \Omega \parallel 6\ \Omega = 4\ \Omega$$



$$4 + 6 + 12 = 22\ \Omega$$

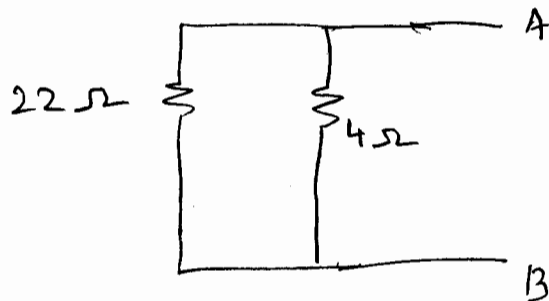

$$22\ \Omega \parallel 4\ \Omega = 3.38\ \Omega$$

$$R_{AB} = 3.38\ \Omega$$

(3) Find the value of R in the circuit below.

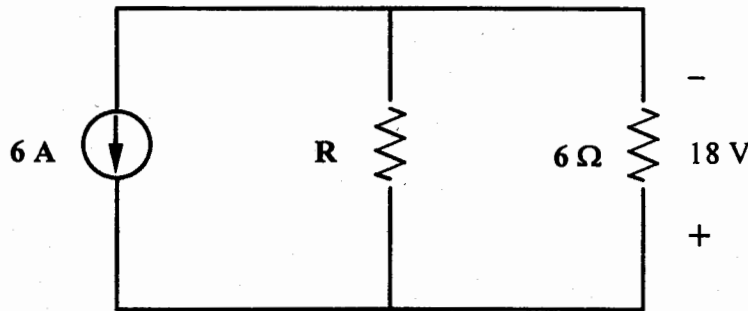


Figure 3: Circuit for problem 3.

The current through the 6Ω resistor will be

$$I = \frac{18V}{6\Omega} = 3A$$

This means the 6 A of current is split 3 A and 3 A in the two branches.

Since the currents in the two branches are equal the resistances must be equal

$$\text{hence } R = 6\Omega$$