
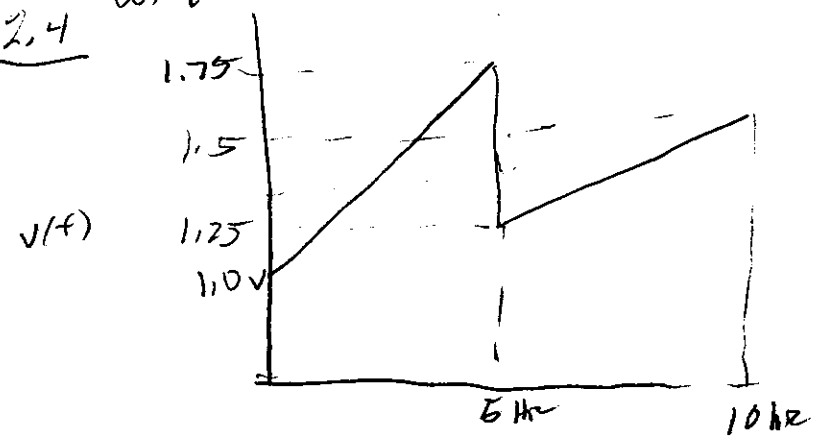


2.4 W/g

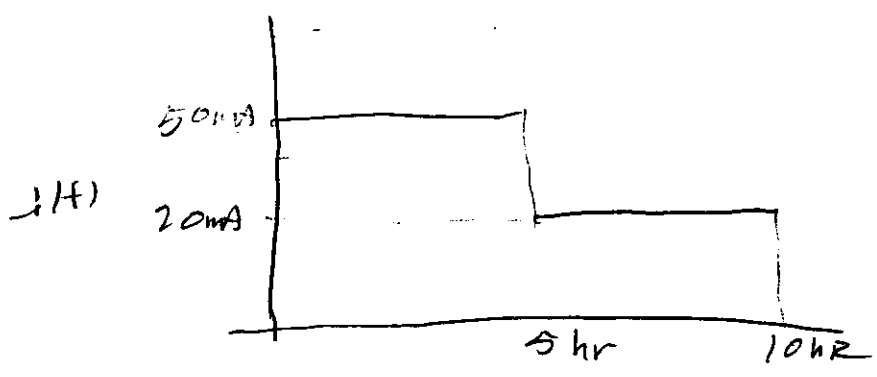

$$W = \int V i dt$$



(a) Find Q

since $i = \frac{dq}{dt}$

$$q(t) = \int_{t_0}^t i(t) dt = \int_0^{5 \times 3.6 \times 10^3} 50 \times 10^{-3} dt + \int_{5 \times 3.6 \times 10^3}^{10 \times 3.6 \times 10^3} 20 \times 10^{-3} dt$$

$$q(t) = 50 \times 5 \times 3.6 + 20 \times 5 \times 3.6$$

$$q(t) = 900 + 360$$

$$q(t) = 1260 \text{ Coulombs}$$

$$t = 10 \text{ hr}$$

2.4 continued

$$(b) \quad p = \frac{dW}{dt} \rightarrow W = \int p(t) dt$$

For $0 \leq t \leq 5 \text{ hr}$

$$v(t) = a_1 t + b_1 = \frac{0.75}{5 \times 3.6 \times 10^3} t + 1 = \frac{.75t}{18000} + 1$$

$5 \text{ hr} \leq t \leq 10 \text{ hr}$

$$v(t) = a_2 t + b_2 = \frac{-.25}{5 \times 3.6 \times 10^3} t + 1 = \frac{.25t}{18000} + 1$$

$$W(t) = \int_0^{5 \times 3.6 \times 10^3} 50 \times 10^{-3} \left(\frac{0.75t}{18000} + 1 \right) dt + \int_{5 \times 3.6 \times 10^3}^{10 \times 3.6 \times 10^3} 20 \times 10^{-3} \left(\frac{.25t}{18000} + 1 \right) dt$$

$$W(t) = 50 \times 5 \times 3.6 + \frac{.75 (5 \times 3.6 \times 10^3)^2}{36000} \times 50 \times 10^{-3}$$

$$+ 20 \times 5 \times 3.6 + \frac{.25 (5 \times 3.6 \times 10^3)^2}{36000} \times 20 \times 10^{-3}$$

$$W(t) = (900 + 337.5) + (360 + 45)$$


$$W(t) \Big|_{t=10 \text{ hr}} = 1642.5 \text{ J}$$

2.6 Why

(a) The load attached to the voltage source; Also, the physics of the voltage source, how it is made, current rating,

(b) The load attached; The physical make-up of the source.

2.15

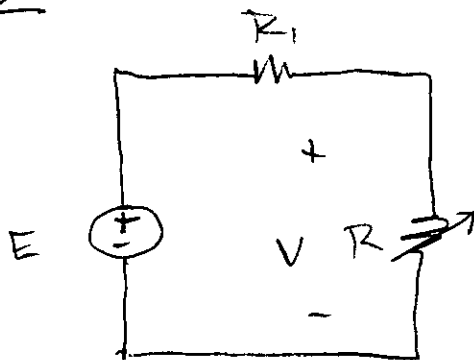

Find the general expression for power delivered to R .

$$V = \frac{E \times R}{R_1 + R}$$

$$P = \frac{V^2}{R} = \frac{E^2 R^2}{(R_1 + R)^2 R}$$

$$P = \frac{E^2 R}{(R_1 + R)^2}$$

(1)

$$\frac{dP}{dR} = \frac{E^2 (R_1 + R)^2 - E^2 R \cdot 2 \cdot (R_1 + R)}{[(R_1 + R)^2]^2} \quad (2)$$

2.15 cont.

Dividing out terms leaves

wlg

C:\MATLAB6p5\work\max_power_transfer.m
August 25, 2004

```
% Making a plot of power across the output resistor of two resistors  
% in parallel. The supplied voltage is 20 V and the non-load resistor  
% is 5 ohms. The equation to plot from R = 0 to R = 20 is
```


```
%           P = 400*R/(5+R)  
% Program under      max_power_transfer.m  
% written by: wlg: office computer 8/26/04 for ECE 301
```

```
R = 0:.05: 21;
```


```
P = (400*R)./((5+R).^2);
```

```
plot(R,P)  
grid  
ylabel('Output Power, P, Watts')  
xlabel('Load Resistance, R, Ohms')  
title('Illustrating Maximum Power Transfer')
```

Illustrating Maximum Power Transfer

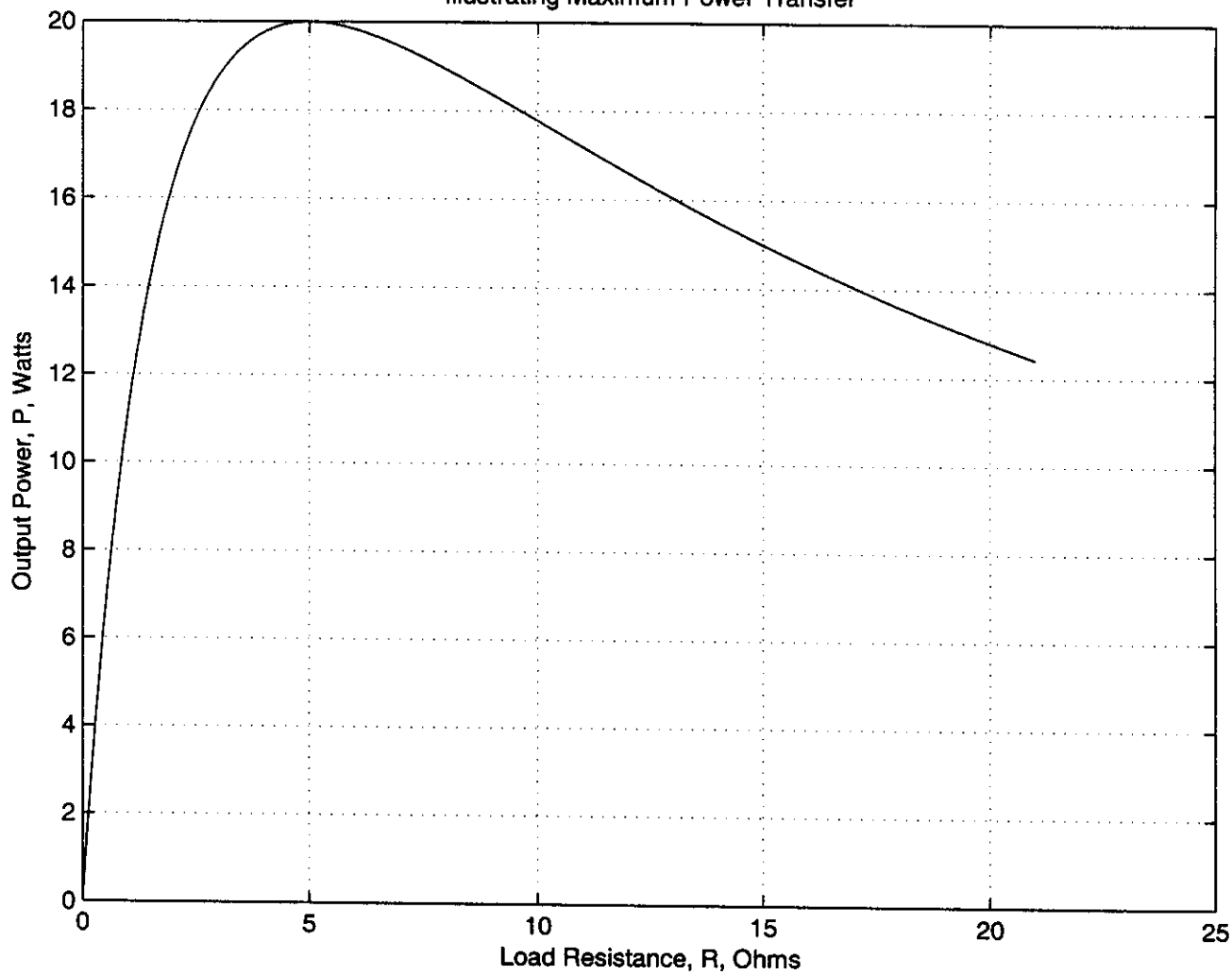

2.21 wky

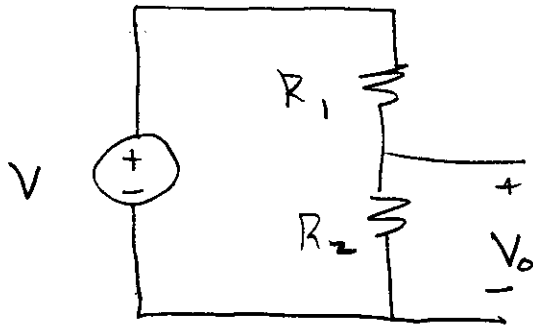

(a) $V = 30\text{ V}$, $R_1 = 10\text{ k}\Omega$, $V_0 = 10\text{ V}$
Find R_2 & wattage

$$V_0 = \frac{V \times R_2}{R_1 + R_2} = \frac{30 \times R_2}{10\text{ k} + R_2} = 10$$

$$3R_2 = 10\text{ k} + R_2$$

$$R_2 = \underline{5\text{ k}}$$

$$P_0 = \frac{V_0^2}{R_2} = \frac{100}{5\text{ k}} = 20 \times 10^{-3}$$

$$P_0 = 0.02\text{ W} \rightarrow \underline{1/8\text{ W}}$$
 resistor

(b) $V = 12\text{ V}$, $R_2 = 140\Omega$, $V_0 = 8.5\text{ V}$

$$V_0 = \frac{12 \times 140}{140 + R_1} = 8.5$$

$$1680 = 1190 + 8.5R_1$$

$$8.5R_1 = 490\Omega$$


$$R_1 = 57.6\Omega$$

$$P_2 = \frac{8.5^2}{140} = 0.52\text{ W} \rightarrow 1\text{ W resistor}$$

$$P_1 = 0.213\text{ W} \rightarrow 1/4\text{ W resistor}$$

2.24

w/ky

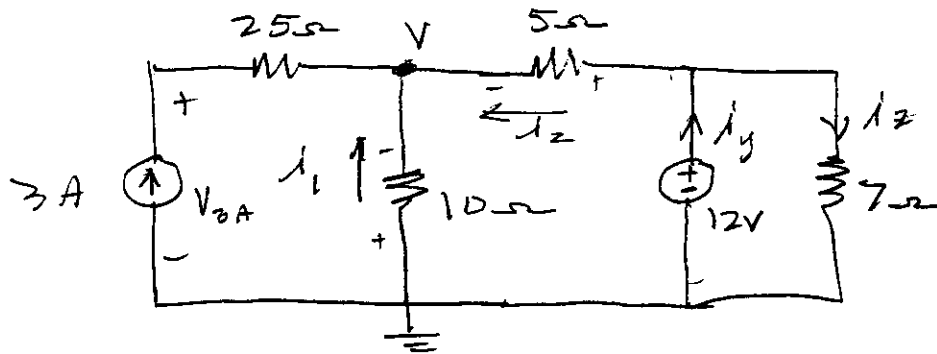Given(a) Find i_1 and i_2

$$i_1 + i_2 = -3$$

$$-10i_1 + 5i_2 = 12$$

Solving:

$$i_1 = -1.8 \text{ A}, \quad i_2 = -1.2 \text{ A}$$

(b) Find the power delivered by the 3A source and by the 12V source

$$P_{3A} = 3 \times V_{3A}$$

$$\text{where } V_{3A} = 3 \times 25 - i_1 \times 10$$

$$V_{3A} = 75 + 18 = 93 \text{ V}$$

$$P_{3A} = 93 \times 3 = 279 \text{ W}$$

del

$$P_{12} = i_y \times 12$$

2.24 cont.

$$i_2 = \frac{12}{7}$$

$$i_2 = -1.2$$

$$i_y = \frac{12}{7} - 1.2 = 0.514 \text{ A}$$

$$P_{12} = 0.514 \times 12 = 6.17 \text{ W}$$

$$P_{3A} = 279 \text{ W}$$

Total power develop:

$$P_{\text{Total dev}} = 279 + 6.17 = 285.2 \text{ W}$$

#

$$P_{\text{diss } 7} = \frac{12^2}{7} = 20.57 \text{ W}$$

$$P_{\text{diss } 5} = i_2^2 \cdot 5 = (-1.2)^2 \cdot 5 = 7.2 \text{ W}$$

$$P_{\text{diss } 10} = i_1^2 \cdot 10 = (-1.8)^2 \cdot 10 = 32.4 \text{ W}$$


$$P_{\text{diss } 25} = 3^2 \cdot 25 = 225 \text{ W}$$

$$\Sigma P_{\text{diss}} = 285.2 \text{ W}$$

check

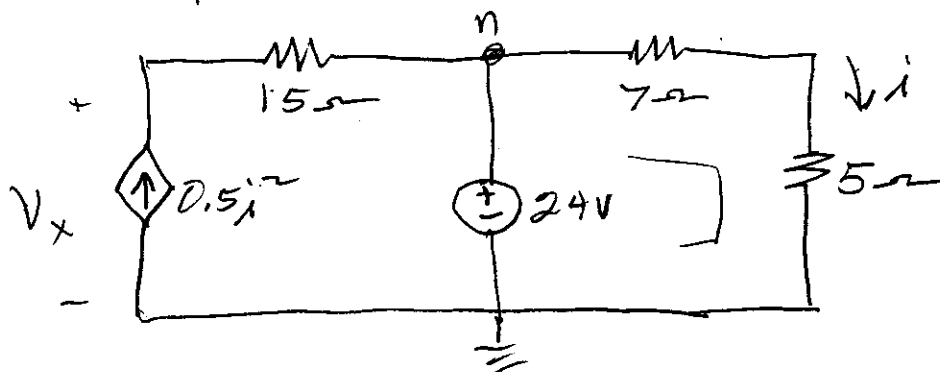2.25 wky

Determine the power delivered by the dependent source.



Going around the right mesh using Σ drops = 0, cw (clockwise)

$$-24 + 7i + 5i = 0$$

$$12i = 24$$

$$i = 2 \text{ A}$$

Must find V_x

$$-V_x + 15 \times 0.5i^2 + 24 = 0$$


$$V_x = 7.5 \times 4 + 24 = 54$$

$$P_{del} = 54 \times (0.5i^2) = 27 \times 2^2$$

$$P_{del} = 108 \text{ W}$$

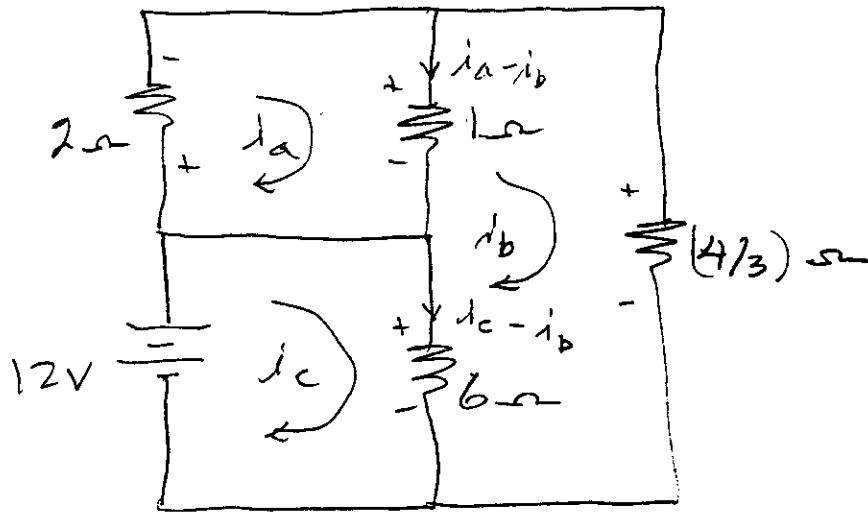2.34 w/qr

For the circuit below, use KVL and Ohm's Law to find
(a) i_a , i_b , i_c
(b) current through each resistor



For the mesh with i_a :

$$2i_a + (i_a - i_b)1 = 0$$

$$3i_a - i_b + 0i_c = 0$$

For the mesh with i_b :

$$(i_a - i_b)1 + (i_c - i_b)6 - (4/3)(i_b) = 0$$

$$i_a - 8.33i_b + 6i_c = 0$$

For the mesh with i_c :

$$(i_c - i_b)6 - 12 = 0$$

$$0i_a - 6i_b + 6i_c = 12$$

2.74 continued

2

$$\begin{bmatrix} 3 & -1 & 0 \\ 1 & -8.33 & 6 \\ 0 & -6 & 6 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 12 \end{bmatrix}$$

$$i_a = 2 \text{ A}, \quad i_b = 6 \text{ A}, \quad i_c = 8 \text{ A}$$

(b)

$$i_{R_0} = i_a = 2 \text{ A up}$$


$$i_{R_1} = \underset{\text{up}}{i_b} - \underset{\text{up}}{i_a} = 4 \text{ A}$$

$$i_{R_2} = i_p = \underset{\text{down}}{6 \text{ A}}$$

$$i_{R_3} = \underset{\text{down}}{i_c} - \underset{\text{down}}{i_b} = 8 - 6 = 2 \text{ A}$$

2,36 w/g

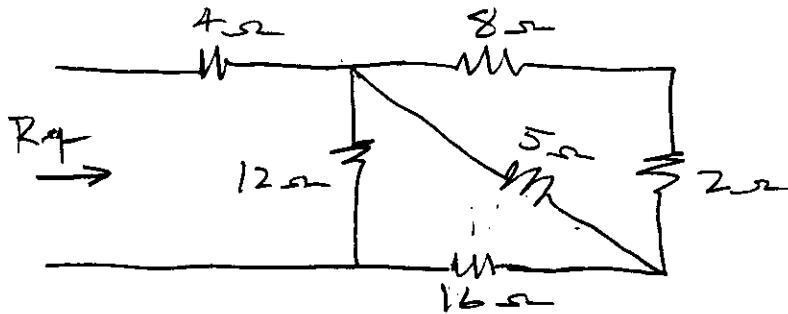Find the equivalent resistance for the circuit below



$$10\ \Omega \parallel 5\ \Omega = \frac{10 \times 5}{15} = \frac{50}{15}\ \Omega = 3,33\ \Omega$$


$$16\ \Omega + 3,33\ \Omega = 19,33\ \Omega$$

$$19,33\ \Omega \parallel 12\ \Omega = \frac{19,33 \times 12}{19,33 + 12} = 7,4\ \Omega$$

$$R_{eq} = 4 + 7,4 = 11,4\ \Omega$$

$$R_{eq} = 11,4\ \Omega$$

2.43 W/g

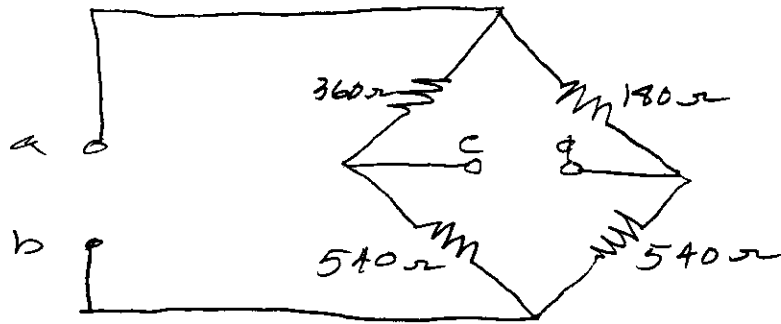

Find R

- (a) Looking into a-b if c-d are open
- (b) Looking into a-b if c-d are shorted
- (c) Looking into c-d if a-b are open
- (d) Looking into c-d if a-b are shorted

(a)

$$R_{ab} = (540 + 360) \parallel (540 + 180)$$

$$R_{ab} = 900 \parallel 720 = 400 \Omega$$

c-d open

(b)

$$R_{ab} = 360 \parallel 180 + 540 \parallel 540$$

c-d shorted

$$R_{a-b} = 120 + 270 = 390 \Omega$$

c-d shorted

(c)

$$R_{cd} = (540 + 540) \parallel (360 + 180)$$



$$R_{cd} = 1080 \parallel 540$$

a-b open


$$R_{cd} = 360 \Omega$$

a-b open

2.43 cont

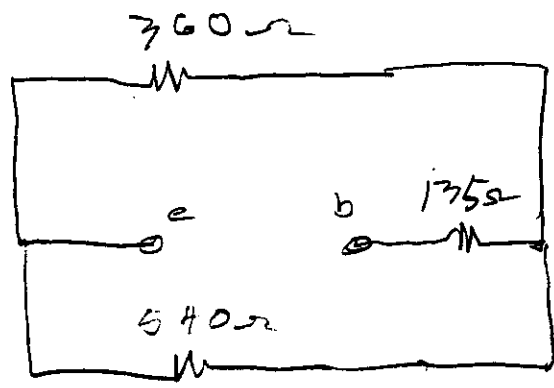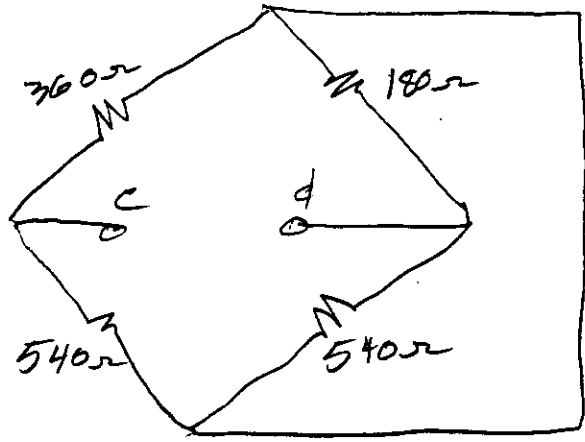

$$180 \parallel 540 = 135 \Omega$$

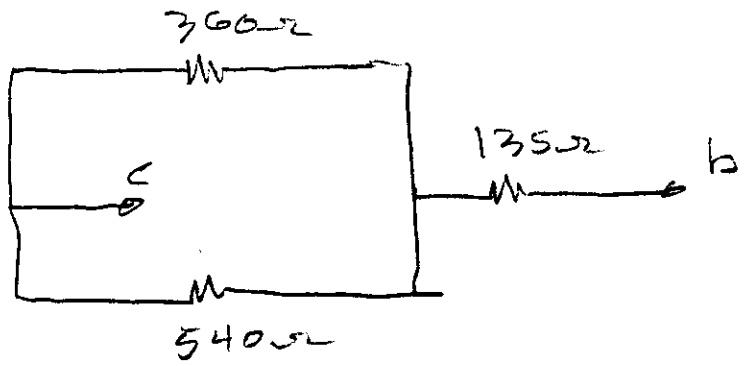


$$R_{cd} = (360 \parallel 540) + 135$$

a-b shorted

$$= 351 \Omega$$

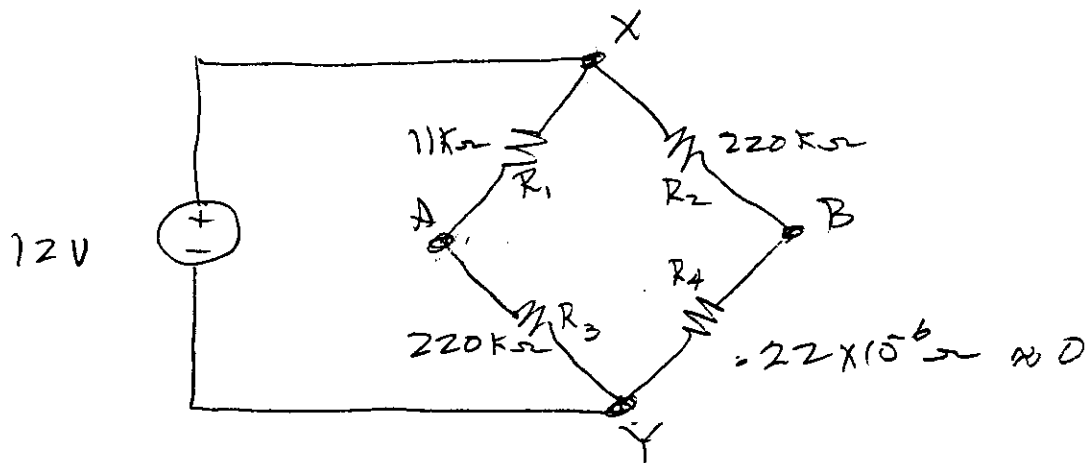2.49 Wfg


Determine the voltage V_{AB} in the circuit below.



$$V_{XA} = \frac{12 \times 11K}{6.8 + 11K} = 7.42$$

$$V_{XB} = \frac{12 \times 220K}{0 + 220K} = 12V$$

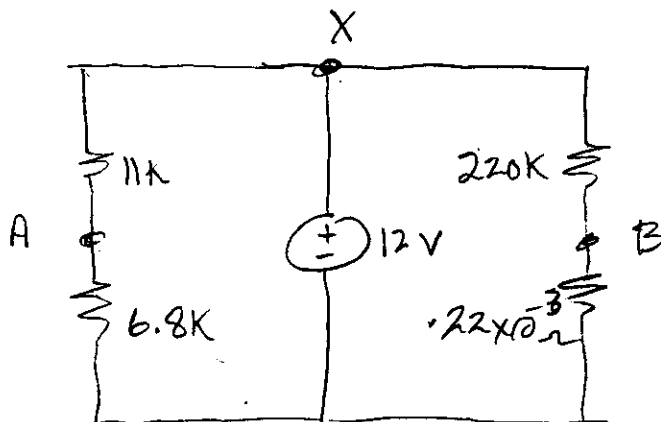
$$V_{AB} = V_{XB} - V_{XA} = 12 - 7.42 = 4.58V$$



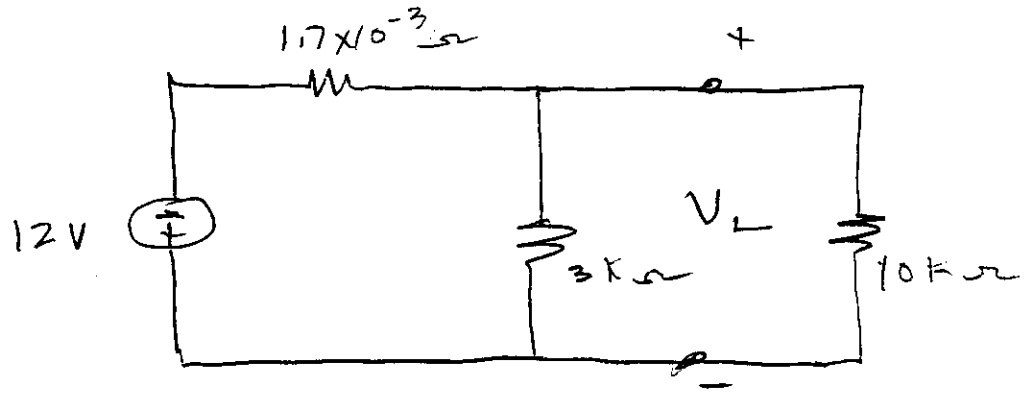2.51 wkg

absolute value of the voltage across

Determine the voltage across R_3 in the circuit below




$$R_{load} = 3k \parallel 10k = 2.3k$$

since $2.3k \gg 1.7 \times 10^{-3}$ ohms

$$|V_L| = |12| = 12V$$

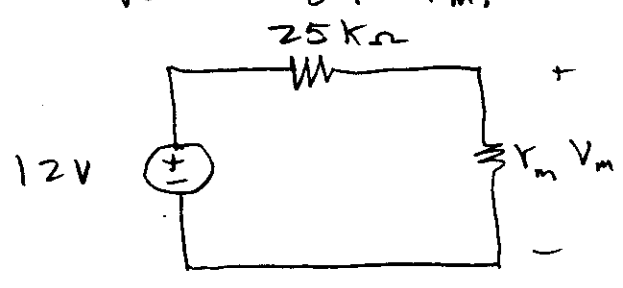2.61 In the circuit below, the voltage across r_m is 11.81V. Determine the value of r_m .



$$V_m = \frac{12 \times r_m}{r_m + 25k} = 11.81V$$

so,

$$12r_m = 11.81r_m + 292.2k$$

$$r_m = \frac{292.2k}{0.19} = 1537.9k \Omega$$

	with meter in circuit	without meter in circuit
a	10.15 mA	9.99 mA
b	24.03 mA	23.15 mA
c	27.84 mA	26.67 mA
d	28.29 mA	27.08 mA

Problem 2.65

Solution:

Known quantities:

Schematic of the circuit and geometry of the beam shown in Figure P2.65, characteristics of the meter reads on the bridge.

Find:

The force applied on the beam.

Assumptions:

Gage Factor for Strain gauge is 2

Analysis:

R_1 and R_2 are in series; R_3 and R_4 are in series.

$$\text{Voltage Division: } V_{R_2} = \frac{V_S R_2}{R_1 + R_2} = \frac{V_S (R_0 - \Delta R)}{R_0 + \Delta R + R_0 - \Delta R} = \frac{V_S (R_0 - \Delta R)}{2R_0}$$

$$\text{Voltage Division: } V_{R_4} = \frac{V_S R_4}{R_3 + R_4} = \frac{V_S (R_0 - \Delta R)}{R_0 - \Delta R + R_0 + \Delta R} = \frac{V_S (R_0 + \Delta R)}{2R_0}$$

$$\text{KVL: } -V_{R_2} - V_{BA} + V_{R_4} = 0$$

$$V_{BA} = V_{R_4} - V_{R_2} = \frac{V_S (R_0 + \Delta R)}{2R_0} - \frac{V_S (R_0 - \Delta R)}{2R_0} = \frac{V_S 2\Delta R}{2R_0} = V_S GF \epsilon = \frac{V_S (2)(6)L}{wh^2 Y}$$

$$F = \frac{V_{BA} wh^2 Y}{V_S 12L} = \frac{0.050 \text{ V} (0.025 \text{ m})(0.100 \text{ m})^2 69 \times 10^9 \frac{\text{N}}{\text{m}^2}}{12 \text{ V} (12) 0.3 \text{ m}} = 19.97 \text{ kN.}$$

Problem 2.66

Solution:

Known quantities:

Schematic of the circuit and geometry of the beam shown in Figure P2.65, characteristics of the meter reads on the bridge.

Find:

The force applied on the beam.