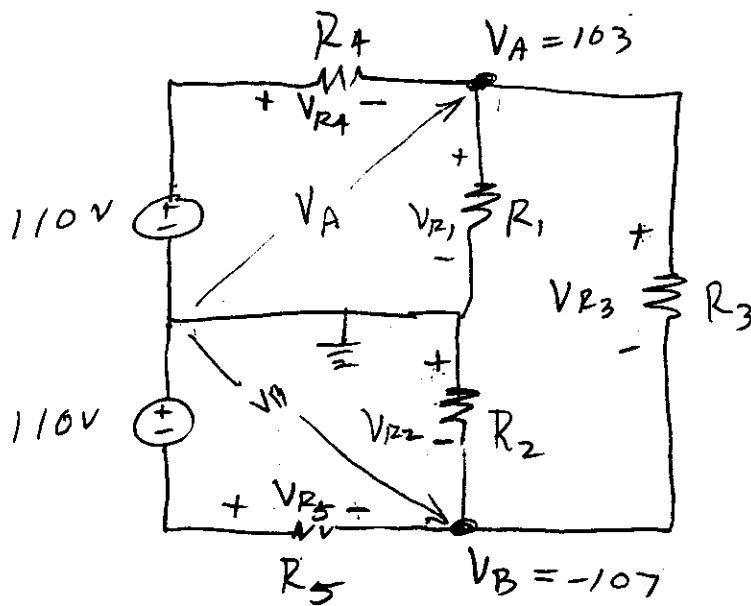


Wk 3

H.W. # 2
ECE 301
Fall Semester 07

3.2

Determine the voltage across each resistor in the following circuit by using Nodal Analysis. Check by using Mesh analysis.



$$V_{R1} = V_A = 103 \text{ V}$$

$$V_B + V_{R2} = 0$$

$$V_{R2} = -V_B = +107 \text{ V}$$

$$V_A - V_{R3} - V_B = 0$$

$$V_{R3} = V_A - V_B = 103 - (-107)$$

$$V_{R3} = 210 \text{ V}$$

3.2 cont.

$$V_A + V_{R4} - 110 = 0$$

$$V_{R4} = 110 - V_A = 110 - 103 = 7 \text{ V}$$

$$V_{R4} = +7 \text{ V}$$

$$V_B + V_{R5} + 110 = 0$$


$$V_{R5} = -V_B - 110 :$$

$$V_{R5} = 107 - 110$$

$$V_{R5} = -3 \text{ V}$$

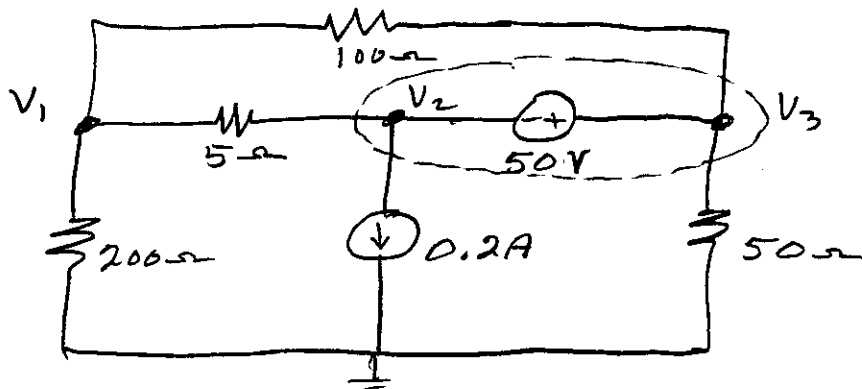3.5

Use nodal analysis to find the current i as indicated in the following diagram.



Form a supernode as shown.

At V_1 :

$$\frac{V_1}{200} + \frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{100} = 0$$

OR

$$V_1 + 40V_1 - 40V_2 + 2V_1 - 2V_3 = 0$$

$$43V_1 - 40V_2 - 2V_3 = 0$$

At the supernode:

$$\frac{V_2 - V_1}{5} + 0.2 + \frac{V_3 - V_1}{100} + \frac{V_3}{50} = 0$$

$$20V_2 - 20V_1 + V_3 - V_1 + 2V_3 = -20$$

$$-21V_1 + 20V_2 + 3V_3 = -20$$

3.5

$$V_2 + 50 - V_3 = 0$$

$$0V_1 + V_2 - V_3 = -50$$

$$\begin{bmatrix} 43 & -40 & -2 \\ -21 & 20 & 3 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -20 \\ -50 \end{bmatrix}$$

$$V_1 = -45.23V \quad V_2 = -48.29V \quad V_3 = 1.31V$$


We have at V_2

$$\frac{V_2 - V_1}{5} + 0.2 + i = 0$$

$$i = -0.2 + \frac{V_1 - V_2}{5} = -0.2 + \frac{(-45.23 + 48.29)}{5}$$

$$i = 1.494A$$

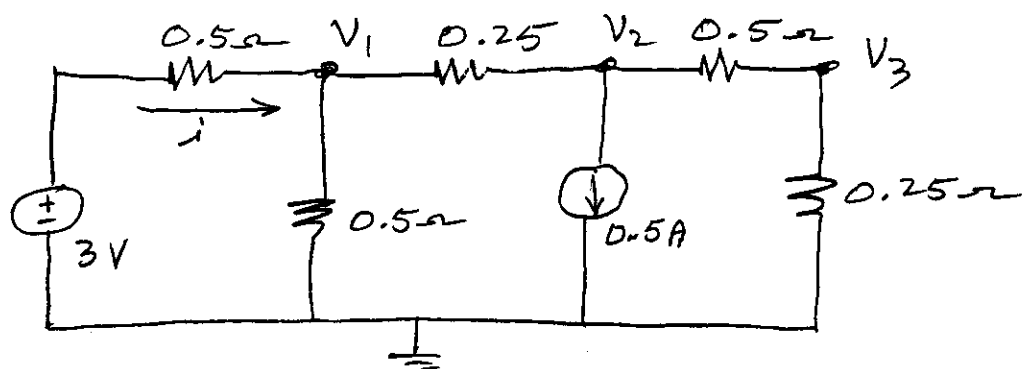3.7 For the circuit below, use nodal analysis to find the current i .



At V_1

$$\frac{V_1 - 3}{0.5} + \frac{V_1}{0.5} + \frac{V_1 - V_2}{0.25} = 0$$

$$V_1 - 3 + V_1 + 2V_1 - 2V_2 = 0$$

$$4V_1 - 2V_2 = 3$$

At V_2

$$\frac{V_2 - V_1}{.25} + \frac{V_2}{.75} + 0.5 = 0$$

$$3V_2 - 3V_1 + V_2 = -0.375$$

$$\boxed{-3V_1 + 4V_2 = -0.375}$$

You don't need node V_3 .

3.2 continued

$$\begin{bmatrix} 4 & -2 \\ -3 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 3 \\ -3.75 \end{bmatrix}$$

$$v_1 = 1.125 \text{ V} \quad v_2 = 0.75 \text{ V}$$


$$3 - 0.5 i_1 - v_1 = 0$$

$$i_1 = 6 - 2v_1 = 6 - 2 \times 1.125$$

$$i_1 = 3.75 \text{ A}$$

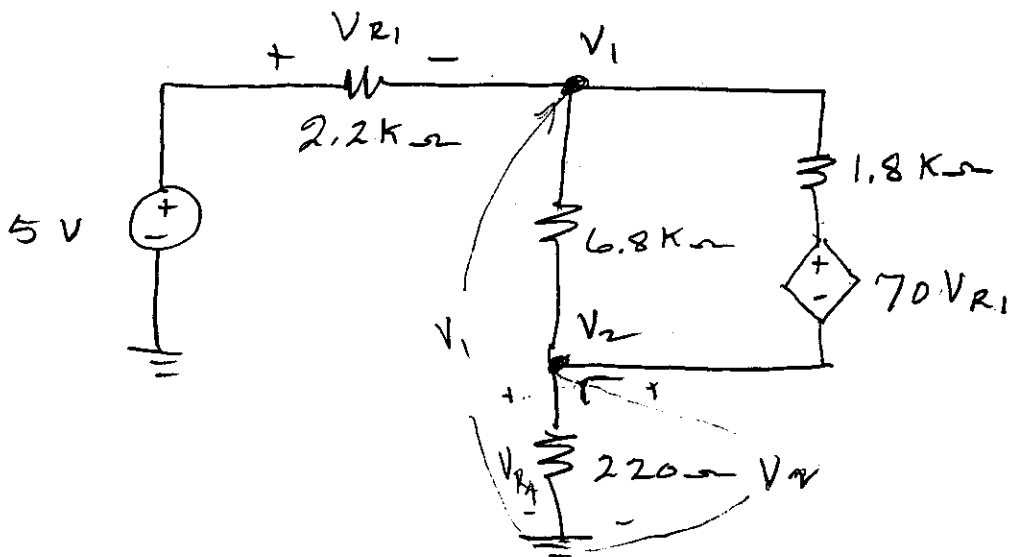3.13 Given the circuit below.

Find the voltage across R_4 .
Use nodal analysis.



At V_1

$$\frac{V_1 - 5}{2.2K} + \frac{V_1 - V_2}{6.8K} + \frac{V_1 - 70V_{R1} - V_2}{1.8K} = 0$$

Also

$$5 - V_{R1} - V_1 = 0$$

$$V_{R1} = 5 - V_1$$

$$3.09V_1 - 15.5 + V_1 - V_2 + 3.78V_1$$

$$- 264.4(5 - V_1) - 3.78V_2 = 0$$

$$272.3V_1 - 4.78V_2 = 1337.5$$

At V_2

$$\frac{V_2}{0.220\text{K}} + \frac{V_2 - V_1}{6.8\text{K}} + \frac{(V_2 + 70V_{R1} - V_1)}{1.8\text{K}} = 0$$

Again; $V_{R1} = 50 - V_1$

mult by 6.8K

$$30.91V_2 + V_2 - V_1 + 3.78V_2 + 264.4(5 - V_1) - 3.78V_1 = 0$$

$$-269.2V_1 + 35.7V_2 = -1322$$

$$\begin{bmatrix} 272.3 & -4.78 \\ -269.2 & 35.7 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1337.5 \\ -1322 \end{bmatrix}$$

$$V_1 = 4.91 \text{ V}$$


$$V_2 = 0.00882 \text{ V}$$

$$V_2 = V_{124} = .00882 \text{ V}$$

Answer book gives 5.1 mV

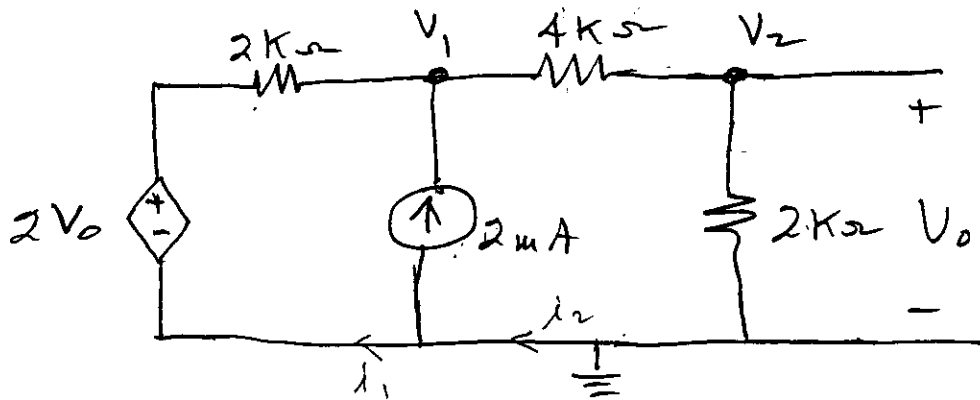3.X1

For the circuit below, use nodal analysis to find V_o .



At V_1 :

$$\frac{V_1 - 2V_o}{2K} + \frac{V_1 - V_2}{4K} = 2\mu A$$

$$2V_1 - 4V_o + V_1 - V_2 = 8$$

but $V_o = V_2$

$$3V_1 - 5V_2 = -8$$

At V_2

$$\frac{V_2 - V_1}{4K} + \frac{V_2}{2K} = 0$$

$$V_2 - V_1 + 2V_2 = 0$$

$$-V_1 + 3V_2 = 0$$


✓

3. X1

$$\begin{bmatrix} 3 & -5 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} -8 \\ 0 \end{bmatrix}$$

$$v_1 = -6V$$

$$v_2 = -2V$$

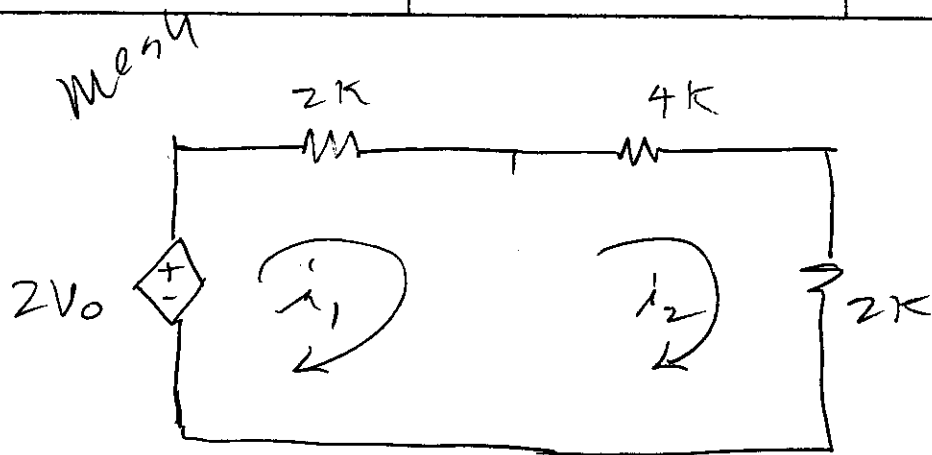

$$2K i_1 + 6K i_2 = 2V_0$$

$$V_0 = 2K i_2$$

$$2K i_1 + 6K i_2 = 4K i_2$$

$$2K i_1 + 2K i_2 = 0$$

$$i_1 + i_2 = 0$$

AND


$$i_1 - i_2 = -2 \times 10^{-3}$$

$$i_2 = 1 \text{ mA}$$

$$V_0 = 2 \text{ V}$$

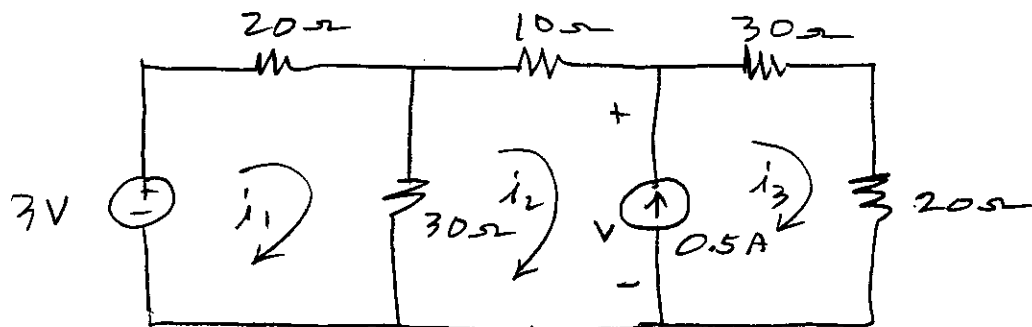3.15

Use mesh analysis to find the voltage V in the circuit below.



$$50i_1 - 30i_2 = 3$$

$$-30i_1 + 40i_2 + 50i_3 = 0$$

$$-i_2 + i_3 = 0.5$$


$$\begin{bmatrix} 50 & -30 & 0 \\ -30 & 40 & 50 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 0 \\ 0.5 \end{bmatrix}$$

$$i_1 = -0.13 \text{ A}, \quad i_2 = -0.32 \text{ A}, \quad i_3 = 0.178 \text{ A}$$

$$V = 50i_3 = 8.89 \text{ V}$$

3.15

Alternate solution

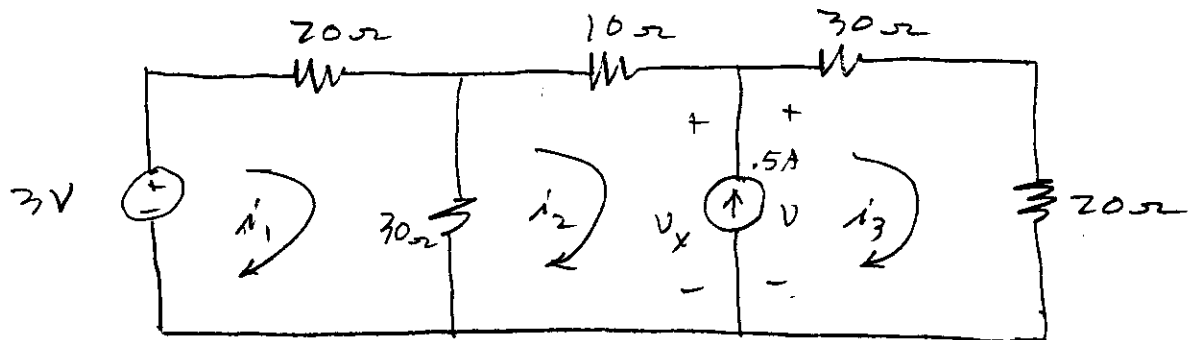

$$50i_1 - 30i_2 = 3$$

$$-30i_1 + 40i_2 + V_x = 0$$

$$50i_3 - V_x = 0$$


$$-i_2 + i_3 = 0.5 \text{ A}$$

$$\begin{array}{cccc}
 i_1 & i_2 & i_3 & V_x \\
 \begin{bmatrix} 50 & -30 & 0 & 0 \\ -30 & 40 & 0 & 1 \\ 0 & 0 & 50 & -1 \\ 0 & -1 & 1 & 0 \end{bmatrix} & \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ V_x \end{bmatrix} & = & \begin{bmatrix} 3 \\ 0 \\ 0 \\ 0.5 \end{bmatrix}
 \end{array}$$

$$i_1 = -0.13 \text{ A}, i_2 = -0.32 \text{ A}, i_3 = 0.178 \text{ A}, V_x = 0.89 \text{ V}$$

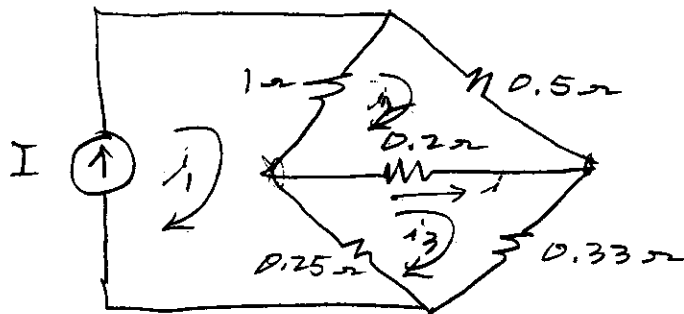3.19

Use mesh analysis to find the current i in the following circuit



Open the source, I .

$$-i_1 + 1.7i_2 - 0.2i_3 = 0$$

$$-.25i_1 - .2i_2 + 0.783i_3 = 0$$

$$i_1 = I$$

$$\begin{bmatrix} 1.7 & -.2 \\ -.2 & 0.783 \end{bmatrix} \begin{bmatrix} i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} I \\ .25I \end{bmatrix}$$

$$i_2 = 0.645I$$


$$i_3 = 0.484I$$

$$i = i_3 - i_2 = (0.484 - 0.645)I$$

$$i = -0.161I$$

Assume $I = 1$,
multiply solutions
by I .

3.20

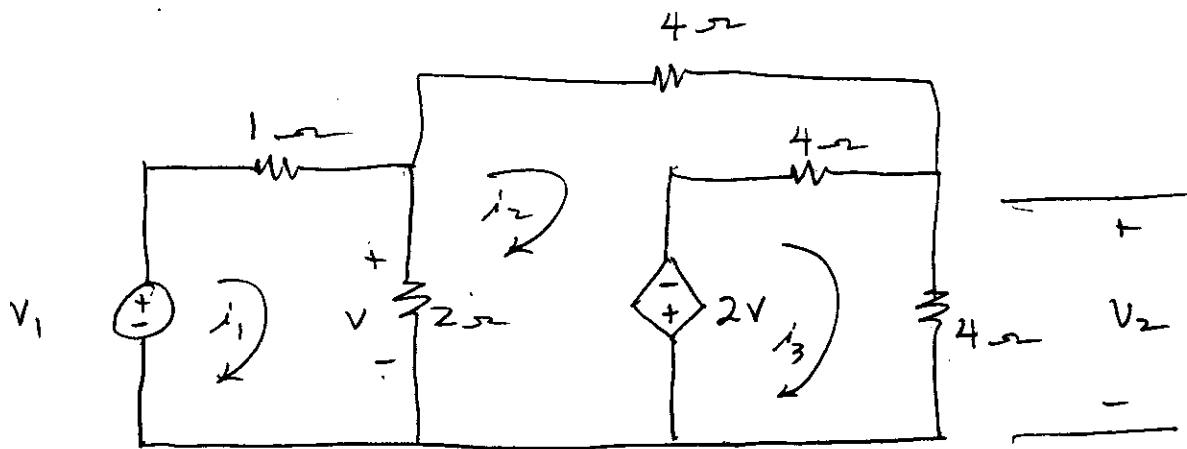

mesh 1

$$3i_1 - 2i_2 = V_1$$

mesh 2

$$-2i_1 + 10i_2 - 4i_3 - 2V = 0$$

$$-4i_1 + 4i_2$$

but

$$V = 2(i_1 - i_2)$$

40,

$$-6i_1 + 14i_2 - 4i_3 = 0$$

mesh 3

$$-4i_2 + 8i_3 + 2V = 0$$

$$4i_1 - 4i_2$$

but

$$V = 2(i_1 - i_2)$$

30,

$$4i_1 - 8i_2 + 8i_3 = 0$$

$$\begin{bmatrix} 3 & -2 & 0 \\ -6 & 14 & -4 \\ 4 & -8 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ 0 \end{bmatrix}$$

7.20 cont.

$$i_3 = \frac{\begin{vmatrix} 3 & -2 & V_1 \\ -6 & 14 & 0 \\ 4 & -8 & 0 \end{vmatrix}}{\begin{vmatrix} 3 & -2 & 0 \\ -6 & 14 & -4 \\ 4 & -8 & 8 \end{vmatrix}} = \frac{V_1(48-56)}{176} = \frac{-8V_1}{176}$$

$$i_3 = \frac{-8}{176} V_1 = -0.045455 V_1$$


$$V_2 = 4 i_3$$

$$V_2 = -0.1818 V_1$$

40

$$\frac{V_2}{V_1} = -0.1818$$

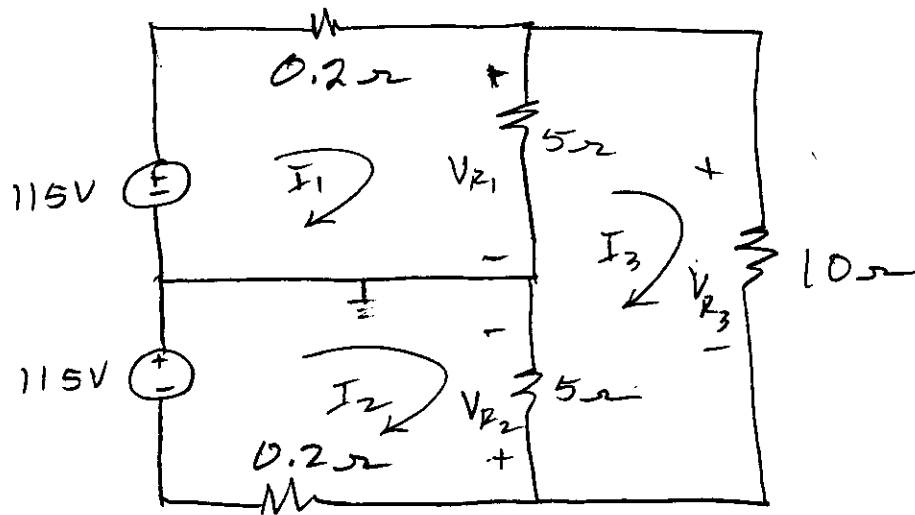3.28 You are given the following circuit.



$$5.2 I_1 - 5 I_3 = 115 \text{ V}$$

$$5.2 I_2 - 5 I_3 = 115 \text{ V}$$

$$-5 I_1 - 5 I_2 + 20 I_3 = 0$$

$$\begin{bmatrix} 5.2 & 0 & -5 \\ 0 & 5.2 & -5 \\ -5 & -5 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 115 \\ 115 \\ 0 \end{bmatrix}$$


$$I_1 = 42.6 \text{ A}, \quad I_2 = 42.6 \text{ A}, \quad I_3 = 21.3 \text{ A}$$

$$V_{R1} = 5 (I_1 - I_3) = 106.5 \text{ V} \quad \text{positive up}$$


$$V_{R2} = 5 (I_3 - I_2) = -106.5 \text{ V} \quad \text{positive down}$$

$$V_{R3} = 10 I_3 = 213 \text{ V} \quad \text{positive up}$$

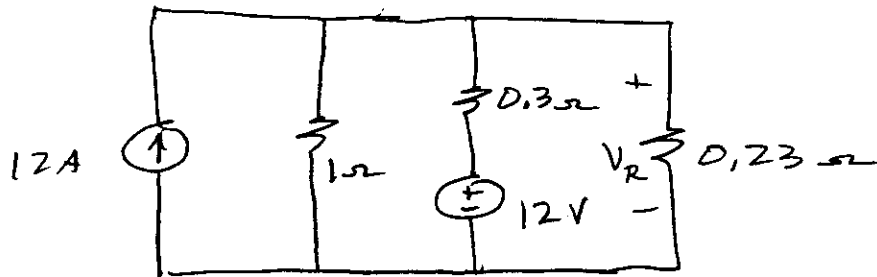3.33 Determine the voltage across $R(V_R)$ using superposition.




Deactivate the current source,

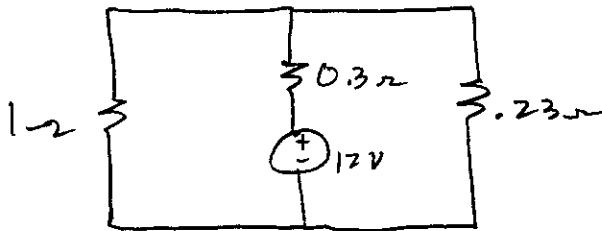

$$\hat{V}_{R1} = \frac{12 \times \left(\frac{0.23 \times 1}{1 + 0.23} \right)}{0.3 + \left(\frac{0.23 \times 1}{1 + 0.23} \right)} = 4.59 \text{ V}$$

Deactivate the voltage source

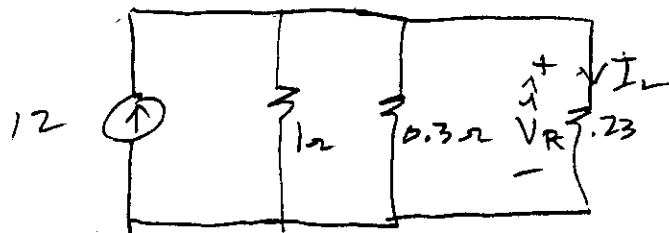

$$I_L = 6 \text{ A}$$

$$I_L = 6 \text{ A}$$

$$\hat{V}_R = 6 \times 0.23 = 1.38 \text{ V}$$

$$\underline{V_R} = \hat{V}_R + \hat{V}_R = 4.59 + 1.38 = 5.97 \text{ V}$$


close to
ANSWER book

3,48


(a) Find the Thevenin resistance seen looking in terminals a-b

(b) Find the Thevenin voltage between a-b with the load resistor removed,

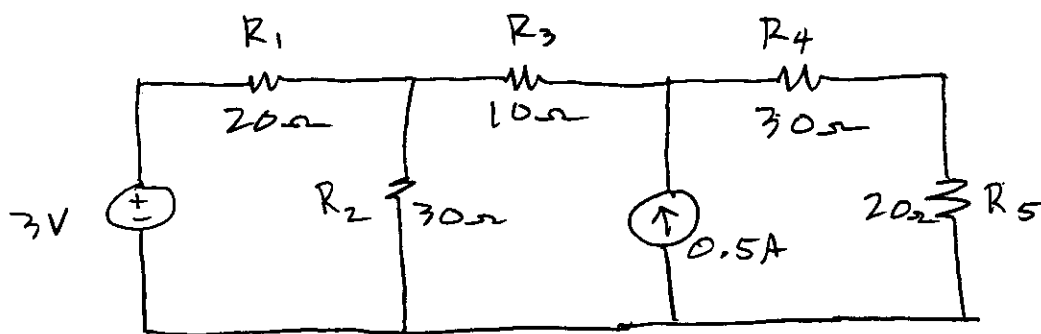(c) Replace R_5 with a short and thereby find I_{Norton}



(a) Thevenin resistance.

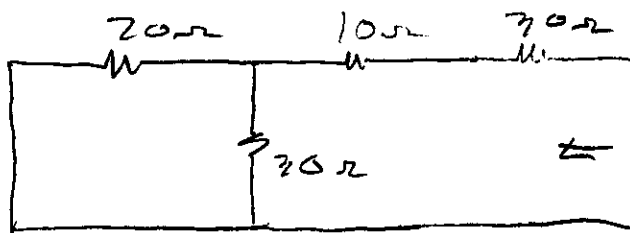


$$R_{TH} = 40 + 20 \parallel 30 = 40 + 12 = 52 \Omega$$

V_{TH} is the open-circuit voltage for the following circuit,

3,48 cont.

2

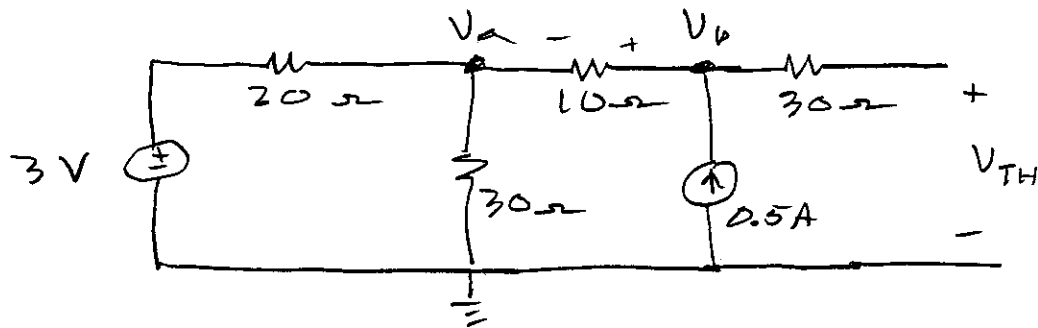

No current flows in the 30Ω resistor since that portion of the circuit is open. Thus, no voltage drop. Thus $V_{TH} = V_b$

At V_a by nodal analysis,

$$\frac{V_a - 3}{20} + \frac{V_a}{30} = 0.5$$

$$3V_a - 9 + 2V_a = 30$$

$$5V_a = 39$$

$$V_a = 7.8V$$

Then

$$V_b - 10 \times 0.5 - V_a = 0$$


$$V_b = 5 + 7.8 = 12.8V = V_{TH}$$

$$I_{NORTON} = \frac{V_{TH}}{R_{TH}} = \frac{12.8}{52} = 0.246A$$

Can also find I_{NORTON} by direct definition.

3.48

3)

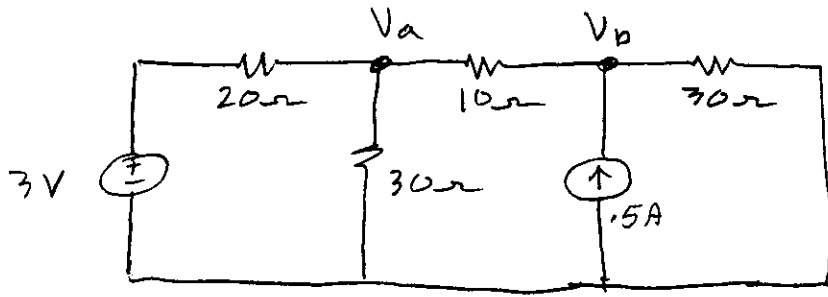

$$\frac{V_a - 3}{20} + \frac{V_a}{30} + \frac{V_a - V_b}{10} = 0$$

60

$$3V_a - 9 + 2V_a + 6V_a - 6V_b = 0$$

$$11V_a - 6V_b = 9$$

$$\frac{V_b - V_a}{10} + \frac{V_b}{30} = 0.5$$



$$3V_b - 3V_a + V_b = 15$$

$$-3V_a + 4V_b = 15$$


$$V_b = 7.385 \text{ V}$$

$$I_{\text{NORTON}} = \frac{7.385}{30} = 0.246 \text{ A}; \text{ AS BEFORE}$$

3.48

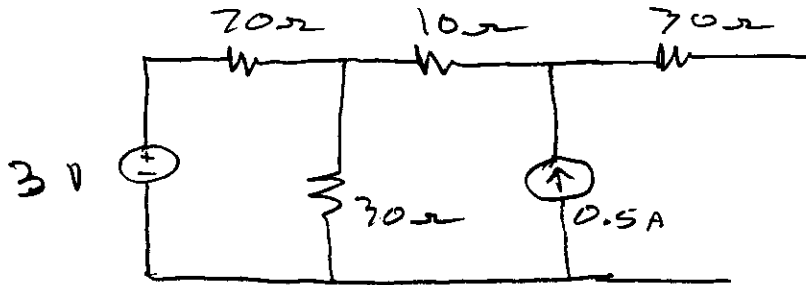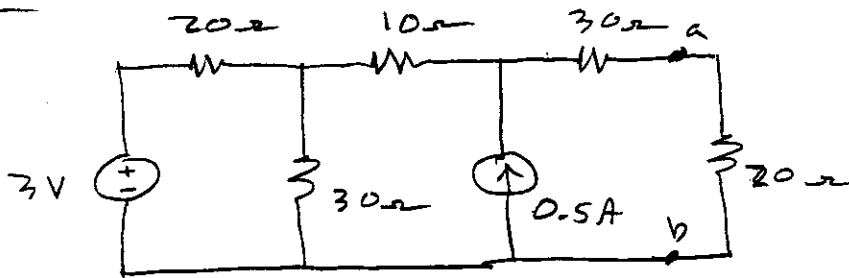


R_{TH} :

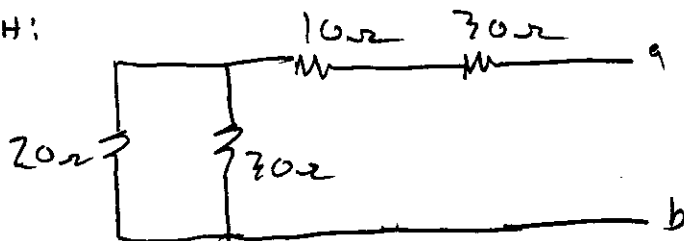

$$20 \parallel 30 = 12 \Omega$$

$$R_{TH} = 12 + 10 + 30 = 52 \Omega$$

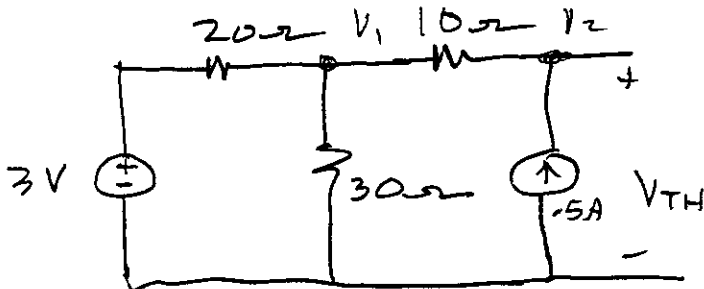

$$\frac{V_1 - 3}{20} + \frac{V_1}{30} + \frac{V_1 - V_2}{10} = 0$$

$$3V_1 - 9 + 2V_1 + 6V_1 - 6V_2 = 0$$


$$11V_1 - 6V_2 = 9$$

3.48 mA.

$$\frac{V_2 - V_1}{10} = 0.5$$


$$-V_1 + V_2 = 5$$

$$V_2 = 12.8 \text{ V}$$

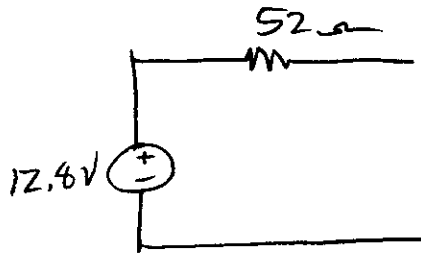

$$I_{\text{NORTON}} = \frac{12.8}{52} = 246 \text{ mA}$$

Also, find I_{NORTON} from ckt below

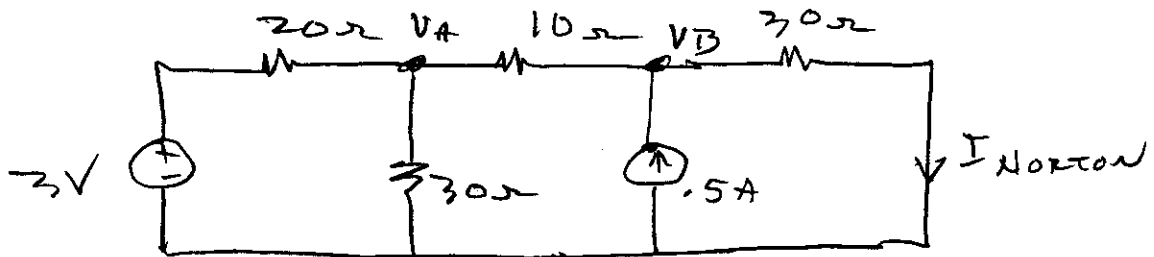

$$I_{\text{NORTON}} = \frac{V_B}{30}$$

$$\frac{V_A - 3}{20} + \frac{V_A}{30} + \frac{V_A - V_B}{10} = 0$$

$$11V_1 - 6V_2 = 9$$

3.48 mA,

3

$$\frac{V_B - V_A}{10} + \frac{V_B}{30} = 0.5$$

$$3V_B - 3V_A + V_B = 15$$

$$\boxed{-3V_A + 4V_B = 15}$$

$$V_A = 4.85 \text{ V}, \quad V_B = 7.385 \text{ V}$$

$$I_{\text{NORTON}} = \frac{V_B}{30} = \frac{7.385}{30} = 0.246$$


40

$$\boxed{I_{\text{NORTON}} = 246 \text{ mA}}$$

As before

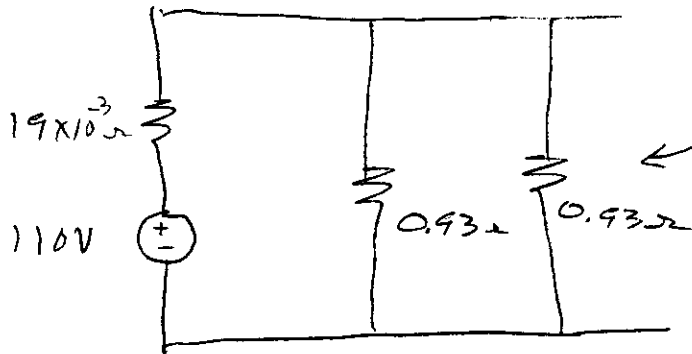3.51


Find the Thevenin for the following circuit.



$$\frac{1}{R_{TH}} = \frac{1}{.019} + \frac{1}{.93} + \frac{1}{.93} = 54.785$$

$$R_{TH} = 0.01825 \Omega$$
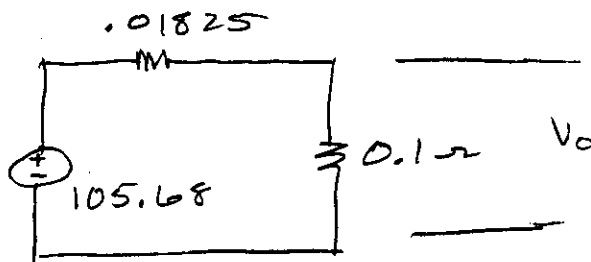
$$V_{TH} = \frac{110 \times 0.465}{0.465 + 0.019} = 105.68 \text{ V}$$



$$V_o = \frac{105.68 \times 0.1}{0.1 + 0.01825} = 89.37 \text{ V}$$

$$\Delta V = 89.37 - 105.68$$

$$\Delta V = -16.3 \text{ V}$$