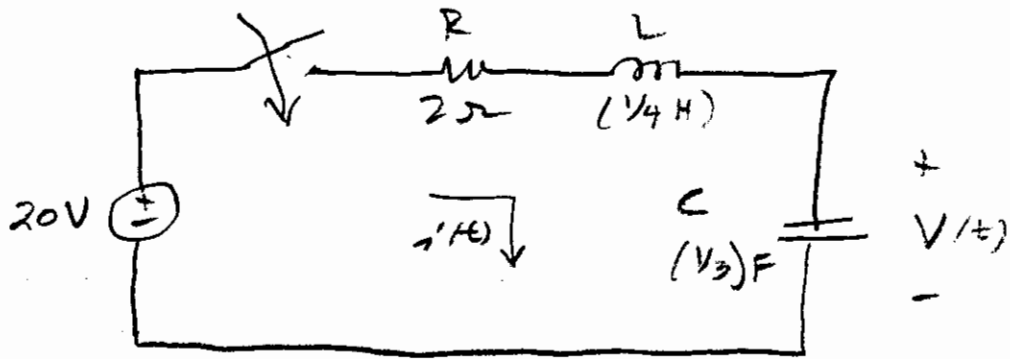


H.W. 6

①



(a)

$$Ri + L \frac{di}{dt} + v(t) = 20$$

$$i = C \frac{dv}{dt}$$

$$LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v(t) = 20$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v(t)}{LC} = \frac{20}{LC}$$

(b) with numbers

$$\frac{d^2v}{dt^2} + 8 \frac{dv}{dt} + 12v(t) = 240$$

$$s^2 + 8s + 12 = 0$$

$$(s+2)(s+6) = 0$$

(c)
$$v(t) = K_3 + K_1 e^{-2t} + K_2 e^{-6t}$$

$$K_3 = 20$$

(1) cont.

1.2

$$V(t) = 20 + k_1 e^{-2t} + k_2 e^{-6t}$$

$$V(0) = 0, \quad i(0^+) = 0$$

$$\text{with } i(0^+) = 0, \quad \frac{dV(0^+)}{dt} = 0$$

$$V(0^+) = 0 = 20 + k_1 + k_2$$

$$\frac{dV(0^+)}{dt} = 0 = -2k_1 - 6k_2$$

$$k_1 + k_2 = -20$$


$$k_1 + 3k_2 = 0$$

$$k_1 = -30, \quad k_2 = 10$$

$$V(t) = 20 - 30e^{-2t} + 10e^{-6t}$$

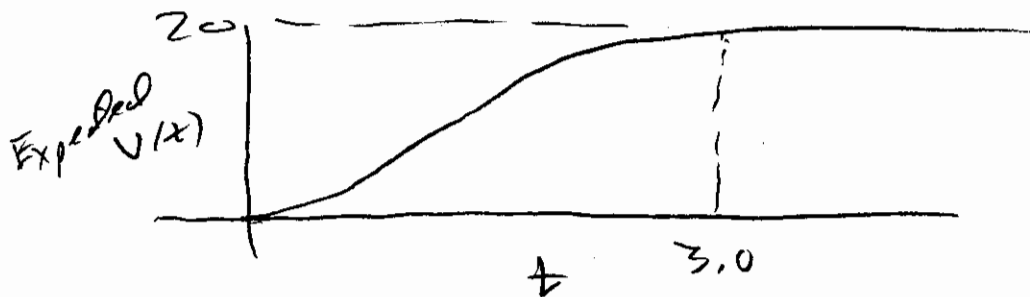(2) MATLAB program:

- slowest time constant = 0.5,
RUN FOR $6 \times 0.5 = 3.0$ sec



```
% program for homework set 6 for ECE 301, Fall 2004, Probalem 1
% Want to write a program that will plot
%  $v = 20 - 30\exp(-2*t) + 10\exp(-6*t)$ 
% Written by W. Green, October 19, 2004, Office computer
% program name rlc_overdamped.m

t = 0 : .03 : 3;


v = 20 - 30*exp(-2*t) + 10*exp(-6*t);

plot(t,v)
grid
ylabel('Voltage, V')
xlabel('t (sec)')
title('Capacitor Voltage Responce of an RLC overdamped circuit to 20 volt step input')
```


1.3

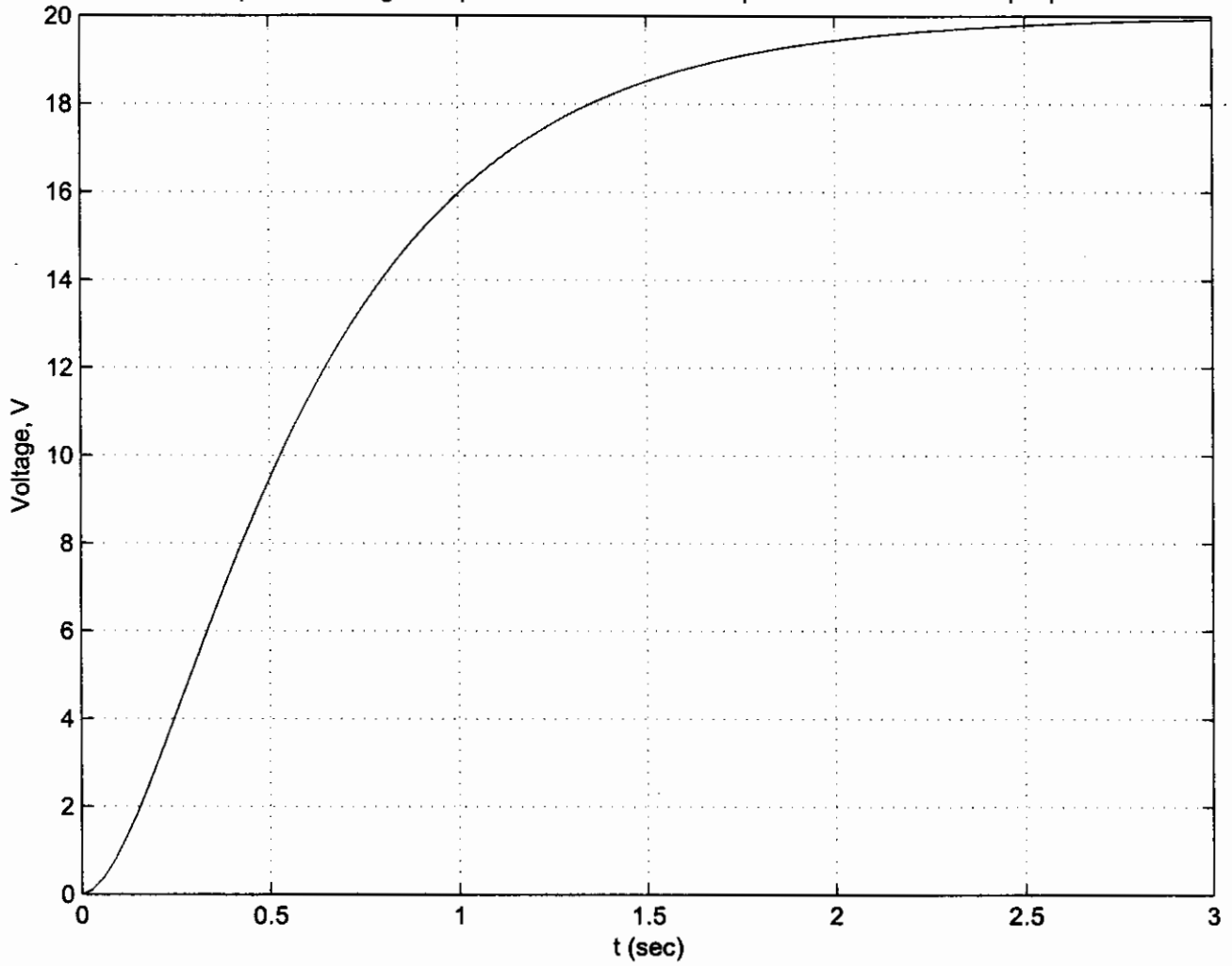1.4

Capacitor Voltage Response of an RLC overdamped circuit to 20 volt step input



(2) Given the circuit

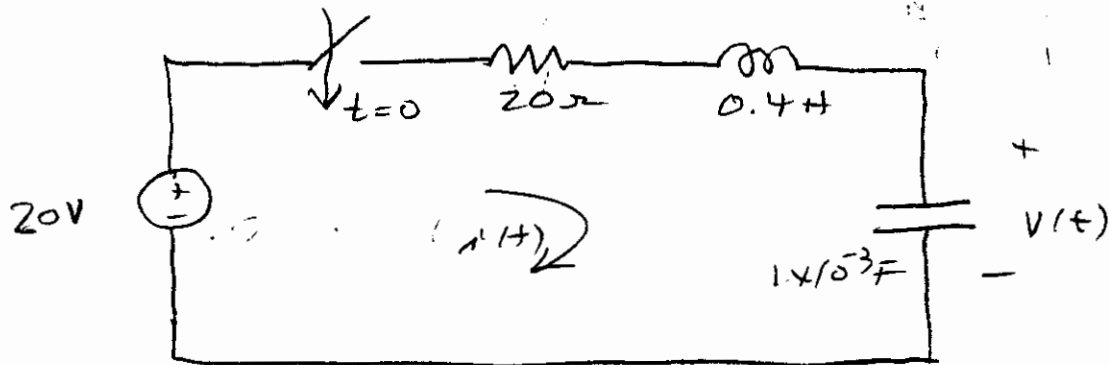

We have

$$Ri + L \frac{di}{dt} + v = 20 \quad \text{Eq (1)}$$

so

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v(t)}{LC} = \frac{20}{LC}$$

In standard form this would be

$$\frac{d^2 v}{dt^2} + 2\zeta\omega_n \frac{dv}{dt} + \omega_n^2 v(t) = \omega_n^2 K = \omega_n^2 20$$

This leads to (underdamped case)

$$v(t) = 20 + e^{-\zeta\omega_n t} [K_1 \cos(\omega_d t) + K_2 \sin(\omega_d t)]$$

compared to

$$v(t) = A + e^{-\beta t} [K_1 \cos \omega_d t + K_2 \sin \omega_d t]$$

(b)

From

$$i(t) = C \frac{dV}{dt}$$

2.2

since

$$i(0^+) = 0, \quad \frac{dV(0^+)}{dt} = 0$$

(c)

The characteristic equation, with numbers, is

$$s^2 + \frac{20}{.4} s + \frac{1}{0.4 \times 1 \times 10^{-3}} = 0$$

$$s^2 + 50s + 2500$$

$$\omega_n = \sqrt{2500} = 50$$

$$2\zeta\omega_n = 50$$

$$2\zeta \times 50 = 50$$

$$\zeta = 0.5$$

$$\zeta\omega_n = 0.5 \times 50 = 25$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2} = 50 \sqrt{1 - .25}$$

$$\omega_d = 43.3$$

∴ Comparing coefficients


$$A = 20,$$

$$B = \zeta\omega_n = 25$$

$$C = D = \omega_d = 43.3$$

(3) Given

3.1

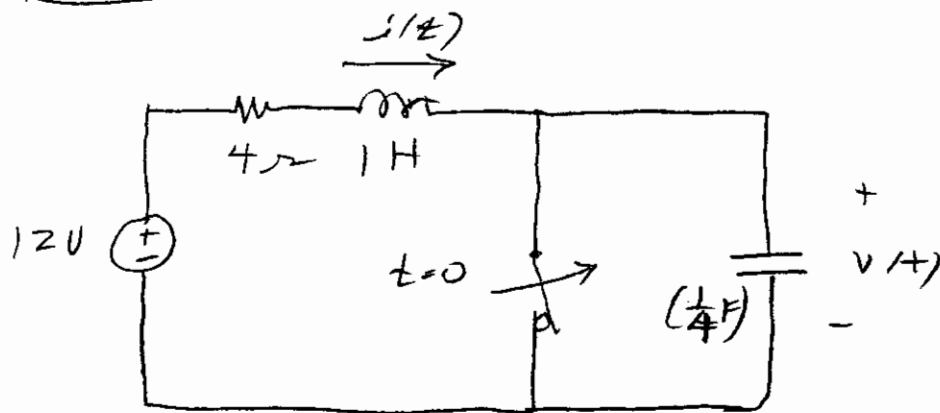

$$t < 0$$

$$i(t) = 3 \text{ A}$$

$$v(t) = 0 \text{ V}$$

$t > 0$ (series RLC)

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v(t)}{LC} = \frac{12}{LC}$$

putting in numbers

$$\frac{d^2 v}{dt^2} + 4 \frac{dv}{dt} + 4 v(t) = 4 \times 12$$

$$s^2 + 4s + 4 = 0$$

$$(s+2)(s+2) = 0$$

repeated roots

$$v(t) = K_3 + (K_1 + K_2 t) e^{-2t}$$

$$K_3 = 12 \quad (\text{inspection})$$

$$v(t) = 12 + (K_1 + K_2 t) e^{-2t}$$

3.2

$$v(0) = 0 \text{ gives}$$

$$0 = 12 + K_1$$

$$K_1 = -12$$

$$\text{From } i(t) = C \frac{dv}{dt}$$

evaluated at $t = 0^+$

$$3 = \frac{1}{4} \frac{dv(0^+)}{dt}$$

$$\frac{dv(0^+)}{dt} = 12$$

$$\frac{dv}{dt} = -2K_1 e^{-2t} - 2K_2 t e^{-2t} + K_2 e^{-2t}$$

evaluated at $t=0$

$$12 = -2K_1 + K_2 = +24 + K_2$$

$$12 = 24 + K_2$$

$$K_2 = -12$$

$$\therefore v(t) = 12 - 12e^{-2t} - 12te^{-2t}$$