

Dest Logo

ECE 300  
HW #13

wlg

Due: December 4, '07 Revision A

Name wlg

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

(13.9)  $V_X = 2.07 \angle 21.1^\circ \text{ V}$

(13.15)  $I_N = 0.687 \angle 6.37^\circ \text{ A}; \quad Z_N = (1 + j19.5) \text{ ohms} = 19.53 \angle 87^\circ \Omega$

(13.18)  $Z_{TH} = 11.32 \angle 85^\circ \text{ ohms}; \quad V_{TH} = 174.17 \angle 9.76^\circ \text{ V}$

(13.21)  $I_1 = 4.25 \angle -8.51^\circ \text{ A}; \quad I_2 = 1.56 \angle 27.5^\circ \text{ A}; \quad P_4 = 4.89 \text{ W}$

(13.37) (a)  $n = 5$ ; (b)  $I_p = I_1 = 104.17 \text{ A}$ ; (c)  $I_s = I_2 = 20.83 \text{ A}$

(13.46) (a)  $I_1 = 1.07 \angle 5.88^\circ \text{ A}; \quad I_2 = 0.536 \angle 185.88^\circ \text{ A}$

(b)  $I_1 = 0.625 \angle 25^\circ \text{ A}; \quad I_2 = 0.313 \angle 25^\circ \text{ A}$


(13.51)  $Z_{IN} = (8 - j1.5) \text{ ohms}; \quad I_1 = 3.95 \angle 10.6^\circ \text{ A}$

(13.56)  $P_{10} = 80 \text{ W}$


wlz

BCE 300  
H.W. #13

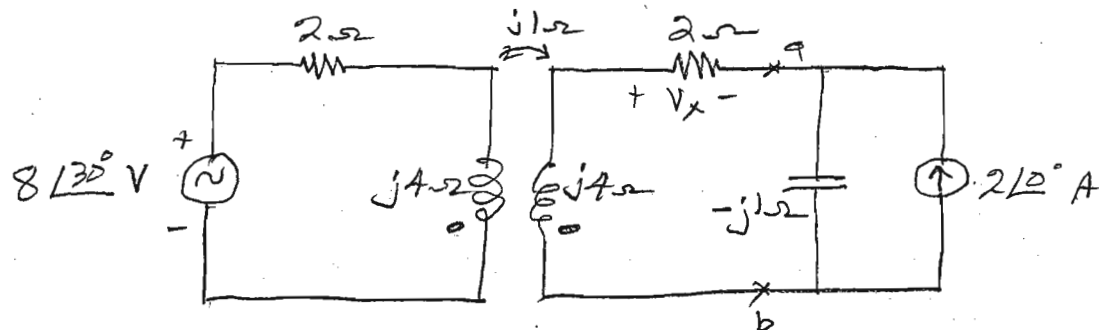(13.9) Find  $V_x$  in the network below.



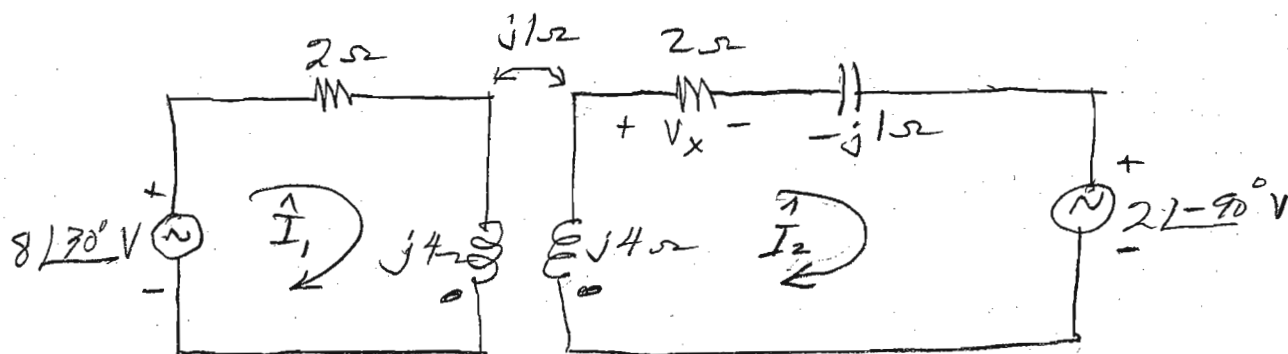Look into a-b and change to a Thevenin equivalent. Also assume  $\vec{I}_1$  and  $\vec{I}_2$  as shown below.



$$(2 + j4)\vec{I}_1 - j\vec{I}_2 = 8\angle 30^\circ$$

$$(2 - j)\vec{I}_2 + 2\angle -90^\circ + j4\vec{I}_2 - j\vec{I}_1 = 0$$

$$-j\vec{I}_1 + (2 + j3)\vec{I}_2 = -2\angle -90^\circ = 2\angle 90^\circ$$


$$\begin{bmatrix} 2 + j4 & 0 - j \\ 0 - j & 2 + j3 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 8\angle 30^\circ \\ 2\angle 90^\circ \end{bmatrix}$$

$$\vec{I}_2 = 1.04\angle 21.1^\circ \text{ A}$$

$$V_x = 2 \times \vec{I}_2 = 2.08\angle 21.1^\circ \text{ V}$$

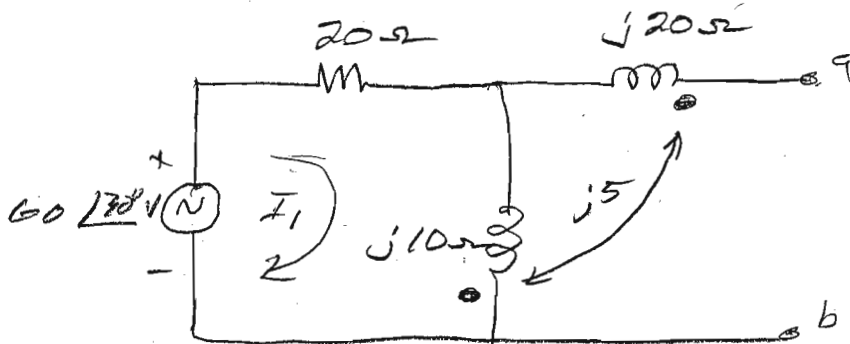(13.15)

Find the Norton equivalent at terminals a-b for the following circuit.



The approach. Find  $V_{ab}$ , open-circuit.  
Then find  $I_{ab}$  short circuit


$$(20 + j10) I_1 = 60 \angle 30^\circ$$

$$I_1 = 2.68 \angle 3.43^\circ \text{ A}$$

$$V_{ab} = (j10) I_1 - j5 I_1 = j5 I_1$$

$$V_{ab} = V_{TH} = 13.42 \angle 93.4^\circ \text{ V}$$

Now for  $I_N$ :

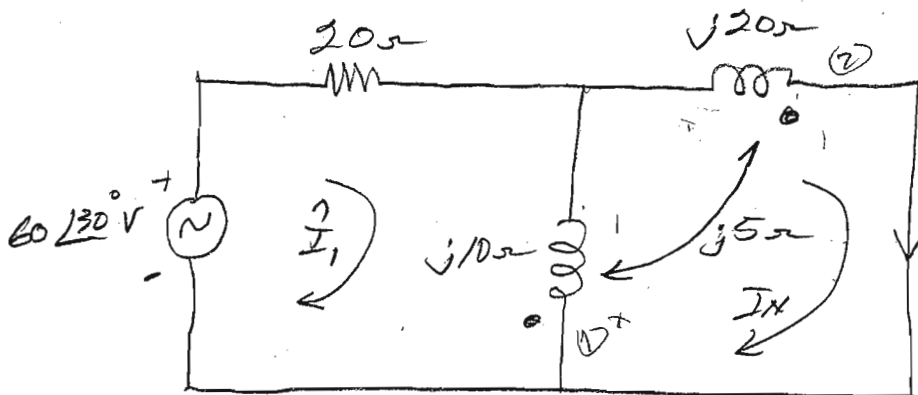

(13.15) cont.

$$(20 + j10) I_1 - j10 I_N + j5 I_N = 60 \angle 30^\circ$$

$$(20 + j10) I_1 - j5 I_N = 60 \angle 30^\circ$$

$$(j10 + j20) I_N - j10 I_1 - j5 I_N - (I_N - I_1) j5 = 0$$

$$(10 - j5) I_1 + j20 I_N = 0$$

$$\begin{bmatrix} (20 + j10) & (0 - j5) \\ (0 + j5) & (0 + j20) \end{bmatrix} \begin{bmatrix} I_1 \\ I_N \end{bmatrix} = \begin{bmatrix} 60 \angle 30^\circ \\ 0 \end{bmatrix}$$

$$I_N = 0.687 \angle 6.37^\circ$$

$$Z_{TH} = \frac{V_{oc}}{I_N} = \frac{13.42 \angle 93.4^\circ}{0.687 \angle 6.37^\circ} =$$

$$Z_{TH} = 19.53 \angle 87^\circ \Omega$$


So:

$$I_N = 0.687 \angle 6.37^\circ \text{ A}$$

$$Z_{TH} = 19.53 \angle 87^\circ \Omega$$

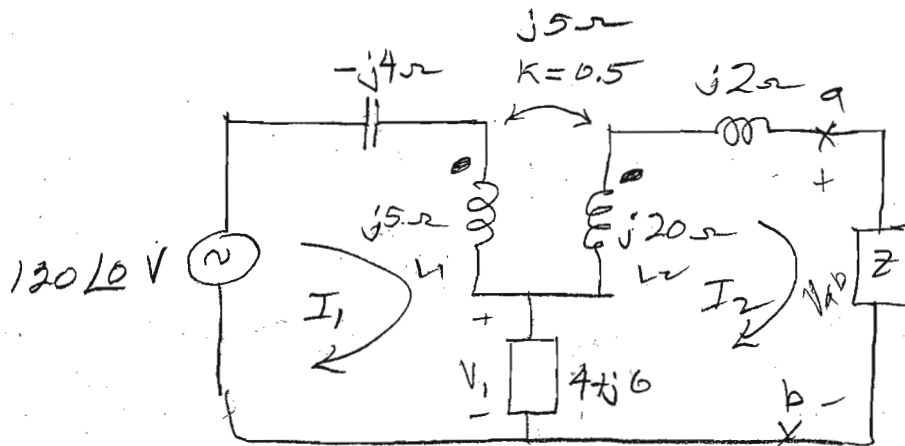(3.18)

Find the Thevenin equivalent to the left of the load  $Z_L$  in the following circuit.



$$k = 0.5 = \frac{M}{\sqrt{L_1 L_2}} = \frac{M}{\sqrt{5 \times 20}}$$

$$M = 0.5 \sqrt{100} = 5$$

Find the open circuit voltage at a-b.

Remove  $Z_L$  in doing this.

$$(-j4 + j5 + 4 + j6) I_1 = 120 \angle 0 \quad (\text{No } I_2, \text{ open})$$

$$I_1 = \frac{120 \angle 0}{4 + j7} = 14.88 \angle -60.26^\circ \text{ A}$$

$$V_{ab} = V_1 + j5 I_1 = (14.88 \angle -60.26^\circ) [(4 + j6) + j5]$$

$$V_{ab} = (14.88 \angle -60.26^\circ) (4 + j11)$$

$$V_{ab} = V_{TH} = 174.17 \angle 9.76^\circ \text{ V}$$


(3.18)

To find  $Z_i$  use

$$V_{TH} = I_{sc} Z$$

$$Z = \frac{V_{TH}}{I_{sc}} \text{, we need to solve for}$$

$I_{sc}$  in the following circuit.

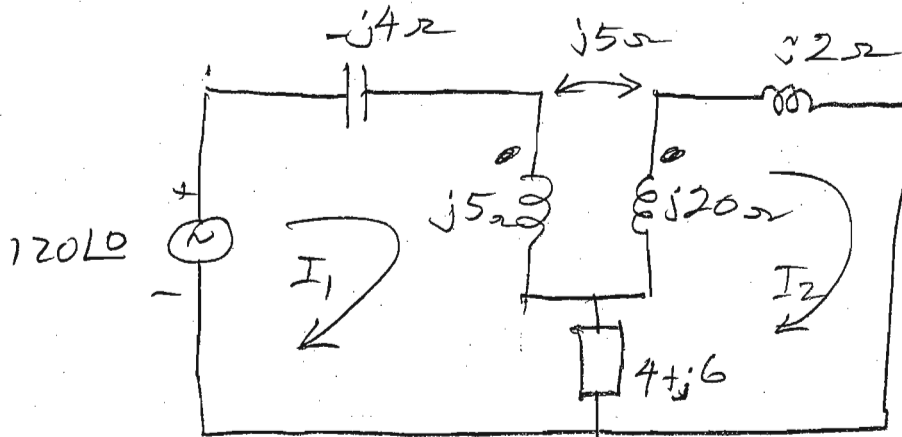

$$I_2 = I_{sc} = I_N$$

$$(-j4 + j5 + 4 + j6)I_1 - (4 + j6)I_2 - j5I_2 = 120 \angle 0^\circ$$

$$(4 + j7)I_1 + (-4 - j11)I_2 = 120 \angle 0^\circ$$


$$(4 + j6)(I_2 - I_1) + j22I_2 - j5I_1 = 0$$

$$(-4 - j11)I_1 + (4 + j28)I_2 = 0$$

$$I_2 = I_N = I_{sc} = 15.39 \angle -75.24^\circ$$

$$Z_{TH} = \frac{174.17 \angle 9.76^\circ}{15.39 \angle -75.24^\circ} = 11.32 \angle 85^\circ \Omega$$

(13.21) Find  $\vec{I}_1$  and  $\vec{I}_2$  in the following circuit. Calculate the power absorbed by the  $4\Omega$  resistor.

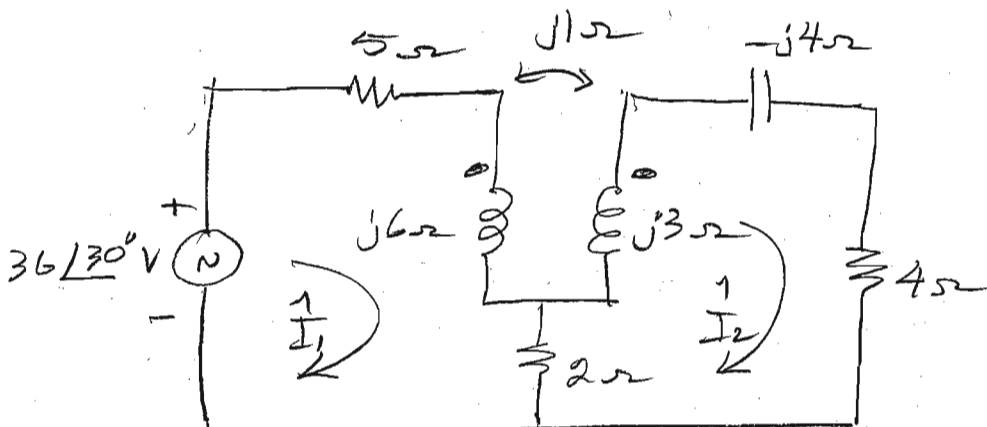

Mesh 1

$$(7 + j6)\vec{I}_1 - 2\vec{I}_2 - j\vec{I}_2 = 36\angle 30^\circ$$

$$(7 + j6)\vec{I}_1 + (-2 - j)\vec{I}_2 = 36\angle 30^\circ$$

Mesh 2

$$2(\vec{I}_2 - \vec{I}_1) + (j3 - j4 + 4)\vec{I}_2 - j\vec{I}_1 = 0$$

$$(-2 - j)\vec{I}_1 + (6 - j)\vec{I}_2 = 0$$

$$\begin{bmatrix} 7 + j6 & (-2 - j) \\ (-2 - j) & (6 - j) \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 36\angle 30^\circ \\ 0 \end{bmatrix}$$

$$\vec{I}_1 = 4.25\angle -8.5^\circ \text{ A} \quad \vec{I}_2 = 1.56\angle 27.5^\circ \text{ A}$$

$$P_A = \frac{|\vec{I}_2|^2}{2} \times 4 = 4.87 \text{ W}$$

(13.37) A 480/2400 V rms step-up ideal transformer delivers 50 kW to a resistive load. Calculate

(a) the turns ratio.

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

$$\frac{2400}{480} = n$$

$$\text{so } n = 5$$

(b) the primary current

$$V_2 I_2 = 50 \text{ kW}$$

$$I_2 = \frac{50,000}{2400} = 20.83 \text{ A}$$

$$\frac{I_1}{I_2} = n = 5$$

$$I_1 = 5 \times I_2 = 5 \times 20.83$$

$$I_1 = 104 \text{ A}$$

(c) the secondary current


$$I_2 = \frac{I_1}{5} = \frac{104}{5}$$

$$I_2 = 20.8 \text{ A}$$




(13,46)

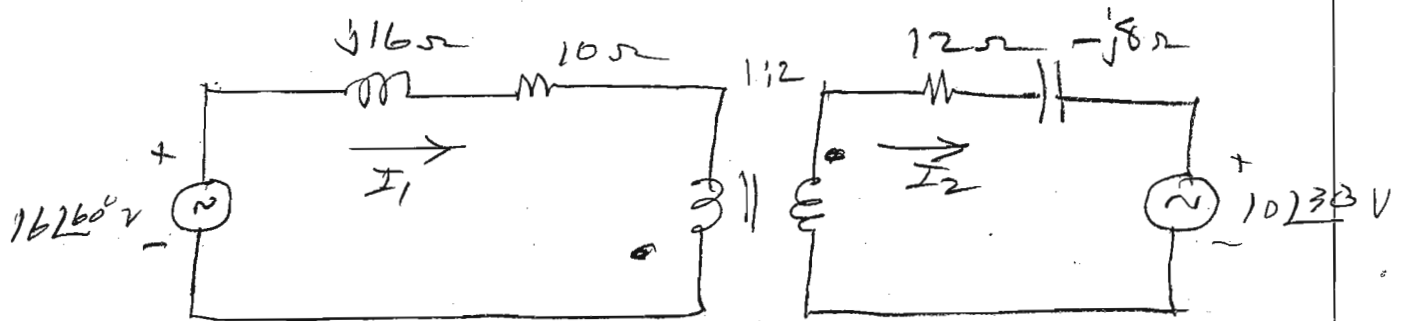(a) Find  $I_1$  and  $I_2$  in the following circuit



Reflect the secondary to the primary

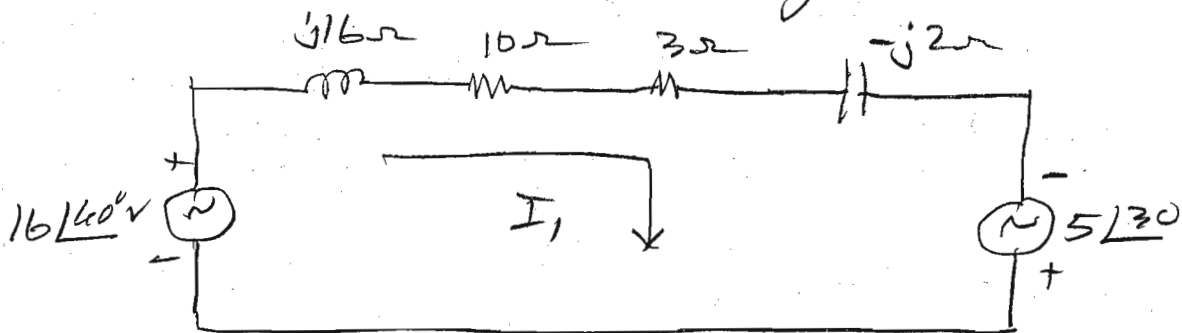

$$(j16 + 10 + 3 - j2)I_1 = 16\angle 60^\circ + 5\angle 30^\circ$$

$$(13 + j14)I_1 = (16\angle 60^\circ + 5\angle 30^\circ)$$

$$I_1 = 1.07\angle 5.87^\circ$$

$$\frac{I_1}{I_2} = -2$$


$$I_2 = \frac{1.07\angle 5.87^\circ}{-2} = 0.535\angle 185.87^\circ \text{ A}$$

13.46-2

(13.46) continued

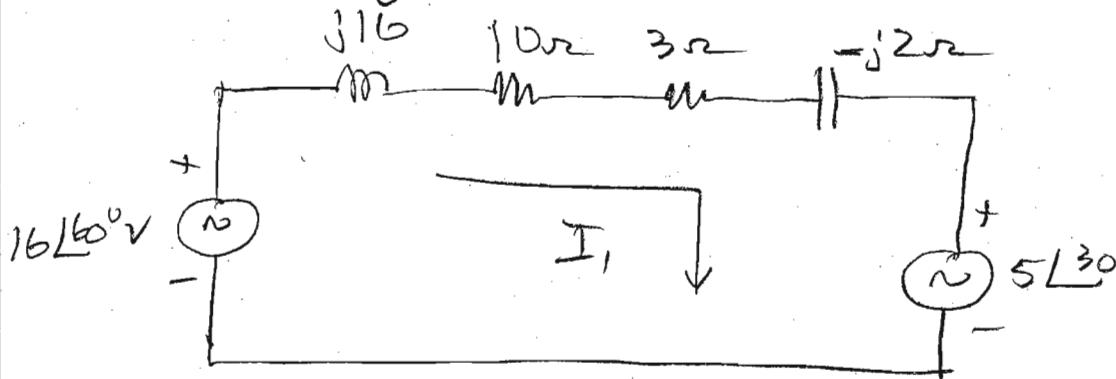(b) Switch the dot on the winding  
and find  $I_1$  and  $I_2$ .

Switching the one dot reverses  
the polarity of the  $5\angle 30^\circ$  source



$$(13 + j14) I_1 = (16 \angle 60^\circ) - (5 \angle 30^\circ)$$


$$I_1 = 0.625 \angle 24.97^\circ \text{ A}$$

$$\frac{I_1}{I_2} = +2$$

$$I_2 = \frac{I_1}{2} = 0.313 \angle 25^\circ \text{ A}$$

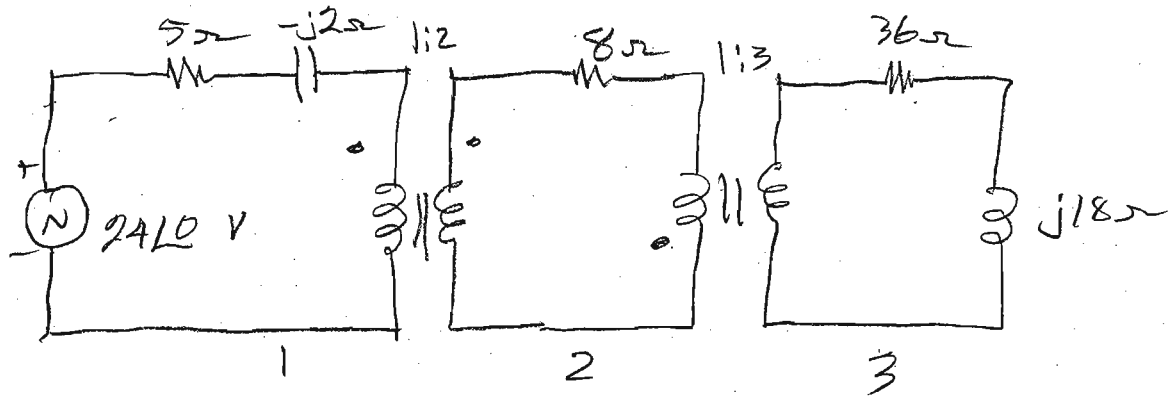
(13.51)

Use the concept of reflected impedance to find the input impedance and  $I_1$  in the following circuit.




Reflecting 3 to 2 we have
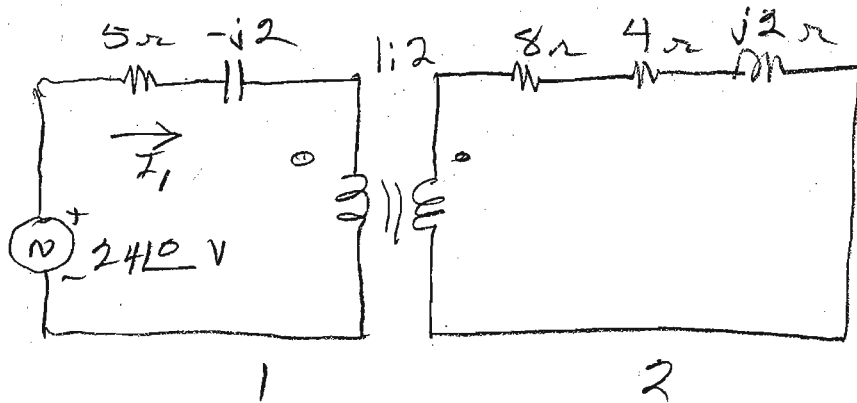
$$\frac{36 + j18}{9} = \frac{36 + j18}{9} = 4 + j2$$




Reflecting 2 to 1

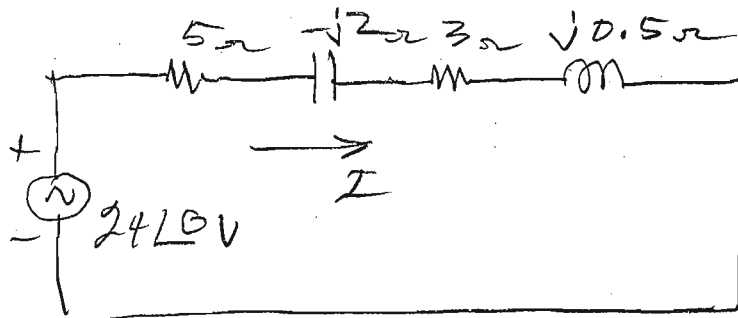

$$Z_{in} = (8 - j1.5) \Omega; I_1 = \frac{240}{8 - j1.5} = 2.95 \angle 10.6^\circ$$

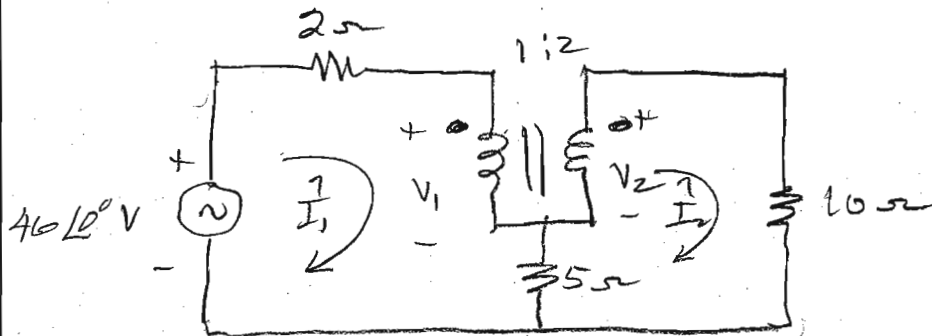(13.56)

Find the power absorbed by the  $10\Omega$  resistor in the ideal transformer circuit below.



Find  $I_2$ ; then  $P_{10} = \frac{1I_2^2}{2} \times 10$

Mesh 1

$$7I_1 - 5I_2 + V_1 + 0V_2 = 46 \angle 0$$

$$-5I_1 + 15I_2 + 0V_1 - V_2 = 0$$

$$\frac{V_2}{V_1} = 2$$

$$0I_1 + 0I_2 + 2V_1 - V_2 = 0$$

$$\frac{I_1}{I_2} = 2$$

$$I_1 - 2I_2 + 0V_1 + 0V_2 = 0$$

$$\begin{bmatrix} 7 & -5 & 1 & 0 \\ -5 & 15 & 0 & -1 \\ 0 & 0 & 2 & -1 \\ 1 & -2 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 46 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$I_2 = 4;$$

$$P_{10} = \frac{4^2}{2} \times 10 = 80 \text{ W}$$