

ECE 300
Spring Semester, 2005
HW Set #5

Due: February 24, 2005

wlg

AM

PM

Name _____

Print(last, first)

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers. Each problem counts 5 points.**

Work the following problems from the text. Answers to the problems, except 4.68, are in the Appendix of the text. You should visit my web site and review the power point slides on op-amps before attempting this homework.

4.68

4.69

4.75

5.9

5.11

5.13

5.15

5.19

5.27

5.31