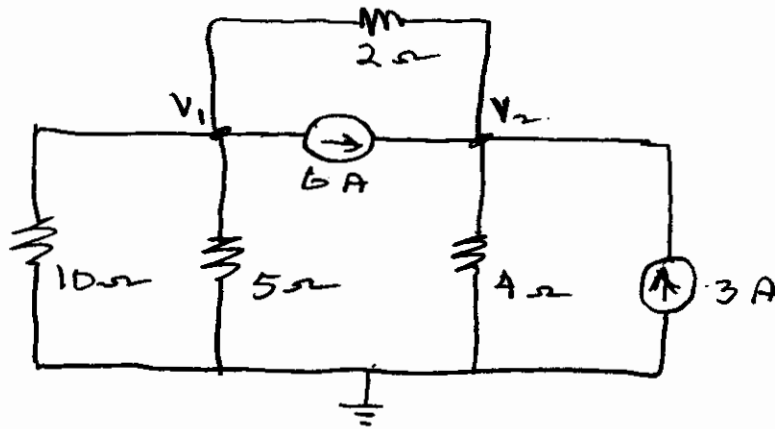


Wly

ECE 300  
HW #3

3.2 Using nodal analysis, obtain  $V_1$  &  $V_2$  for the following circuit.



At  $V_1$   
(10)

$$\frac{V_1}{10} + \frac{V_1}{5} + 6 + \frac{V_1 - V_2}{2} = 0$$

gives

$$V_1 + 2V_1 + 60 + 5V_1 - 5V_2 = 0$$

clearing

$$8V_1 - 5V_2 = -60$$

At  $V_2$

(4)

$$\frac{V_2}{4} + \frac{V_2 - V_1}{2} - 6 - 3 = 0$$

gives

$$V_2 + 2V_2 - 2V_1 = 36$$

clearing

$$-2V_1 + 3V_2 = 36$$


$$\begin{bmatrix} 8 & -5 \\ -2 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -60 \\ 36 \end{bmatrix}$$

$$V_1 = 0$$

$$V_2 = 12V$$

W2g

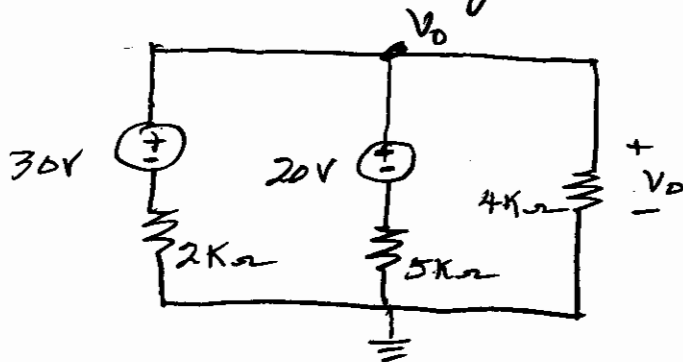3.5 Use Nodal analysis to find  $V_0$  in the following circuit.



Just make  $V_0$  the node voltage.

$$\frac{V_0 - 30}{2K} + \frac{V_0 - 20}{5K} + \frac{V_0}{4K} = 0$$

70 com Rem


$$10V_0 - 300 + 4V_0 - 80 + 5V_0 = 0$$

clearing

$$19V_0 = 380$$

$$\boxed{V_0 = 20V}$$

3.8 Use nodal analysis to find  $V_0$ .

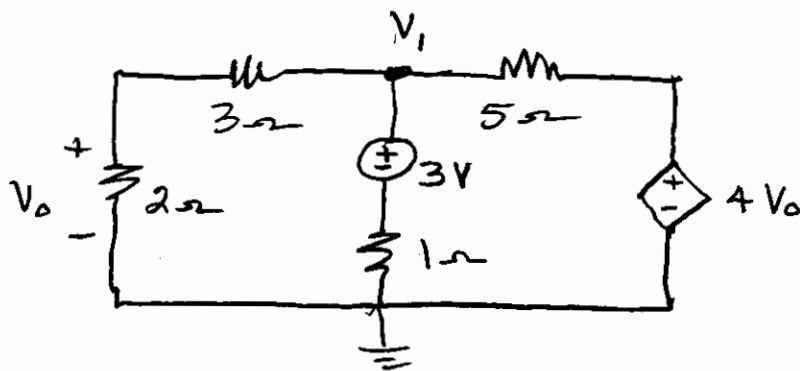

$$\frac{V_1}{5} + \frac{V_1 - 3}{1} + \frac{V_1 - 4V_0}{5} = 0 \quad (1)$$

$$\text{but } V_0 = 2 \left( \frac{V_1}{5} \right) \quad (2)$$

substitute (2) into (1)

$$\frac{V_1}{5} + \frac{V_1 - 3}{1} + \frac{V_1 - 8 \frac{V_1}{5}}{5} = 0$$

OR

$$\frac{V_1}{5} + \frac{V_1 - 3}{1} + \frac{-3V_1}{25} = 0$$

com. den: 25

$$5V_1 + 25V_1 - 75 - 3V_1 = 0$$


$$27V_1 = 75$$

$$V_1 = \frac{75}{27}$$

$$V_0 = \frac{2}{5} \left( \frac{75}{27} \right) = 1.111 \text{ V}$$

$$V_0 = 1.111 \text{ V}$$

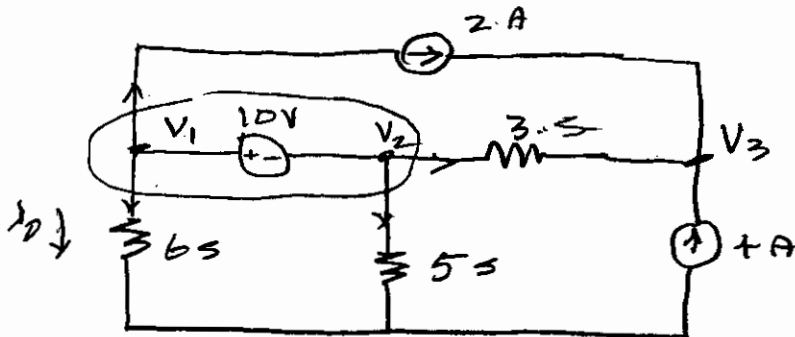3.15 Using nodal analysis, find  $i_o$  and the power dissipated in each resistor in the following circuit.



At the super node

at super node

$$6V_1 + 2 + 5V_2 + (V_2 - V_3)3 = 0$$

$$6V_1 + 8V_2 - 3V_3 = -2$$

at  $V_3$

$$3(V_3 - V_2) - 2 - 4 = 0$$

$$0V_1 - 3V_2 + 3V_3 = 6$$

constraint Eq:

$$V_1 - 10 - V_2 = 0$$

OR

$$-V_1 - V_2 + 0V_3 = 10$$

$$\begin{bmatrix} 6 & 8 & -3 \\ 0 & -3 & 3 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -2 \\ 6 \\ 10 \end{bmatrix}$$

$$V_1 = 4.91 \text{ V} \quad V_2 = -5.09 \text{ V} \quad V_3 = -3.09 \text{ V}$$

$$i_o = V_1 \times 6 = 4.91 \times 6 = 29.46 \text{ A}$$

$$i_o = 29.46 \text{ A}$$

3.15 cont.

2.

$$P_{6s} = V_1^2 \times 6 = (4.91)^2 \times 6 = 144.6 \text{ W}$$

$$P_{6s} = 144.6 \text{ W}$$


$$P_{5s} = (V_2^2) \times 5 = (-5.09)^2 \times 5 = 129.5 \text{ W}$$

$$P_{5s} = 129.5 \text{ W}$$

$$P_{3s} = (V_3 - V_2)^2 \times 3 = (-3.09 + 5.09)^2 \times 3$$

$$P_{3s} = 12 \text{ W}$$

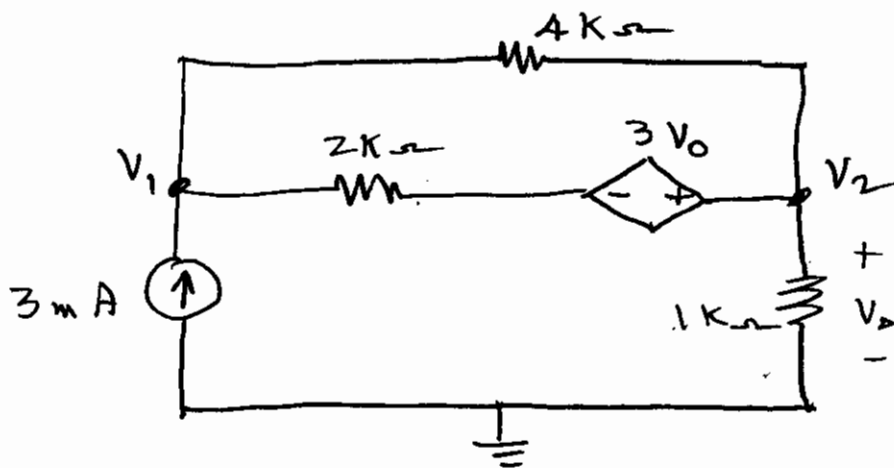3.21 Use nodal analysis to find  $V_1$  and  $V_2$  in the following circuit.



At  $V_1$

$$\frac{V_1 + 3V_0 - V_2}{2K} + \frac{V_1 - V_2}{4K} - 3K^{-1} = 0$$

multiply thru by  $4K$

$$2V_1 + 6V_0 - 2V_2 + V_1 - V_2 = 12$$

$$V_0 = V_2$$

$$3V_1 + 3V_2 = 12$$

At  $V_2$


$$\frac{V_2}{1K} + \frac{V_2 - V_1}{4K} + \frac{V_2 - 3V_0 - V_1}{2K}$$

$$4V_2 + V_2 - V_1 + 2V_2 - 6V_0 - 2V_1$$

$$-3V_1 + V_2 = 0$$

$$V_1 = 1V, \quad V_2 = 3V$$

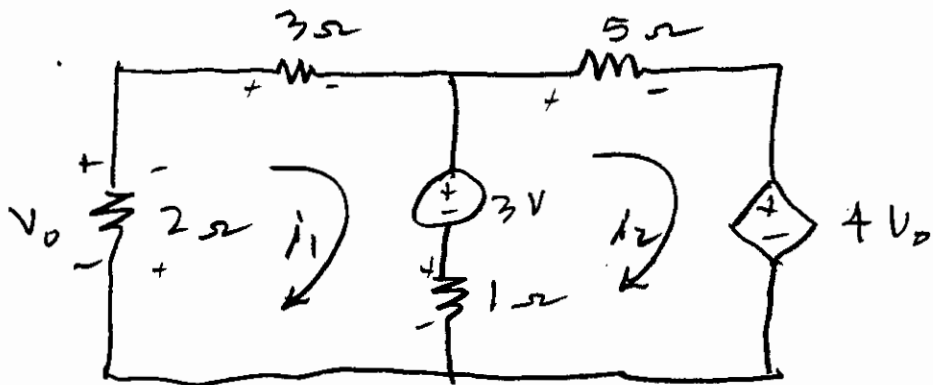3.37 Find  $V_0$  in the following circuit by using mesh analysis.



$$2i_1 + 3i_1 + (i_1 - i_2) + 3 = 0$$

$$\boxed{6i_1 - i_2 = -3}$$

$$-(i_1 - i_2) + 5i_2 - 3 + 4V_0 = 0$$

$$V_0 = -2i_1$$

$$-i_1 + i_2 + 5i_2 - 8i_1 = 3$$

$$\boxed{-9i_1 + 6i_2 = 3}$$


$$i_1 = -0.555$$

$$V_0 = -2i_1 = -1.111 \text{ V}$$

$$\boxed{V_0 = -1.111 \text{ V}}$$

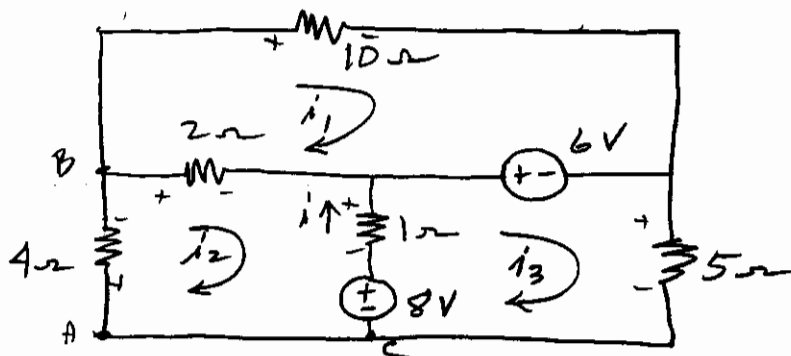3.41

Use mesh analysis to find  $i$  in the following circuit.



At A, cw,  $\sum \text{drops} = 0$

$$4i_2 + 2(i_2 - i_1) + 1(i_2 - i_3) + 8 = 0$$

$$\boxed{-2i_1 + 7i_2 - i_3 = -8}$$

At B, cw,  $\sum \text{drops} = 0$

$$10i_1 - 6 - 2(i_2 - i_1) = 0$$

$$\boxed{12i_1 - 2i_2 + 0i_3 = 6}$$

At C, cw,  $\sum \text{drops} = 0$

$$-8 - 1(i_2 - i_3) + 6 + 5i_3 = 0$$

$$\boxed{0i_1 - i_2 + 6i_3 = 2}$$

$$\begin{bmatrix} 12 & -2 & 0 \\ -2 & 7 & -1 \\ 0 & -1 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ -8 \\ 2 \end{bmatrix}$$


$$i_1 = 0.329 \quad i_2 = -1.026 \quad i_3 = 0.162$$

$$i = i_3 - i_2 = 0.162 - (-1.026) =$$

$$\boxed{i = 1.188 \text{ A}}$$



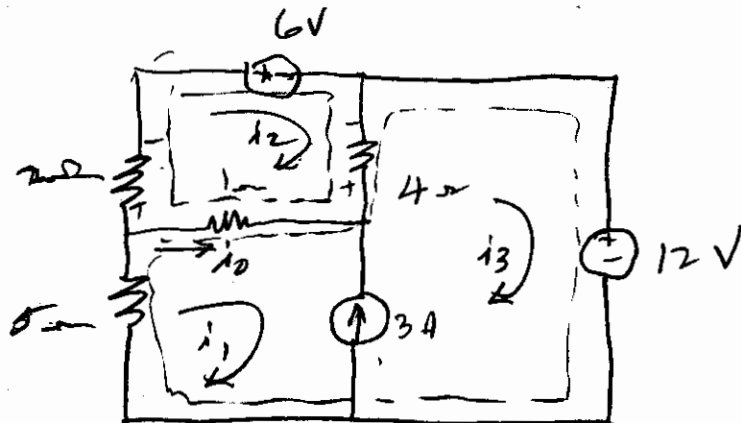3.44 Use mesh analysis to find  $i_0$  in the following circuit.



$$5i_1 + 1(i_1 - i_2) + 4(i_3 - i_2) + 12 = 0$$

$$6i_1 - 5i_2 + 4i_3 = -12$$

$$2i_2 + 6 + 4(i_2 - i_3) + 1(i_2 - i_1) = 0$$

$$-i_1 + 7i_2 - 4i_3 = -6$$

$$-i_1 + 0i_2 + i_3 = 3$$

$$\begin{bmatrix} 6 & -5 & 4 \\ -1 & 7 & -4 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -12 \\ -6 \\ 3 \end{bmatrix}$$


$$i_1 = -3.067A, \quad i_2 = -1.333, \quad i_3 = -0.666$$

$$i_0 = i_1 - i_2 = -3.067 + 1.333 = -1.734A$$

$$i_0 = -1.734A$$


-1.733

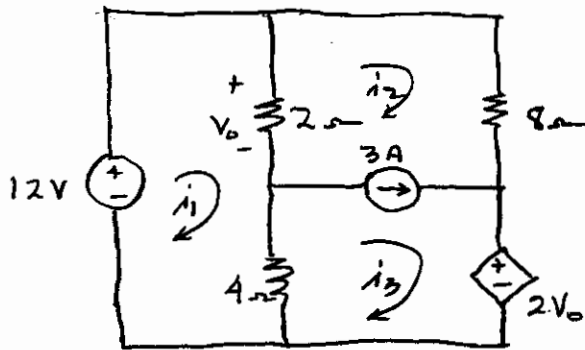3.52 Use mesh analysis to find  $i_1, i_2, i_3$ .



Original circuit

Fig 1:

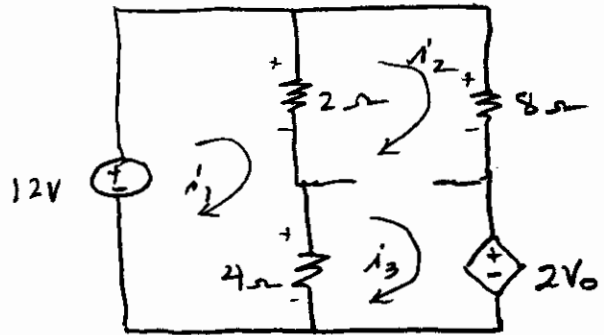

With current source removed

Fig 2:

From Figure 2 we write;

$$-12 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0$$

or

$$6i_1 - 2i_2 - 4i_3 = 12 \quad (1)$$

$$-4(i_1 - i_3) - 2(i_1 - i_2) + 8i_2 + 2V_0 = 0 \quad (2)$$

with  $V_0 = 2(i_1 - i_2)$  into (2)

$$-4(i_1 - i_3) - 2(i_1 - i_2) + 8i_2 + 2[2(i_1 - i_2)] = 0 \quad (3)$$

clearing

$$-2i_1 + 6i_2 + 4i_3 = 0 \quad (4)$$

constraint equation is

$$i_3 - i_2 = 3$$

or

$$0i_1 - i_2 + i_3 = 3 \quad (5)$$

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 6 & 4 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 3 \end{bmatrix}$$

$$i_1 = 3.5 \text{ A}, \quad i_2 = -0.5 \text{ A}, \quad i_3 = 2.5 \text{ A}$$

3.61

Calculate the current gain  $i_o/i_s$  in the circuit below:

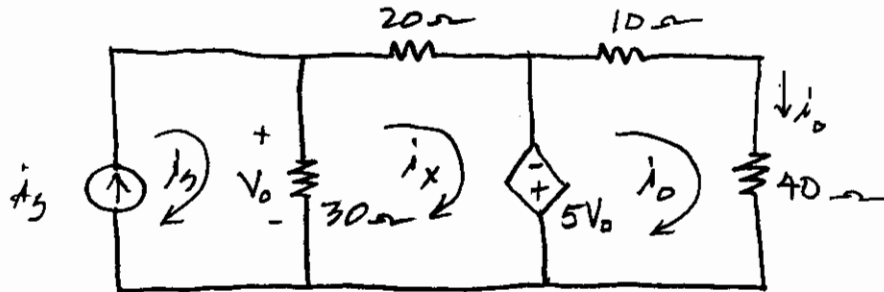


Figure 1  
Nodal analysis would probably be easier but I will work this using mesh

Redrawing Figure 1 with the current source removed gives;

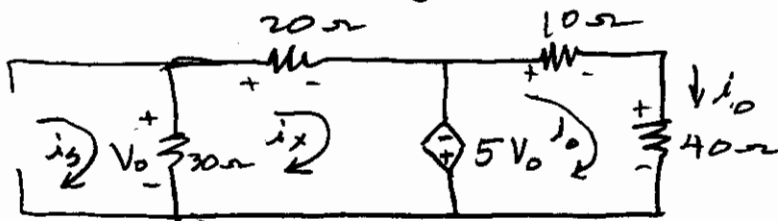


Figure 2

From Figure 2 we write

$$-30(i_s - i_x) + 20i_x - 5V_o = 0 \quad (1)$$

$$\text{but } V_o = 30(i_s - i_x) \quad (2)$$

Substitute (2) into (1)

$$-30(i_s - i_x) + 20i_x - 5[30(i_s - i_x)] = 0 \quad (3)$$

clearing gives,

$$-30i_s + 30i_x + 20i_x - 150i_s + 150i_x = 0$$

$$\text{OR } \boxed{-180i_s + 200i_x + 0i_s = 0} \quad (4)$$

3.61 CONTINUED

2

From Figure 2, second mesh,

$$5V_0 + 10i_0 + 40i_0 = 0 \quad (5)$$

Substituting Eq (2) into (5) gives

$$5[30(i_s - i_x)] + 50i_0 = 0$$
$$\boxed{150i_s - 150i_x + 50i_0 = 0} \quad (6)$$

So, we have from (4) and (6)

$$-180i_s + 200i_x + 0i_0 = 0 \quad (7)$$

$$150i_s - 150i_x + 50i_0 = 0 \quad (8)$$

Strategy: Eliminate  $i_x$  from (7) & (8)

mult:ply (7) by 1.5; multiply (8) by 2

$$-270i_s + 300i_x + 0i_0 = 0 \quad (9)$$

$$300i_s - 300i_x + 100i_0 = 0 \quad (10)$$

ADD (9) and (10)

$$30i_s + 100i_0 = 0$$

OR

$$100i_0 = -30i_s$$


$$i_0 = -0.3i_s$$

OR

$$\frac{i_0}{i_s} = -0.3$$

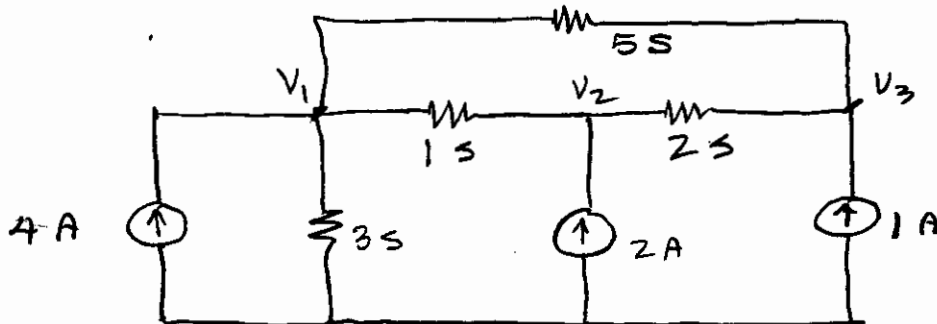3.68

By inspection, write the node-voltage equations for the following.



The equations will be of the form;

$$\begin{bmatrix} G_{11} & -G_{12} & -G_{13} \\ -G_{21} & G_{22} & -G_{23} \\ -G_{31} & -G_{32} & G_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \Sigma i_1 \\ \Sigma i_2 \\ \Sigma i_3 \end{bmatrix}$$

$G_{11}$  = sum of admittance tied to node  $V_1$

$G_{22}$  = sum of admittance tied to node  $V_2$

$G_{33}$  = sum of admittance tied to node  $V_3$

$G_{12} = G_{21}$  = sum of admittance connected between nodes  $V_1$  and  $V_2$

$G_{13} = G_{31}$  = sum of admittance connected between nodes  $V_1$  and  $V_3$

$G_{23} = G_{32}$  = sum of admittance connected between nodes  $V_2$  and  $V_3$

We have

$$G_{11} = 3 + 1 + 5 = 9 \text{ S}$$

$$G_{22} = 2 + 1 = 3 \text{ S}$$

$$G_{33} = 2 + 5 = 7 \text{ S}$$

3.68 CONTINUED

2

$$G_{12} = G_{21} = -15$$

$$G_{13} = G_{31} = -55$$

$$G_{23} = G_{32} = -25$$

We have


$$\begin{bmatrix} 9 & -1 & -5 \\ -1 & 3 & -2 \\ -5 & -2 & 75 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 2 \\ 1 \end{bmatrix}$$

solving for  $V_1, V_2, V_3$

$$V_1 = 2.33 \text{ V}, \quad V_2 = 3.27 \text{ V}, \quad V_3 = 2.75 \text{ V}$$

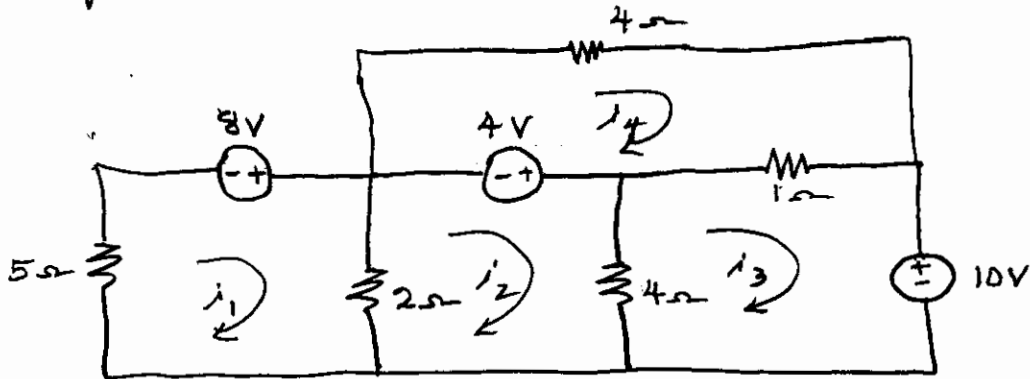3.72

By inspection, write the mesh equations for the following circuit



From mesh 1

$$7i_1 - 2i_2 = 8$$

From mesh 2

$$6i_2 - 4i_3 = 4$$

From mesh 3

$$-4i_2 + 5i_3 - i_4 = -10$$

From mesh 4

$$-i_3 + 5i_4 = -4$$

OR

$$\begin{bmatrix} 7 & -2 & 0 & 0 \\ 0 & 6 & -4 & 0 \\ 0 & -4 & 5 & -1 \\ 0 & 0 & -1 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 8 \\ 4 \\ -10 \\ -4 \end{bmatrix}$$