

Desk Copy

ECE 300
Spring Semester, 2005
HW Set #10

Due: April 14, 2005

wlg

AM

PM

Name

Green

Print(last, first)

Version 2

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 5 points.

11.4 $P_{\text{supplied}} = 42.7 \text{ W}$, $P_{20} = 30.5 \text{ W}$, $P_{10} = 12.2 \text{ W}$; $P_c = P_L = 0$

11.13 $Z_L = 12.8 + j49.6 \text{ ohms}$, $P_{\text{max}} = 90.1 \text{ W}$

11.15 $Z_L = 5 - j0.5 \text{ ohms}$, $V_{\text{th}} = 78.97 \angle 71.57 \text{ V}$, $P_o = 89.97 \text{ W}$

11.22 $I_{\text{RMS}} = 2.449 \text{ A}$

11.33 $I_{\text{RMS}} = 6.667 \text{ A}$

11.49 (a) $S = 4 + j2.37 \text{ kVA}$; (b) $S = 1.6 - j1.2 \text{ kVA}$; (c) $S = 0.46 + j1.27 \text{ kVA}$
(d) $S = 110.8 + j166.2 \text{ VA}$

11.51 (a) $\text{pf} = 0.9956 \text{ lagging}$; (b) $P = 15.56 \text{ W}$; (c) $Q = 1.466 \text{ VAR}$
(d) $S = 15.63 \text{ VA}$; (e) $S = 15.56 + j1.466 \text{ VA}$


15.56 $S = 4.54 + j1.4 \text{ VA}$

11.60 $V_o = 7.1 \angle 32.3^\circ \text{ kV}$ $\text{pf} = 0.8454 \text{ lagging}$

11.74 (a) $\text{pf} = 0.8992 \text{ lagging}$; (b) $C = 5.74 \text{ mF}$

H.W. # 10

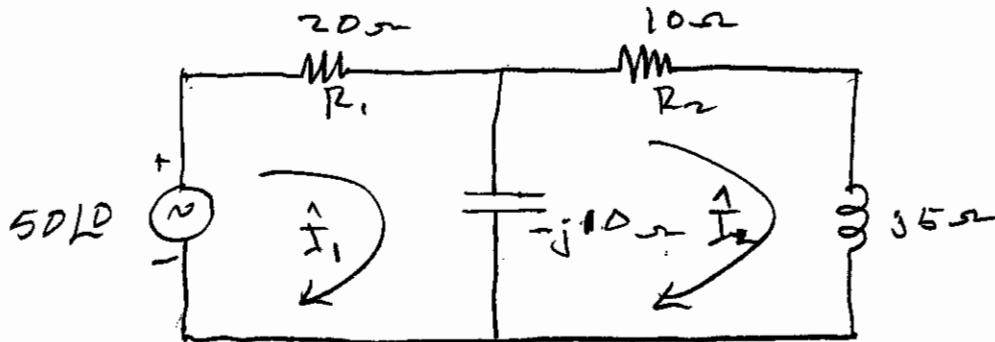11.4 Find the average power absorbed by each element (device) in the following circuit.



Use mesh analysis to find \hat{I}_1 and \hat{I}_2 .

$$\begin{bmatrix} 20-j10 & j10 \\ j10 & 10-j5 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 50\angle 0 \\ 0 \end{bmatrix}$$

$$\hat{I}_1 = 1.74 \angle 12.2^\circ \quad \hat{I}_2 = 1.56 \angle -51.3^\circ \text{ A}$$

$$\underline{P_{20}} = \frac{1}{2} |\hat{I}_1|^2 R_1 = \underline{30.3 \text{ W}}$$

$$\underline{P_{10}} = \frac{1}{2} (1.56)^2 \times 10 = \underline{12.17 \text{ W}}$$

$$P_{\text{supplied}} = \frac{50 \times 1.74 \cos(12.2)}{2}$$


$$\underline{P_{\text{supplied}} = 42.6 \text{ W}}$$

11.13

For the following circuit find;

(a) Load impedance for maximum power transfer.

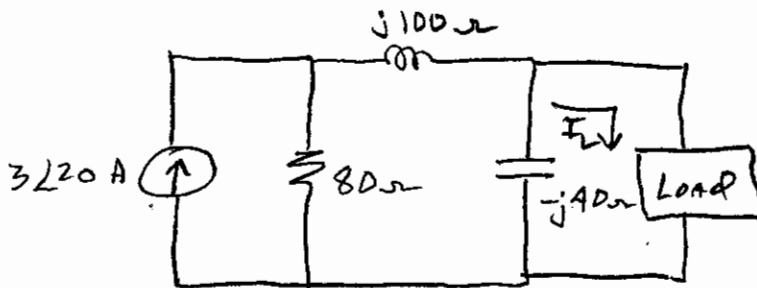(b) the value of power delivered to the load of part (a)



(a) For maximum power transfer make

$$Z_L = Z_{TH}^*$$

$$Z_{TH} = \frac{(80 + j100)(40 \angle -90^\circ)}{80 + j100 - j40}$$

$$Z_{TH} = 12.8 - j49.6 \Omega$$

$$\therefore Z_L = 12.8 + j49.6 \Omega$$

(b)

$$V_{TH} = \frac{(3/20)(80)(40 \angle -90^\circ)}{(80 + j60)} = 96 \angle -46.9^\circ \text{ V}$$


$$I_L = \frac{V_{TH}}{Z_L} ; P_L = \frac{I_L^2}{2} R_L = \frac{|V_{TH}|^2}{8 R_L}$$

$$P_L = \frac{(96)^2}{8 \times 12.8} = 90 \text{ W}$$

$$P_L = 90 \text{ W}$$

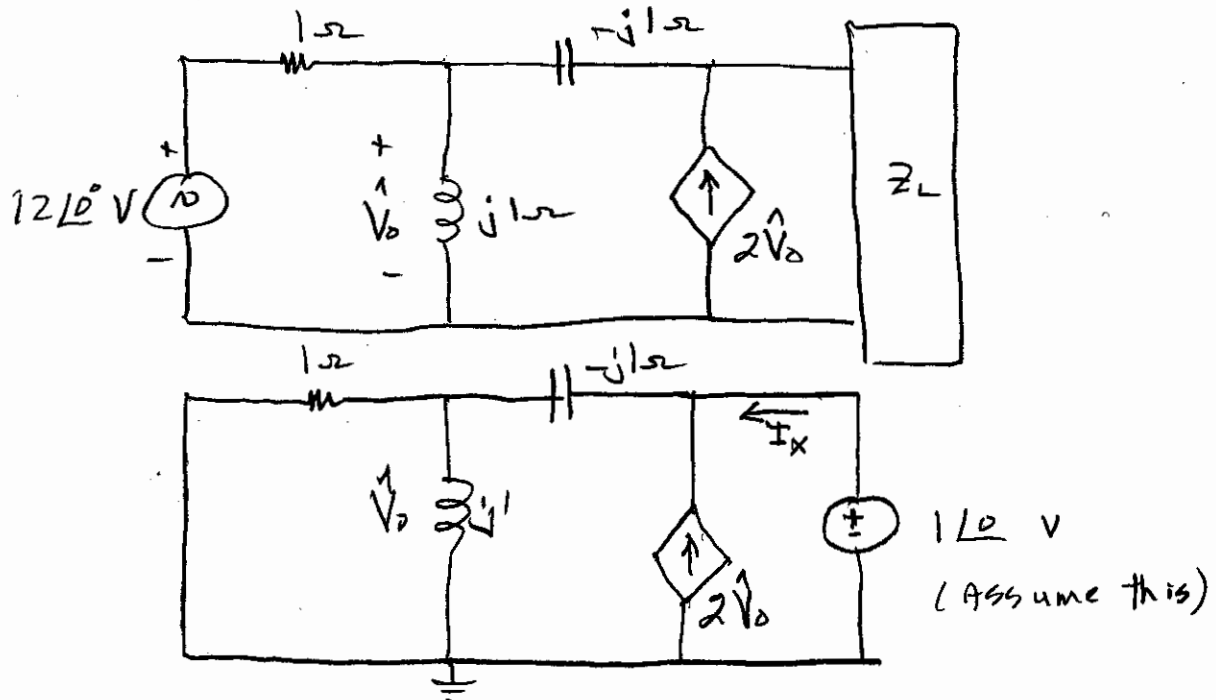11.15

Given the circuit below. Find Z_L for maximum power transfer and find the power delivered to the resulting load resistance.



$$\frac{\hat{V}_0}{1} - j\frac{\hat{V}_0}{1} + j\frac{\hat{V}_0 - 1}{1} = 0$$

$$\hat{V}_0 - j\hat{V}_0 + j\hat{V}_0 = j$$

$$I_x + 2V_0 = \frac{1 - V_0}{-j} = j - jV_0$$

$$I_x = j - jV_0 + 2V_0 = j + V_0(-2 - j)$$

$$I_x = j + j(-2 - j) = j - 2j + 1 = 1 - j$$

$$Z_{TH} = \frac{1}{I_x} = \frac{1}{1 - j} = 0.5 + j0.5 \text{ } \Omega$$


11.15 continued

2

for maximum power transfer make

$$\boxed{Z_L = Z_{TH}^* = 0.5 - j0.5}$$

Now find V_{TH}

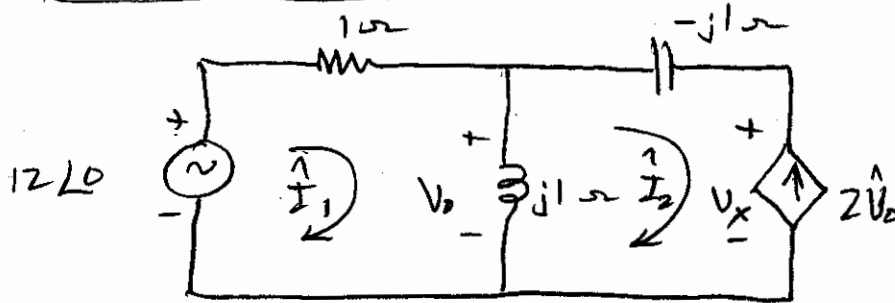

$$(1+j)I_1 - jI_2 = 12 \quad (1)$$

$$-jI_1 + V_x = 0 \quad (2)$$

$$I_2 = -2V_o = -2j(I_1 - I_2)$$

$$(1-2j)I_2 = -2jI_1$$

$$I_2 = \frac{-j2I_1}{1-j2} \quad (3)$$

Put (3) into (1)

$$(1+j)I_1 - j\left(\frac{-j2I_1}{1-j2}\right) = 12$$

Gives

$$I_1 = \frac{12(1-j2)}{1-j}$$

From (2),


$$V_x = V_{TH} = jI_1$$

11.15 continued

3

$$V_{TH} = \frac{12j(1-j2)}{(1-j)} = \frac{12(2+j)}{(1-j)}$$
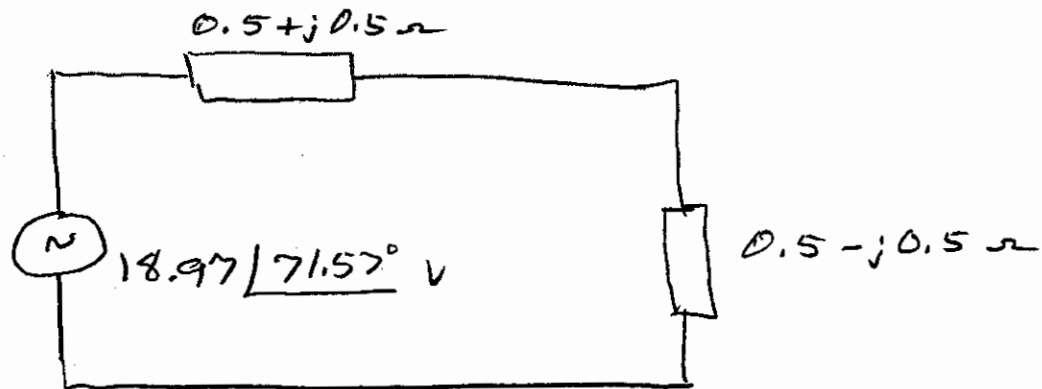
$$\vec{V}_{TH} = 18.97 \angle 71.57^\circ \text{ V}$$




$$P_o = \frac{|\vec{V}_{TH}|^2}{8 \times 0.5} = \frac{(18.97)^2}{4}$$

$$P_o = 89.97 \text{ W}$$

11.22

Find the rms value of the signal below.

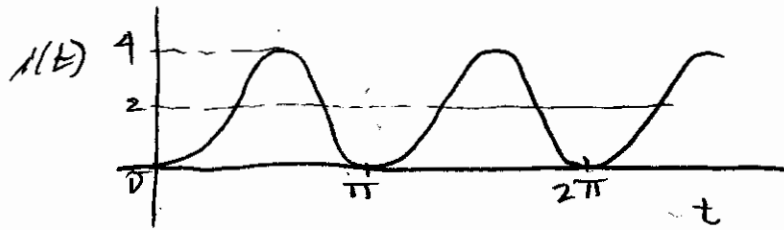

$$i(t) = 2 - 2\cos 2t$$

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (2 - 2\cos 2t)^2 dt}$$

$$(2 - 2\cos 2t)^2 = 4 - 8\cos 2t + 4\cos^2 2t$$

$$4 - 8\cos 2t + 4\cos^2 2t = 4 - 8\cos 2t + \frac{4}{2}(1 + \cos 4t)$$

So,

$$\begin{aligned} (2 - 2\cos 2t)^2 &= 4 - 8\cos 2t + 2 + 2\cos 4t \\ &= 6 - 8\cos 2t + 2\cos 4t \end{aligned}$$


$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (6 - 8\cos 2t + 2\cos 4t) dt}$$

Reduces to (because of integrating the cosine)

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} 6 dt} = \sqrt{\frac{1}{\pi} 6\pi} = \sqrt{6}$$

$$I_{rms} = 2.449 \text{ A}$$

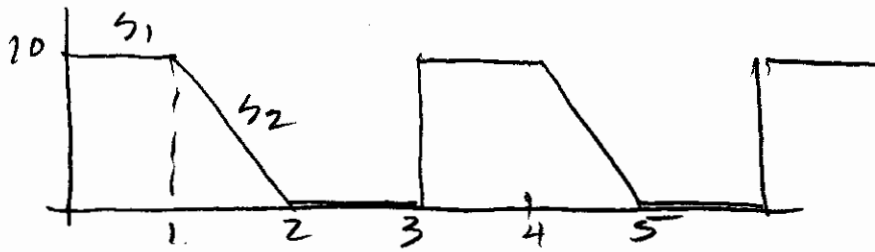11.33 Find the rms of the following signal.



$$s_1 = 10; \quad s_1^2 = 100$$

$$s_2 = -10(t-2); \quad s_2^2 = 100t^2 - 400t + 400$$

$$I_{rms} = \sqrt{\frac{1}{3} \left[\int_0^1 100 dt + \int_1^2 (100t^2 - 400t + 400) dt \right]}$$

$$I_{rms} = \sqrt{\frac{1}{3} \left[\left. 100 + \frac{100t^3}{3} \right|_1^2 - \left. 200t^2 \right|_1^2 + \left. 400t \right|_1^2 \right]}$$

$$= \sqrt{\frac{1}{3} \left[100 + \frac{800}{3} - \frac{100}{3} - 800 + 200 + 400 \right]}$$

$$= \sqrt{\frac{1}{3} \left[\frac{700}{3} - 100 \right]}$$

$$I_{rms} = 6.67 \text{ A}$$


11.49

Find the complex power of the following cases.

(a) $P = 4000 \text{ W}$, P.F. = .86 lagging

$$\cos \theta = .86$$

$$\theta = 30.68^\circ$$

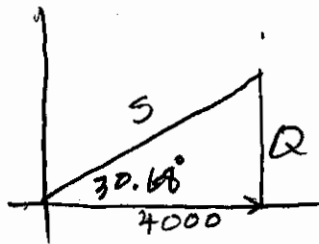


$$\tan 30.68 = \frac{Q}{4000}$$

$$Q = 2373 \text{ VARs}$$

$$\therefore \underline{S} = (4000 + j2373) \text{ KVA}$$

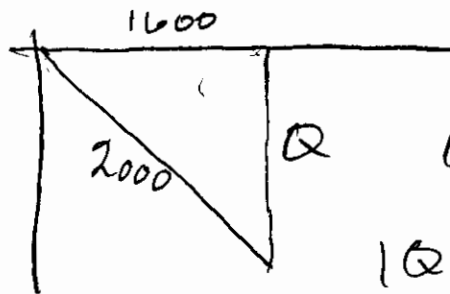(b) $S = 2 \text{ KVA}$ $P = 1.6 \text{ KW}$ (capacitive)



$$Q^2 = 2000^2 - 1600^2$$

$$|Q| = \sqrt{2000^2 - 1600^2}$$

$$= 1200$$

$$\underline{S} = 1600 - j1200 \text{ KVA}$$

11.49

$$(c) \hat{V}_{rms} = 208 \angle 20^\circ \text{ V}$$

$$\hat{I}_{rms} = 6.5 \angle -50^\circ \text{ A}$$

$$\hat{S} = \hat{V}_{rms} \hat{I}_{rms}^*$$

$$\hat{S} = 208 \times 6.5 \angle 70^\circ$$

$$\hat{S} = 1352 \angle 70^\circ$$

$$\hat{S} = 462.4 + j 1270$$

$$\hat{S} = (0.464 + j1.27) \text{ kVA}$$

$$(d) \hat{V}_{rms} = 120 \angle 30^\circ ; \hat{Z} = 40 + j60$$

$$\hat{S} = \frac{|\hat{V}_{rms}|^2}{\hat{Z}^*} = \frac{120^2}{40 - j60}$$

$$\hat{S} = (0.1107 + j0.1662) \text{ kVA}$$

OR

$$\hat{S} = (110.7 + j166.2) \text{ VA}$$

11.51 continued

2

$$(b) P_{\text{source}} = \frac{16 \times 1.95 \cos(45 - 39.62)}{2}$$

$$P_{\text{source}} = 15.53 \text{ W}$$

(c) Q

$$Q = \frac{16 \times 1.95 \sin(45 - 39.62)}{2}$$

$$Q = 1.46 \text{ VARs}$$

(d)

$$S = \frac{16 \times 1.95}{2}$$


$$S = 15.6 \text{ VA}$$

$$(e) \vec{S} = P + jQ$$

$$\vec{S} = (15.53 + j1.46) \text{ VA}$$

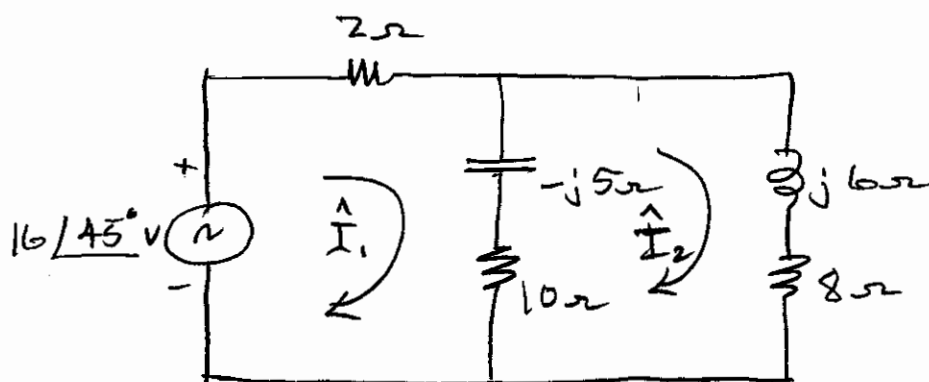11.51

- For the entire circuit calculate
- power factor
 - average power delivered by the source
 - the reactive power
 - the apparent power
 - the complex power



$$\begin{bmatrix} 12 - j5 & -10 + j5 \\ -10 + j5 & 18 + j \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 16 \angle 45 \\ 0 \end{bmatrix}$$


$$\hat{I}_1 = 1.505 + j1.246 = 1.95 \angle 39.62^\circ$$

$$\hat{I}_2 = 1.21 \angle 9.89^\circ \text{ A}$$


$$(a) \hat{V} = 16 \angle 45; \hat{I}_1 = 1.95 \angle 39.62$$

$$\text{pf} = \cos(45 - 39.62) = 0.9956 \text{ lagging}$$

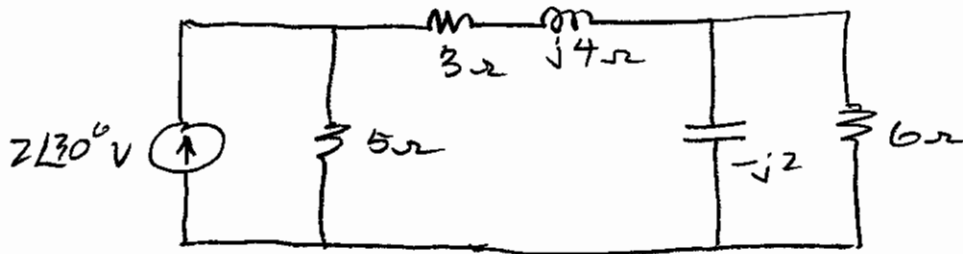15.56 FIND the complex power delivered by the current source in the following circuit.



Reduces to

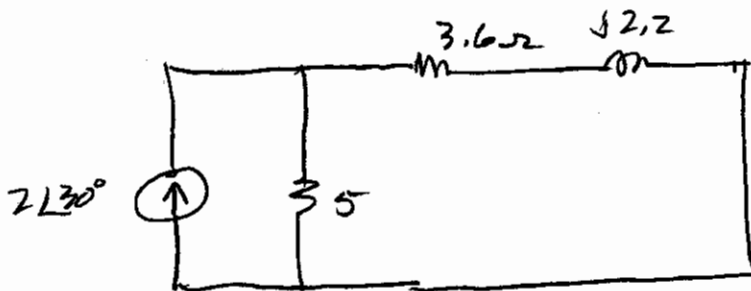

$$Z = 5 \parallel (3.6 + j2.2)$$

$$Z = 2.376 \angle 17.08^\circ$$

$$\hat{S} = \frac{1}{2} \hat{V} \hat{I}^*$$


$$\hat{V} = Z \hat{I}$$

$$\hat{S} = \frac{1}{2} |\hat{I}|^2 Z = \frac{1}{2} (2)^2 \times 2.376 \angle 17.08^\circ \text{ VA}$$

$$\hat{S} = 4.54 + j1.396 \text{ VA}$$

11.60 (See text for problem) Find V_o and P.f.


LOAD 1

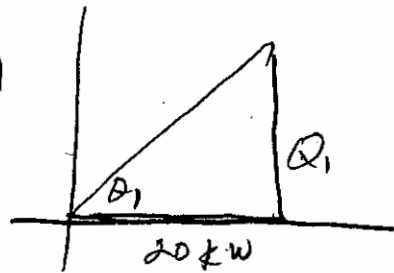

$$\cos \theta = .8$$
$$\theta_1 = 36.87^\circ$$

$$Q_1 = 20 \text{ kW} \tan 36.87 = 15 \text{ kVARs}$$

LOAD 2

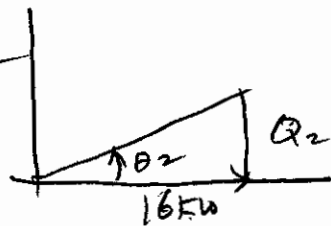

$$\cos \theta_2 = .9$$
$$\theta_2 = 25.84^\circ$$

$$Q_2 = 16 \text{ kW} \tan 25.84 = 7.75 \text{ kVARs}$$

$$S_{\text{TOTAL}} = (20 + 16) \text{ kW} + j(15 + 7.75) \text{ kVARs}$$

$$S_{\text{TOTAL}} = (36 + j22.75) \text{ VA}$$

$$S = I_{\text{rms}}^2 Z$$


$$Z = \frac{(36 + j22.75) \text{ K}}{6^2} = (1 + j0.632) \text{ K}\Omega$$

$$Z = 1000 + j632 \Omega$$

$$V_o = I Z = 6 (1000 + j632) = 7.098 \angle 32.3^\circ \text{ V}$$


$$\text{P.f.} = \cos(\theta_v - \theta_i) = \cos(32.3) = 0.845 \text{ lagging}$$

11.74 Given

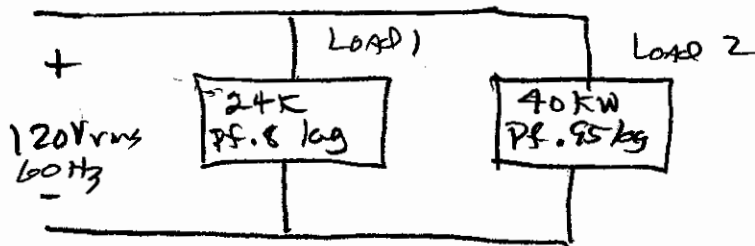


- (a) Find the power factor of the combined load
 (b) What C placed in parallel with the load to change the pf to 1?

(a)

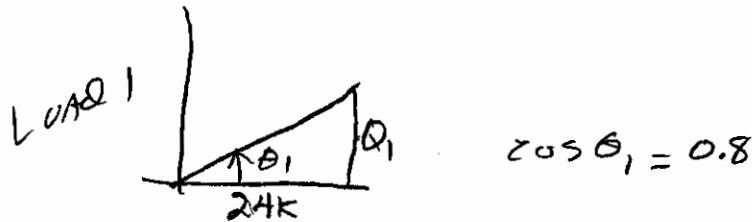
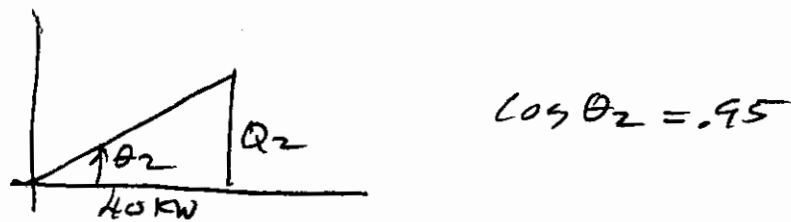
$$Q_1 = 24K \tan(\cos^{-1} 0.8) = 18 \text{ KVA}$$



$$Q_2 = 40K \tan(\cos^{-1} 0.95) = 13.15 \text{ KVA}$$

$$\hat{S}_{\text{TOTAL}} = (40 + 24)K + j(18 + 13.15)K$$

$$\hat{S}_{\text{TOTAL}} = (64 + j31.15) \text{ KVA} = 71.18 \angle 25.95^\circ$$

$$\text{PF} = \cos^{-1}(25.95) = 0.899 \text{ lagging}$$

(b)

$$\hat{Z} = \frac{V_{\text{rms}}^2}{\hat{S}} = -j31.15 = \frac{120^2}{j/\omega C} = -j \frac{120^2 \omega C}{1}$$

$$C = \frac{31.15 \times 10^3}{120^2 \times 377} = 5.74 \text{ mF}$$