

Due: April 20, 2006  
wlg

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

13.7  $V_o = 540.5 \angle 144.2^\circ \text{ mV}$

13.18  
 $Z_{TH} = (2.215 + j29.12) \Omega$


$V_{TH} = 61.37 \angle -46.2^\circ \text{ V}$

13.26  
 $I_o = 3.755 \angle -36.34^\circ \text{ A}$

$I_o = 3.755 \angle 143.66^\circ \text{ A}$


13.35  $I_1 = 1.48 \angle -21.4^\circ \text{ A}; I_2 = 0.0775 \angle -134.85^\circ \text{ A}; I_3 = 0.77 \angle -110.41^\circ \text{ A}$

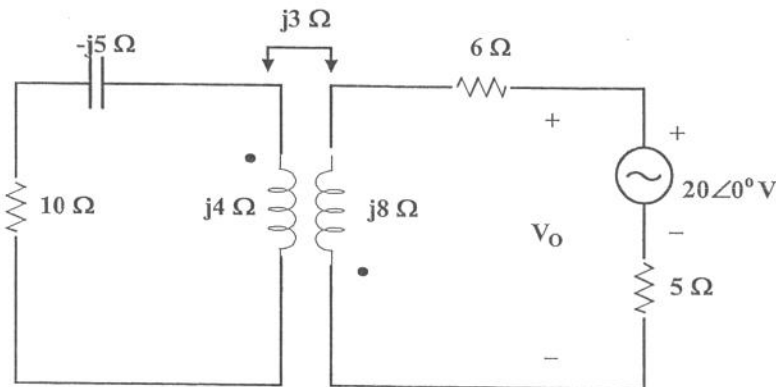13.xx Extra credit (10 points). Find  $V_o$



13.7

Given, Find  $V_0$

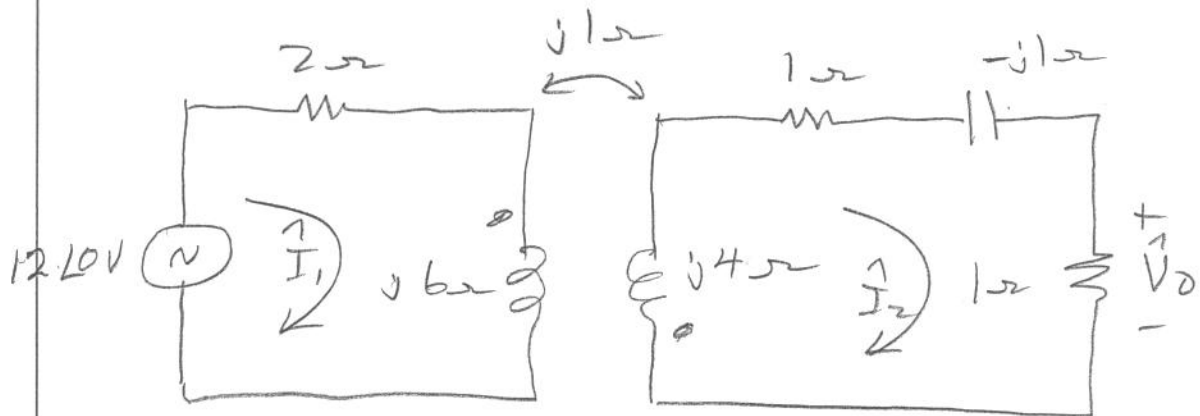

Assume currents as shown:

Mesh 1

$$(2 + j6)I_1 + j1I_2 = 12\angle 0$$

Mesh 2

$$-j1I_1 + (2 + j3)I_2 = 0$$


$$\begin{bmatrix} 2 + j6 & j1 \\ j1 & 2 + j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12\angle 0 \\ 0 \end{bmatrix}$$

$$I_1 = 0.685 - j1.83 \text{ A}$$

$$I_2 = -0.438 + j0.316 = 0.541 \angle 144.16^\circ \text{ A}$$

$$\therefore V_0 = 0.541 \angle 144.16^\circ \text{ V}$$

13.18

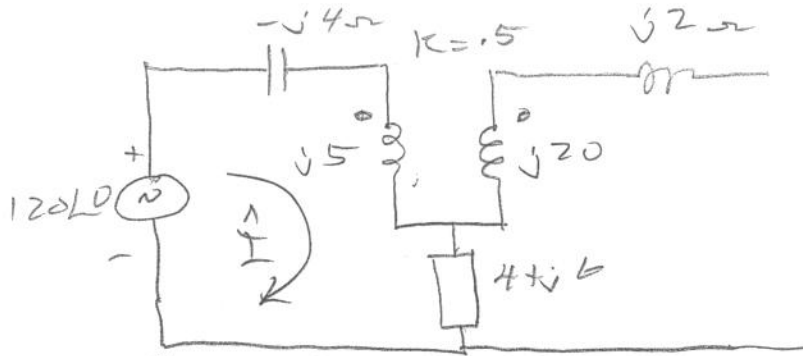

Transform to a T:

$$L_a = L_1 - M \quad L_b = L_2 - M \quad L_c = M$$


inducting  $k = \frac{M}{\sqrt{L_1 L_2}}$

$$0.5 = \frac{M}{\sqrt{5 \cdot 20}}$$

$$M = 5$$

$$j\omega L_a = j\omega L_1 - j\omega M = j\omega 5 - j\omega 5 = 0$$
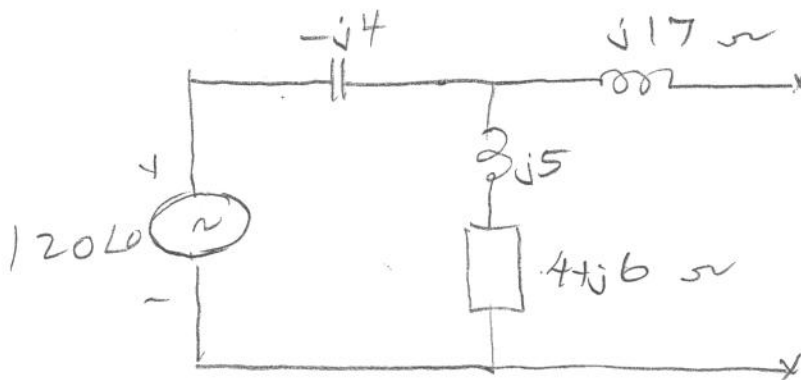
$$j\omega L_b = j\omega 20 - j\omega 5 = j\omega 15$$



$$V_{TH} = \frac{120 \times (4 + j11)}{(4 + j7)} = 174.21 \angle 9.76^\circ \text{ V}$$

13.18 cont.

work by straight circuit theory

$$(-j4 + j5 + 4 + j6) \overset{?}{I} = 120 \angle 0$$


$$\overset{?}{I} = \frac{120 \angle 0}{4 + j7}$$

$$V_{TH} = (j5 + 4 + j6) \overset{?}{I}$$

$$V_{TH} = \frac{(4 + j11) \times 120 \angle 0}{(4 + j7)}$$

same answer.

To find  $Z_{Th}$

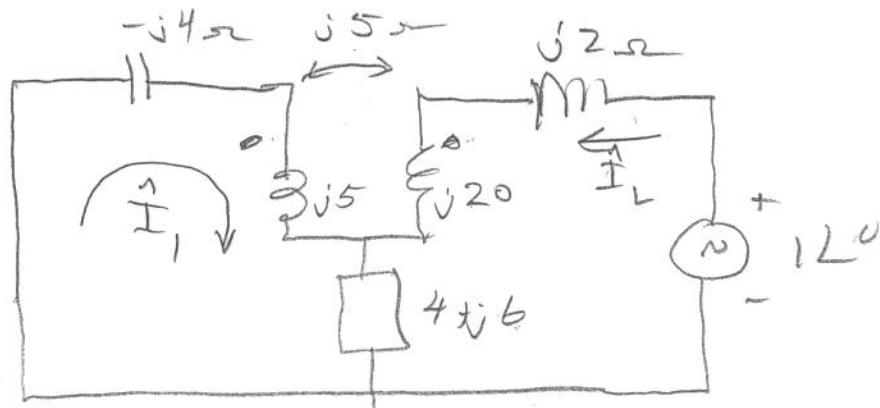

Find  $\overset{?}{I}_L$ : Then  $Z_{TH} = \frac{120}{\overset{?}{I}_L}$

$$(-j4 + j5 + 4 + j6) \overset{?}{I}_1 + j5 \overset{?}{I}_L + (4 + j6) \overset{?}{I}_L = 0$$

$$(4 + j7) \overset{?}{I}_1 + (4 + j11) \overset{?}{I}_L = 0$$

13.18 cont

4x2nd mesh

$$(j5 + 4 + j6) I_1 + (j2 + j20 + 4 + j6) I_2 = 1 \angle 0^\circ$$

$$(4 + j11) I_1 + (4 + j28) I_2 = 1$$

so


$$\begin{bmatrix} 4 + j7 & 4 + j11 \\ 4 + j11 & 4 + j28 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$I_2 = 0.0883 \angle -85^\circ$$

∴

$$Z = \frac{1}{I_2} = 11.32 \angle 85^\circ \Omega$$

Now use the equivalent T circuit.

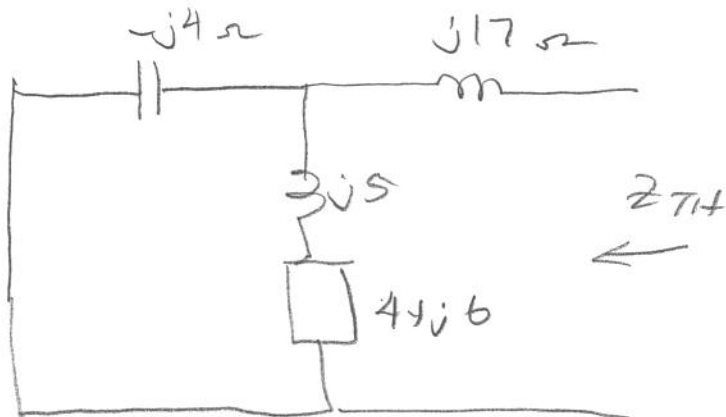

$$Z_{TH} = j17 + \frac{(4 \angle -90^\circ)(4 + j11)}{(4 + j7)}$$

$$Z_{TH} = 11.32 \angle 85.0^\circ \Omega$$


checks with other methods.

conclusion:


$$V_{TH} = 174.21 \angle 9.76^\circ \text{ V}$$

$$Z_{TH} = 11.32 \angle 85^\circ \Omega$$

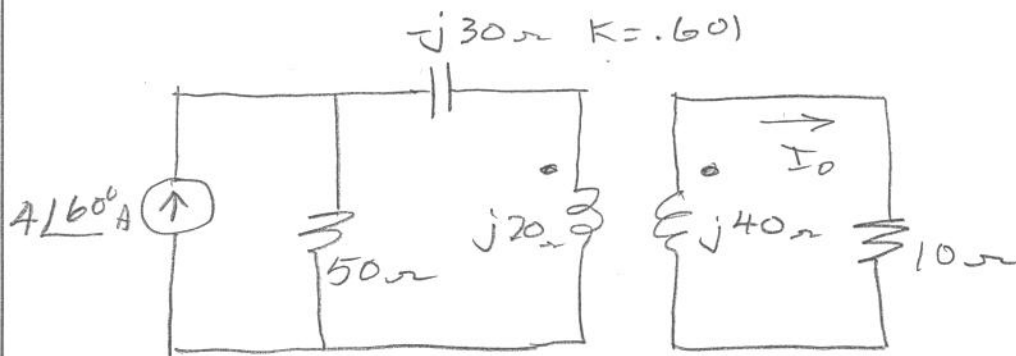13.26 Find  $I_o$  in the circuit. Switch the dot on the winding on the right and find  $I_o$  again.


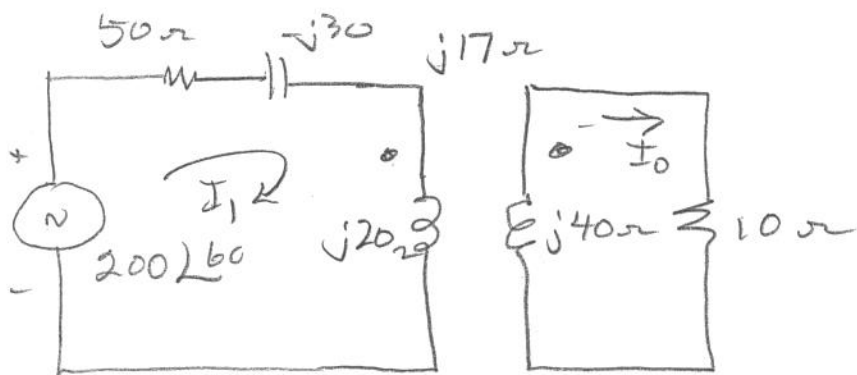
$$0.60 = \frac{WM}{\sqrt{20 \times 40}} ; WM = 16.97$$



$$(50 - j30 + j20)I_1 - j17I_0 = 200\angle 60$$

$$(50 - j20)I_1 - j17I_0 = 200\angle 60$$

$$= j17I_1 + (10 + j40)I_0 = 0$$

$$I_0 = 1.416 \angle 101.44 \text{ A}$$

13.26

Reverse the dot on the right

You get


$$(50 - j20)I_1 + j17I_0 = 200 \angle 60^\circ$$

$$j17I_1 + (10 + j40)I_0 = 0$$

$$I_0 = 1.416 \angle -78.56^\circ \text{ A}$$



13,35

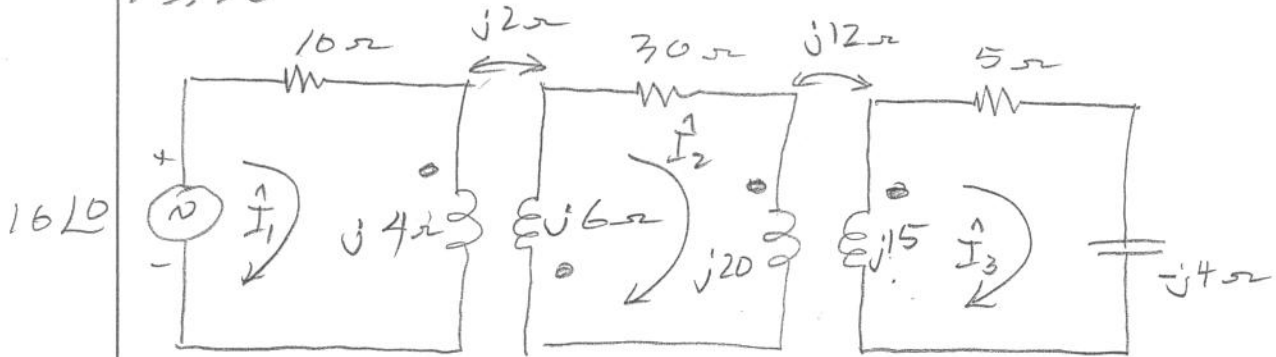

$$(10 + j4)I_1 + j2I_2 + 0I_3 = 16\angle 0$$

$$j2I_1 + (30 + j26)I_2 - j12I_3 = 0$$

$$0I_1 - j12I_2 + (5 + j11)I_3 = 0$$

$$I_1 = 1.374 - j0.5385$$

$$I_2 = -0.0547 - j0.0549$$

$$I_3 = -0.0268 - j0.0721 = 0.077 \angle -110.4^\circ \text{ A}$$