

Solutions to Exam #1

Test A

ECE 300

Spring Semester, 2006


**University of Tennessee, Knoxville, TN
ECE Department**

Test A

WPA

- (1) You are given the circuit of Figure 1.
 (a) Find V_{eb} .
 (b) Find the power supplied by the 15 V source.

15%

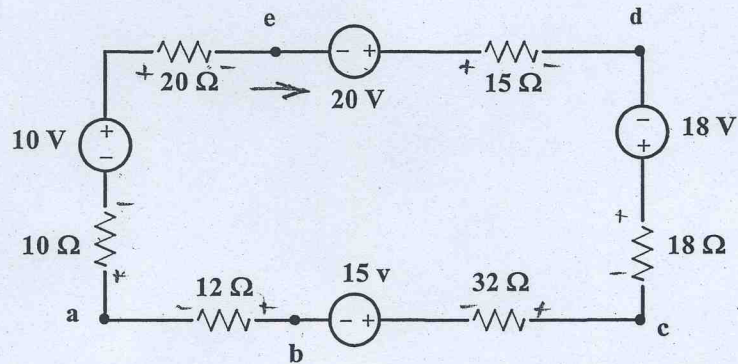

Assume I as shown. Use default sign convention. Start from "a".

(a)

$$10I - 10 + 20I - 20 + 15I - 18 + 18I + 32I + 15 + 12I = 0$$

$$107I = 33$$

$$I = \frac{33}{107} = 0.308 \text{ A}$$

$$-V_{eb} - 20I + 10 - 10I - 12I = 0$$

$$V_{eb} = -42I + 10 =$$

$$V_{eb} = -2.94 \text{ V}$$

(b)


$$P_{sup} = -15 \times I = -4.62 \text{ W}$$

(being charged)

A

(2) You are given the circuit shown in Figure 2. Find the voltage V_s .

15%

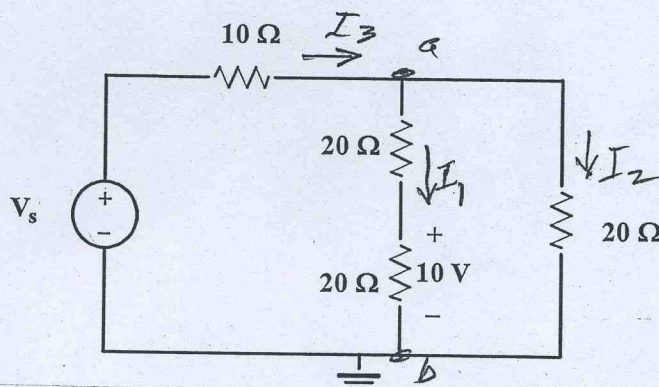

From the diagram, using Ohm's law

$$I_1 = \frac{10}{20} = 0.5 \text{ A}$$

$$V_{ab} = 40 I_1 = 20 \text{ V}$$

$$I_2 = \frac{20}{20} = 1 \text{ A}$$

$$I_3 = I_1 + I_2 = 1.5 \text{ A}$$

$$V_s = 10 I_3 + 20$$

$$V_s = 35 \text{ V}$$


~~##~~

1-33

A

(3) You are given the circuit of Figure 3. Find the resistance R_{eq} .

15%

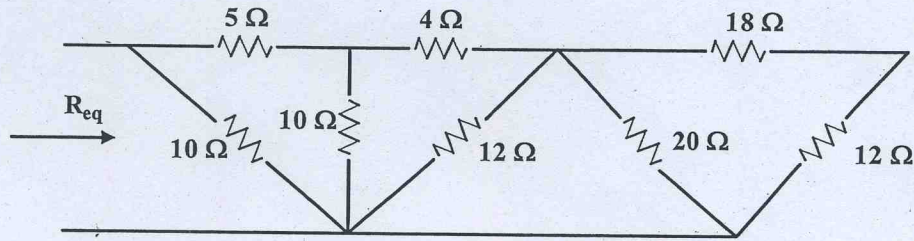

At the right side we have
 30Ω in parallel with 20Ω

$$\frac{30 \times 20}{30 + 20} = 12\Omega$$

Then we have 12Ω in parallel with
 12Ω , giving

$$\frac{12 \times 12}{12 + 12} = 6\Omega$$

Then we have 6Ω in series with
 4Ω , giving $6 + 4 = 10\Omega$

Then we have 10Ω in parallel with
 10Ω , giving

$$\frac{10 \times 10}{10 + 10} = 5\Omega$$


Then we have 5Ω in series with 5Ω
giving $5 + 5 = 10\Omega$

Then we have 10Ω in parallel with
 10Ω giving $R_{eq} = 5\Omega$

A

(4) You are given the circuit of Figure 4. Find the gain v_o/v_s .

15%

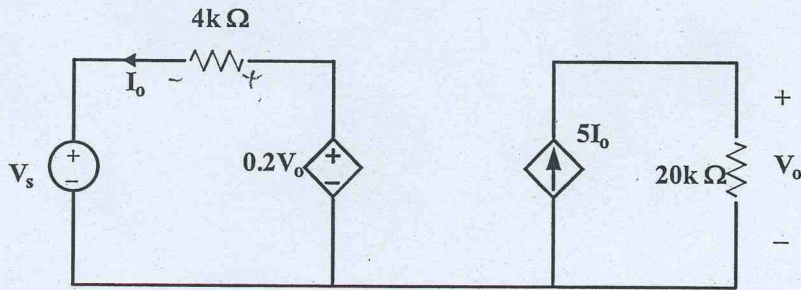

$$V_o = (20k)(5I_o) \quad (\#1) \quad (\text{at the right side})$$

On the left;

$$-V_s - 4kI_o + 0.2V_o = 0$$

$$\text{so } 4kI_o = 0.2V_o - V_s$$

$$I_o = \frac{0.2V_o - V_s}{4k} \quad (\#2)$$

Substitute (#2) into (#1)

$$V_o = 20k \times 5 \left[\frac{0.2V_o - V_s}{4k} \right] = 25 [0.2V_o - V_s]$$

$$V_o = 15V_o - 25V_s$$


$$-4V_o = -25V_s$$

$$\frac{V_o}{V_s} = 6.25$$


A

(5) You are given the circuit of Figure 5. Use mesh analysis to find the current I_o .

20%

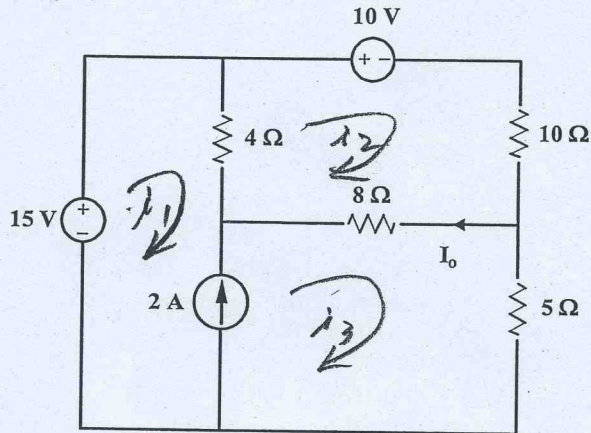

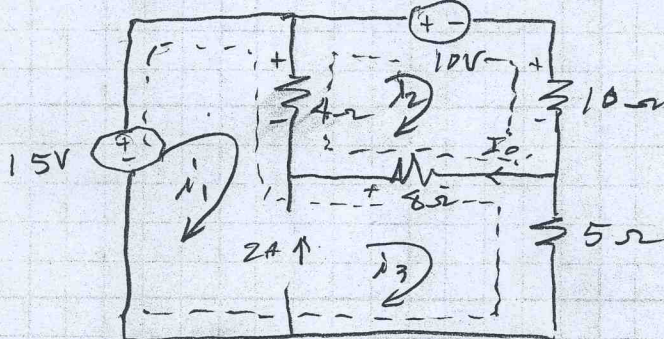Assign mesh currents as shown above. Redraw the circuit with the current inactive, as such.



Write the two mesh equations:

$$-15 + 4(i_1 - i_2) + 8(i_3 - i_2) + 5i_3 = 0$$

OR

$$4i_1 - 12i_2 + 13i_3 = 15 \quad (\#1)$$

AROUND MESH 2

$$-4(i_1 - i_2) + 10 + 10i_2 - 8(i_3 - i_2) = 0$$

$$-4i_1 + 22i_2 - 8i_3 = -10 \quad (\#2)$$

CONSTRAINT Equation:

$$i_3 - i_1 = 2$$

$$-i_1 + 0i_2 + i_3 = 2 \quad (\#3)$$

A

#5 (continued)

2

FROM (#1), (#2) (#3)

$$\begin{bmatrix} 4 & -12 & 13 \\ -4 & 22 & -8 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 15 \\ -10 \\ 2 \end{bmatrix}$$

$$i_1 = -0.739 \text{ A}, \quad i_2 = -0.130 \text{ A}, \quad i_3 = 1.26 \text{ A}$$


$$I_0 = i_2 - i_3$$

$$I_0 = -0.13 - 1.26$$

$$I_0 = -1.39 \text{ A}$$

5

Nodal Analysis

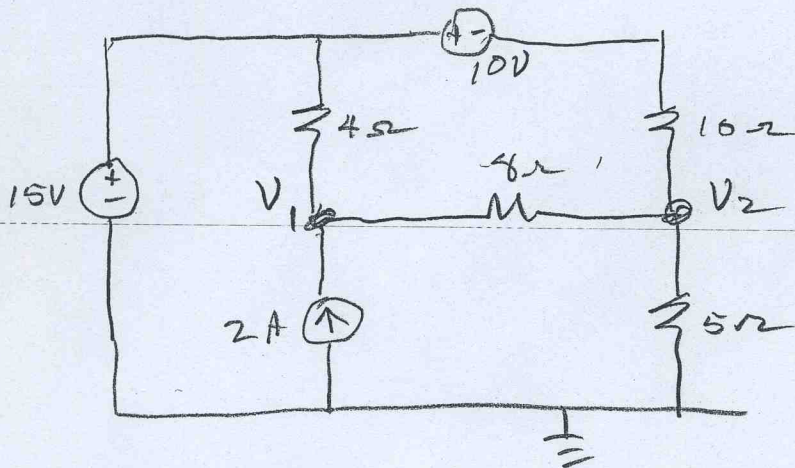At V_1

$$\frac{V_1 - 15}{4} + \frac{V_1 - V_2}{8} - 2 = 0$$

$$2V_1 - 30 + V_1 - V_2 = 16$$

$$3V_1 - V_2 = 46$$

At V_2

$$\frac{V_2 - V_1}{8} + \frac{V_2 + 10 - 15}{10} + \frac{V_2}{5} = 0$$

x 40

$$5V_2 - 5V_1 + 4V_2 - 20 + 8V_2 = 0$$

$$-5V_1 + 17V_2 = 20$$

$$V_1 = 17.43V, \quad V_2 = 6.3V$$

$$I_0 = \frac{V_2 - V_1}{8} = \frac{6.3 - 17.43}{8} = -1.39A$$


check

✓

A

(6) You are given the circuit of Figure 6. Use nodal analysis to find v_1 and v_2 .

20%

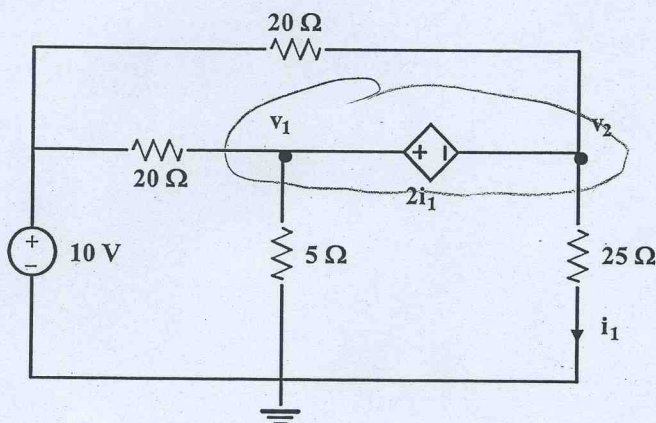

A supernode is present as shown:
we have;

$$\frac{v_1 - 10}{20} + \frac{v_1}{5} + \frac{v_2 - 10}{20} + \frac{v_2}{25} = 0$$

$$.05v_1 - 0.5 + .2v_1 + .05v_2 - 0.5 + 0.04v_2 = 0$$

$$\boxed{.25v_1 + 0.09v_2 = 1}$$

constraint

$$v_1 - 2i_1 - v_2 = 0$$

$$i_1 = \frac{v_2}{25} = .04v_2$$

$$v_1 - .08v_2 - v_2 = 0$$


$$\boxed{v_1 - 1.08v_2 = 0}$$

$$\boxed{v_1 = 2v_1} \quad \boxed{v_2 = 2.78V}$$

Test (A)
#6

Mesh Analysis

For checking

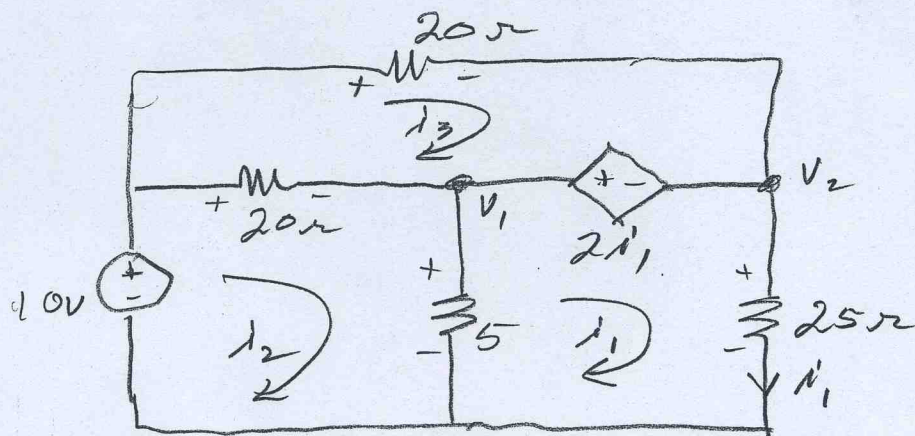

$$-10 + 20(i_2 - i_3) + 5(i_2 - i_1) = 0$$

$$-5i_1 + 25i_2 - 20i_3 = 10$$

$$-5(i_2 - i_1) + 2i_1 + 25i_1 = 0$$

$$32i_1 - 5i_2 + 20i_3 = 0$$

$$-20(i_2 - i_3) + 20i_3 - 2i_1 = 0$$

$$-2i_1 - 20i_2 + 40i_3 = 0$$

$$\begin{bmatrix} -5 & 25 & -20 \\ 32 & -5 & 0 \\ -2 & -20 & 40 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$i_1 = 0.111 \quad i_2 = 0.711, \quad i_3 = 0.361$$

$$V_2 = 25i_1 = 2.78 \text{ V check}$$

$$V_1 = (i_2 - i_1)5 = 3 \text{ V check}$$