

Desk Copy

Desk Copy

ECE 300  
Spring Semester, 2006  
Test #2

wlg Exam A

Name wlg  
Print (last, first)

Work the exam on the space provided below the problem. Work on one side of your paper only. Problems 1 through 4 count 20% each. Problem 5 counts 10%. Take home problem counts 10%.

(1) Find the output voltage,  $V_o$ , for the opamp circuit shown in Figure 1.

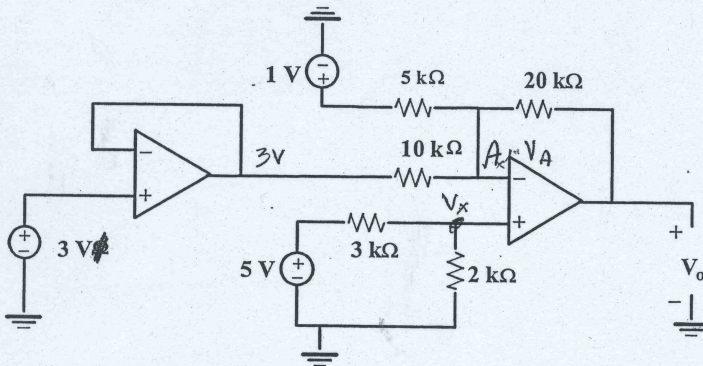


Figure 1: Circuit for problem 1.

$$V_x = \frac{5 \times 2K}{3K + 2K} = 2V \quad ; \quad \text{At } A, \quad V_A = V_x = 2V$$

At A:

$$\frac{2-3}{10K} + \frac{2-1}{5K} + \frac{2-V_o}{20K} = 0$$

$$-\cancel{2} + 4 + \cancel{2} - V_o = 0$$

$$V_o = 4V$$

- (2) You are given the circuit shown in Figure 2.
- Find the Thevenin equivalent circuit, with respect to terminals a-b. Hint: If mesh doesn't work try nodal.
  - Draw the Thevenin equivalent circuit: include  $V_{TH}$  and  $R_{TH}$ .
  - What resistor placed between terminals a-b will give maximum power Transfer to this resistor? Determine the value of this power.

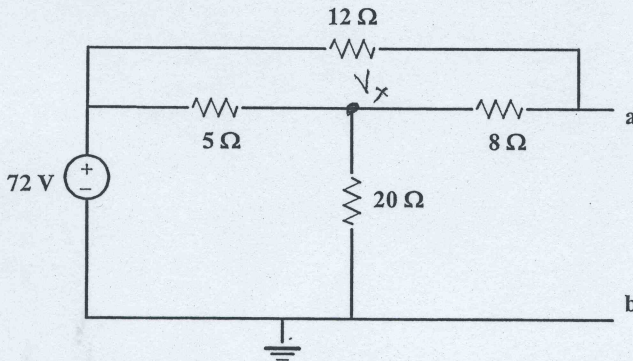


Figure 2: Circuit for problem 2.

1a)

At  $V_x$

$$\frac{V_x - 72}{5} + \frac{V_x}{20} + \frac{V_x - V_{ab}}{8} = 0$$

$$8V_x - 576 + 2V_x + 5V_x - 5V_{ab} = 0$$

$$15V_x - 5V_{ab} = 576$$

At a

$$\frac{V_{ab} - V_x}{8} + \frac{V_{ab} - 72}{12} = 0$$

$$12V_{ab} - 12V_x + 8V_{ab} - 576 = 0$$

$$-12V_x + 20V_{ab} = 576$$


$$\begin{bmatrix} 15 & -5 \\ -12 & 20 \end{bmatrix} \begin{bmatrix} V_x \\ V_{ab} \end{bmatrix} = \begin{bmatrix} 576 \\ 576 \end{bmatrix}$$

$$V_x = 60V$$

$$V_{ab} = V_{TH} = 64.8V$$

Thevenin voltage


(2) cont. FOR  $R_{TH}$

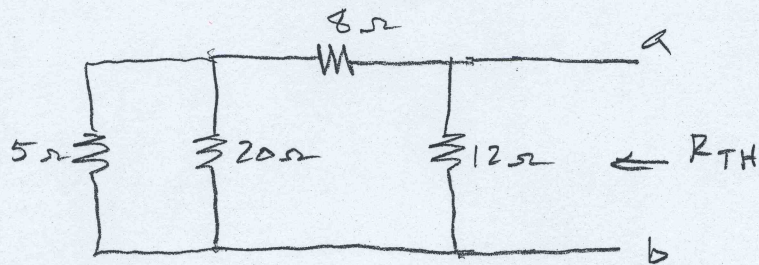

$$5 \parallel 20 = 4 \Omega$$
$$R_{TH} = 6 \Omega$$


THEVENIN RESISTANCE

(b)

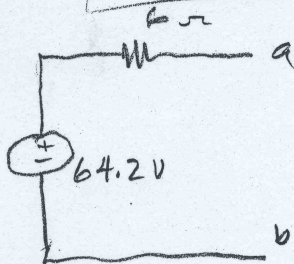

THEVENIN CIRCUIT

(c)

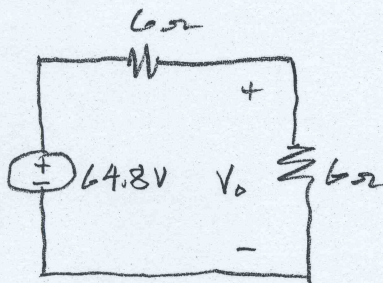

FOR MAXIMUM POWER TRANSFER.

$$P_o = \frac{V_o^2}{6}$$

$$V_o = 32.4$$

$$P_o = \frac{(32.4)^2}{6}$$

$$P_o = 175 \text{ W}$$

Output power

- (3) You are given the circuit of Figure 3.
- (a) Find the Norton equivalent circuit with respect to terminals a-b. You are required to find  $I_{NORTON}$  by actually finding the short circuit current.
- (b) Draw your Norton equivalent circuit showing the  $I_{NORTON}$ ,  $R_{TH}$  and terminals a-b.



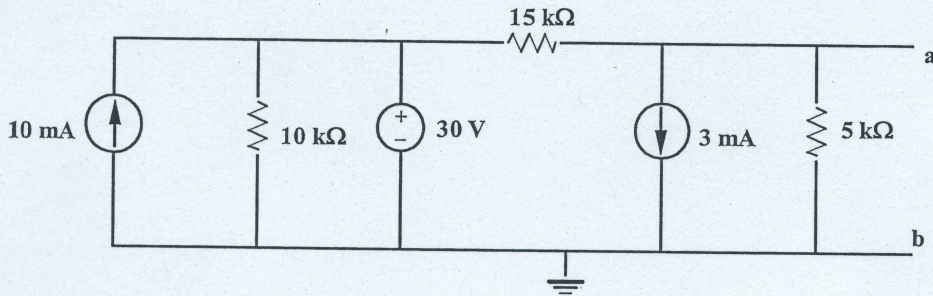


Figure 3: Circuit for problem 3.

(a) The circuit is the same as follows:

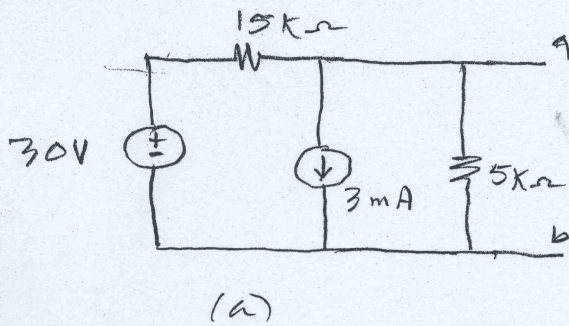

with output shorted


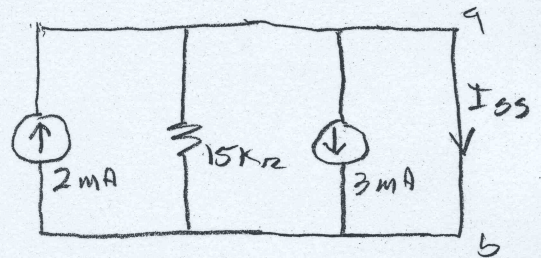


(b) shorting the output, shorts out the 5kΩ resistor

From (b);

$$I_{ss} = -1 \text{ mA}; \quad \text{From (a)}$$
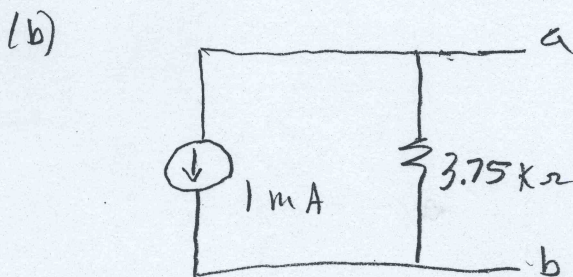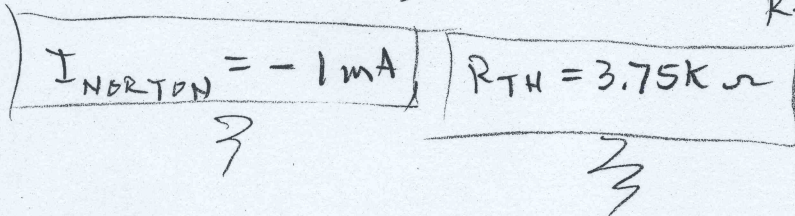
$$R_{TH} = \frac{(5K)(15K)}{5K + 15K} = 3.75K\Omega$$



Norton Circuit

A

- (4) You are given the circuit of Figure 4.  
 (a) Give the value of the Thevenin voltage seen looking into terminals a-b.  
 (b) Determine the resistance  $R_{TH}$  seen looking into terminals a-b.  
 (c) Draw your Thevenin equivalent circuit.

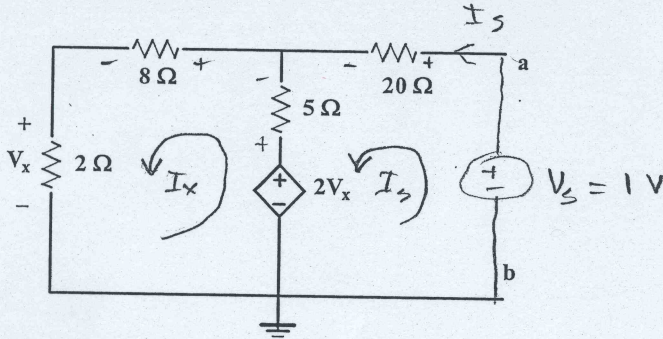


Figure 4: Circuit for problem 4.

(a) Since there are no independent sources,  $V_{TH} = 0$ .  
 (It is a dead circuit).

(b) Apply a source voltage of 1V at terminals a-b.  
 Determine  $I_s$  as shown;  $R_{TH} = \frac{V_s}{I_s} = \frac{1}{I_s}$

Writing mesh equations.

mesh  $I_x$

$$-2V_x + 5(I_x - I_s) + 10I_x = 0 \quad (1)$$

but  $V_x = 2I_x$  (2) substitute (2) into (1), clear

$$11I_x - 5I_s = 0 \quad (3)$$

mesh  $I_s$

$$-1 + 20I_s - 5(I_x - I_s) + 2V_x = 0 \quad (4)$$

Substitute (4) into (2), clear

$$-I_x + 25I_s = 1 \quad (5)$$

-5I\_x  
+4I\_s

(4) continued

From (3) and (5)


$$\begin{bmatrix} 11 & -5 \\ -1 & 25 \end{bmatrix} \begin{bmatrix} I_x \\ I_s \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$I_s = 0.04074$$

$$R_{TH} = \frac{V_s}{I_s} = \frac{1}{0.04074} = 24.5 \Omega$$

$$R_{TH} = 24.5 \Omega$$

(c)

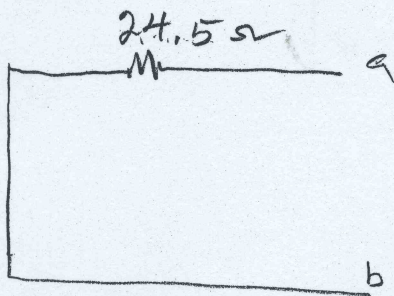

Thevenin  
Circuit

(5) Find the voltage across each capacitor in the circuit show in in Figure 5.

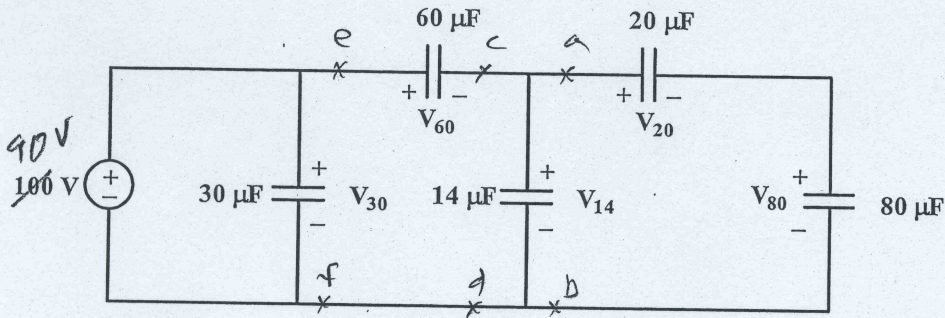


Figure 5: Circuit for problem 5.

To the right of a-b;  $C_{ab} = \frac{20 \times 80}{20 + 80} = 16 \mu F$

To the right of cd;  $C_{cd} = (14 + 16) \mu F = 30 \mu F$

To the right of e-f;  $C_{ef} = \frac{60 \times 30}{60 + 30} \mu F = 20 \mu F$

$$V_{30} = 90 V$$

$$V_{60} = \frac{90 \times 30}{30 + 60} = 30 V$$

$$V_{14} = 60 V \quad \text{KVL}$$

$$V_{20} = \frac{60 \times 80}{80 + 20} = 48 V$$

$$V_{80} = 12 V$$

$$\frac{100V}{V_{60}} = \frac{100 \times 30}{40} = 33.3 V$$

$$V_{14} = \frac{100 \times 60}{40} = 66.6 V$$

$$V_{20} = \frac{66.6 \times 80}{100} = 53.28 V$$

$$V_{80} = \frac{66.6 \times 20}{100} = 13.32 V$$