

Desk Copy

ECE 300
Spring Semester, 2007
HW Set #7

Due: March 22, 2007

wlg

Name _____

Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

7.24 (b) $i(t) = -10u(t) + 20u(t-3) - 10u(t-5)$ A; (d) $y(t) = 2u(-t) - 5u(t) + 5u(t-1)$

7.26 (a) $v_1(t) = u(t+1) - 2u(t) + u(t-1)$ V; (b) $v_2(t) = 2u(t-2) - r(t-2) + r(t-4)$ V

7.39 (a) @ $t=0$, $v(t) = 4V$; $v(t) = (20 - 16e^{-t/8})u(t)$ V; (b) at $t = 0$ $v(t) = 4V$;
 $v(t) = (12 - 8e^{-t/6})u(t)$ V

7.41 $v(t) = 10(1 - e^{-0.2t})u(t)$ V (make a hand sketch (approx.) for $v(t)$)

7.41XX Repeat problem 7.41 by programming in p-spice. Show your circuit diagram and your plot. Compare the computer plot with your sketch in 7.41.

7.46 $v(t) = 30(1 - e^{-t/2})u(t)$ V

7.59 $v_o(t) = 6e^{-4t}u(t)$ V

7.60 $v(t) = 16e^{-0.5t}u(t)$ V

7.69 $v(t) = 48(e^{-t/3000} - 1)u(t)$ V (make a hand sketch (approx.) for $v(t)$)

7.69XX Repeat problem 7.69 by programming in p-spice. Show your circuit diagram and your plot. Compare the computer plot with your sketch in 7.69. Use the uA741 op amp

Wley


ECE 300
HW # 7
Spring 2007

7.24

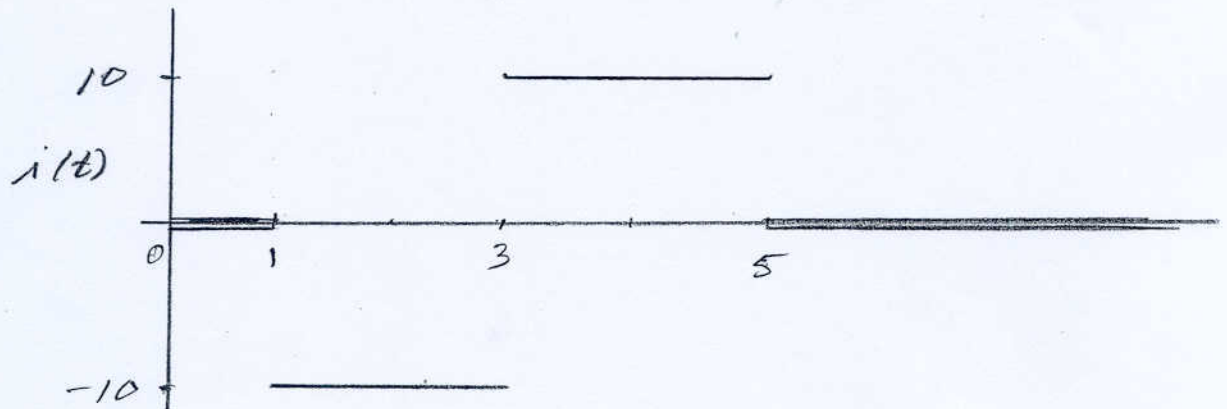(b) Express the following signals in terms of singularity functions.

(b)

$$i(t) = \begin{cases} 0, & t < 1 \\ -10 & 1 < t < 3 \\ 10 & 3 < t < 5 \\ 0 & t > 5 \end{cases}$$




By inspection:

$$i(t) = -10u(t-1) + 20u(t-3) - 10u(t-5)$$

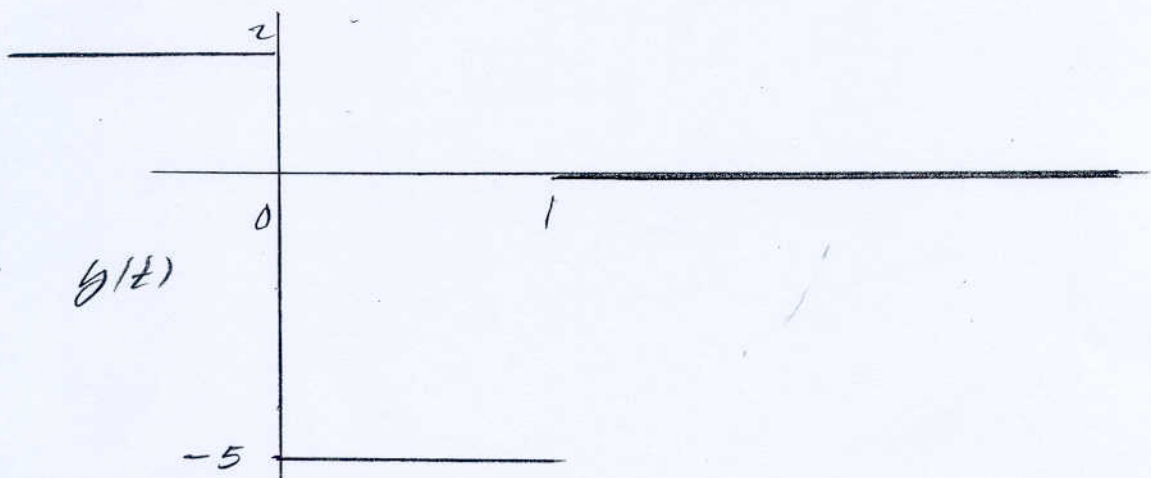7.24 continued

(d)

$$y(t) = \begin{cases} 2 & t < 0 \\ -5 & 0 < t < 1 \\ 0 & t > 1 \end{cases}$$




By inspection:

$$y(t) = 2u(-t) - 5[u(t) - u(t-1)]$$


(window)

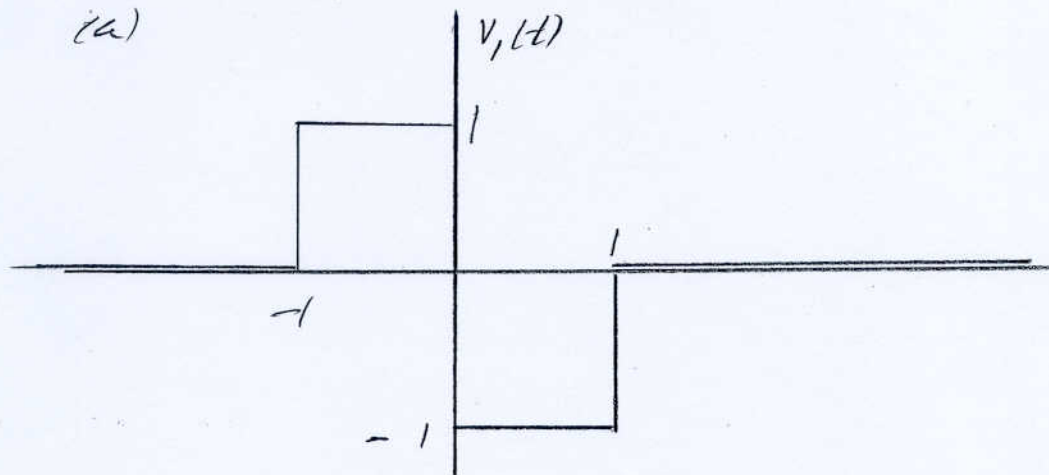7.26 Express the signals below in terms of singularity functions.



By inspection:

$$v_1(t) = u(t+1) - 2u(t) + u(t-1)$$

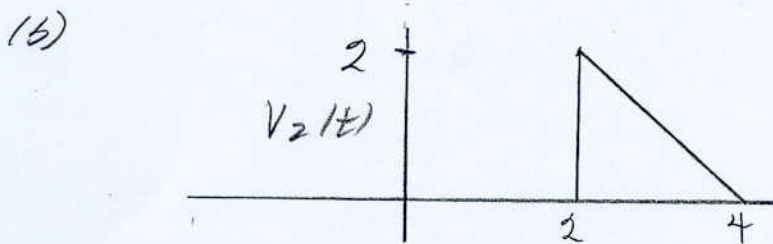


Use a gate function
 $u(t-2) - u(t-4)$

to window out the line that
falls on the above function.
see next page.

7.26 continued

2

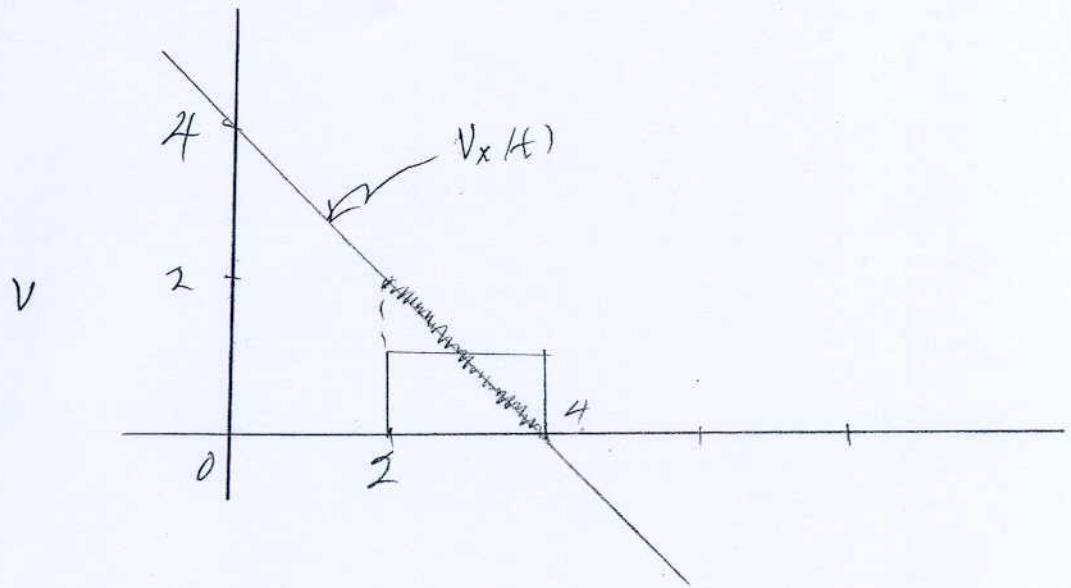

$$v_x(t) = 4 - t$$

$$v_2(t) = (4-t) [u(t-2) - u(t-4)]$$


$$= (4-t)u(t-2) + (t-4)u(t-4)$$

$$= (2-t+2)u(t-2) + (t-4)u(t-4)$$

$$= 2u(t-2) - (t-2)u(t-2) + (t-4)u(t-4)$$

$$v_2(t) = 2u(t-2) - r(t-2) + r(t-4)$$

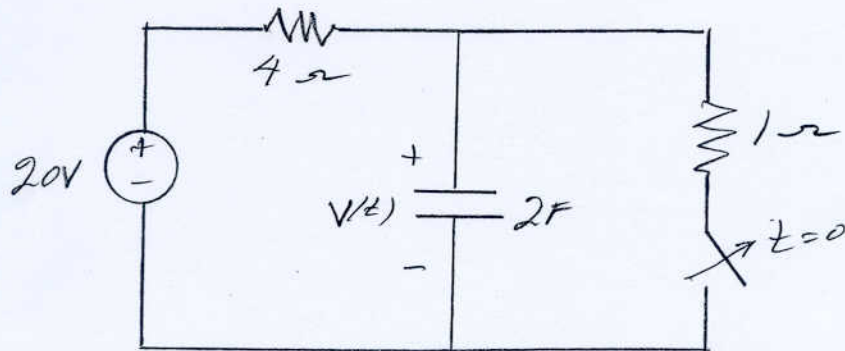7.39 Calculate the capacitor voltage for $t < 0$ and $t > 0$ for the following circuits.



For $t < 0$:

$$v(t) = \frac{20 \times 1}{1 + 4} = 4 \text{ V}$$

$$v(t) \Big|_{t=0^-} = v(t) \Big|_{t=0^+} = 4 \text{ V}$$

$$v(0^+) = 4 \text{ V}$$

$$\underline{v(\infty) = 20 \text{ V}}$$

$$\tau = RC = 2 \times 4 = 8$$


Use

$$v(t) = v(\infty) + (v(0^+) - v(\infty)) e^{-\frac{t}{\tau}}$$

$$v(t) = 20 + (4 - 20) e^{-\frac{t}{8}}$$

$$\underline{v(t) = [20 - 16e^{-\frac{t}{8}}] \text{ u(t)} \text{ V}}$$

7.39 (b)

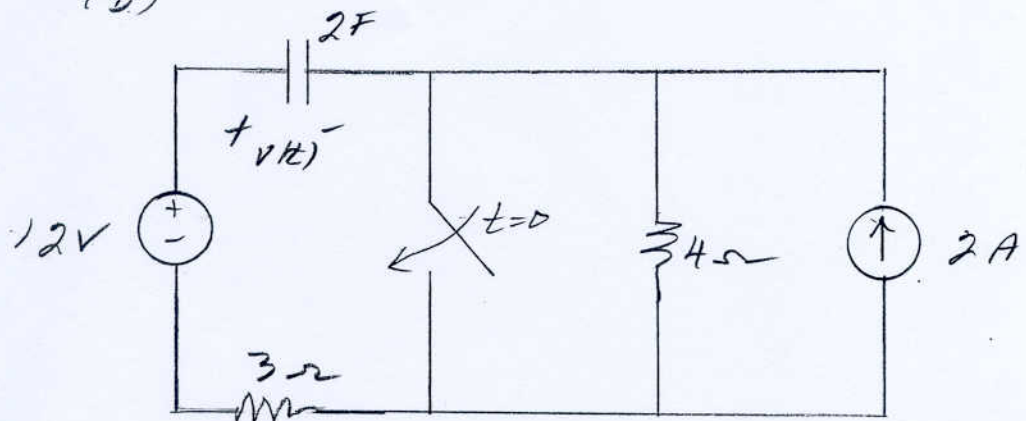


$t < 0$;

$$-12 + V(0^-) + 8 = 0$$

$$V(0^-) = V(0^+) = 4V$$

$t > 0$

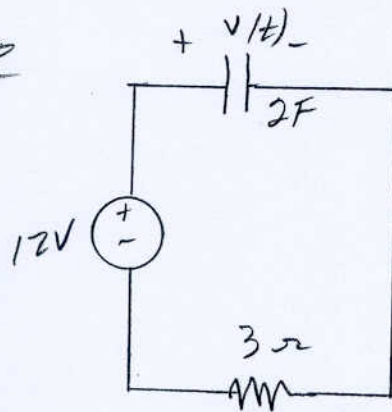

$$V(\infty) = 12V, \quad \tau = 6\text{ms}, \quad V(0^+) = 4$$

\therefore


$$V(t) = V(\infty) + [V(0^+) - V(\infty)]e^{-\frac{t}{\tau}}$$

$$V(t) = 12 + [4 - 12]e^{-\frac{t}{6}}$$

$$V(t) = [12 - 8e^{-\frac{t}{6}}]u(t) \text{ V}$$

7.41

For the circuit below find $v(t)$ for $t > 0$.

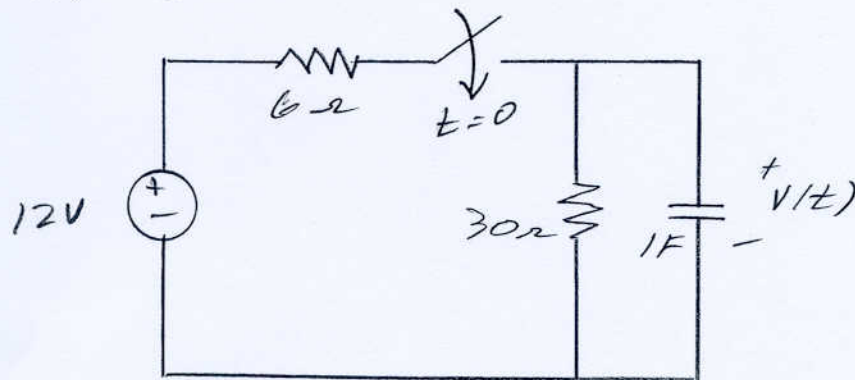 $t < 0$

$$v(0^-) = v(0^+) = 0 \text{ V}$$

 $t > 0$


$$v(\infty) = \frac{12 \times 30}{30 + 6} = 10 \text{ V}$$


$$R_{eq} = 30 \parallel 6 = \frac{6 \times 30}{36} = 5 \Omega$$

$$\tau = R_{eq} C = 5 \times 1 = 5 \text{ sec}$$


$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-\frac{t}{\tau}}$$

$$v(t) = 10 - 10 e^{-0.2t}$$

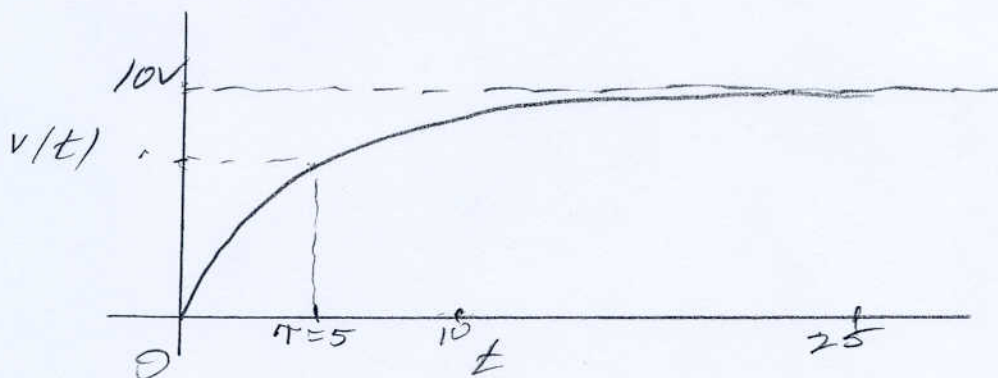

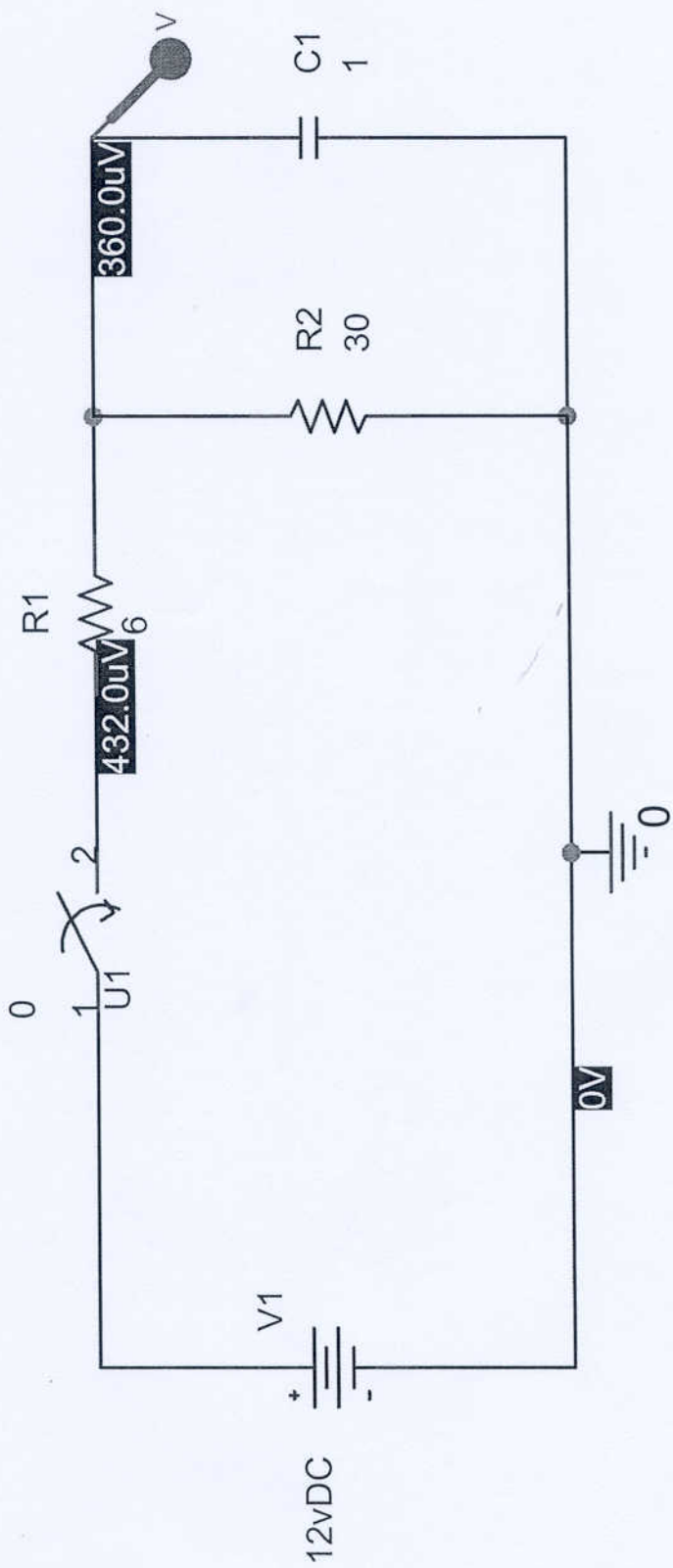


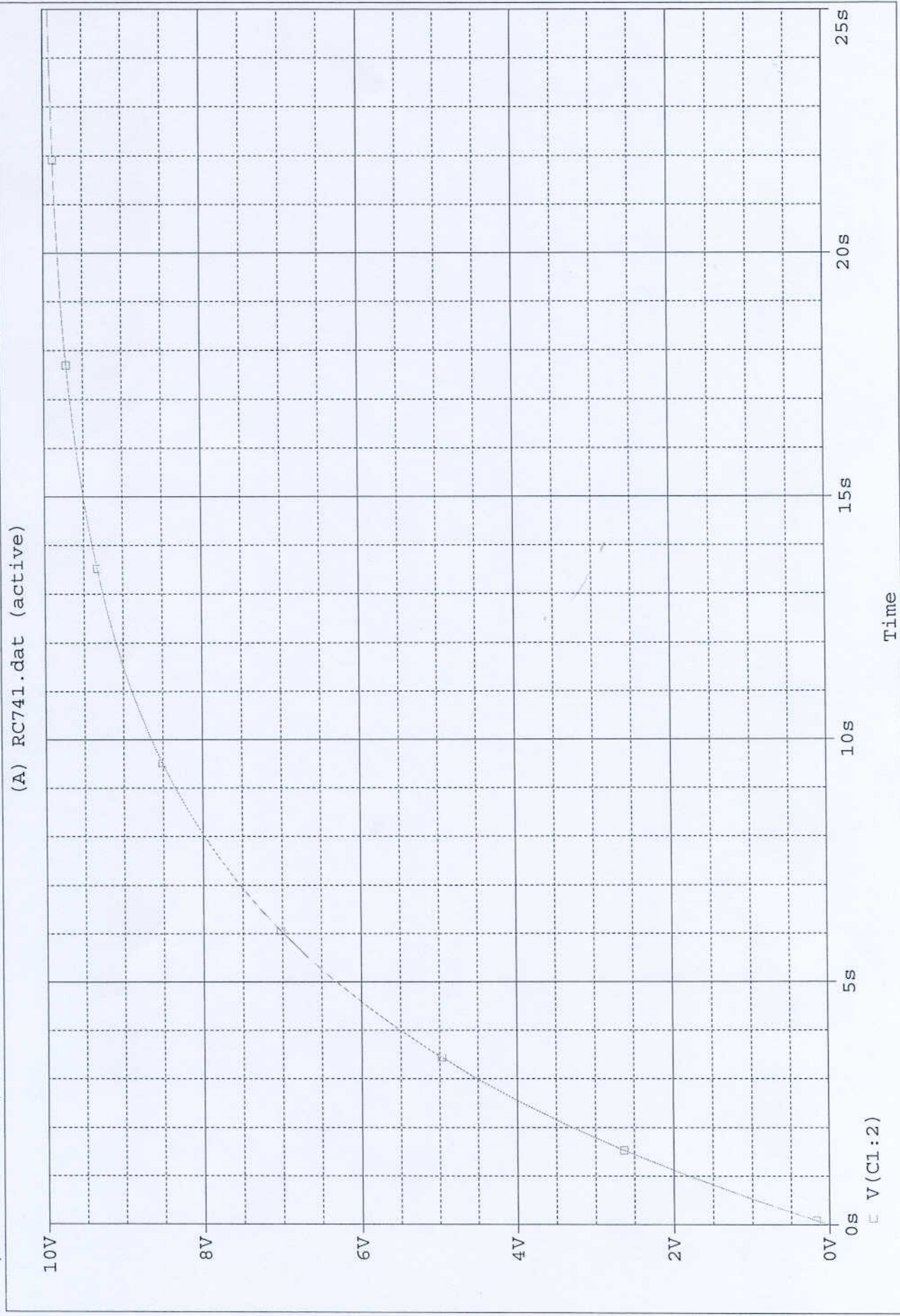** Profile: "SCHEMATIC1-RC741" [C:\ORCAD\ORCAD_15.7\TOOLS\P_Circuits\7_41 HW7_ECE300-PSpiceFiles\S...
Date/Time run: 03/19/07 12:28:26 Temperature: 27.0



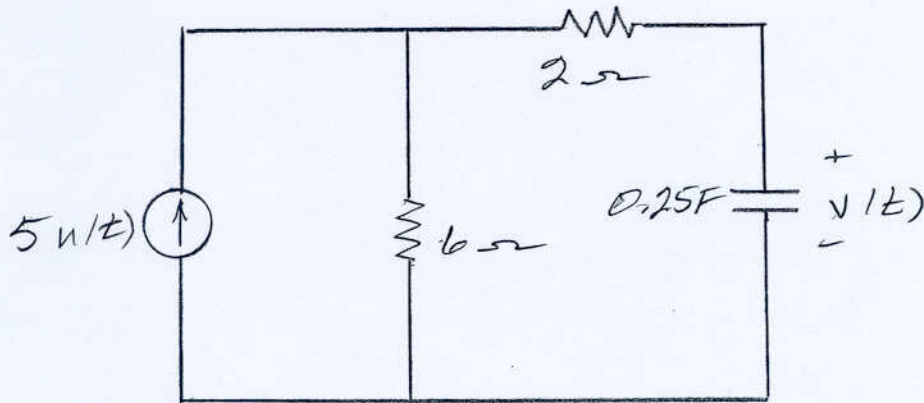7.46

For the following circuit $i_b(t) = 5u(t)$, FIND $V(t)$



$t < 0$

$$V(0^-) = 0 = V(0^+)$$

$t > 0$


$$V(\infty) = 30V$$

$$\tau = R_{eq}C ; R_{eq} = 2 + 6 = 8$$

$$\tau = 8 \times \frac{1}{4} = 2$$


$$V(t) = V(\infty) + [V(0^+) - V(\infty)]e^{-\frac{t}{\tau}}$$
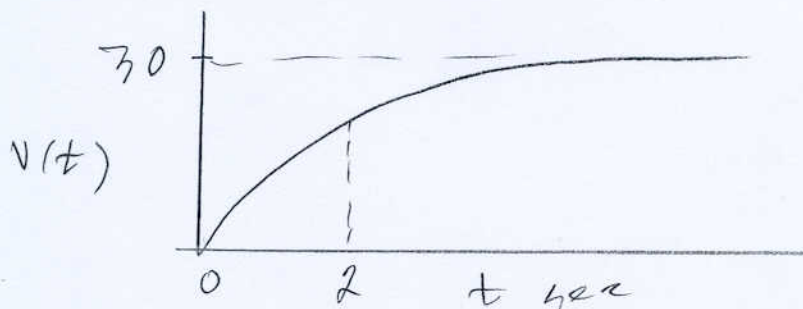
$$V(t) = 30(1 - e^{-t/2})u(t) \text{ V}$$



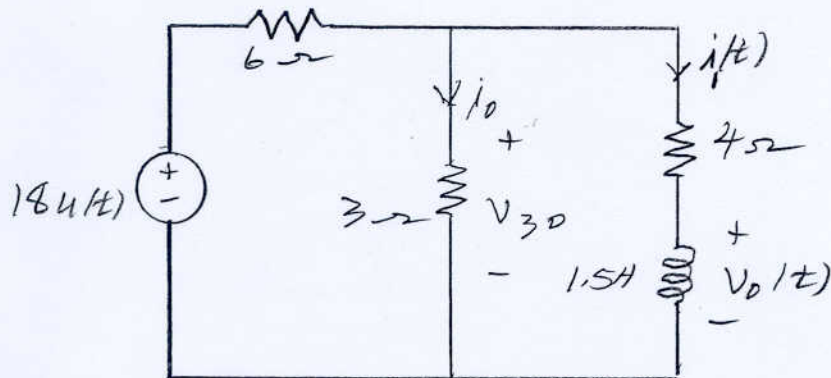7.59

Determine $V_0(t)$ for $V_s(t) = 18 u(t)$.



$t < 0$

$$i_1(0^-) = 0 \quad (\text{no source applied})$$

$$i_1(0^+) = 0 \quad (\text{current in the coil cannot change inst.})$$

$t > 0$

At $t = 0^+$, coil looks like an open circuit. $i_1(0^+) = 0$.

$$V_{30}(0^+) = \frac{18 \times 3}{3+6} = 6V$$

$$\underline{V_0(0^+) = V_{30}(0^+) = 6V}$$

$$V_0(\infty) = 0$$

$$\tau = \frac{L}{R_T}; \quad R_T = 4 + 3 \parallel 6 = 6 \Omega$$

$$\tau = \frac{1.5}{6} = \frac{1}{4}$$


$$V_0(t) = V_0(\infty) + [V_0(0^+) - V_0(\infty)] e^{-\frac{t}{\tau}}$$

7.59

i_o


$$V_o(t) = 0 + [6 - 0] e^{-4t}$$
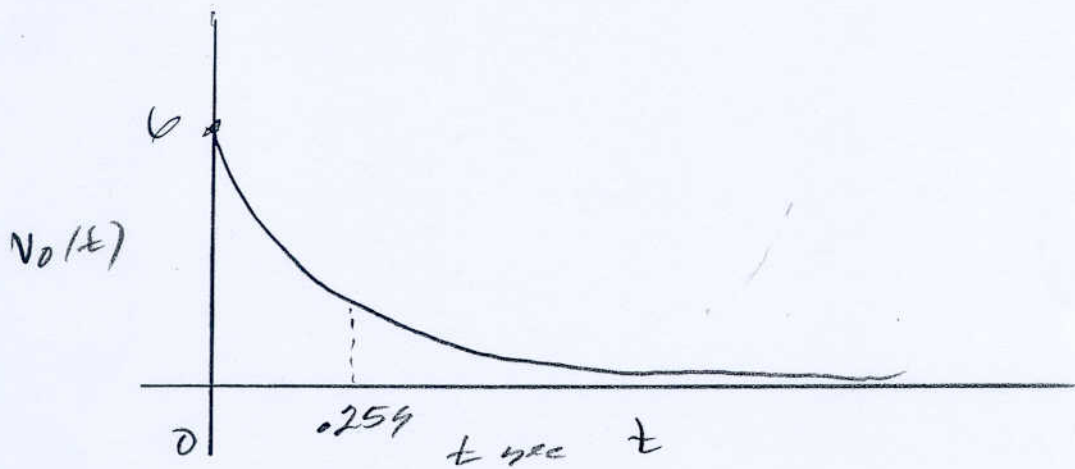
$$V_o(t) = \underbrace{6 e^{-4t}}_{\rightarrow} u(t) \text{ V}$$



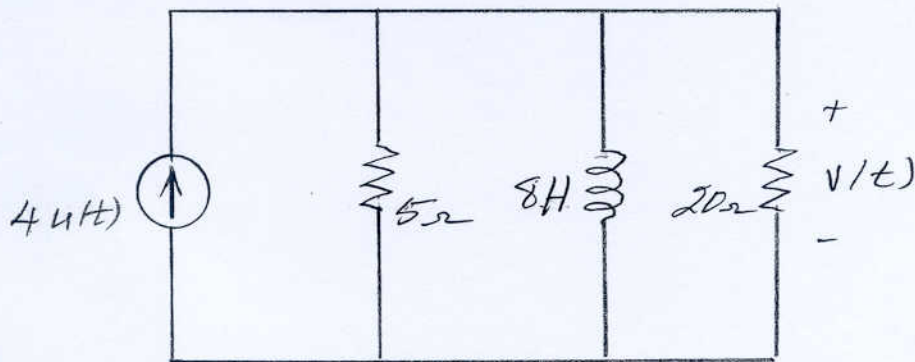7.60

FIND $V(t)$ for $t > 0$ in the following circuit: Given that the initial current in the inductor is zero.



The voltage across the $20\ \Omega$ resistor is also the voltage across the inductor.

$t < 0$
 $V(0^-) = 0$

$t > 0$
inductor looks like an open circuit.


$$\therefore V(0^+) = \left(\frac{4 \times 5}{5 + 20} \right) \times 20 = 16\text{V}$$

$$V(\infty) = 0 \quad (\text{inductor looks like a short} - \text{thus } V(\infty) = 0)$$

$$R_{eq} = 20 \parallel 5 = 4\ \Omega \quad \tau = \frac{L}{R} = \frac{8}{4} = 2$$


$$V(t) = V(\infty) + [V(0^+) - V(\infty)] e^{-\frac{t}{\tau}}$$

$$V(t) = 16 e^{-0.5t}$$

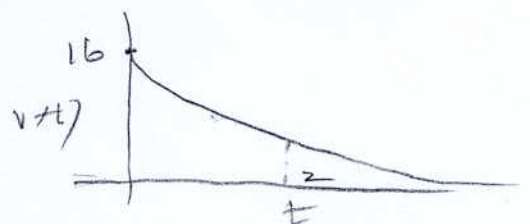

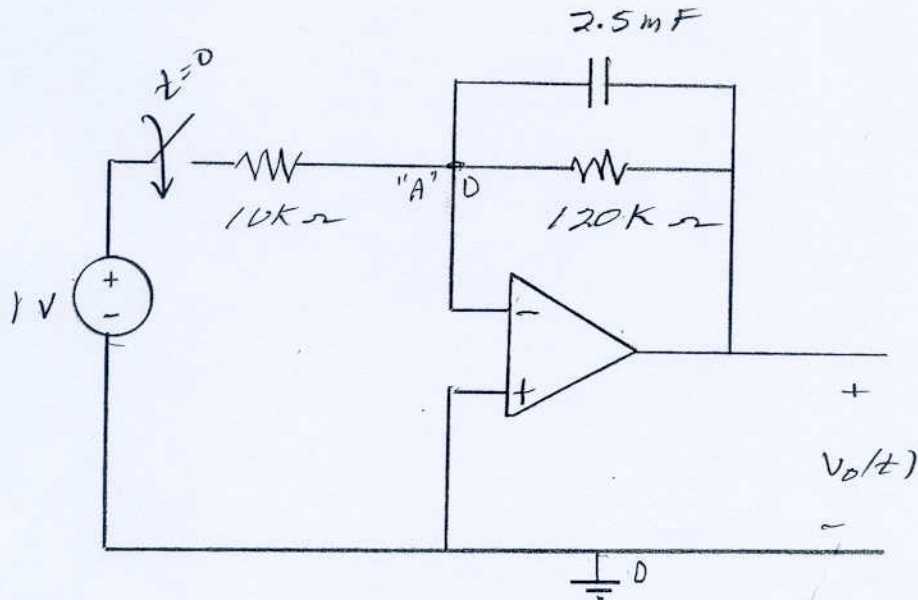7.69

For the op-amp circuit below find $V_o(t)$ for $t > 0$.



At "A"

$$\frac{-1}{10k} - \frac{V_o}{120k} - 2.5 \times 10^{-3} \frac{dV_o}{dt} = 0$$

$$2.5 \frac{dV_o}{dt} + \frac{V_o}{120} = \frac{-1}{10}$$

$$\frac{dV_o}{dt} + \frac{V_o}{300} = \frac{-1}{25}$$


$$V_o(t) = V_{o_{ss}} + V_{o_t}$$



$$V_{o_{ss}} = K = \frac{300}{25} = -12$$

(will not saturate)

$$V_o(t) = -12 + K_t e^{-\frac{t}{300}}$$

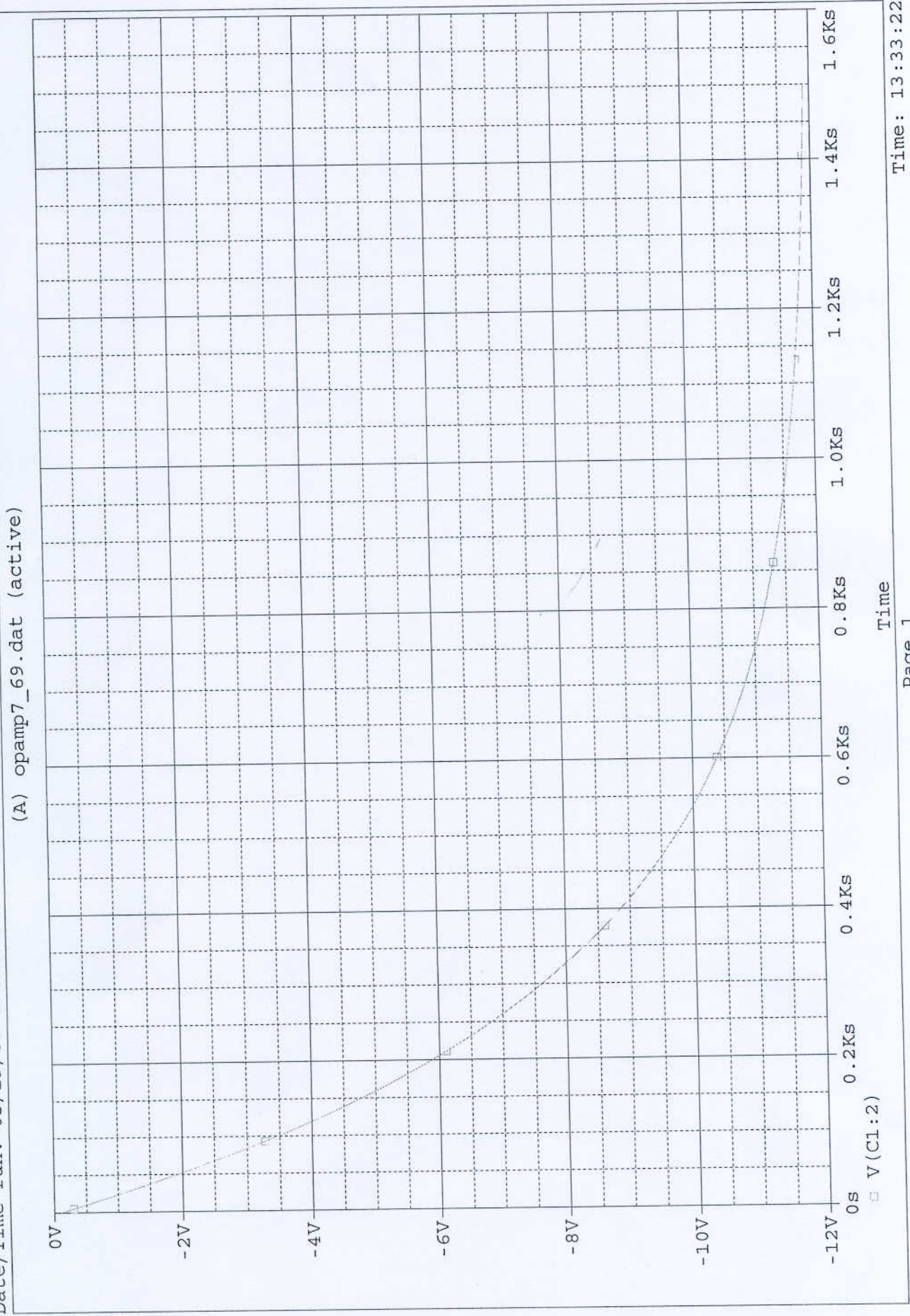** Profile: "SCHEMATIC1-opamp7_69" [C:\ORCAD\ORCAD_15.7\TOOLS\P_Circuits\HW7_69ECE300-PSpiceFiles\...
Temperature: 27.0
Date/Time run: 03/19/07 13:32:47



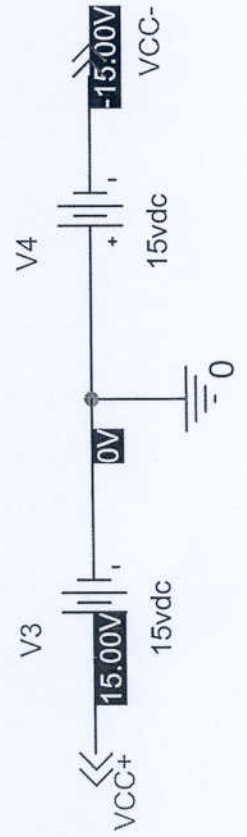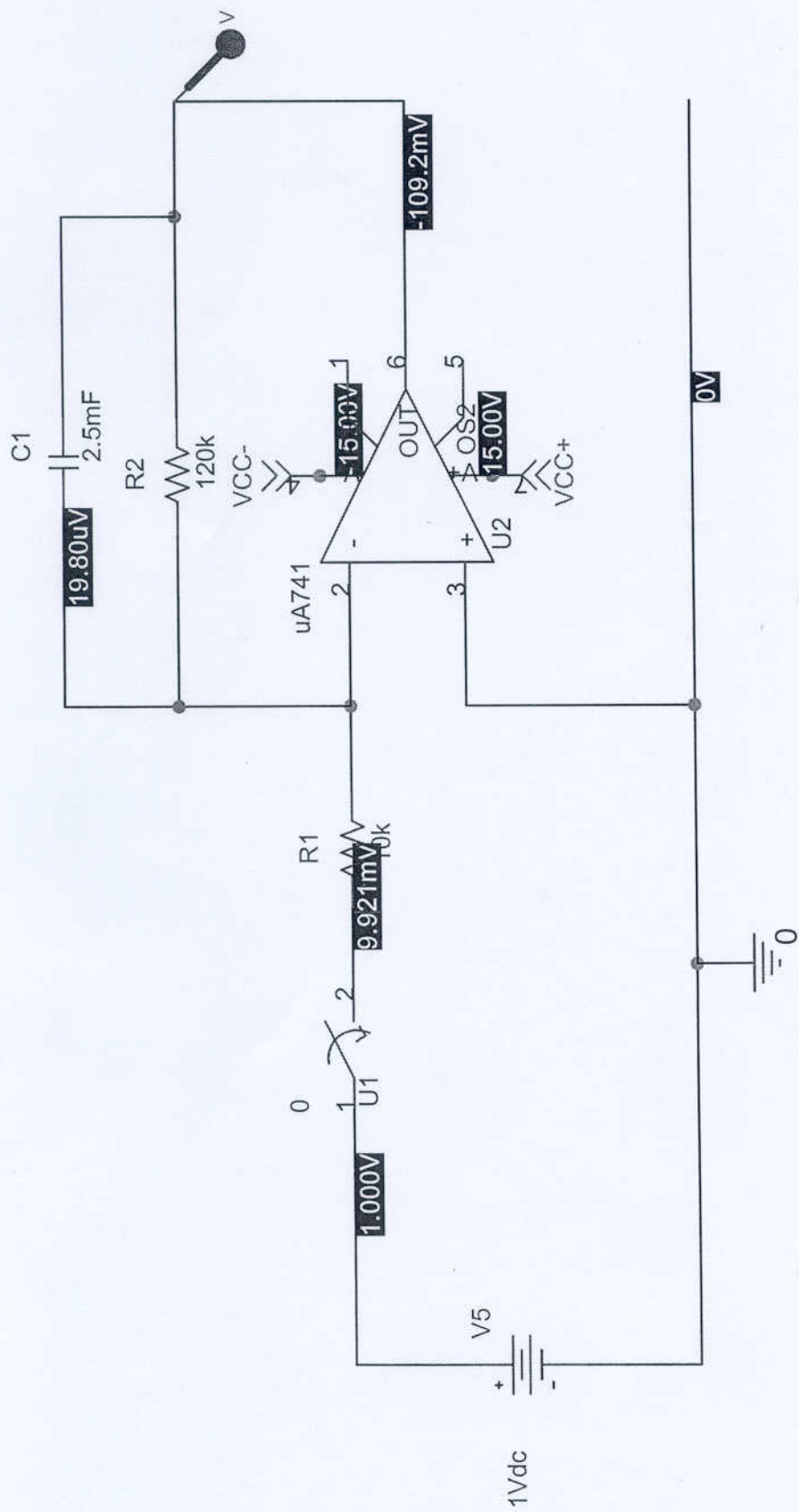

7.69 cont

$$V_0(0) = 0, \rightarrow K_t = 12$$

$$V_0(t) = -12 \left(1 - e^{-\frac{t}{300}}\right) u(t) \text{ V}$$