

ECE 300
Spring Semester, 2007
HW Set #9

Desk copy

Due: March 29, 2007 : version 2

Name Wly
Print (last, first)

wlg

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 20 points.

8.35 Ans: $v(t) = [12 - e^{-t}(4\cos 2t + 2\sin 2t)] u(t)$ V


8.47 Ans: $v_o(t) = 200te^{-10t} u(t)$ V

8.57 Ans: (a) $s^2 + 20s + 36 = 0$
(b) $i_x(t) = [-0.75e^{-2t} - 1.25e^{-18t}] u(t)$ amps : $v_r(t) = [6e^{-2t} + 10e^{-18t}] u(t)$ volts

W13

H.W. # 9
ECE 300
Sp. 2007

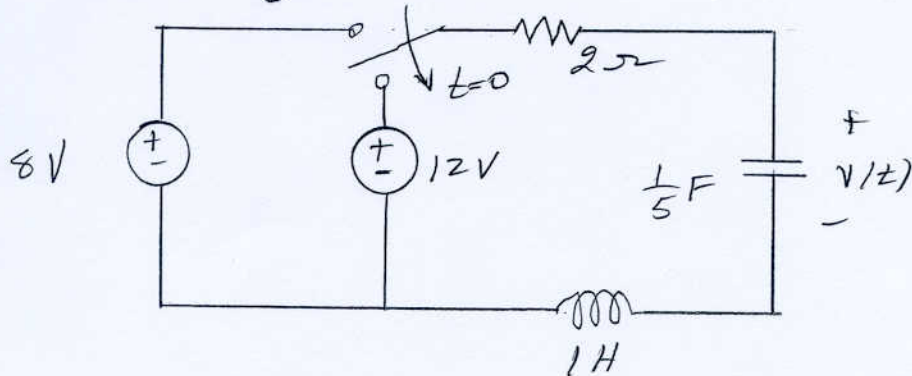
8.35 Determine $v(t)$ for $t > 0$ for the following circuit.



$t < 0$

$$v(0^-) = v(0^+) = 8V$$

$t > 0$

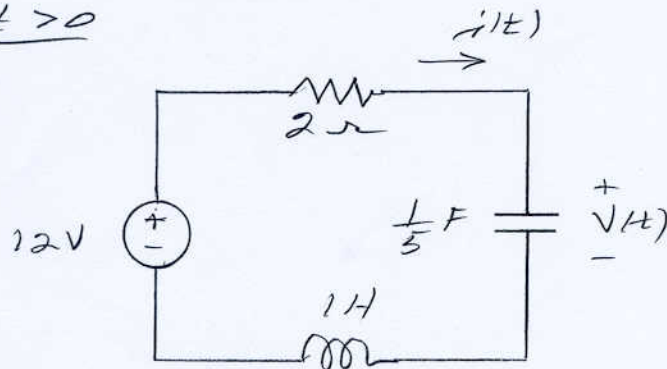

$$Ri + L \frac{di}{dt} + v(t) = 12$$

$$RC \frac{dV}{dt} + LC \frac{d^2V}{dt^2} + v(t) = 12$$

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{v(t)}{LC} = \frac{12}{LC}$$

6.35 cont

6.35 2

putting in numbers

$$\frac{d^2v}{dt^2} + 2\frac{dv}{dt} + 5v(t) = 60$$

$$(s+1+j2)(s+1-j2) = 0$$

$$\frac{1}{2} \omega_n = 1, \quad \omega_d = 2$$

$$v(t) = V_{ss} + v_t$$

$$V_{ss} = K_{ss}$$

$$5K_{ss} = 60 \rightarrow K_{ss} = 12 = V_{ss}$$

$$v(t) = 12 + e^{-t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$v(0) = 8 = 12 + e^{-t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t] \Big|_{t=0}$$

$$8 = 12 + B_1$$

$$B_1 = -4$$

$$i(0^-) = i(0^+) = C \frac{dv}{dt}$$

$$i(0^+) = 0 \therefore \frac{dv(0^+)}{dt} = 0$$

$$\left. \begin{aligned} \frac{dv}{dt} &= e^{-t} [-\omega_d B_1 \sin \omega_d t + \omega_d B_2 \cos \omega_d t] \\ &- e^{-t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t] \Big|_{t=0} \end{aligned} \right\}$$

$$0 = \omega_d B_2 - B_1$$

8.35 (cont)


8.35 3

$$B_2 = \frac{B_1}{\omega} = \frac{-4}{2} = -2$$

\therefore

$$v(t) = \left[12 - e^{-t} [4 \cos 2t + 2 \sin 2t] \right] u(t) \text{ V}$$

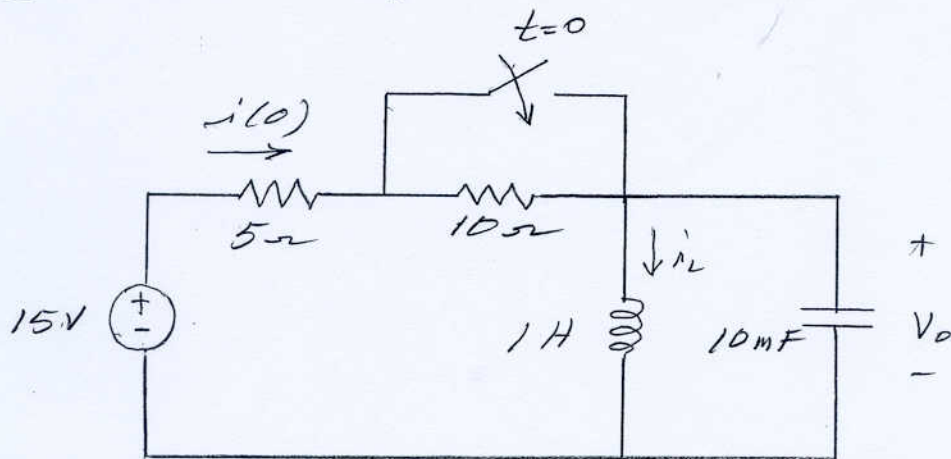8.47 Find the output voltage $v_o(t)$ for the following circuit.



$t < 0$


$$i(0^-) = 1 \text{ A}, \quad \therefore i_L(0^-) = 1 \text{ A}; \quad v_o(0^-) = 0$$

Now look at the circuit for

$t > 0$:

8.47 (cont)

8.47 2

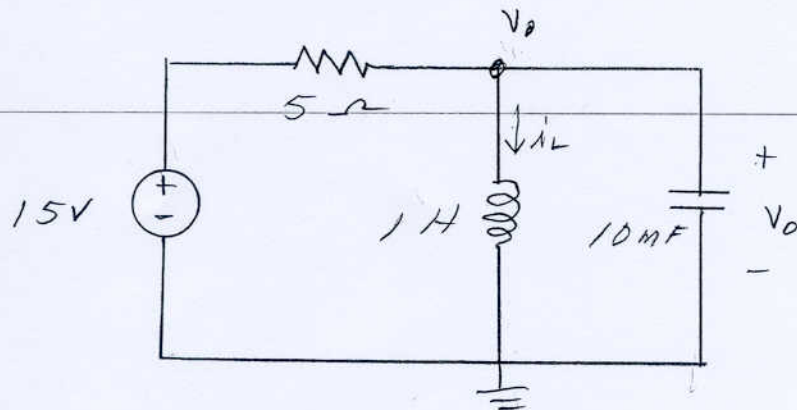

Nodal Analysis

$$\frac{V_0 - 15}{5} + \frac{1}{L} \int V_0 dt + i_L(0) + C \frac{dV_0}{dt} = 0 \quad (1)$$

At $t = 0^+$

$$\frac{V_0(0^+) - 15}{5} + 1 + 10 \times 10^{-3} \frac{dV_0(0^+)}{dt} = 0$$

$$V_0(0^+) = 0$$

$$10 \times 10^{-3} \frac{dV_0(0^+)}{dt} = 2$$

$$\frac{dV_0(0^+)}{dt} = \underline{200}; \quad V_0(0^+) = 0$$

Take the derivative of (1)

$$2 \frac{dV_0}{dt} + V_0(t) + 10 \times 10^{-3} \frac{d^2 V_0}{dt^2} = 0$$

$$\frac{d^2 V_0}{dt^2} + 20 \frac{dV_0}{dt} + 100 V_0 = 0$$

8.47 cont

8.47 3

Char. Eq.

$$s^2 + 20s + 100 = 0$$

$$(s+10)(s+10) = 0$$

repeated roots

$$V_o(t) = (A_1 + A_2 t) e^{-10t}$$

$$V_o(0) = 0 = (A_1 + A_2 t) e^{-10t} \Big|_{t=0} = A_1$$

$$\therefore A_1 = 0$$

$$V_o(t) = A_2 t e^{-10t}$$

$$\frac{dV_o}{dt} = -10A_2 t e^{-10t} + A_2 e^{-10t}$$

$$\frac{dV_o}{dt} \Big|_{t=0} = 200 = \left[-10A_2 t e^{-10t} + A_2 e^{-10t} \right] \Big|_{t=0}$$


$$200 = A_2$$

$$\therefore V_o(t) = 200t e^{-10t} \text{ V}$$

8.57 Given the circuit below.


(a) Find the characteristic equation.

(b) Find i_x and V_R

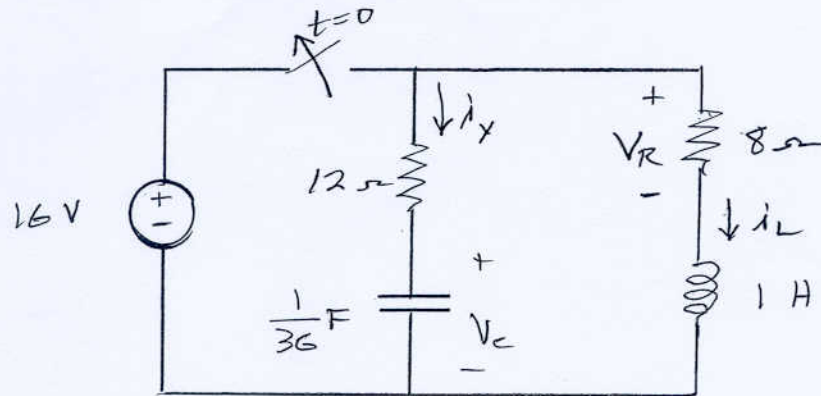

$t < 0$

Circuit becomes

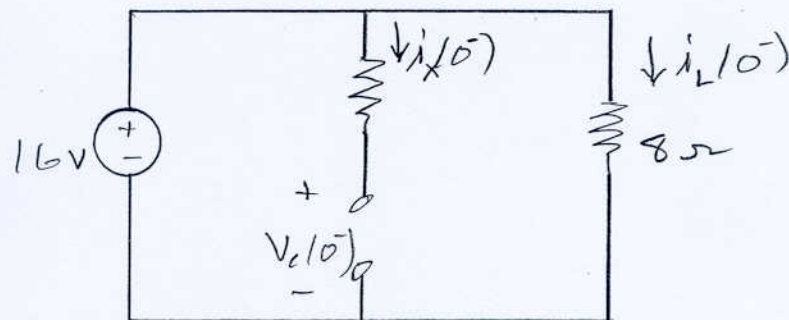

$$V_c(0^-) = V_c(0^+) = 16V \quad \#$$

$$i_L(0^-) = i_L(0^+) = 2A \quad \#$$


Now for $t > 0$

8.57 continued

8.57

2

$t > 0$

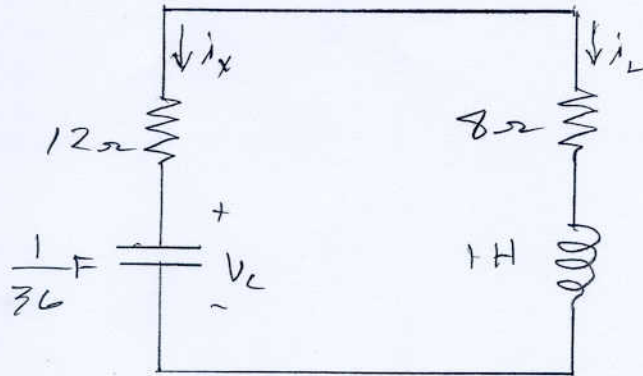

$$20i_x + 36 \int_0^t i_x dt + V_C(0^+) + L \frac{di_x}{dt} = 0 \quad (1)$$

At $t = 0^+$

$$20i_x(0) + 16 + \frac{di_x(0^+)}{dt} = 0$$

$$i_x(0^+) = -i_L(0^+) = -2 \text{ A}$$

into (1)

$$20 \times (-2) + 16 + \frac{di_x(0^+)}{dt} = 0$$

so

$$\frac{di_x(0^+)}{dt} = 24 \text{ V/s}$$

$$i_x(0^+) = -2$$

initial
conditions

8.57 continued

8.57 3

Take the derivative of (1) with respect to t .

$$20 \frac{di_x}{dt} + 36i_x + \frac{d^2 i_x}{dt^2} = 0$$

OR

$$\frac{d^2 i_x}{dt^2} + 20 \frac{di_x}{dt} + 36i_x(t) = 0$$

(a) The characteristic equation is

$$s^2 + 20s + 36 = 0$$

(b) Characteristic equation factors

$$As \quad (s+2)(s+18) = 0$$

overdamped

$$i_x(t) = A_1 e^{-2t} + A_2 e^{-18t}$$

$$i_x(0) = -2 = A_1 e^{-2t} + A_2 e^{-18t} \Big|_{t=0}$$

$$A_1 + A_2 = -2$$

8.57 continued

8.57 (4)

$$\frac{di_x}{dt} = -2A_1 e^{-2t} - 18A_2 e^{-18t}$$

$$\frac{di_x(0)}{dt} = 24 = \left[-2A_1 e^{-2t} - 18A_2 e^{-18t} \right] \Big|_{t=0}$$

$$24 = -2A_1 - 18A_2$$

$$\boxed{2A_1 + 18A_2 = -24}$$

$$\begin{bmatrix} 1 & 1 \\ 2 & 18 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} -2 \\ -24 \end{bmatrix}$$

$$A_1 = -0.75, \quad A_2 = -1.25$$

$$\boxed{i_x(t) = \left[-0.75 e^{-2t} - 1.25 e^{-18t} \right] u(t) \text{ A}} *$$

$$v_R = -8 i_x(t)$$

$$\boxed{v_R = \left[6 e^{-2t} + 10 e^{-18t} \right] u(t) \text{ V}} *$$