

ECE 300
Spring Semester, 2007
HW Set #12

Desk Copy

Due: April 25, 2007

Wlg: Version 2

Name wly
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

11.4 $P_5 = 14.86 \text{ W}$, $P_8 = 5.588 \text{ W}$, $P_S = 20.43 \text{ W}$

11.7 160 W

11.28 $V_{\text{RMS}} = 2.92 \text{ V}$, $P = 4.27 \text{ W}$

11.46 (a) (i) $S = (95.25 - j55) \text{ VA} = 110 \angle -30^\circ \text{ VA}$;

(ii) $|S| = 110 \text{ VA}$

(iii) $P = 95.26 \text{ W}$

(iv) $Q = 55 \text{ VARs}$

(v) $\text{Pf} = \cos(-30) = .866 \text{ leading}$

(b) $S = (1497.2 + j401.2) \text{ VA} = 1550 \angle 15^\circ \text{ VA}$

(i) $S = (1497.2 + j401.2) \text{ VA}$

(ii) $|S| = 1550 \text{ VA}$

(iii) $P = 1497.2 \text{ W}$

(iv) $Q = 401.2 \text{ VARs}$

(v) $\text{Pf} = .9659 \text{ lagging}$

(vi)

11.52 (a) $\text{pf} = 0.9845 \text{ leading}$; (b) $I_{\text{RMS}} = 35.55 \angle 55.11^\circ \text{ A}$

11.64 $I_S = 39.47 \angle -159.9^\circ \text{ V}$ (previous answer used RMS source which was no indicated in the text)

11.71 (a) $Z = 0.05107 \angle 2^\circ \Omega$

(b) $\text{pf} = 0.9994 \text{ lagging}$


(c) $I_{\text{RMS}} = 2.392 \angle -2^\circ \text{ KA}$

11.74 (a) $\text{pf} = 0.8992 \text{ lagging}$

(b) $C = 5.74 \text{ mF}$

ECE 300
H.W. #12
SPRING 2007

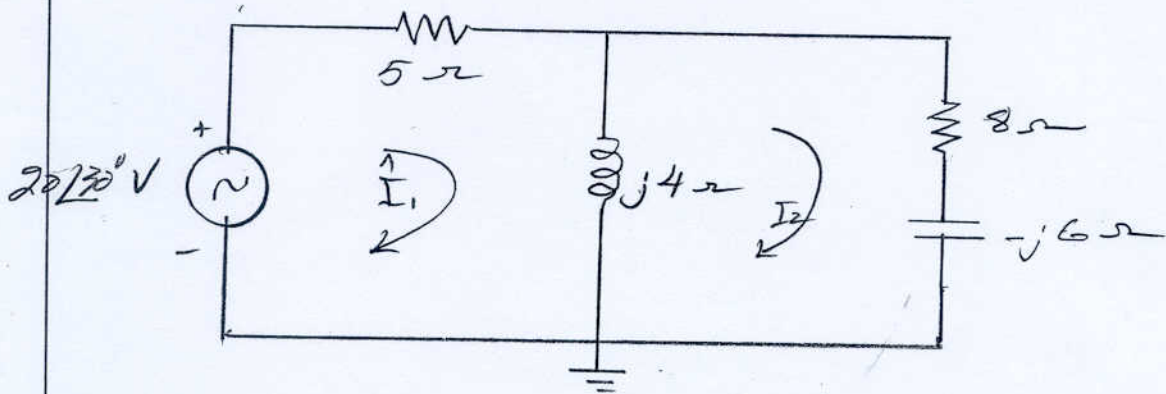11.04 For the circuit below, find the power supplied to the 2 resistors. Verify that this power is the same that is supplied by the $20\angle 30^\circ$ V source.



$$\begin{bmatrix} 5+j4 & -j4 \\ -j4 & 8-j2 \end{bmatrix} \begin{bmatrix} \vec{I}_1 \\ \vec{I}_2 \end{bmatrix} = \begin{bmatrix} 20\angle 30^\circ \\ 0 \end{bmatrix}$$

$$\vec{I}_1 = 2.434 - j.128 = 2.44\angle -3^\circ \text{ A} \quad \vec{I}_2 = 1.18\angle 101^\circ \text{ A}$$

$$P_5 = \frac{1}{2} |\vec{I}_1|^2 5 = 14.88 \text{ W}$$

$$P_8 = \frac{1}{2} |\vec{I}_2|^2 8 = 5.57 \text{ W}$$


$$P_5 + P_8 = 20.45 \text{ W}$$

$$P_{20\text{ source}} = \frac{1}{2} (20) \times (2.44) \cos(30+3)$$

$$P_{20} = 20.46 \text{ W} \quad \text{check}$$

11.7

Find the average power absorbed by the 10Ω resistor in the following circuit.

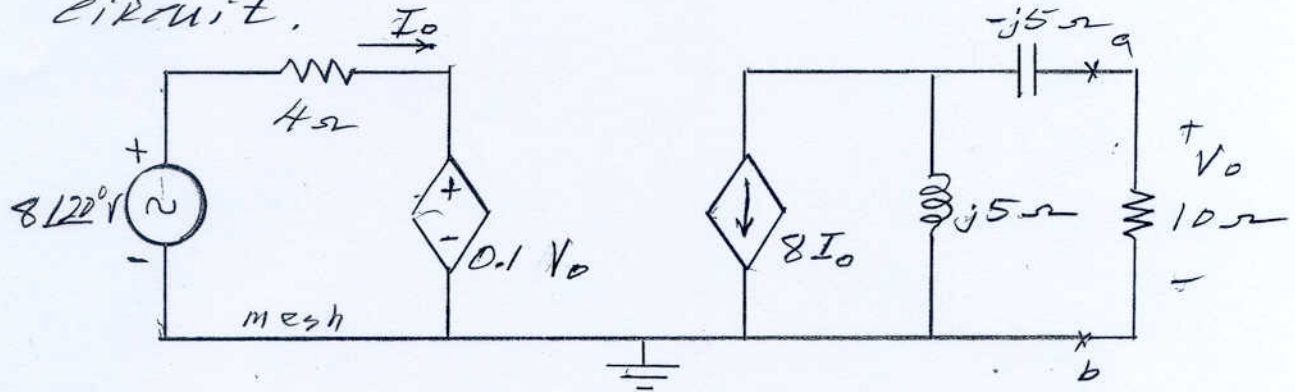

mesh 1

$$4\vec{I}_0 + 0.1\vec{V}_0 = 8\angle 20^\circ$$

$$\vec{V}_0 = \frac{-10 \times 8\vec{I}_0 (5\angle 90^\circ)}{10 + j5 - j5}$$

$$\vec{V}_0 = 40\angle -90^\circ \vec{I}_0$$

$$40\angle -90^\circ \vec{I}_0 - \vec{V}_0 = 0$$


$$\begin{bmatrix} 0.1 & 4 \\ -1 & 40\angle -90^\circ \end{bmatrix} \begin{bmatrix} \vec{V}_0 \\ \vec{I}_0 \end{bmatrix} = \begin{bmatrix} 8\angle 20^\circ \\ 0 \end{bmatrix}$$

$$\vec{V}_0 = 56.57\angle -25^\circ \text{ V}$$

$$P_{10} = \frac{1}{2} \frac{|\vec{V}_0|^2}{10} = \frac{56.57^2}{20} = 160 \text{ W}$$

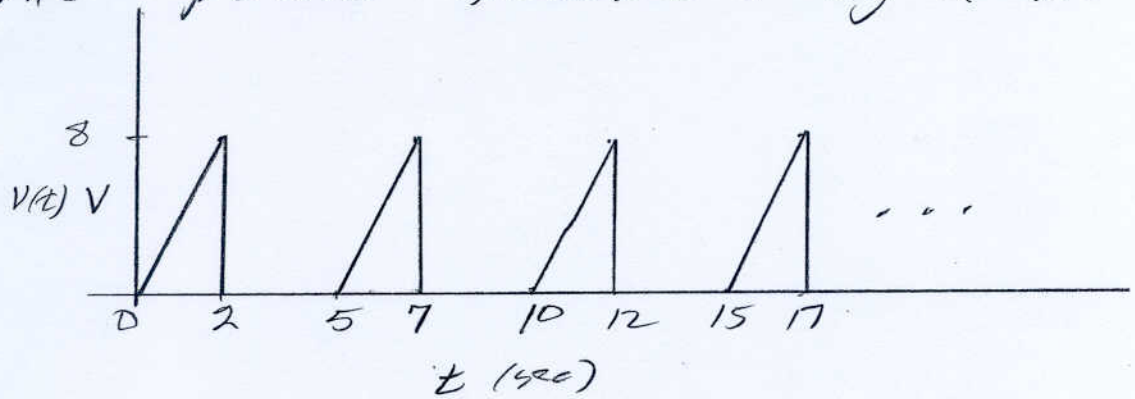11.28

Find the RMS value of the following periodic voltage waveform. Also find the power absorbed by a $2\ \Omega$ resistor



$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{\frac{1}{5} \int_0^2 (4t)^2 dt}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{5} \times \frac{16t^3}{3} \Big|_0^2} = \sqrt{\frac{1}{5} \times \frac{16 \times 2^3}{3}}$$

(a)

$$V_{\text{rms}} = 2.92\ \text{V}$$

$$(b) \quad P = \frac{V_{\text{rms}}^2}{R} = \frac{(2.92)^2}{2}$$

$$P_a = 4.26\ \text{W}$$

11.46

For the following voltage and current phasors, calculate the (i) complex power (ii) apparent power, (iii) real power, (iv) reactive power. Specify whether the PF is leading or lagging.

$$(a) \vec{V} = 220 \angle 30^\circ \text{ V rms} \quad \vec{I} = 0.5 \angle 60^\circ \text{ A rms}$$

$$\vec{S} = \vec{V}_{\text{rms}} \vec{I}_{\text{rms}}^* = (220 \angle 30^\circ)(0.5 \angle -60^\circ)$$

$$\vec{S} = (95.26 - j55) \text{ VA} = 110 \angle -30^\circ \text{ VA}$$

$$(i) \vec{S} = (95.26 - j55) \text{ VA}$$

$$(ii) S = 110 \text{ VA}$$

$$(iii) P = 95.26 \text{ W}$$

$$(iv) Q = -55 \text{ VARs OR}$$

$$Q = 55 \text{ VARs capacitive}$$

$$P.F. = \cos(-30^\circ) \text{ leading}$$

$$P.F. = 0.866 \text{ leading}$$

11.46 (b)

$$\vec{V} = 250 \angle -10^\circ \text{ V RMS}$$

$$\vec{I} = 6.2 \angle -25^\circ \text{ A rms}$$

(i)

$$\vec{S} = \vec{V}_{\text{rms}} \vec{I}_{\text{rms}}^* = (250 \angle -10^\circ)(6.2 \angle 25^\circ)$$

$$\vec{S} = (1497.2 + j 401.2) \text{ VA}$$

(ii) $S = |\vec{S}| = 1550 \text{ VA}$

$$\vec{S} = 1550 \angle 15^\circ \text{ VA}$$

(iii) $P = 1497.2 \text{ W}$


(iv) $Q = 401.2 \text{ VARs inductive}$

$$\text{P.f.} = \frac{P}{S} = \frac{1497.2}{1550} = 0.9657$$

$$\text{P.f.} = 0.9659 \text{ lagging}$$

11.52

Given the configuration below.

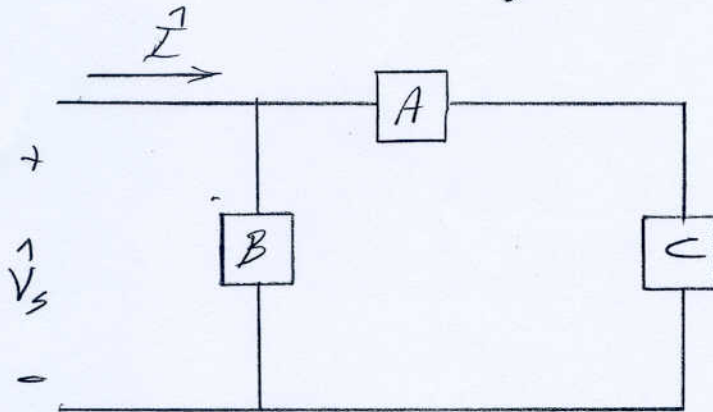

A \rightarrow 2 kW 0.8 p.f. lagging

B \rightarrow 3 kVA 0.4 p.f. leading

C \rightarrow $\vec{S} = 1000 + j500$

(a) Find the p.f. of the entire system


$$\vec{S}_{TOTAL} = \vec{S}_A + \vec{S}_B + \vec{S}_C$$

For \vec{S}_A

$$\cos \theta_A = 0.8$$

$$\cos \theta_A = 0.8 = \frac{2 \text{ kW}}{|\vec{S}_A|}$$

$$|\vec{S}_A| = \frac{2 \text{ kW}}{0.8} = 2500$$

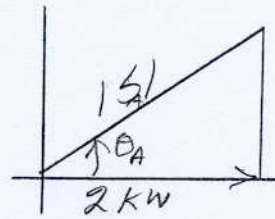

$$\vec{S}_A = 2500 \angle 36.87^\circ \text{ VA}$$

For \vec{S}_B

$$\theta_B = \cos^{-1} 0.4 = -66.4^\circ \text{ (negative because it's leading)}$$

$$\therefore \vec{S}_B = 3000 \angle -66.4^\circ \text{ VA}$$

11.52

For \vec{S}_e

Given directly

$$\vec{S}_e = 1000 + j500 = 1118 \angle 26.57^\circ \text{ VA}$$

Now

$$\vec{S}_{\text{TOTAL}} = (2500 \angle 36.87) + (3000 \angle -66.4) + (1118 \angle 26.57)$$

$$\vec{S}_{\text{TOTAL}} = (4200.97 - j749) \text{ VA}$$

$$|\vec{S}_{\text{TOTAL}}| = 4267.22 \angle -10.11^\circ \text{ VA}$$

$$\text{P.F.} = \frac{P}{|S|} = \frac{4200.97}{4267.22} = \underline{\underline{0.9845}} \text{ leading}$$

leading because $\angle S$ is negative

$$(b) \vec{S}_{\text{source}} = V_{\text{rms}} \vec{I}_{\text{rms}}^*$$


$$\vec{I}_{\text{rms}}^* = \frac{4267.22 \angle -10.11}{120 \angle 45}$$

$$\vec{I}_{\text{rms}}^* = 35.56 \angle -55.1 \text{ A}$$

$$\vec{I}_{\text{rms}} = 35.56 \angle 55.1 \text{ A}$$

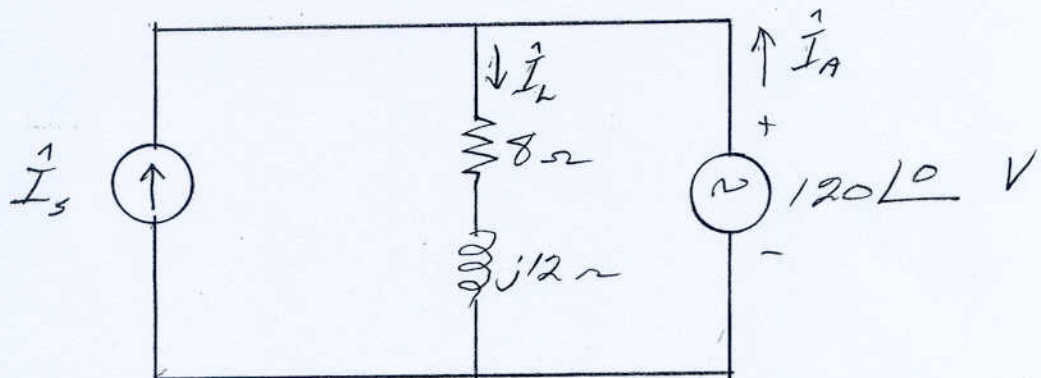11.64

Given the following circuit, Determine \vec{I}_s if the $120 \angle 0^\circ$ V source supplies 2.5 kW with 0.4 kVA leading (i.e. $\vec{S} = (2.5 - j0.4) \text{ kVA} = 2.532 \angle -9.1^\circ \text{ kVA}$)



Now;

$$\vec{I}_L = \frac{(120 \angle 0^\circ)}{(8 + j12)} = 8.32 \angle -56.31^\circ \text{ A}$$

At the voltage source

$$\vec{S} = 2532 \angle -9.1^\circ = \frac{(120 \angle 0^\circ)(\vec{I}_A^*)}{2} \text{ kVA}$$

$$\vec{I}_A^* = \frac{2 \times 2532 \angle -9.1^\circ}{120} \text{ kVA} = 42.2 \angle -9.1^\circ \text{ A}$$

$$\vec{I}_A = 42.2 \angle 9.1^\circ \text{ A}$$

$$\vec{I}_s = -\vec{I}_A + \vec{I}_L = -(42.2 \angle 9.1^\circ) + (8.32 \angle -56.31^\circ)$$

$$\vec{I}_s = 39.47 \angle -159.9^\circ \text{ A}$$


using park values

$$\vec{I} = 19.19 \angle -147.7^\circ \text{ A leading}$$

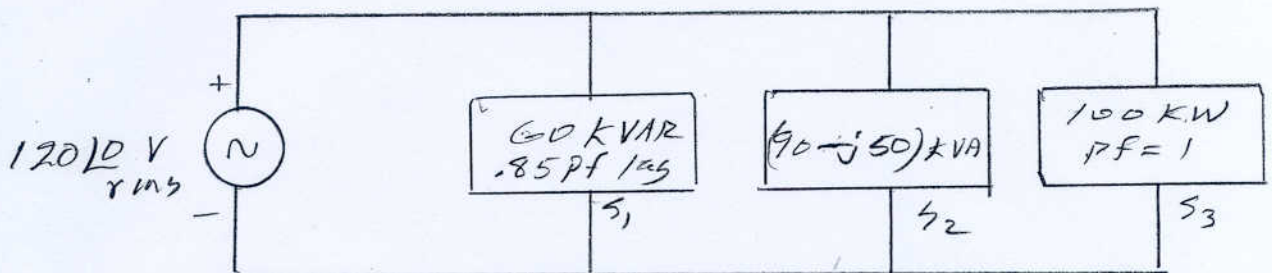11.71

Given the following power circuit.


- Find the equivalent \vec{S} .
- Calculate the p.f. for the total circuit.
- Determine the current supplied by the source.



For \vec{S}_1

$$\theta_1 = \cos^{-1} .85$$

$$\theta_1 = 31.79^\circ$$

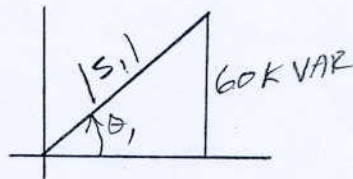

$$|\vec{S}_1| = \frac{60 \text{ K}}{\sin 31.79} = 113.89 \text{ KVA}$$

$$\vec{S}_1 = 113.89 \angle 31.79 \text{ KVA}$$

For \vec{S}_2

$$\vec{S}_2 = (90 - j50) \text{ KVA}$$

For \vec{S}_3

$$\vec{S}_3 = 100 \text{ KVA}$$

$$\vec{S}_{\text{TOTAL}} = \vec{S}_1 + \vec{S}_2 + \vec{S}_3 = 286.2 \angle 1.91^\circ$$

11.71 cont,

(2)

$$S = \frac{V_{rms}^2}{Z^*}$$

$$Z^* = \frac{(120)^2}{286.2 \angle 1.91 \times 10^3} = \frac{50.31 \angle -1.91}{1 \times 10^3}$$

$$\frac{1}{Z} = 50.31 \times 10^{-3} \angle 1.91$$

$$\frac{1}{Z} = .0503 \angle 1.91^\circ \Omega$$

(b)


$$P.f. = \cos 1.91 = 0.9994$$

$$(c) I = \frac{V_{source}}{\frac{1}{Z}} = \frac{120 \angle 0}{.0503 \angle 1.91}$$

$$\vec{I} = 2.386 \angle -1.91 \text{ kA} \quad \text{wow!}$$

lot of amps

11.74 Given the following power system.

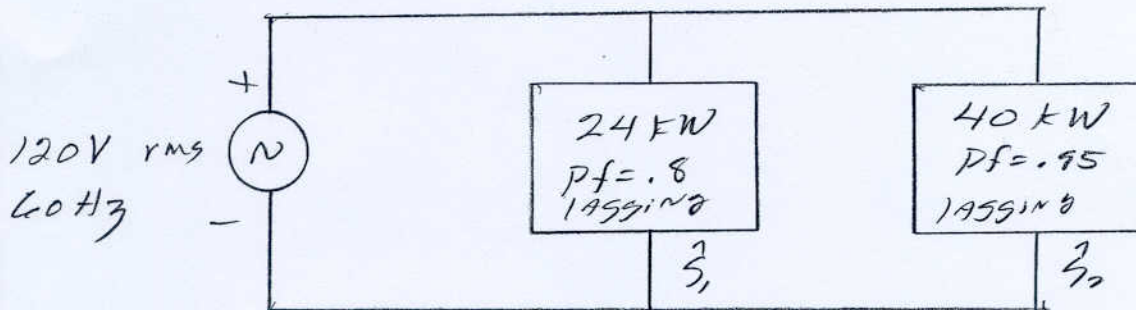

(a) Find the p.f. of the combination load.

(b) Determine C , connected in parallel with the loads, that will provide a unity power factor.

For S_1

$$|S_1| = \frac{24 \text{ K}}{0.8} = 30 \text{ KVA} \quad \theta_1 = \cos^{-1} 0.8 = 36.87^\circ$$

$$\vec{S}_1 = 30 \angle 36.87^\circ \text{ KVA} = (24 + j18) \text{ KVA}$$

For S_2

$$|S_2| = \frac{40 \text{ K}}{0.95} = 42.1 \quad \theta_2 = \cos^{-1} 0.95 = 18.19^\circ$$

$$\vec{S}_2 = 42.1 \angle 18.19^\circ \text{ KVA} = (40 + j13.14) \text{ KVA}$$

The reactive part of the load is

$$Q_T = Q_1 + Q_2$$

$$Q_T = (18 + 13.14) \text{ KVAR}$$

11.74 cont.

(a) For the combined p.f. (2)

$$S_{\text{TOTAL}} = \left[(24 + j18) + (40 + j13.14) \right] \text{ KVA}$$

$$S_{\text{TOTAL}} = (64 + j31.14) \text{ KVA}$$

$$\tan \theta_{pf} = \frac{31.14}{64} = \text{p.f.}$$

$$\theta = 25.95^\circ$$

$$\cos \theta = \text{p.f.} = \cos 25.95^\circ = 0.8992$$

(b) You want to cancel out

$$(18 + 13.14) \text{ KV} = 31.14$$

Do this with the parallel capacitors.

$$C = \frac{31140}{2\pi \times 60 \times 120^2}$$

$$C = 5.74 \text{ mF}$$