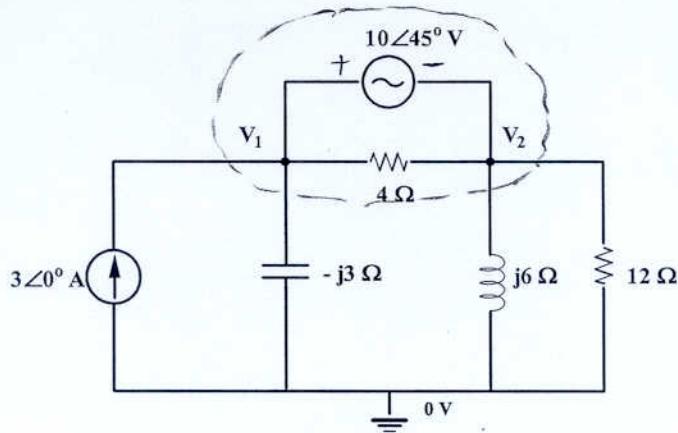


wlg

ECE 300  
Test 3A  
Spring 2007

- (1) You are given the circuit of Figure 1. Use Nodal Analysis to find the phasor voltages  $V_1$  and  $V_2$ . Express your answers in polar form.



Super node as shown:

$$\frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12} = 3$$

$$j0.333V_1 - j0.1667V_2 + 0.0833V_2 = 3$$

$$\boxed{j0.333V_1 + (0.0833 - j0.1667)V_2 = 3}$$

Constraint


$$V_1 - 10\angle45^\circ - V_2 = 0$$

$$\begin{bmatrix} j0.333 & 0.0833 - j0.1667 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 \\ 10\angle45^\circ \end{bmatrix}$$

$$\boxed{V_1 = 25.8 \angle -70.43^\circ \text{ V} \quad V_2 = 31.45 \angle -87.13^\circ \text{ V}}$$


Test A

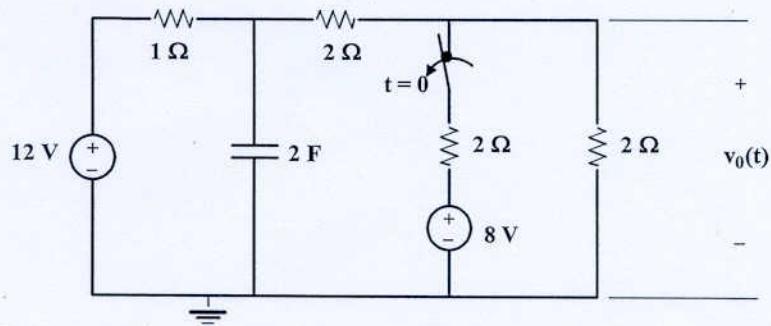- (2) You are given the circuit shown in Figure 2. The switch has been closed for a very long time and is opened at  $t=0$ . Use the step-by-step method to find  $v_o(t)$ .





$t < 0$

(make a Thevenin)

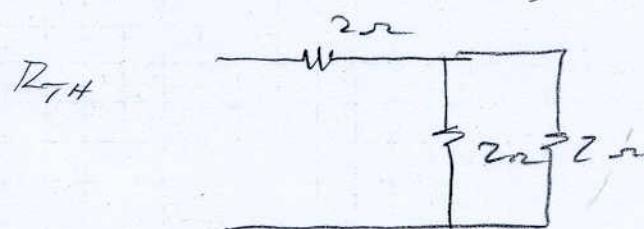

$$R_{TH} = 3\Omega$$

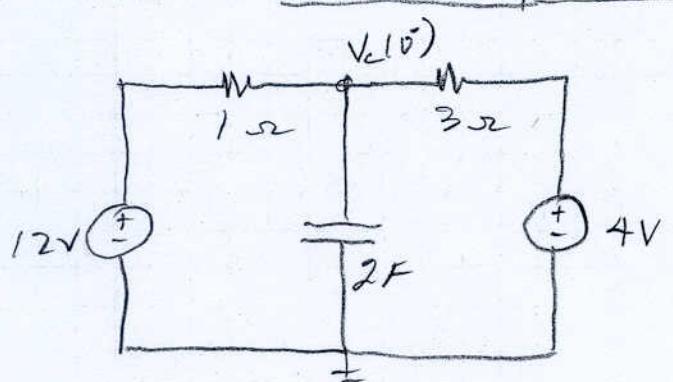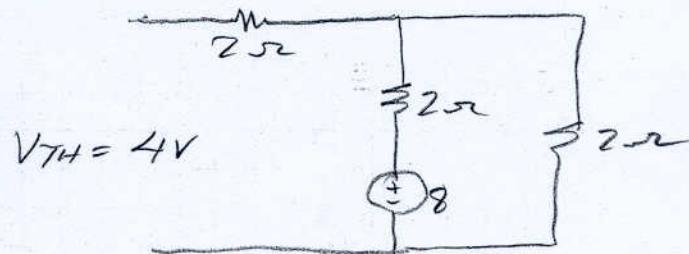


$$\frac{V_c - 12}{1} + \frac{V_c - 4}{3} = 0 \Rightarrow 3V_c - 36 + V_c - 4 = 0$$

$$V_c(0^+) = 10V$$

## Text A

2.2

(2)

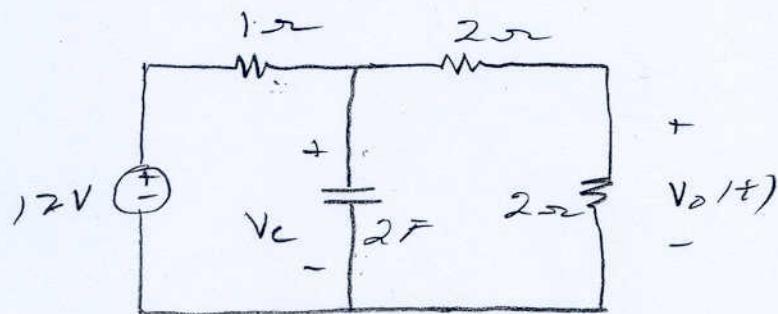 $t \geq 0$ 

$$V_c(10^-) = V_c(10^+)$$

$$V_o(10^+) = \frac{V_c(10^+) \times 2}{2+2} = 0.5 V_c(10^+)$$

$$\underline{V_o(10^+) = 5V}$$

$$V_o(100) = \frac{12 \times 2}{5} = \underline{\frac{24}{5}V} = 4.8V$$

$$R_{eq} = 1/1/4 = \frac{4}{3}$$

$$\tau = \frac{4}{5} \times 2 = 1.6 \text{ sec}$$

$$V_o(t) = V_o(100) + [V_o(10^+) - V_o(100)] e^{-\frac{t}{\tau}}$$


$$V_o(t) = \frac{24}{5} + \left[ 5 - \frac{24}{5} \right] e^{-0.625t} \quad V$$

$-0.625t$

$$V_o(t) = 4.8 + 0.2 e$$

# Test A

- (3) Use mesh analysis to find the phasor current  $I_0$  shown in the circuit of Figure 3. Express your answer in polar form.

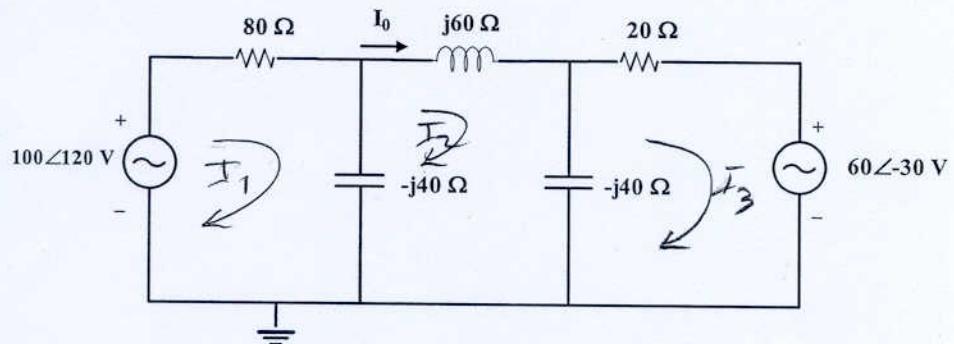

mesh 1

$$80(I_1) - j40(I_1 - I_2) = 100 \angle 120^\circ$$

$$\boxed{(80 - j40)I_1 + j40I_2 + 0I_3 = 100 \angle 120^\circ}$$

mesh 2

$$-j40(I_2 - I_1) + j60I_2 - j40(I_2 - I_3) = 0$$

$$\boxed{j40I_1 - j20I_2 + j40I_3 = 0}$$

mesh 3

$$-j40(I_3 - I_2) + 20I_3 = -60 \angle -30^\circ$$

$$\boxed{0I_1 + j40I_2 + (20 - j40)I_3 = -60 \angle -30^\circ}$$

$$\begin{bmatrix} 80 - j40 & j40 & 0 \\ j40 & -j20 & j40 \\ 0 & j40 & 20 - j40 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \angle 120^\circ \\ 0 \\ -60 \angle -30^\circ \end{bmatrix}$$

$$I_1 = 0.0412 + j0.5819$$

$$I_2 = 1.042 + j1.914 = \boxed{I_0 = 2.1797 \angle 61.43^\circ A}$$

$$I_3 = 0.48 + j0.375$$

Test A

- (4) You are given the circuit of Figure 4. The switch has been in position 1 for a very long time. At  $t = 0$ , the switch is moved to position 2.

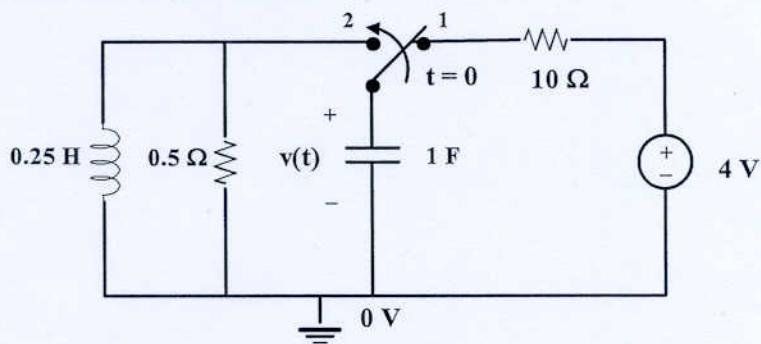


Figure 4: Circuit for Problem 4.

(a) Determine  $v(0^+)$  and  $\frac{dv(0^+)}{dt}$ .

(b) Develop the differential equation that can be used to determine  $v(t)$ . The equation is of the form

$$\frac{d^2v(t)}{dt^2} + K_1 \frac{dv(t)}{dt} + K_2 v(t) = K_3$$

Determine  $K_1$ ,  $K_2$ , and  $K_3$  using numerical values.

(c) Give the characteristic equation and the roots of the characteristic equation.

(d) Which of the following apply?

- (i) The response for  $v(t)$  is overdamped.
- (ii) The response for  $v(t)$  is underdamped.
- (iii) The response for  $v(t)$  is critically damped.
- (iv) Since this is a linear, time invariant, second order differential equation, none of the above apply.

(e) Determine  $\xi$ ,  $\omega_n$  and  $\omega_d$ .

(f) Determine the solution for  $v(t)$  for  $t \geq 0$ .

(g) Approximately how long will it take (within 20%) before the response decays to 1% of its initial value?

(a) Looking at the circuit we see the capacitor is charged to the source value:


$$\therefore V(0^-) = V(0^+) = 4V$$

To get  $\frac{dv(0^+)}{dt}$  we need to write an equation. (next page)

## Test (A)

(4) cont

4.2

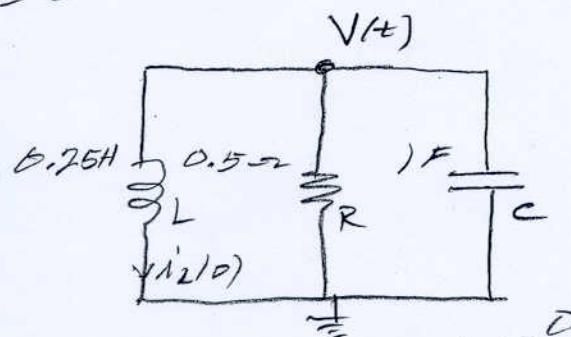 $t \geq 0$ 

$$\frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int_{t=0}^t V(t') dt' + i_2(0^+) = 0 \quad (A)$$

$$i_2(0^+) = 0$$

Evaluate the above at  $t = 0^+$

$$C \frac{dV(0^+)}{dt} = - \frac{V(0^+)}{RC}$$

$$\frac{dV(0^+)}{dt} = - \frac{4}{0.5 \times 1} = - 8 \text{ V}$$

so  $\boxed{V(0^+) = 4 \text{ V}} \quad \boxed{\frac{dV(0^+)}{dt} = - 8 \text{ V}}$

(b) Take the derivative of Eq (A)

$$\frac{1}{R} \frac{dV}{dt} + C \frac{d^2V}{dt^2} + \frac{V(t)}{L} = 0$$

OR

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V(t)}{LC} = 0$$

OR

$$\frac{d^2V}{dt^2} + 2 \frac{dV}{dt} + 4V(t) = 0 \quad (B)$$

(4) cont

Compare Eq (B) to

$$\frac{\partial^2 V}{\partial t^2} + k_1 \frac{\partial V}{\partial t} + k_2 V(t) = 0$$

we see

$$\boxed{k_1 = 2} \quad \boxed{k_2 = 4} \quad \boxed{k_3 = 0}$$

(c) The characteristic equation is

$$s^2 + 2s + 4 = 0$$

roots

$$(s+1+j1.732)(s+1-j1.732) = 0$$

$$s_1 = -1 - j1.732, \quad s_2 = -1 + j1.732$$

(d) is underdamped

$$\omega_n^2 = 4$$

$$\boxed{\omega_n = 2}$$

$$2\xi\omega_n = 2$$

$$\boxed{\xi = \frac{1}{\omega_n} = 0.5}$$

$$\omega_d = \omega_n \sqrt{1-\xi^2} = 2 \sqrt{1-0.25}$$

$$\boxed{\omega_d = 1.732 \text{ rad/sec}}$$

$$\xi\omega_n = 1$$

(4) cont.

4.4

$$v(t) = e^{-\xi \omega_n t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$v(0) = 4 = B_1$$

$$\frac{dv}{dt} = e^{-t} [-\omega_d B_1 \sin \omega_d t + \omega_d B_2 \cos \omega_d t] \\ - e^{-t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

with

$$\frac{dv(0)}{dt} = -8$$

$$-8 = 1.732 B_2 - B_1 = 1.732 B_2 - 4$$

$$B_2 = \frac{-4}{1.732} = -2.309$$

$$v(t) = e^{-t} [4 \cos 1.732 t - 2.309 \sin 1.732 t]$$

$$(g) e^{-3} = 0.0497 \rightarrow 4.97\%$$

$$e^{-4} = 0.0183 \rightarrow 1.83\%$$

$$e^{-5} = 0.0067 \rightarrow 0.67\%$$

use 5 time constants

Ans  $\approx$  5 sec

Test A

(b) cont

5.2

(c)

$$I = \frac{V_s}{Z} = \frac{100\text{V}}{20}$$


# Test A

(5) You are given the AC circuit shown in Figure 5. The following phasor voltages are known.

$$V_s = 100 \angle 0^\circ V; \quad V_R = 85.75 \angle 30.96^\circ V; \quad V_L = 51.45 \angle 120.96^\circ V$$

The frequency of the source is  $\omega = 200$  rad/sec.

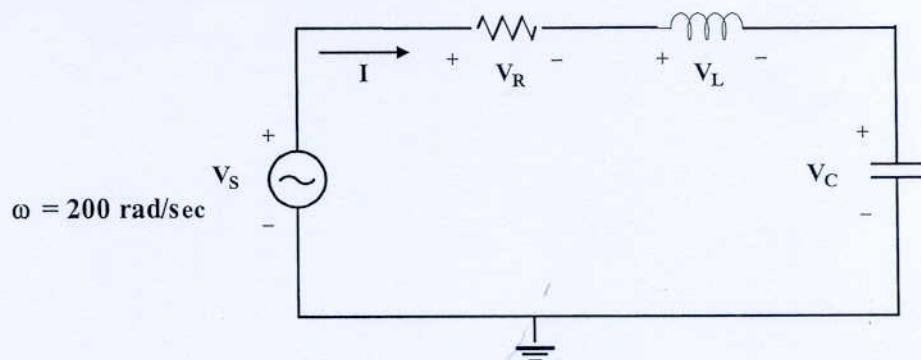- (a) Solve for the phasor voltage  $V_C$ . Express your answer in polar form.
- (b) Draw the phasor diagram (close to scale) showing  $V_s$ ,  $V_R$ ,  $V_L$ , and  $V_C$ .
- (c) Determine the phasor current  $I$  shown in the diagram. Express your answer in polar form.
- (d) Determine the value of the capacitor  $C$ , expressed in  $\mu F$ .




$$(a) V_R + V_L + V_C = V_s$$

$$V_C = V_s - V_R - V_L$$

$$V_C = 100 - 85.75 \angle 30.96^\circ - 51.45 \angle 120.96^\circ$$

$$\boxed{V_C = 102.9 \angle -59^\circ}$$

(b)

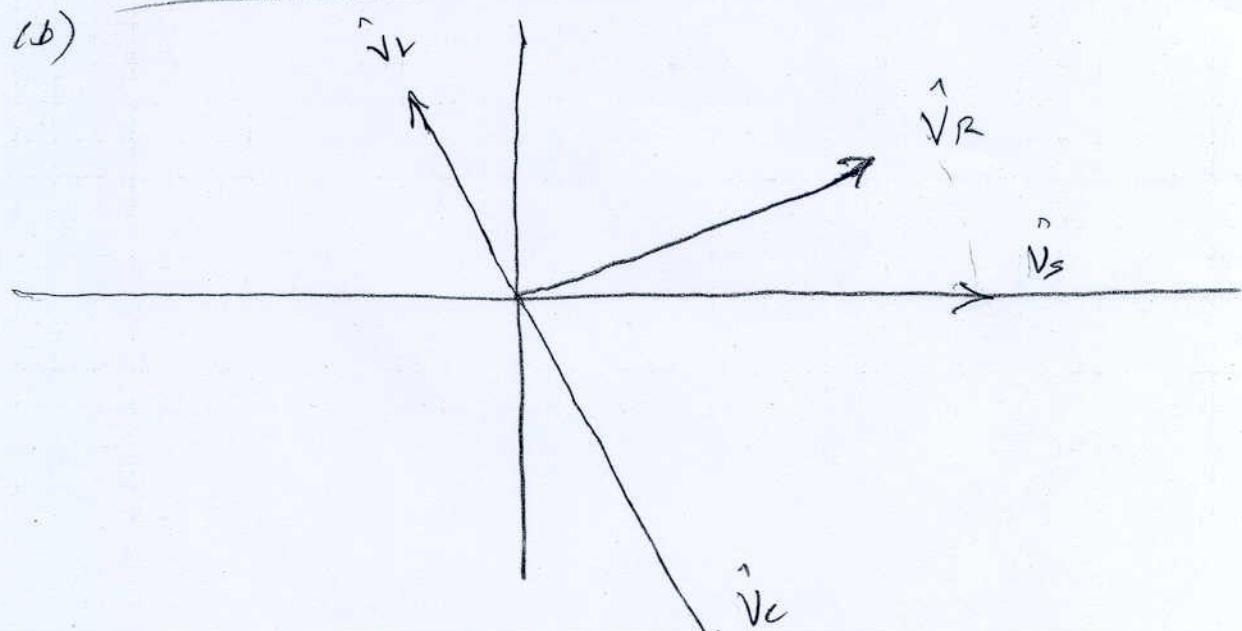

## Test A

5.2

157 cont.

We know

$$\vec{I} = \frac{V_R}{R} = \frac{85.75 \angle 30.96^\circ}{10}$$

$$\boxed{\vec{I} = 8.575 \angle 30.96^\circ \text{ A}}$$

(d)

$$V_C = I \times \left( \frac{1}{j\omega C} \right)$$

$$102.9 \angle -59^\circ = 8.575 \frac{\angle 30.96^\circ}{j200 \text{ C}}$$

$$C = \frac{8.575 \angle 30.96^\circ}{102.9 \angle (-59^\circ) (j200)}$$

$$\boxed{C = 416.67 \text{ nF}}$$