

WLY

Test B

ECE 300

Test 3B
Spring 2007

- (1) You are given the circuit of Figure 1. The make-before-break switch has been in position 1 for a very long time. At $t = 0$, the switch is moved to position 2

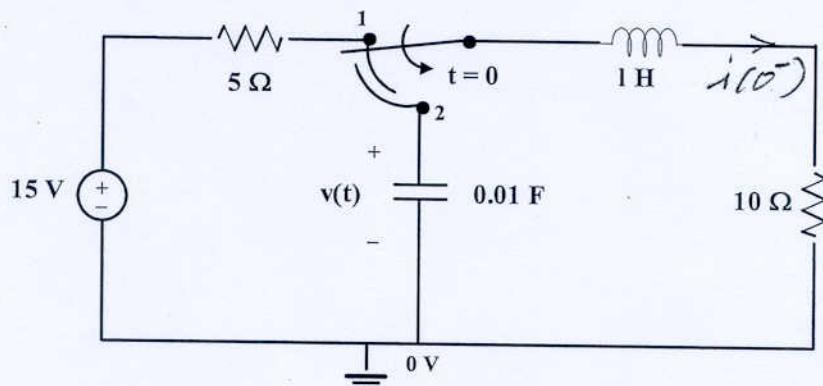


Figure 1: Circuit for Problem 1.

(a) Determine $v(0^+)$ and $\frac{dv(0^+)}{dt}$.

(b) Develop the differential equation that can be used to determine $v(t)$. The equation is of the form

$$\frac{d^2v(t)}{dt^2} + K_1 \frac{dv(t)}{dt} + K_2 v(t) = K_3$$

Determine K_1 , K_2 , and K_3 using numerical values.

(c) Give the characteristic equation and the roots of the characteristic equation.

(d) Which if the following apply?

- (i) The response for $v(t)$ is overdamped.
- (ii) The response for $v(t)$ is underdamped.
- (iii) The response for $v(t)$ is critically damped.
- (iv) Since this is a linear, time invariant, second order differential equation, none of the above apply.

(e) Determine ξ , ω_n and ω_d .

(f) Determine the solution for $v(t)$ for $t \geq 0$.


(g) Approximately how long will it take (within 20%) before the response decays to 1% of its initial value?

(a) Looking at the circuit,
 $v(0^-) = V(0^+) = 0 \text{ V}$

(1) cont

Looking at the circuit
 $t < 0$

$$i(0^-) = \frac{15}{15} = 1 \text{ A}$$

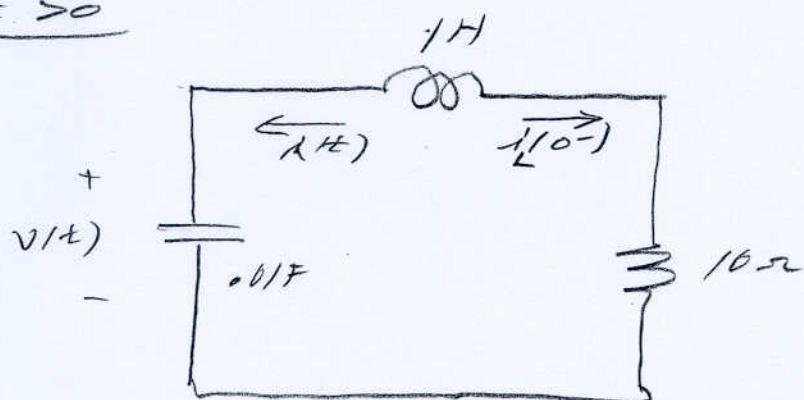 $t > 0$ 

$$L \frac{di}{dt} + V(0^+) + Ri = 0 \quad (A)$$

$$i = C \frac{dV}{dt} \quad (B)$$

$$RC \frac{dV}{dt} + LC \frac{d^2V}{dt^2} + V(0^+) = 0 \quad (C)$$

From (B)

$$i(0^+) = -i_{(0^-)} = -1 \text{ A}$$

$$i(0^+) = -i_{(0^-)} = -1 \text{ A}$$

From (B)

$$\frac{dV(0^+)}{dt} = \frac{i(0^+)}{C} = \frac{-1}{0.1} = -100 \text{ V/sec}$$

so $V(0) = 0 ; \frac{dV(0)}{dt} = -100 \text{ V/sec}$

(1) cont.

$$\frac{\partial^2 V}{\partial t^2} + \frac{R}{L} \frac{\partial V}{\partial t} + \frac{V/I}{LC} = 0$$

with numbers

$$\frac{\partial^2 V}{\partial t^2} + 10 \frac{\partial V}{\partial t} + 100 V/I = 0$$

$$s^2 + 10s + 100 = 0$$

$$(s + 5 + j8.66)(s + 5 - j8.66) = 0$$

$$(b) \quad \frac{\partial^2 V}{\partial t^2} + 10 \frac{\partial V}{\partial t} + 100 V/I = 0$$

$$K_1 = 10, \quad K_2 = 100, \quad K_3 = 0$$

(c) characteristic eq:

$$s^2 + 10s + 100 = 0$$

$$s_1 = -5 - j8.66$$

$$s_2 = -5 + j8.66$$

(d) underdamped

$$(e) \quad \omega_n^2 = 100$$

$$\boxed{\omega_n = 10}$$

$$\sqrt{\omega_n} = 10$$

$$\boxed{\zeta = 0.5}$$

$$\zeta \omega_n = 5 \text{ check}$$

$$\omega_d = 10 \sqrt{1 - 0.5^2} = 8.66 \text{ check}$$

(1) cont

(F)

$$v(t) = e^{-\frac{1}{2} \omega_0 t} [B_1 \cos \omega_0 t + B_2 \sin \omega_0 t]$$

$$v(t) = e^{-5t} [B_1 \cos \omega_0 t + B_2 \sin \omega_0 t]$$

$$\text{at } t=0 : v(0) = 0$$

$$\boxed{0 = B_1}$$

$$v(t) = e^{-5t} B_2 \sin \omega_0 t$$

$$\frac{dv}{dt} = e^{-5t} \omega_0 B_2 \cos \omega_0 t - 5e^{-5t} B_2 \sin \omega_0 t$$

$$\text{at } t=0^+$$

$$\frac{dv(0^+)}{dt} = -100 = \omega_0 B_2$$

$$B_2 = \frac{-100}{8.66} = -11.55$$

$$v(t) = -e^{-5t} [11.55 \sin 8.66t] \quad V$$


$$(2) e^{-4} \quad (t = \frac{4}{5}) = 0.183 = 1.83\%$$

$$e^{-5} \quad (t = 1) = 0.0067 = 0.67\%$$

$100 > t > .8$ will take it to
less than 1%

Test B

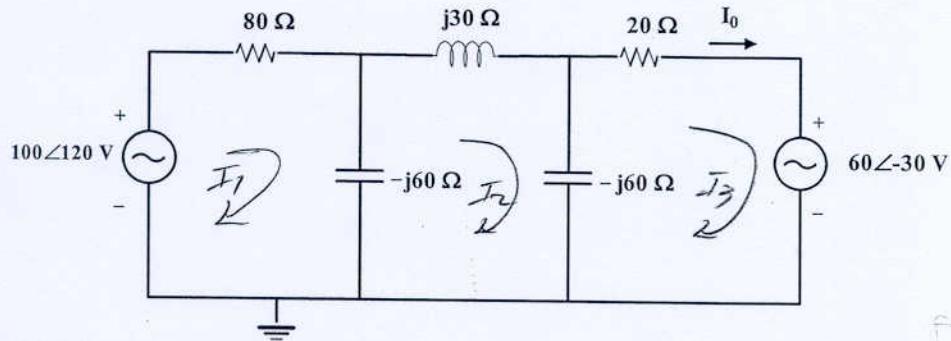- (2) Use mesh analysis to find the phasor current \mathbf{I}_0 shown in the circuit of Figure 2. Express your answer in polar form.



Need I_3

mesh 1

$$\begin{aligned} \cancel{80I_1 - j60(I_1 - I_2) = 100 \angle 120^\circ} \\ \cancel{(80 - j60)I_1 + j60I_2 + 0I_3 = 100 \angle 120^\circ} \end{aligned}$$

mesh 2

$$\begin{aligned} \cancel{-j60(I_2 - I_1) + j30I_2 - j60(I_2 - I_3) = 0} \\ \cancel{j60I_1 - j90I_2 + j60I_3 = 0} \end{aligned}$$

mesh 3

$$\begin{aligned} \cancel{-j60(I_3 - I_2) + 20I_3 = -60 \angle -30^\circ} \\ \cancel{0I_1 + j60I_2 + (20 - j60)I_3 = -60 \angle -30^\circ} \end{aligned}$$

$$\begin{bmatrix} 80 - j60 & j60 & 0 \\ j60 & -j90 & j60 \\ 0 & j60 & 20 - j60 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 100 \angle 120^\circ \\ 0 \\ -60 \angle -30^\circ \end{bmatrix}$$


$$I_1 = -0.356 + j1.464$$

$$I_2 = -0.864 + j1.823$$

$$I_3 = -0.9407 + j1.27 = \sqrt{1.58} \angle 126.5^\circ A = I_0$$

Test B

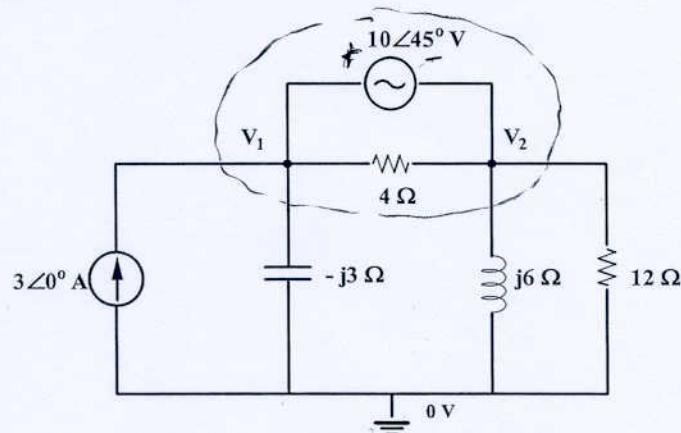- (3) You are given the circuit of Figure 3. Use Nodal Analysis to find the phasor voltages V_1 and V_2 . Express your answers in polar form.



Super node

$$\frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12} = 3$$

$$j0.333V_1 - j0.1667V_2 + 0.08333V_2 = 3$$

$$j0.333V_1 + (0.08333 - j0.1667)V_2 = 3$$

constraint

$$V_1 - 10\angle45^\circ - V_2 = 0$$

$$\begin{bmatrix} j0.333, (0.08333 - j0.1667) \\ 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 \\ 10\angle45^\circ \end{bmatrix}$$

$$V_1 = 25.8\angle-70.43^\circ \quad \checkmark$$

$$V_2 = 31.45\angle-87.13^\circ \quad \checkmark$$

Test B

(4) You are given the AC circuit shown in Figure 4. The following phasor voltages are known.

$$V_s = 100\angle 0^\circ V; \quad V_R = 44.8\angle -63.43^\circ V; \quad V_L = 156.8\angle 26.57^\circ V$$

The source frequency is 300 rad/sec.

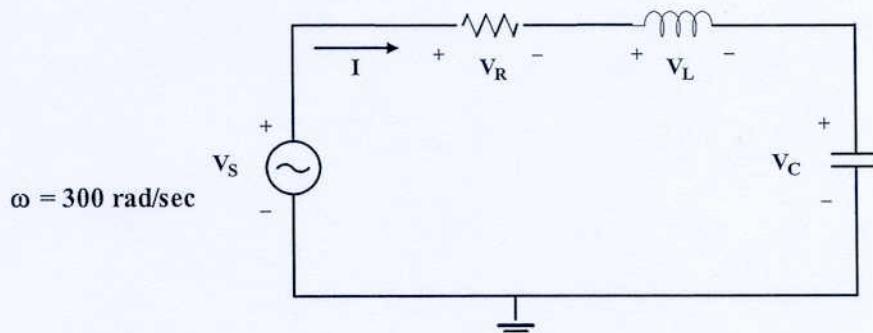


Figure 4: Circuit for Problem 4.

- (a) Solve for the phasor voltage V_C . Express your answer in polar form.
- (b) Draw the phasor diagram (close to scale) showing V_s , V_R , V_L , and V_C .
- (c) Determine the phasor current I shown in the diagram. Express your answer in polar form.
- (d) Determine the value of the capacitor C, expressed in μF .


(a)

$$V_C = V_s - V_R - V_L$$

$$= 100 - 44.8 \angle -63.43^\circ - 156.8 \angle 26.57^\circ$$

$$V_C = 67.36 \angle -153.5^\circ V$$

(b)

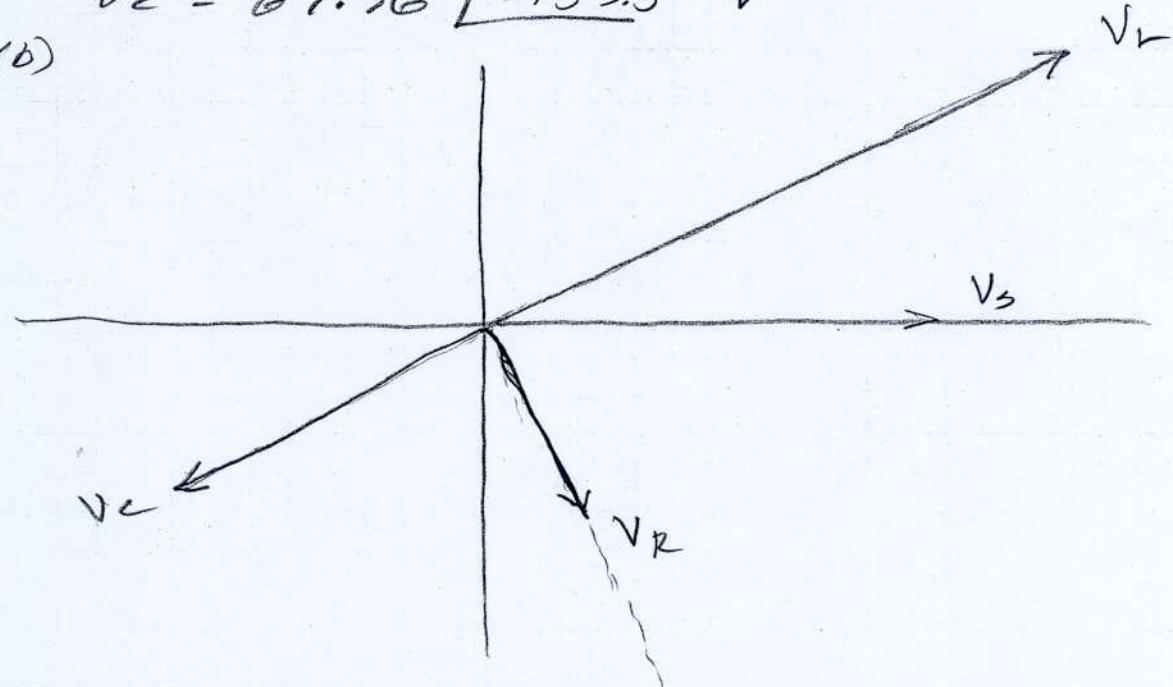

Test B

4.2

(4) cont.

(c)

$$I = \frac{V_R}{R} = \frac{44.8}{10} \angle -63.43^\circ$$

$$I = 4.48 \angle -63.43^\circ A$$

(d)


$$V_C = I \times \left(\frac{1}{j\omega C} \right)$$

$$C = \frac{I}{V_C (j\omega)} = \frac{4.48 \angle -63.43^\circ}{67.36 \angle -153.5^\circ (j300)}$$

$$C = 22.17 \mu F$$

Test B

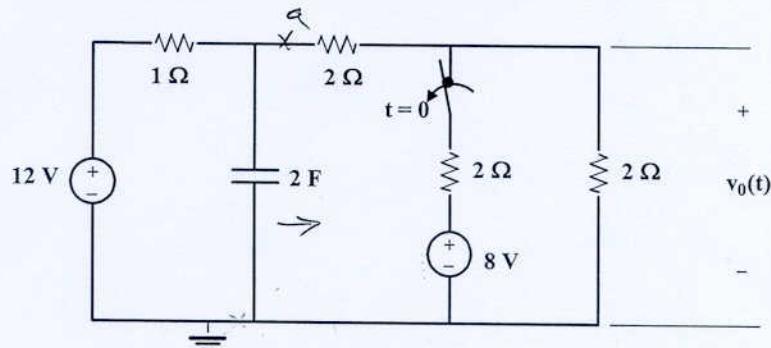- (5) You are given the circuit shown in Figure 5. The switch has been closed for a very long time and is opened at $t=0$. Use the step-by-step method to find $v_o(t)$.




Get the Thevenin to the right of "a"

$$R_{TH} = 2 + 2/2 = 3\Omega$$

$$V_{TH} = \frac{8 \times 2}{4} = 4V$$

$t < 0$

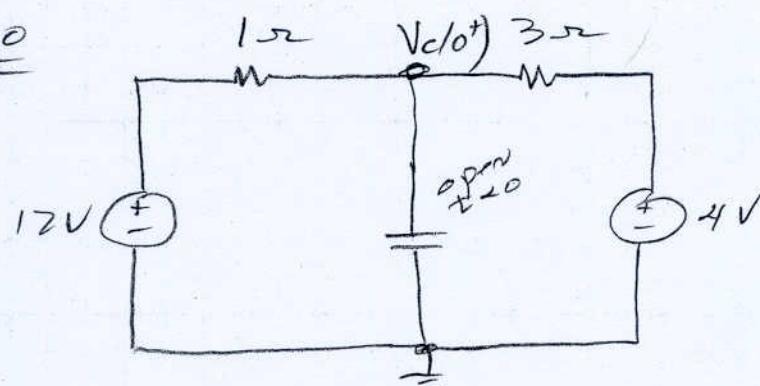


$$\frac{V_c(0^+) - 12}{1} + \frac{V_c(0^+) - 4}{3} = 0$$

$$4V(0^+) = 40$$

$$V_c(0^+) = 10V$$

$t > 0$

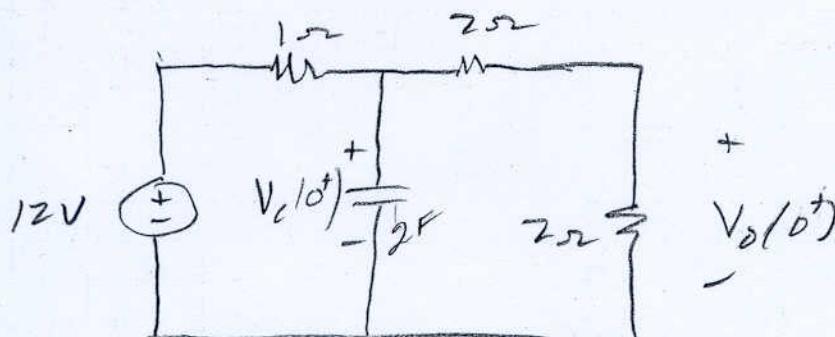

(5) cont

$$V_o(10^+) = \frac{2 \times V_o(10^+)}{2+2} = 0.5 V_o(10^+)$$

$$\boxed{V_o(10^+) = 0.5 \times 10 = 5 V}$$

$$V_o(100) = \frac{12 \times 2}{2+2+1} = \frac{24}{5} = 4.8 V$$

$$\boxed{V_o(100) = 4.8 V}$$

$$R_{eq} = 1 \parallel 4 = \frac{4}{5} = 0.8$$

$$T = R_{eq} C = 0.8 \times 2 = 1.6$$

so

$$V(t) = V(\infty) + [V_o(0^+) - V_o(\infty)] e^{-\frac{t}{T}}$$

$$V(t) = 4.8 + [5 - 4.8] e^{-0.625t} V$$

$$\boxed{V(t) = 4.8 + 0.2 e^{-0.625t} V}$$