

Desk Copy

ECE 300
Spring Semester, 2008
HW Set #3

Due: February 11, 2008
wlg

Name wlg
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.


PP means Practice Problem:

- ✓ PP 4.2 p. 130: linearity
- ✓ PP 4.3 p. 132: superposition
- ✓ 4.26 source transformation: Ans: $i_o = 636 \text{ mA}$
- ✓ PP 4.8 p. 142: Thevenin:
- ✓ PP 4.9 p. 143: Thevenin: Also use **P-spice** to simulate this circuit and actually find V_{TH} from the open circuit voltage. Also, find I_N as the short circuit current from the simulation. Verify R_{TH} from your simulation. Submit diagrams to verify your P-spice work.
- ✓ PP 4.10 p. 145: Thevenin:
- ✓ 4.45 Thevenin and Norton: Work by both Norton and Thevenin. Actually find I_N by finding the short circuit current and find V_{TH} by actually finding the open circuit voltage.
Ans: $I_N = 2 \text{ A}$, $R_{TH} = 3 \Omega$, V_{TH} on your own.
- ✓ 4.46 Thevenin and Norton: Work this by both Norton and Thevenin: Ans: $I_N = 2 \text{ A}$, $R_{TH} = 10 \Omega$
 V_{TH} on your own.
- ✓ 4.50 Norton: Find I_N as the short circuit current, directly, by using circuit theory. Find V_{TH} by actually finding the open circuit voltage. Verify that $I_N = V_{TH}/R_{TH}$. Ans: $I_N = -0.4 \text{ A}$
 $R_{TH} = 10 \Omega$.
- ✓ 4.72 Thevenin: Ans: (a) $V_{TH} = 40 \text{ V}$, $R_{TH} = 12 \Omega$, (b) $I = 2 \text{ A}$, (c) $R_{TH} = 12 \Omega$, (d) $P = 33.3 \text{ W}$
- ✓ 4.85 Thevenin: Ans: (a) $V_{TH} = 24 \text{ V}$, $R_{TH} = 30 \text{k}\Omega$; (b) $V_{ab} = 9.6 \text{ V}$

ECE 300
H.W. #4

P.P. 4.2

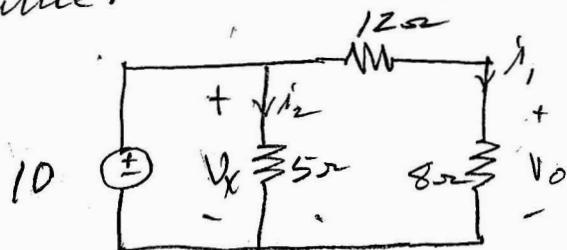For the following circuit, assume $V_b = 1V$ and use linearity to calculate the actual value.



$$\text{With } V_o = 1V,$$

by voltage division

$$V_o = 1V = \frac{V_x 8}{8 + 12} = \frac{V_x 8}{20} = 0.4V_x$$

$$\therefore V_x = \frac{1}{0.4} = 2.5$$

$$\frac{10}{V_x} = \frac{V_o}{1}$$


$$\text{or, } V_o = \frac{10}{V_x} = \frac{10}{2.5} = 4V$$

$$\boxed{V_o = 4V}$$


There are other ways to do the problem.

P.P. 4.3

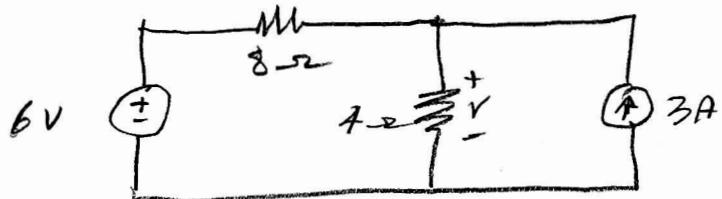In the following circuit, use superposition to find V_1 .




Suppress the 3A source

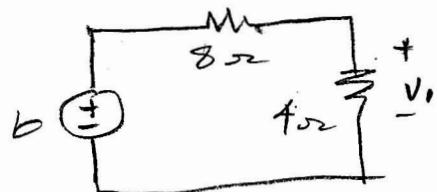

$$V_1 = \frac{6 \times 4}{4+8} = 2V$$

Suppress the 6V source

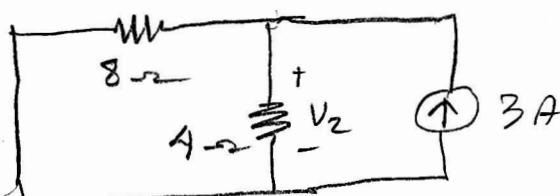

Using current division;



$$V_2 = \left(\frac{3 \times 8}{4+8} \right) \times 4 = \frac{24}{12} \times 4 = 8V$$

$$V = V_1 + V_2 = 2 + 8 = 10V$$

$V = 10V$

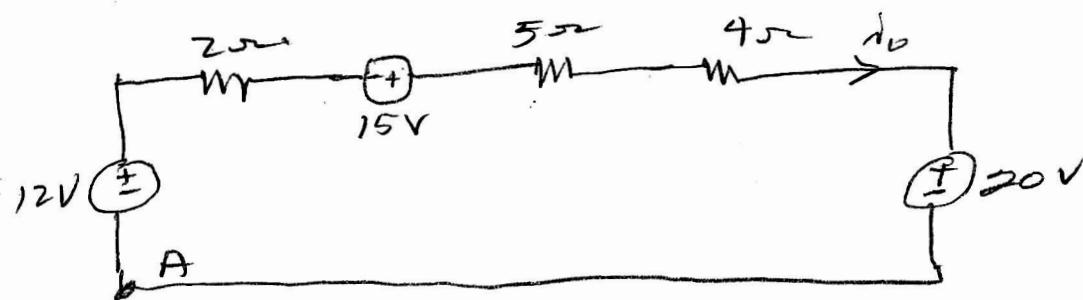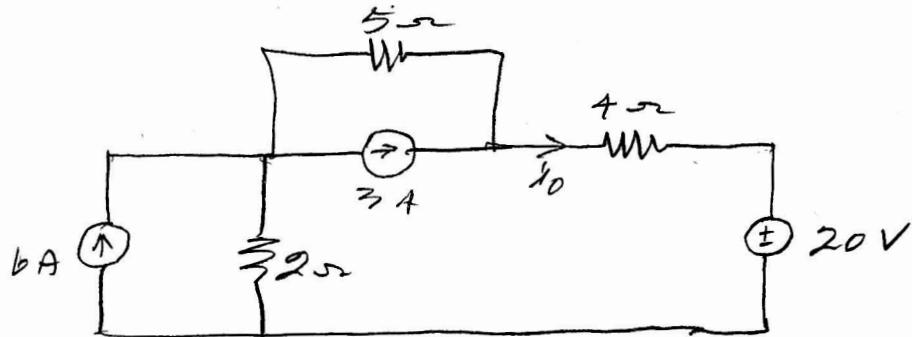4.26

use source transformation to find i_0 in the following circuit.



Start at A, clockwise, Σ drops = 0


$$-12 + 2i_0 - 15 + 5i_0 + 4i_0 + 20 = 0$$

$$11i_0 = 7$$

$$\boxed{i_0 = 63.64 \text{ mA}}$$

PP 4.8

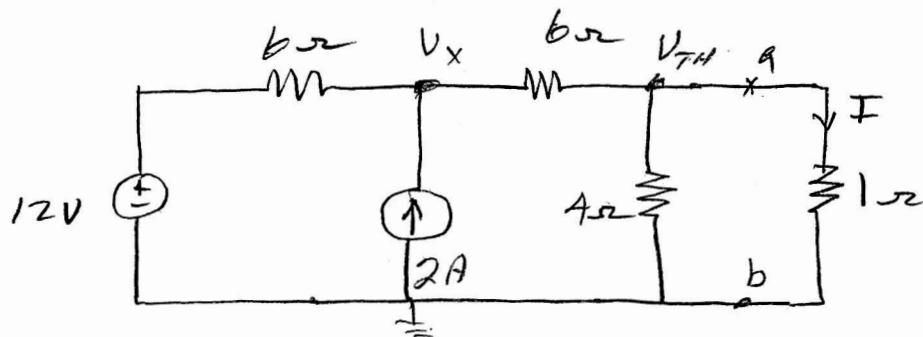For the circuit below, find the Thevenin equivalent circuit to the left of a-b
then use the circuit to find I.



Practically by inspection,

$$R_{TH} = 4 \parallel 12 = 3 \Omega$$

To find V_{TH} .

With 1 Ω removed, we have


$$30 / \frac{V_x - 12}{6} + \frac{V_x}{10} - 2 = 0$$

$$5V_x - 60 + 3V_x - 60 = 0$$

$$8V_x = 120$$

$$V_x = 15 \text{ V}$$

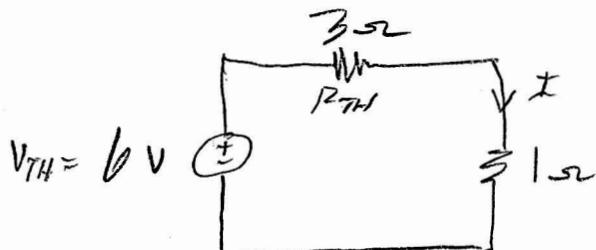
$$V_{TH} = \frac{V_x \times 4}{4+6} = \frac{15 \times 4}{10} = 6 \text{ V}$$



$$I = \frac{6}{4} = 1.5 \text{ A}$$

PP 4.9

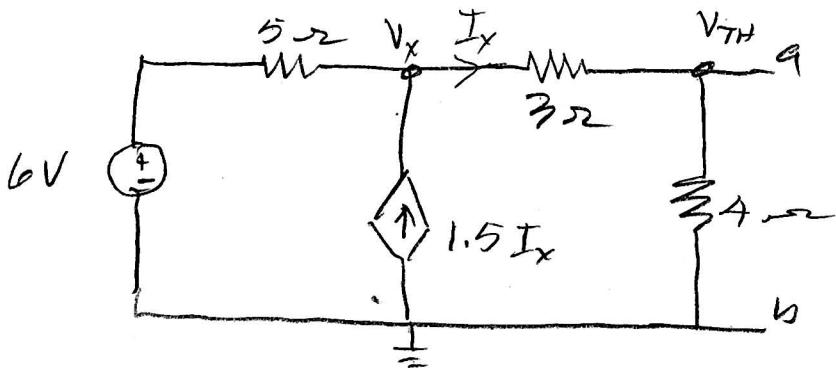Find the Thevenin equivalent circuit to the left of terminals a-b.



$$\frac{V_x - 6}{5} + \frac{V_x}{7} - 1.5I_x = 0$$

$$I_x = \frac{V_x}{7}$$

$$35\left(\frac{V_x - 6}{5} + \frac{V_x}{7} - \frac{1.5V_x}{7}\right) = 0$$

$$7V_x - 42 + 5V_x - 7.5V_x = 0$$

$$4.5V_x = 42$$


$$V_x = 9.33V$$

$$V_{TH} = \frac{4 \times V_x}{3+4} = 5.33V$$

To find R_{TH} , find I_{SC} and use

$$R_{TH} = \frac{V_{TH}}{I_{SC}}$$

PP 4.9 continued

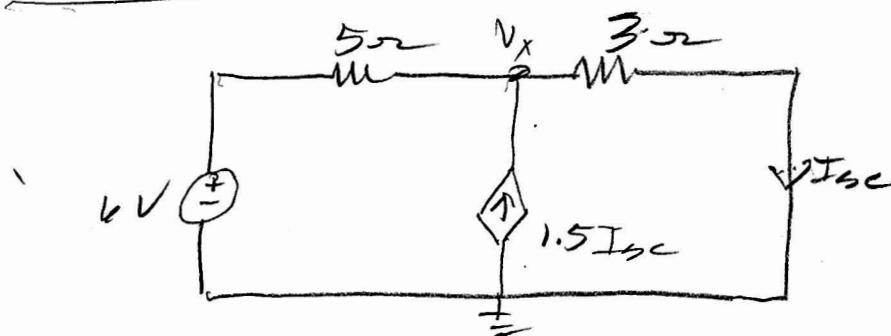

$$\frac{V_x - 6}{5} + \frac{V_x}{3} - 1.5 I_{sc} = 0$$

$$I_{sc} = \frac{V_x}{3}$$

$$15 \left(\frac{V_x - 6}{5} + \frac{V_x}{3} - \frac{1.5 V_x}{3} \right) = 0$$

$$3 V_x - 18 + 5 V_x - 7.5 V_x = 0$$

$$0.5 V_x = 18$$


$$V_x = 36 \text{ V}$$

$$I_{sc} = \frac{V_x}{3} = 12 \text{ A}$$


$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{5.33 \text{ V}}{12 \text{ A}} = 0.44 \Omega$$



Thevenin
equivalent
circuit

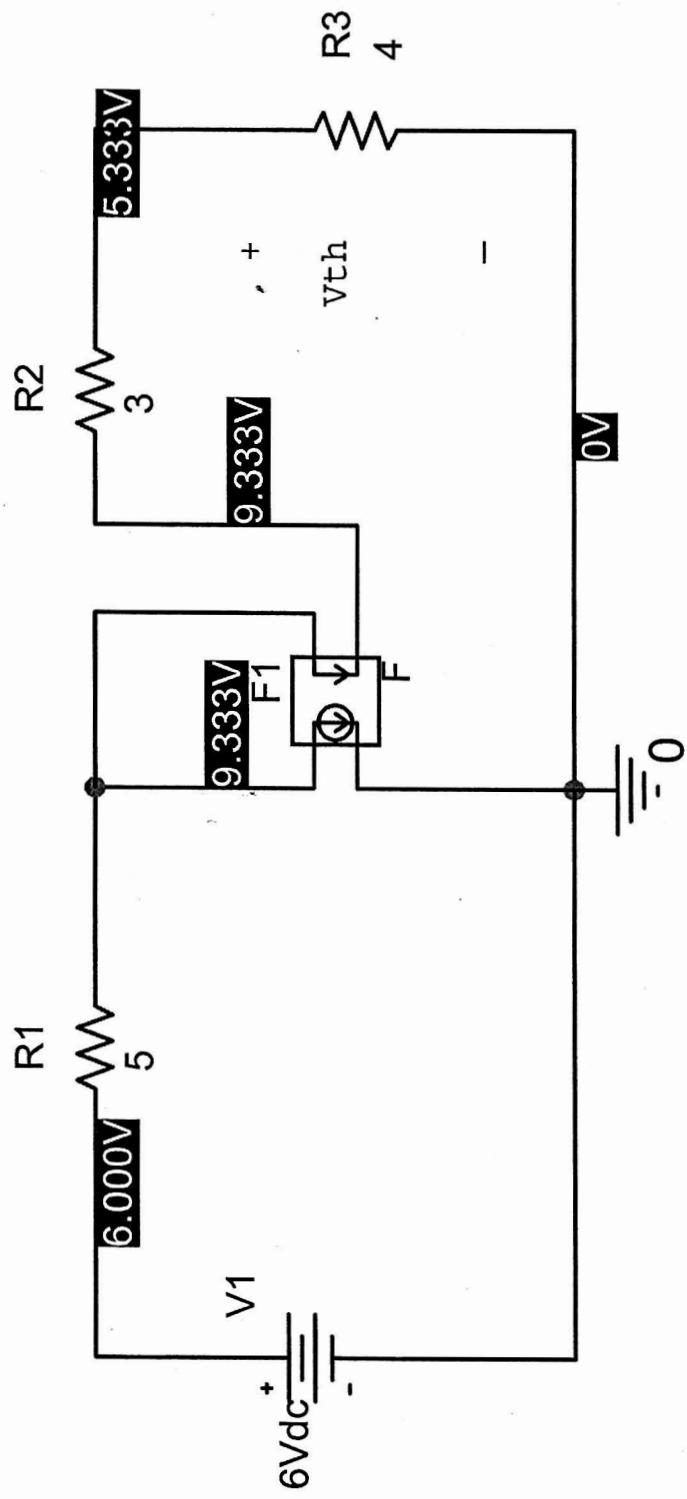


Circuit for finding V_{th}

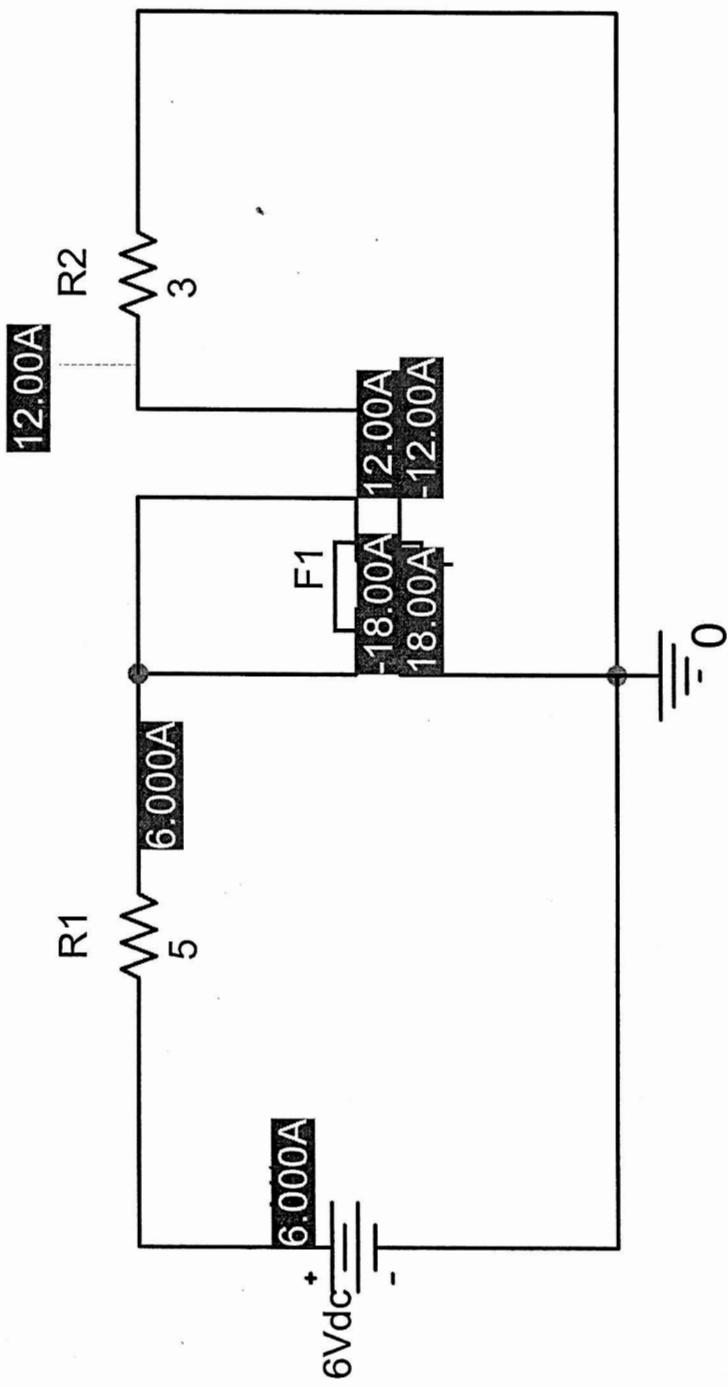

Circuit for getting I short circuit

PP 4.10

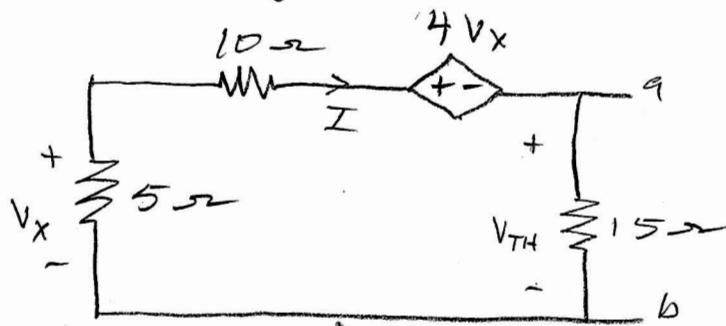Find the Thevenin equivalent for the following.



First find V_{TH}

$$5I + 10I + 4V_x + 15I = 0$$

$$V_x = -5I$$

so,


$$5I + 10I - 20I + 15I = 0$$

As expected, $10I = 0$ (no juice!)

$$I = 0$$

$$\therefore V_{TH} = 0$$

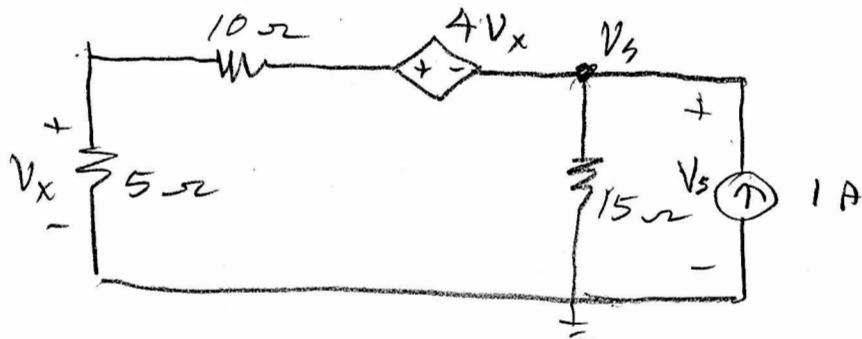Use the following circuit to find R_{TH} .



$$R_{TH} = \frac{V_s}{I}, \text{ since } V_s$$

PP 4.10 cont.

Using nodal analysis:

$$\left(\frac{V_s + 4V_x}{15} + \frac{V_s}{15} - 1 = 0 \right) \quad \#1$$

$$V_x = \left(\frac{V_s + 4V_x}{15} \right)_x 5 = \frac{V_s + 4V_x}{3}$$

$$3V_x = V_s + 4V_x$$

$$V_x = -V_s$$

Back to #1

$$15 \left(\frac{V_s - 4V_s}{15} + \frac{V_s}{15} - 1 = 0 \right)$$

$$V_s - 4V_s + V_s - 15 = 0$$

$$-2V_s = 15$$

$$V_s = -7.5 V$$


$$\therefore R_{TH} = \frac{V_s}{I} = \frac{-7.5}{1} = -7.5 \Omega$$

$$\boxed{R_{TH} = -7.5 \Omega}$$

4.45

Find the Norton equivalent circuit for the following. Find both V_{TH} & I_{TH} circuits.


Thevenin

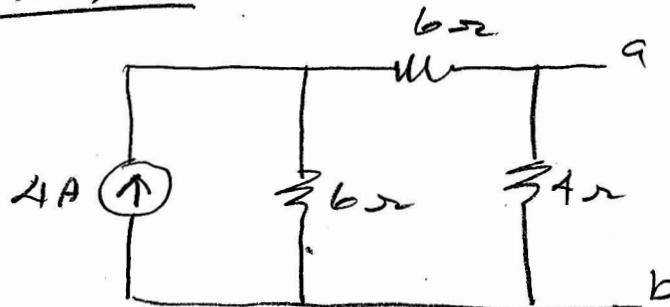

Using current division;

$$V_{ab} = \left(\frac{4 \times 6}{10 + 6} \right) \times 4 = \frac{24 \times 4}{16} = 6V = V_{TH}$$

$$R_{TH} = 4 // 12 = 3\Omega$$

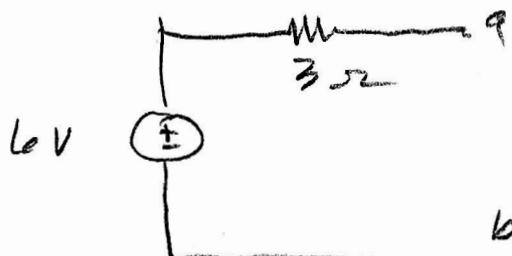

Norton


Find I_{SC}



4.45 cont

$$I_{oc} = 2A \quad (\text{Inspection})$$

Norton Circuit

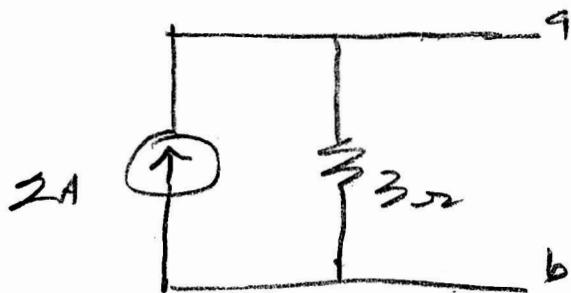


Source transformations shows we
can go from Norton \leftrightarrow Thevenin

4.46

Find the Norton and Thevenin equivalent for the following circuit.

Thevenin

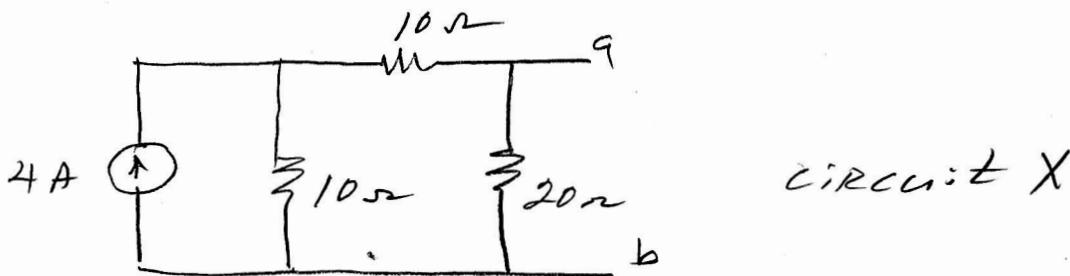


Almost the same problem as 4.45

Mentally doing a source transformation and applying.



$$V_{TH} = 20 \text{ V} \quad (\text{inspection})$$

$$R_{TH} = 20\parallel 20 = 10 \Omega$$

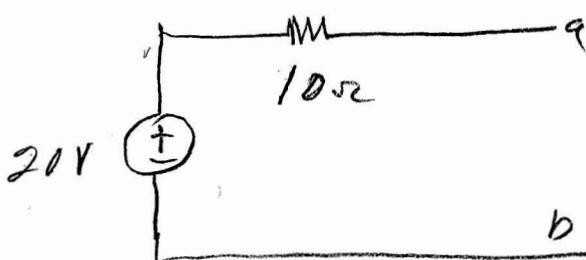

Thevenin
equivalent
circuit

4.46 cont

2


Norton:

Back to circuit X; use current division to get I_{sc} .

Putting a short across a-b, shorts out the 20Ω resistor. So,

$$I_{sc} = \frac{4 \times 10}{20} = 2A = I_N$$


We already found R_N .

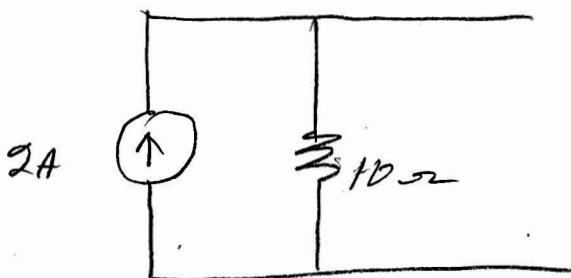

Norton equivalent circuit

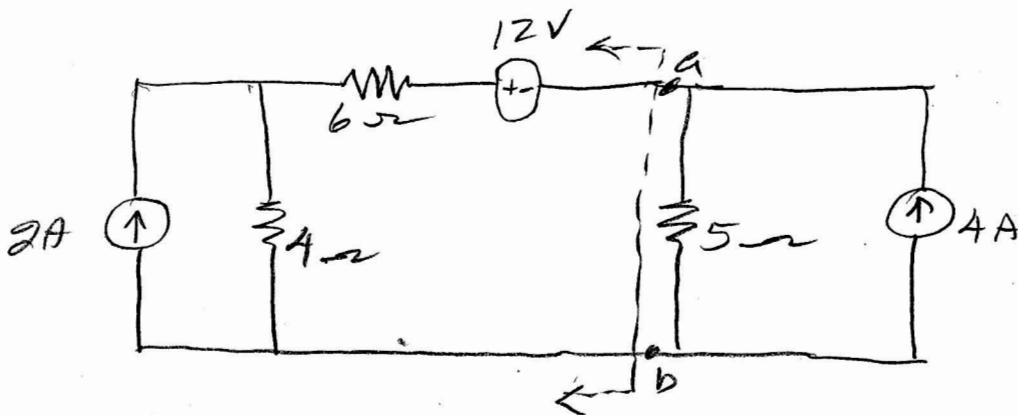
4.50

Obtain the Norton equivalent circuit for the following, as shown, then find




$$R_{TH} = 10 \Omega \quad (\text{inspection})$$

To find I_{SC} , make a transformation, solve

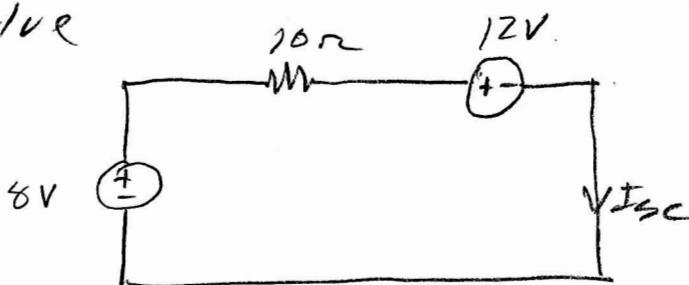

Circuit X

$$I_{SC} = \frac{-4}{10} = -0.4$$

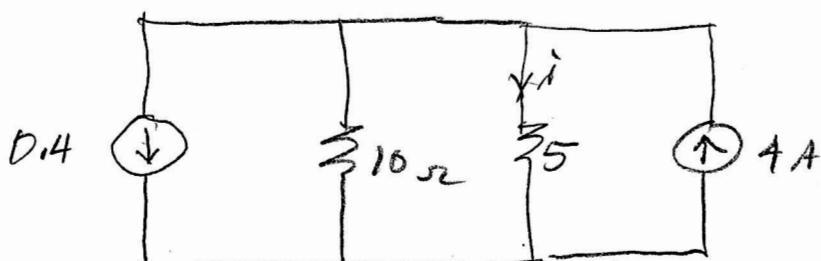


By current division

$$i = \frac{(4 - 0.4) \times 10}{15} = \frac{36}{15} = 2.4 A$$

4.50


Thevenin

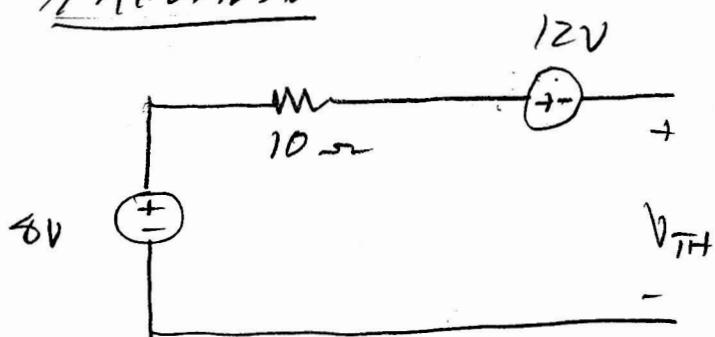


$$V_{TH} = 8 - 12 = -4V$$

$$\therefore I_N = \frac{V_{TH}}{R_{TH}} = \frac{-4}{10} = -0.4A$$

Norton Circuit

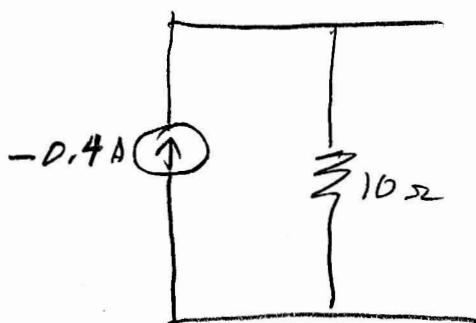


Thevenin Circuit

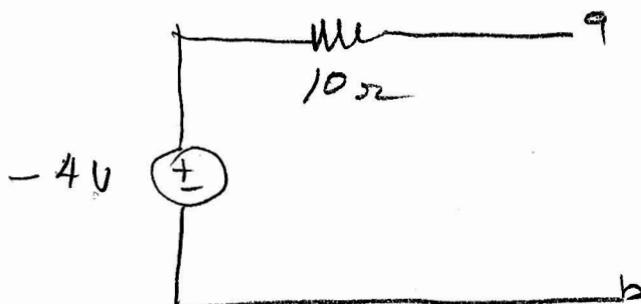


4.72

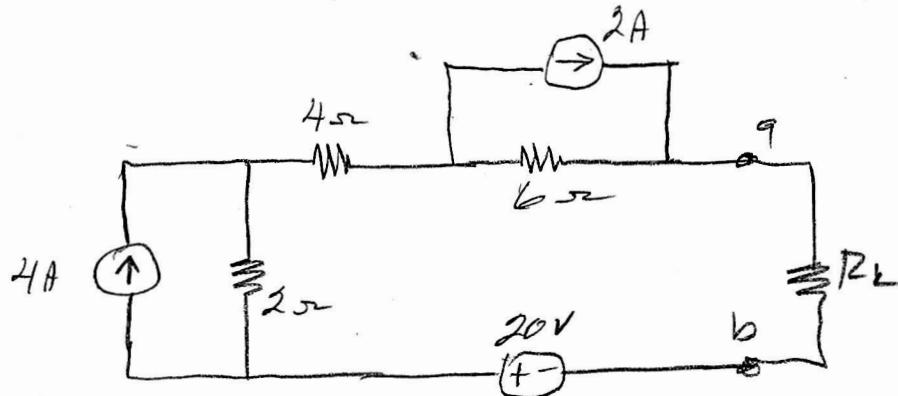- (a) For the following circuit obtain the Thvenin equivalent circuit of terminals a-b.
- (b) Calculate the current in $R_L = 8\Omega$
- (c) Find R_L for maximum power transfer.
- (d) Determine the maximum power.




(a)

With source transformation,

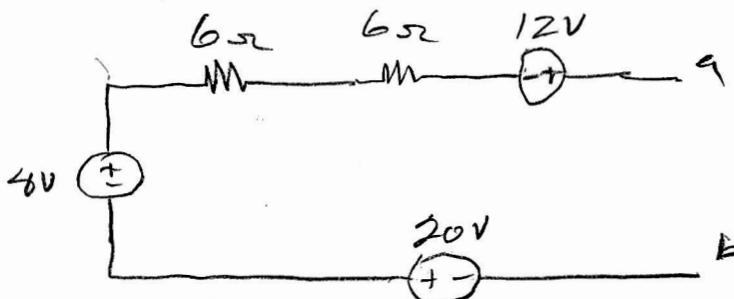
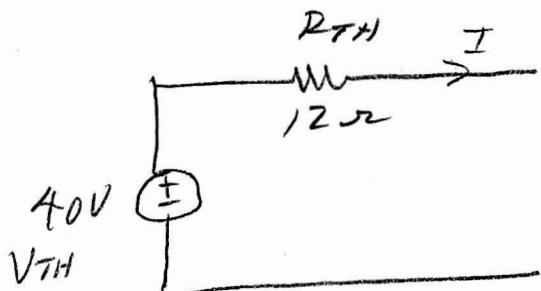
$$V_{OC} = V_{TH} = 40V; \quad R_{TH} = 12\Omega$$



Thvenin equivalent circuit.

4.72 cont.

2

(b) With 8Ω attached to the Thévenin circuit, between terminals ab,

$$I = \frac{40}{20} = 2A$$

(c) Find R_L for maximum power transfer.

$$R_L = R_{TH} = 12\Omega$$

(d) Find this power.

A general expression for this is

$$P_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \times R_L = \left(\frac{V_{TH}}{2R_{TH}} \right)^2$$

$$P_L = \frac{V_{TH}^2}{4R_{TH}}$$

$$P_L = \frac{40^2}{4 \times 12} = \frac{40^2}{48} = 33.33W$$

$$\boxed{P_L = 33.33 W}$$

4.85

The Thevenin equivalent circuit at terminals a-b of the linear network shown below is to be determined by measurement.


When $10\text{-k}\Omega$ is connected to terminals a-b
the voltage, V_{ab} is measured as $6V$.

When $30\text{ k}\Omega$ is connected to terminals a-b
then V_{ab} is measured as $V_{ab} = 12V$.

Determine,

(a) the Thevenin equivalent at terminals a-b

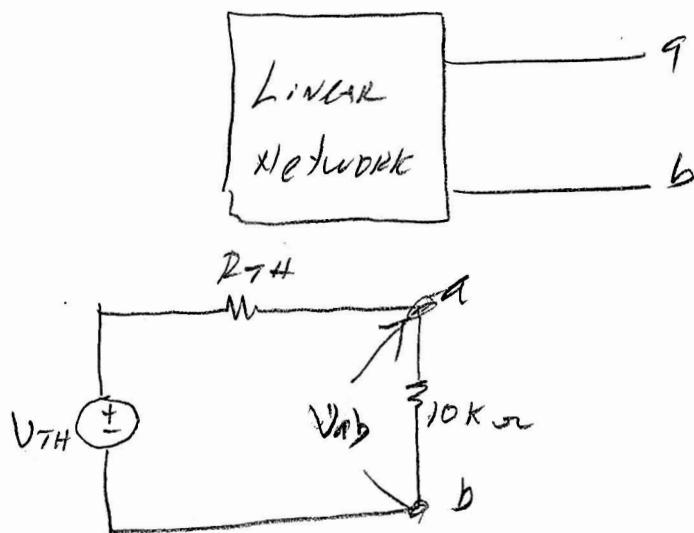(b) V_{ab} when a $20\text{k}\Omega$ resistor is connected to terminals a-b.




$$V_{ab} = \frac{V_{TH} \times 10K}{10K + 20K} = 6V$$

$$10K V_{TH} - 6 R_{TH} = 60K$$

Eq. 11)

4.85 cont

2

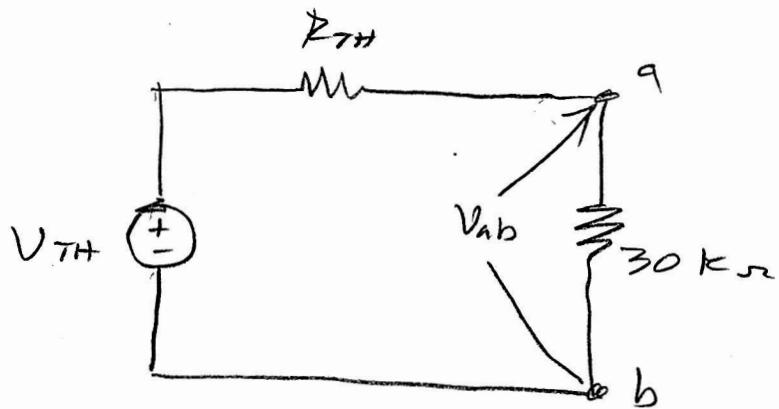

$$V_{ab} = \frac{V_{TH} \times 30k}{R_{TH} + 30k} = 12V$$

or


$$30k V_{TH} - 12 R_{TH} = 360k \quad \text{Eq 1/2)$$

From Equations (1) and (2)

$$\begin{bmatrix} 10k & -6 \\ 30k & -12 \end{bmatrix} \begin{bmatrix} V_{TH} \\ R_{TH} \end{bmatrix} = \begin{bmatrix} 60k \\ 360k \end{bmatrix}$$

$$\boxed{V_{TH} = 24V}; \quad \boxed{R_{TH} = 30k\Omega}$$

16)

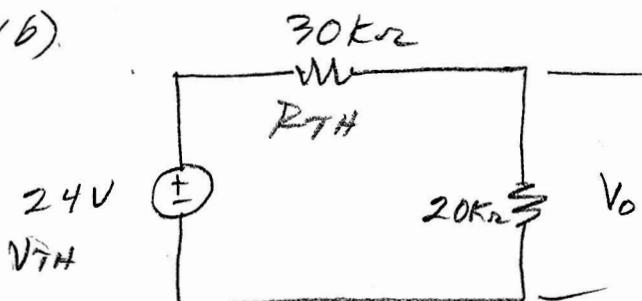

$$\boxed{V_o = \frac{24 \times 20k}{50k} = 9.6V}$$