


ECE 300
 Spring 2008
 Test 2A

W/g

- (1) You are given the op amp circuit of Figure 1. Use ideal op amp assumptions in answer the following questions. V_o can be expressed in the following form:

$$V_o = [A]V_1 + [B]V_2$$

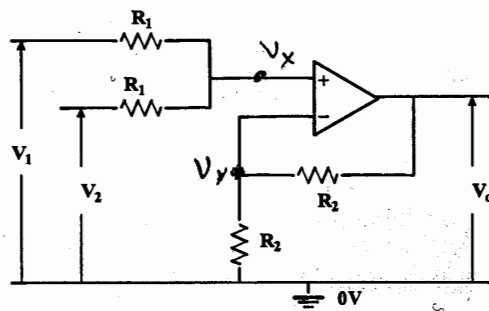- (a) Find the coefficients [A] and [B].
 (b) If $V_1 = 2V$ and $V_2 = 5V$, given the value of V_o .



$$(a) V_x = \frac{V_o R_2}{R_2 + R_2} = \frac{V_o}{2} \quad (1)$$

We also can write;

$$\frac{V_x - V_1}{R_1} + \frac{V_x - V_2}{R_1} = 0$$

$$\text{OR} \quad 2V_x - V_1 - V_2 = 0 \quad (2)$$

substitute (1) into (2);

$$V_o = V_1 + V_2$$

(b) If $V_1 = 2V$, $V_2 = 5V$;

$$V_o = 2 + 5 = 7V$$

Test 2A



(2) For the following problems assume ideal op amps.

(a) Design an inverting op amp circuit using a single op amp such that the gain is given by

$$\frac{V_o}{V_{in}} = +5$$

Show (draw) your op amp circuit and give the values of all resistors on your circuit diagram. Also, show on your diagram, an appropriate ground along with V_o and V_{in} .

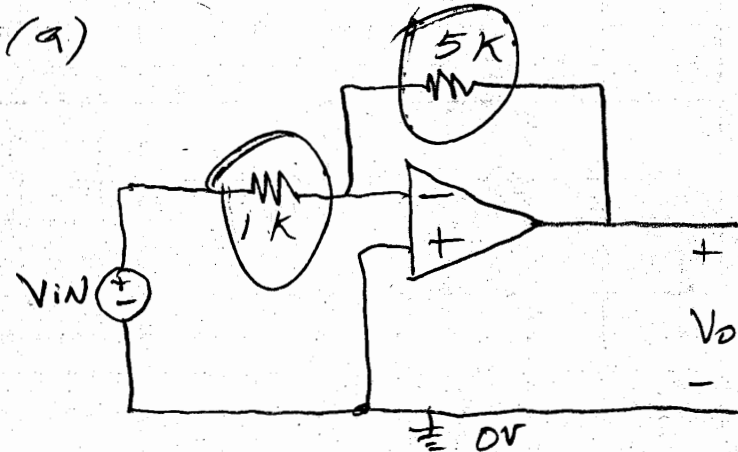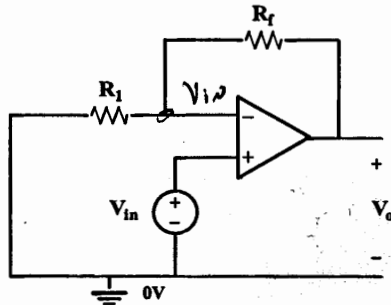(b) You are given the non-inverting op amp circuit shown in Figure 2(b). Determine values of R_f and R_1 so that $V_o = 5V_{in}$. You are restricted to resistors of values 1 k Ω , 2 k Ω , 3 k Ω , 4 k Ω and 5 k Ω .



(b) We have

$$\frac{V_{in}}{R_1} + \frac{V_{in} - V_o}{R_f} = 0$$

OR

$$V_o = R_f \left(\frac{V_{in}}{R_1} + \frac{V_{in}}{R_f} \right) = \left(1 + \frac{R_f}{R_1} \right) V_{in}$$

make $\frac{R_f}{R_1} = 4$ with $R_f = 4k\Omega, R_1 = 1k\Omega$

$$V_o = 5 V_{in}$$

Test 2A

(3) You are given the following circuit.


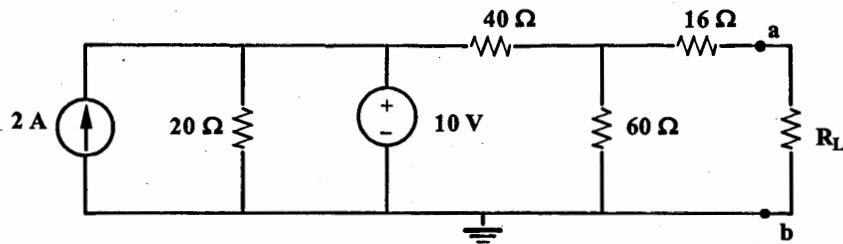


Figure 3: Circuit for Problem 3.

- Determine V_{TH} and R_{TH} looking into terminals a-b with R_L removed.
- Draw your Thevenin circuit. Show V_{TH} and R_{TH} on the circuit diagram connected to R_L .
- Assign a value of R_L that will give maximum power transfer to R_L and Determine this value of power.

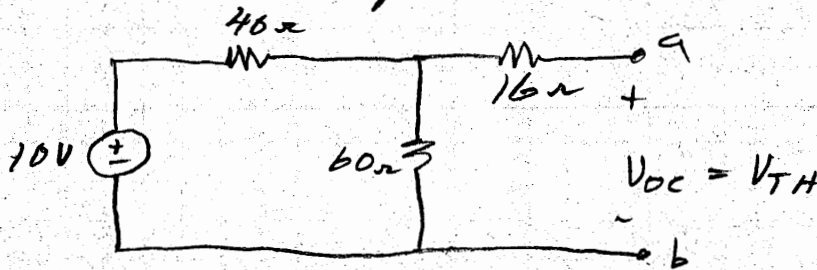
For purposes of finding V_{TH} and R_{TH} , the circuit above is equivalent to the following:



(a) We have;

$$V_{OC} = V_{TH} = \frac{10 \times 60}{40 + 60} = 6V$$

To find R_{TH} ;

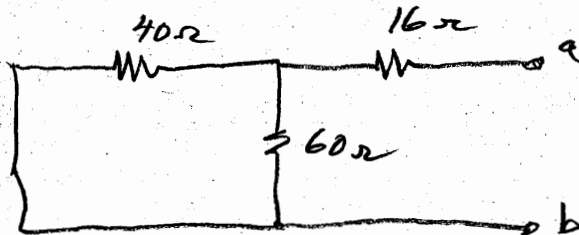

$$R_{TH} = 40 \parallel 60 + 16 = \frac{2400}{100} + 16 = 40\Omega$$


$$V_{TH} = 6V$$

$$R_{TH} = 40\Omega$$

Test 2A


(3) cont.

(b)

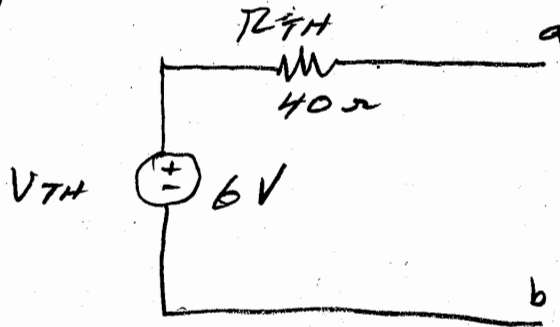

(c) Make $R_L = 40\Omega$;

We then have

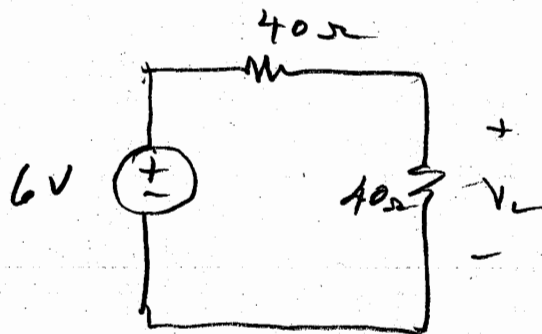

$$V_L = 3V$$

$$P_{out} = \frac{V_L^2}{40} = \frac{9}{40} = 0.225W$$

$$P_{out} = 0.225W$$

Test 2A

(4) You are given the circuit of Figure 4. Assume that the circuit is in steady state.


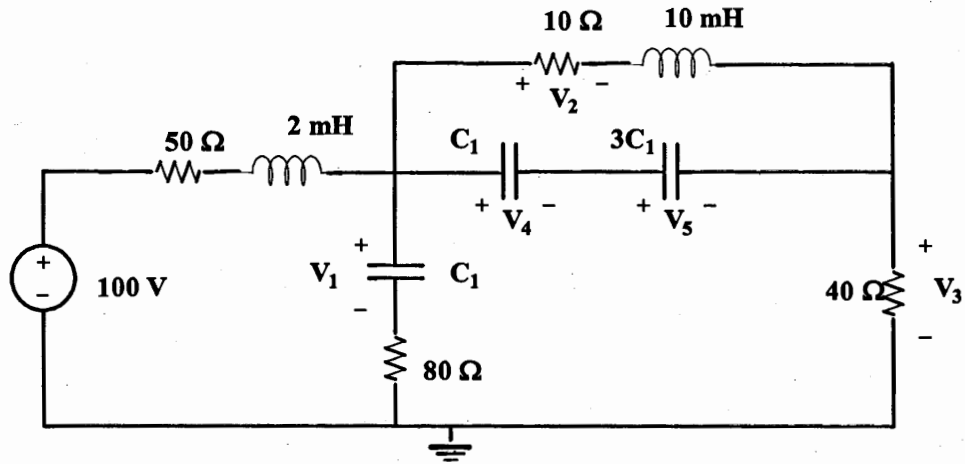


Figure 4: Circuit for Problem 4.


C_1 can be any value you want to use between $1\mu\text{F}$ and $10\mu\text{F}$. You are required to find the values of V_1, V_2, V_3, V_4 and V_5 .

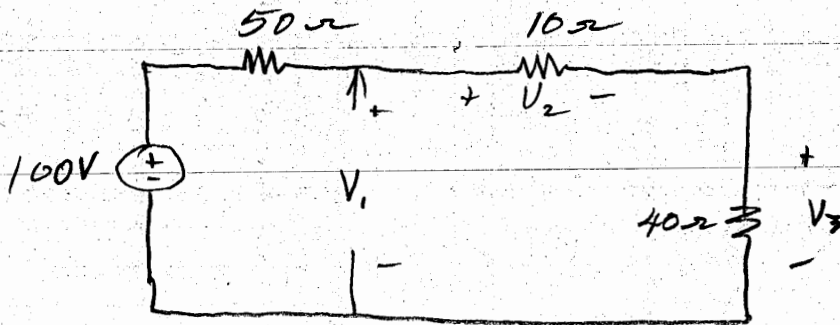In steady state the circuit is equivalent to the following:



$$V_1 = 50\text{V}; \quad V_2 = \frac{50 \times 10}{10 + 40} = 10\text{V}; \quad V_3 = 40\text{V}$$

We also have

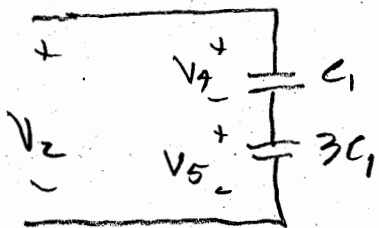

Test 2A

2

(4) continued

Using voltage division for
resistors in series;

$$V_4 = \frac{V_2 \times 3\Omega}{3\Omega + 4\Omega} = 0.75 V_2$$

o.e

$$V_4 = 7.5 V$$

It follows that since $V_2 = 10 V$
and $V_4 = 7.5 V$ that

$$V_5 = 2.5 V$$

Summary

$$V_1 = 50 V$$

$$V_2 = 10 V$$

$$V_3 = 40 V$$

$$V_4 = 7.5 V$$

$$V_5 = 2.5 V$$

Test 2A

(5) You are given the circuit of Figure 5(a).

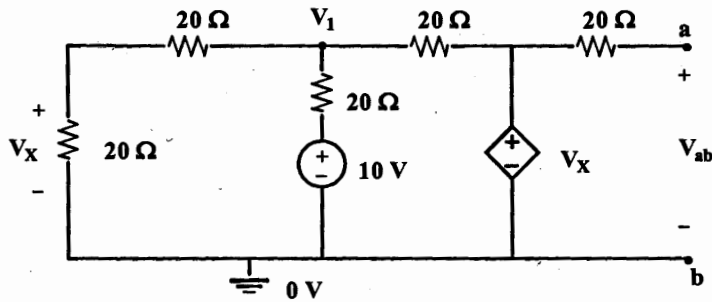


Figure 5 (a): Circuit for Problem 5 (a).

- (a) Use the nodal analysis method to find the open circuit voltage, V_{ab} , as shown in Figure 5 (a).
- (b) Place a short circuit from terminals a to b of the circuit shown in Figure 5 (a). Use the nodal analysis method to find I_{SC} as shown in Figure 5 (b).

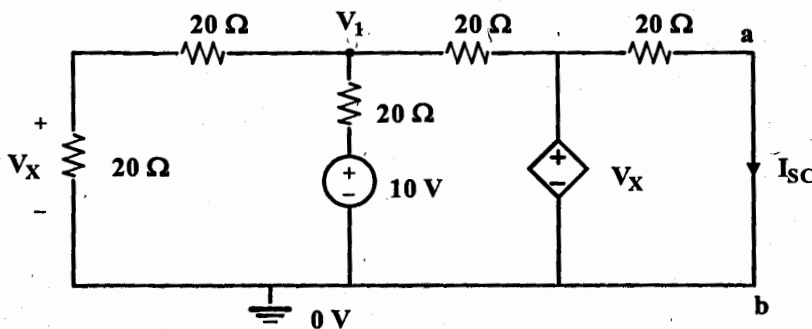


Figure 5 (b): Circuit for Problem 5 (b).

- (c) Using the information of 5 (a) and 5 (b), determine the Norton equivalent circuit. Draw the circuit showing I_{Norton} and R_{Norton} and terminals a-b.

(a) Using Nodal:
At V_1

$$40 \left(\frac{V_1}{40} + \frac{V_1 - 10}{20} + \frac{V_1 - V_x}{20} = 0 \right)$$

$$\text{or } V_1 + 2V_1 - 20 + 2V_1 - 2V_x = 0$$

$$5V_1 - 2V_x = 20$$

$$\text{but } V_x = \frac{V_1}{2}$$

Test 2A

(5) cont.

2

so;

$$5V_1 - \frac{2 \times V_1}{2} = 20$$

$$4V_1 = 20$$

$$\underline{V_1 = 5V}$$

since

$$V_x = \frac{V_1}{2}$$

$$V_x = 2.5V$$

We see that $V_{ab} = V_x = V_{oc} = V_{TH} = 2.5V$

(6) Finding I_{sc} : (Nodal Analysis)

At V_1

$$\frac{V_1}{40} + \frac{V_1 - 10}{20} + \frac{V_1 - V_x}{20} = 0$$

(same as in part (a))

$$V_x = \frac{V_1}{2} = 2.5V$$

$$\underline{I_{sc} = \frac{V_x}{20} = \frac{2.5}{20} = \underline{0.125A} = I_N}$$

so; Summary

$$V_{TH} = V_{oc} = 2.5V$$


$$I_N = I_{sc} = 0.125A$$

(3) cont.


(c)

$$I_H = I_{sc} = 0.125 \text{ A}$$
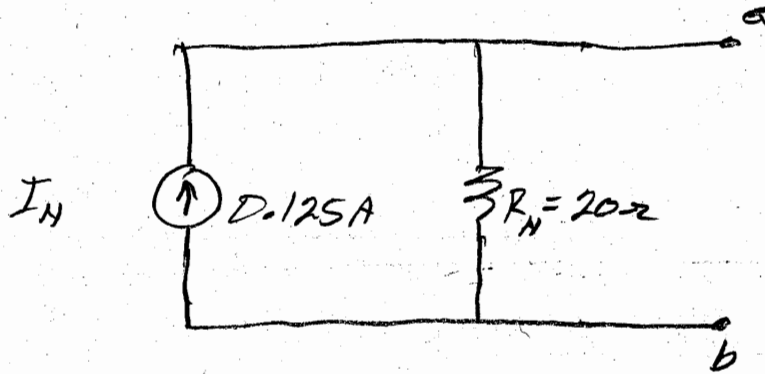
$$R_H = R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{2.5}{0.125} = 20 \Omega$$



Check in V_{oc}

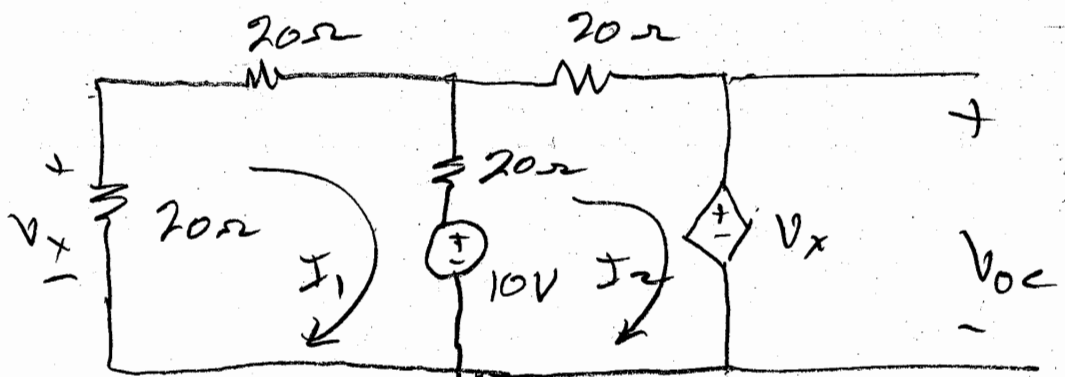

$$60 I_1 - 20 I_2 = -10$$

(5) cont.

4

$$60I_1 - 20I_2 = -10$$

$$-20I_1 + 40I_2 + V_x = 10$$

$$V_x = -20I_1$$

no

$$-40I_1 + 40I_2 = 10$$

$$\begin{bmatrix} 60 & -20 \\ -40 & 40 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -10 \\ 10 \end{bmatrix}$$


$$I_1 = -0.125 \quad I_2 = 0.125$$

$$V_x = -I_1 \times 20 = +2.5 \text{ V check}$$


Test 3A

(6) Use any method you desire to find the voltage V_A in the circuit of Figure 6.

15%

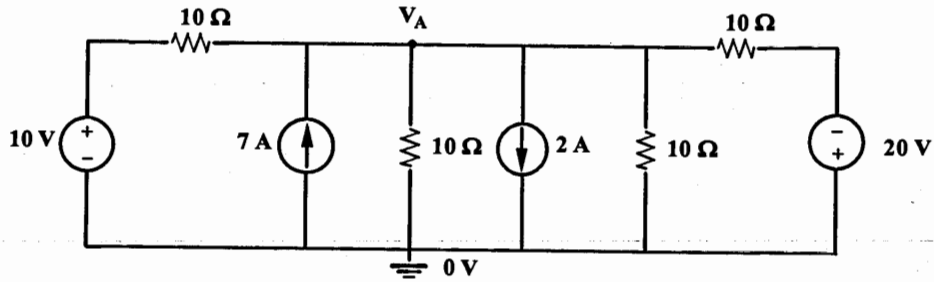


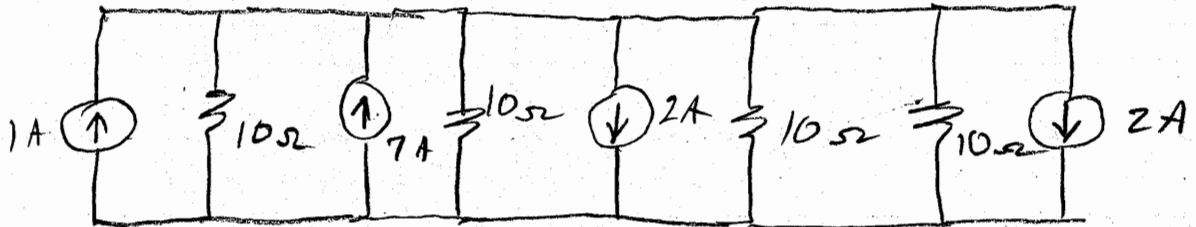Making source transformations, right and left side;



Net current: 4A UP

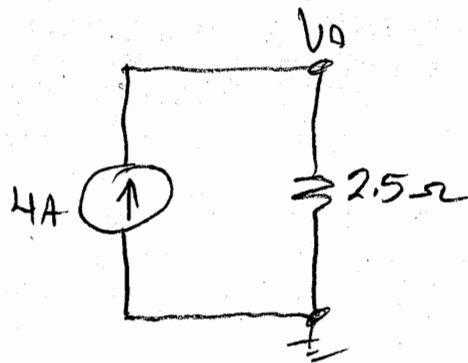Equivalent resistance $\frac{10}{4} = 2.5\Omega$



$$V_A = 4 \times 2.5 = 10V$$