

ECE 300
Spring 2008
Test 2B

wlg

(1) You are given the following circuit.


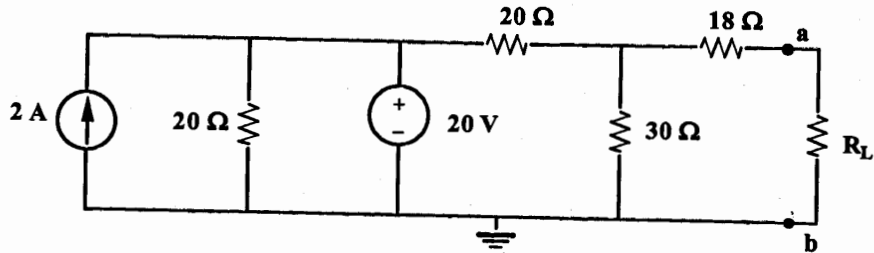


Figure 1: Circuit for Problem 1.

- Determine V_{TH} and R_{TH} looking into terminals a-b with R_L removed.
- Draw your Thevenin circuit. Show V_{TH} and R_{TH} on the circuit diagram connected to R_L .
- Assign a value of R_L that will give maximum power transfer to R_L and determine this value of power.

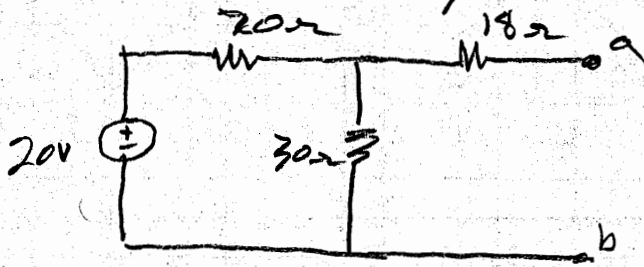
(a) The circuit is equivalent to the following:



$$V_{OC} = V_{TH} = \frac{20 \times 30}{20 + 30} = 12V$$

$$R_{TH} = 20 \parallel 30 + 18 = 12 + 18 = 30\Omega$$

(b)

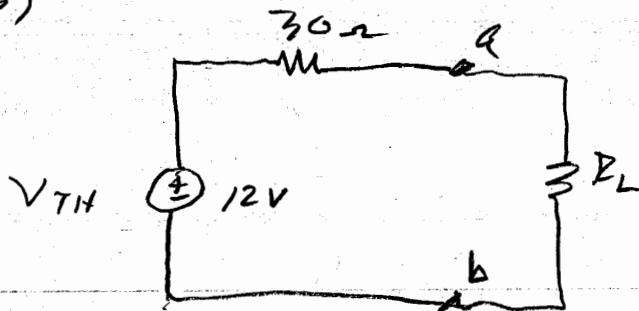


test 2B

2

(1) cont.

(c)

$$R_L = R_{TH} = 30 \Omega$$

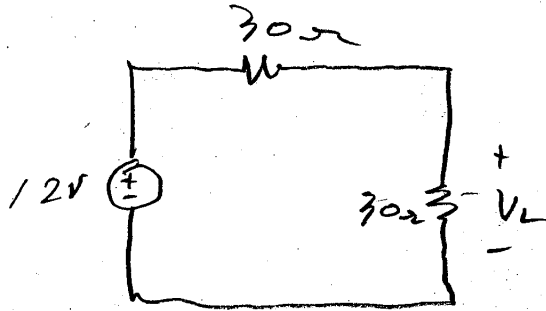

$$P_{OUT} = \frac{V_L^2}{R_L} = \frac{6^2}{30} = 1.2 \text{ W}$$


$$P_{OUT} = 1.2 \text{ W}$$

Test 213

- (2) You are given the op amp circuit of Figure 2. Use ideal op amp assumptions in answer the following questions. V_o can be expressed in the following form:

$$V_o = [C]V_1 + [D]V_2$$

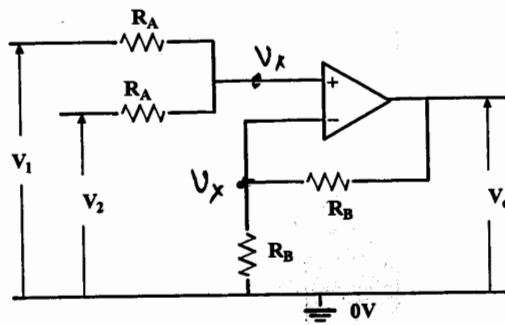- (a) Find the coefficients $[C]$ and $[D]$.
 (b) If $V_1 = 3\text{ V}$ and $V_2 = 1\text{ V}$, find the value of V_o .



1(a)

$$V_x = \frac{V_o R_B}{R_B + R_B} = \frac{V_o}{2} \quad (1)$$

Also

$$\frac{V_x - V_1}{R_A} + \frac{V_x - V_2}{R_A} = 0$$

$$2V_x - V_1 - V_2 = 0 \quad (2)$$

Substitute (1) into (2)

$$V_o - V_1 - V_2 = 0$$

$$\underline{V_o = V_1 + V_2} \quad C=1 ; D=1$$

1(b)

$$V_o = V_1 + V_2 \quad \left| \begin{array}{l} V_1 = 3V \\ V_2 = 1V \end{array} \right.$$

$$V_o = 3 + 1 = 4V$$

$$\boxed{V_o = 4V}$$

Test 2B



(3) For the following problems assume ideal op amps.

(a) Design an inverting op amp circuit using a single op amp such that the gain is given by

$$\frac{V_o}{V_{in}} = -4$$

Show (draw) your op amp circuit and give the values of all resistors on your circuit diagram. Also, show on your diagram, an appropriate ground along with V_o and V_{in} . You are restricted to resistors of values 1 k Ω , 2 k Ω , 3 k Ω , 4 k Ω and 5 k Ω .

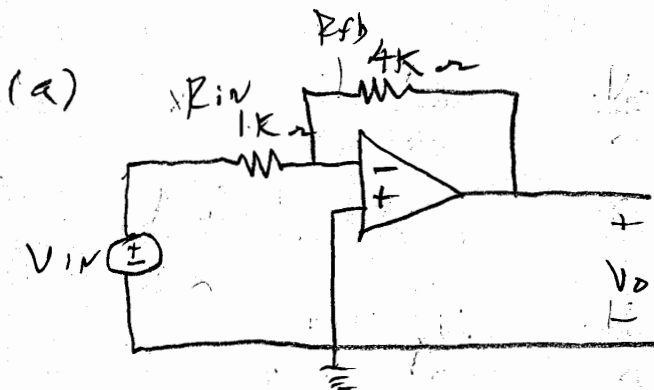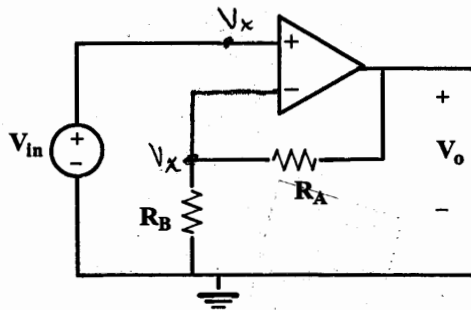(b) You are given the non-inverting op amp circuit shown in Figure 3(b). Determine values of R_A and R_B so that $V_o = 4V_{in}$. You are restricted to resistors of values 1 k Ω , 2 k Ω , 3 k Ω , 4 k Ω and 5 k Ω .



$$\frac{V_o}{V_{in}} = -\frac{R_{fb}}{R_{in}}$$

$$\frac{V_o}{V_{in}} = -4$$

$$(b) \quad V_x = \frac{V_o \times R_B}{R_A + R_B} = V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{R_A + R_B}{R_B} = 1 + \frac{R_A}{R_B}$$

$$V_o = \left(1 + \frac{R_A}{R_B}\right) V_{in} = 4 V_{in}$$

$$\frac{R_A}{R_B} = 3 = \frac{3k\Omega}{1k\Omega}$$

$$R_A = 3k\Omega; \quad R_B = 1k\Omega$$

Test 2B

(4) You are given the circuit of Figure 4(a).

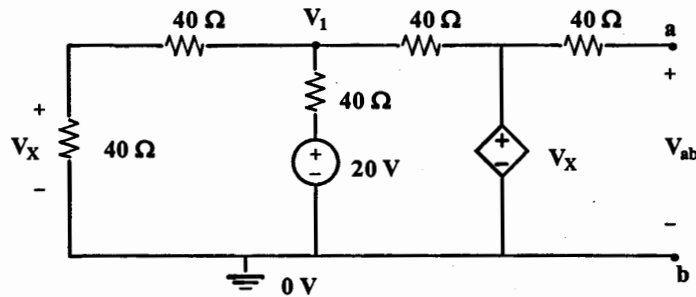


Figure 4 (a): Circuit for Problem 4 (a).

- (a) Use the **nodal analysis method** to find the open circuit voltage, V_{ab} , as shown in Figure 4 (a).
- (b) Place a short circuit from terminals a to b of the circuit shown in Figure 4 (a). Use the **nodal analysis method** to find I_{SC} as shown in Figure 4 (b).

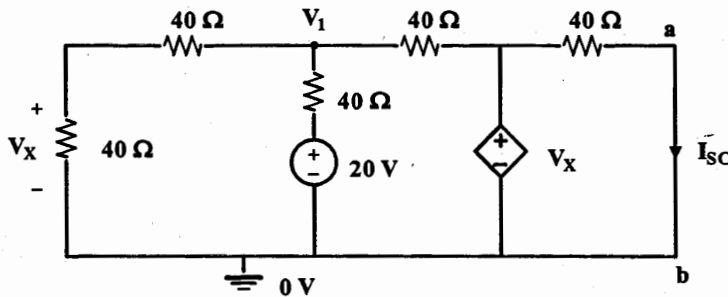


Figure 4 (b): Circuit for Problem 4 (b).

- (c) Using the information of 4 (a) and 4 (b), determine the Norton equivalent circuit. Draw the circuit showing I_{Norton} and R_{Norton} and terminals a-b.

$$(a) \frac{V_1}{80} + \frac{V_1 - 20}{40} + \frac{V_1 - V_x}{40} = 0$$

$$V_1 + 2V_1 - 40 + 2V_1 - 2V_x = 0$$

$$5V_1 - 2V_x = 40$$

$$V_x = \frac{5V_1 - 40}{2}$$

$$4V_1 = 40$$

$$V_1 = 10V$$

$$V_x = 5V = V_{oc} = V_{TH}$$

(4)

(b) FOR I_{sc}

$$\frac{V_1}{80} + \frac{V_1 - 20}{40} + \frac{V_1 - V_x}{40} = 0$$

same as in part (a)

 \therefore


$$V_1 = 10V$$

$$V_x = \frac{V_1}{2} = 5V$$

$$I_{sc} = \frac{V_x}{40} = \frac{5}{40} = 0.125A$$

(c)
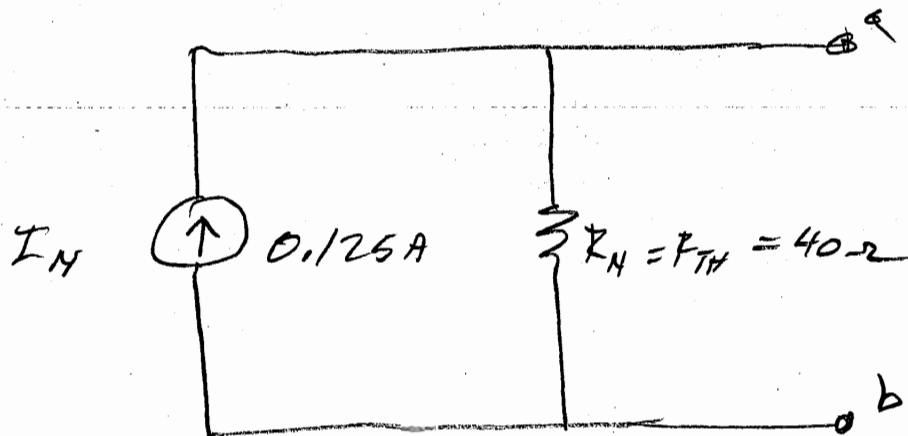
$$R_{TH} = R_N = \frac{V_{oc}}{I_{sc}} = \frac{5}{.125} = 40\Omega$$



(5) Assume the circuit shown in Figure 5 is in steady state.


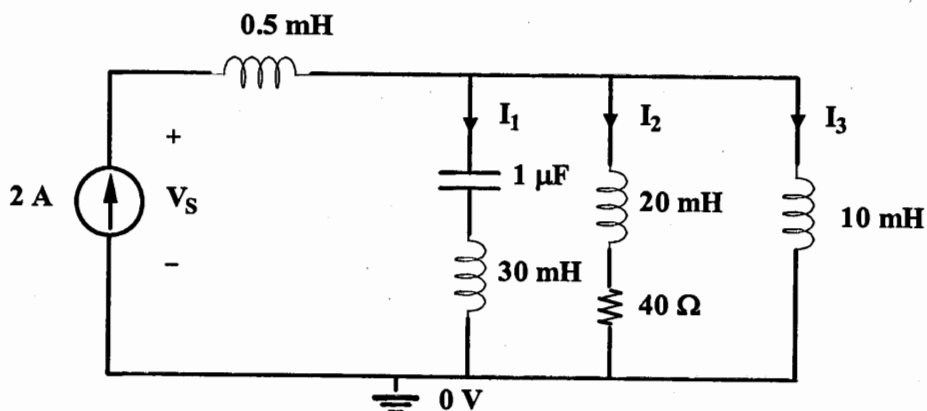


Figure 5: Circuit for Problem 5.

- Determine the steady state values of the currents I_1 , I_2 , and I_3 .
- Determine the steady state value of the voltage V_s .
- Determine the energy stored in the magnetic field of the 10 mH inductor.

(a) In steady state the circuit becomes

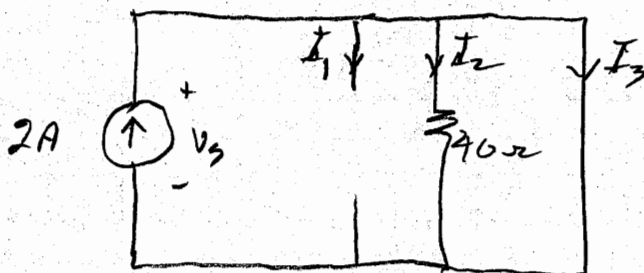

$$I_1 = 0, \quad I_2 = 0, \quad \underline{I_3 = 2 \text{ A}}$$


(b) $V_s = 0$

(c) $W_{10 \text{ mH}} = \frac{1}{2} L I_3^2 = \frac{1}{2} \times 0.01 \times 2^2$


$$W = 0.02 \text{ J}$$

Test 2B

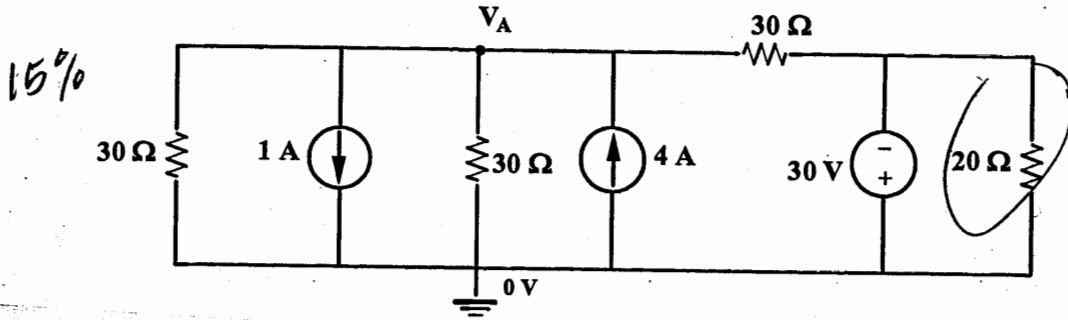(6) Use any method you desire to find the voltage V_A in the circuit of Figure 6.




Circuit becomes;

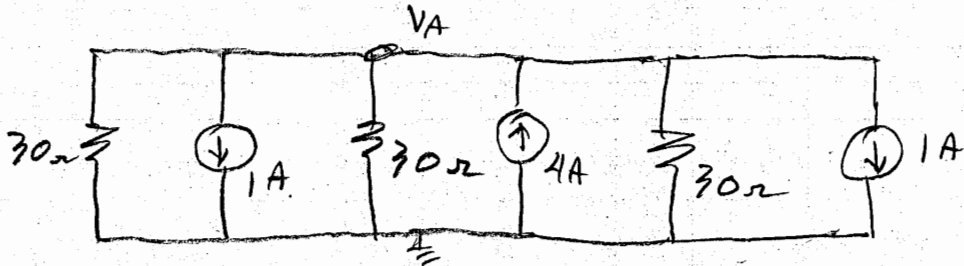

Reduces to

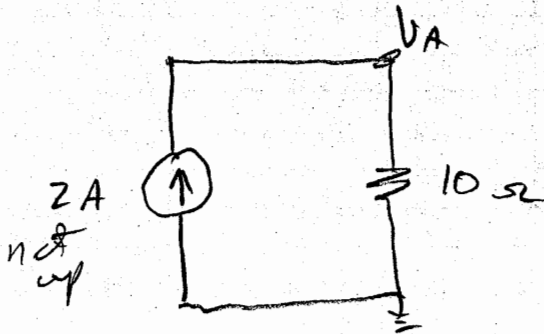3, 30 ohm resistors
 $10 \parallel = \frac{30}{3} = 10 \Omega$



$V_A = 20 V$