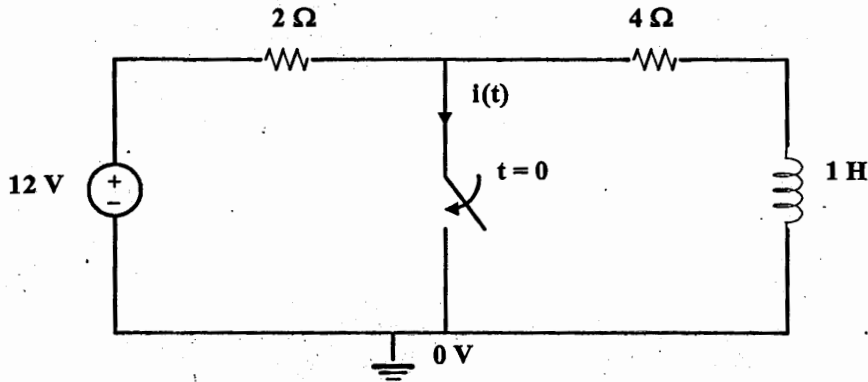



ECE 300
Spring Semester, 2008
Test #3

wlg: Test A:

- (1) The switch in the circuit of Figure 1 has been open for a long time. At $t = 0$ the switch is closed.
- Determine $i(0^+)$ and $i(\infty)$.
 - Determine $i(t)$ for $t \geq 0$. Use any method you desire.
 - How many milliseconds after the switch has been closed will the current $i(t)$ equal 5 A?




For $t < 0$

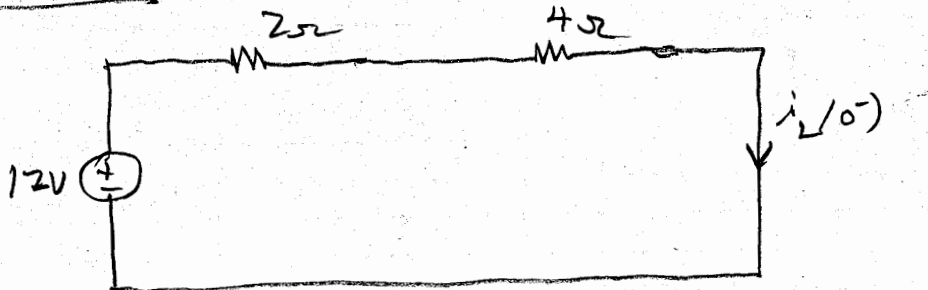

$$i_L(0^-) = \frac{12}{6} = 2 \text{ A} \quad \therefore i_L(0^+) = 2 \text{ A} \quad (1)$$

1a)

For $t = \infty$

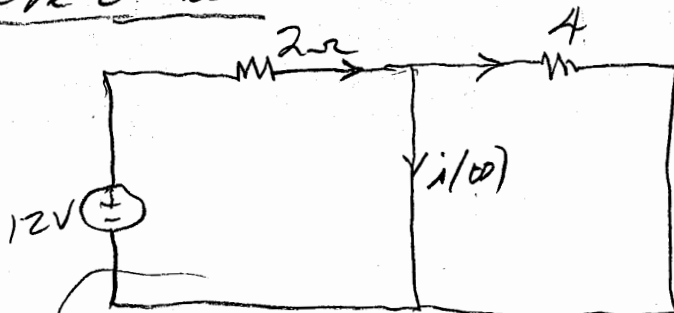


$$\underline{\underline{i(\infty) = 6 \text{ A}}}$$

(2)

(1) cont

2

FOR $t = 0^+$

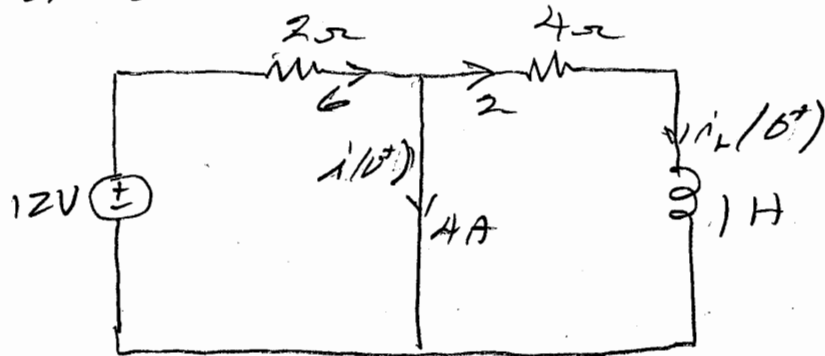

$$\tau = \frac{L}{R} = \frac{1}{4} = 0.25 \text{ sec}$$

$$\underline{i(0^+) = 6 - 2 = 4 \text{ A}}$$

$$i(\infty) = 6 \text{ A}$$

(b)

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-\frac{t}{\tau}}$$

$$i(t) = 6 + [4 - 6] e^{-4t}$$

$$i(t) = (6 - 2e^{-4t}) \text{ u(t) A}$$

(c)

$$5 = 6 - 2e^{-4t}$$

$$-1 = -2e^{-4t}$$

$$0.5 = e^{-4t}$$

$$\ln 0.5 = -4t \ln e = -4t$$

$$t = \frac{\ln 0.5}{-4}$$

$$t = 0.173 \text{ sec}$$

$$t = 173 \text{ msec}$$


(1) cont

Alternate method

Determine $i_L(0^+)$ as before

$$i_L(0^+) = i_2(0^+) = 2A$$

For $t > 0$

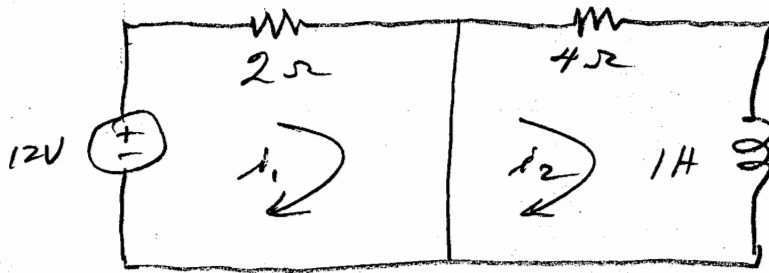

$$i_2 = 2i_1$$

$$\underline{i_1 = 6A}$$

$$4i_2 + \frac{di_2}{dt} = 0$$

$$i_2 = Ke^{-4t}$$


$$i_2(0^+) = 2 \quad K = 4$$

$$i_2 = 2e^{-4t}$$

$$i(t) = i_1(t) - i_2(t)$$

$$i(t) = 6 - 2e^{-4t} \text{ A } \quad u(t)$$

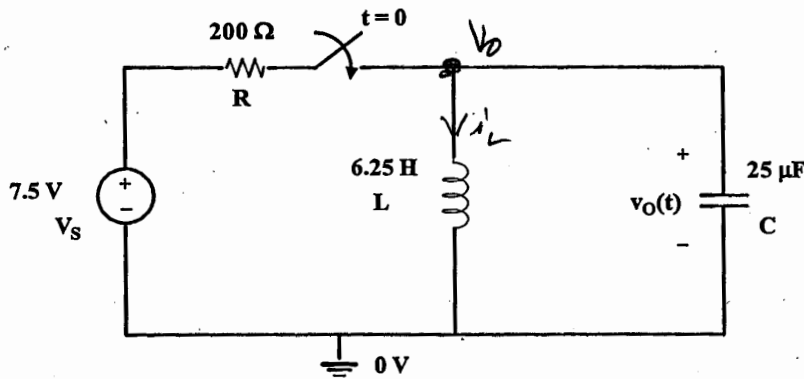- (2) There is no energy stored in the circuit of Figure 2 when the switch is closed at $t = 0$.
- (a) Find $v_o(t)$ for $t \geq 0$. To do this develop a second order differential equation in $v_o(t)$ and solve.
- (b) Determine the time at which $v_o(t)$ will be maximum.



$$\frac{V_o - V_s}{R} + C \frac{dV_o}{dt} + \frac{1}{L} \int_0^t (V_o / R) dt + i_L(0^+) = 0 \quad (1)$$

Take $\frac{d[\cdot]}{dt}$ of (1)

$$\frac{1}{R} \frac{dV_o}{dt} + C \frac{d^2 V_o}{dt^2} + \frac{V_o}{L} = 0$$

$$\frac{d^2 V_o}{dt^2} + \frac{1}{RC} \frac{dV_o}{dt} + \frac{V_o}{LC} = 0 \quad (2)$$

Char. Eq.

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

with numbers

$$s^2 + 200s + 6400 = 0$$

$$(s+40)(s+160) \quad (3)$$

(2) cont

$$V_o(t) = A_1 e^{-40t} + A_2 e^{-160t} \quad (4)$$

$$V_o(0^+) = 0 = \left(A_1 e^{-40t} + A_2 e^{-160t} \right) \Big|_{t=0}$$

$$A_1 + A_2 = 0 \quad (5)$$

Need $\frac{dV_o(t)}{dt}$

From the ckt

$$i(0^+) = \frac{7.5}{200} = C \frac{dV_o(0^+)}{dt}$$

current thru inductor cannot change instantaneously so $i_{cap} = \frac{7.5}{200}$

$$\frac{dV_o(0^+)}{dt} = \frac{7.5}{200 \times 25 \times 10^{-6}} = 1500 \quad (6)$$

Take $\frac{dL.H.S.}{dt}$ of (4)

$$\frac{dV_o(t)}{dt} = -40 A_1 e^{-40t} - 160 A_2 e^{-160t} \quad (7)$$

Evaluate (7) at $t=0^+$

$$\frac{dV_o(0^+)}{dt} = 1500 = -40 A_1 - 160 A_2$$

$$\begin{bmatrix} 1 & 1 \\ -40 & -160 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 1500 \end{bmatrix}$$

$$A_1 = 12.5 \quad A_2 = -12.5$$

(2) cont

$$v_o(t) = [12.5e^{-40t} - 12.5e^{-160t}]u(t) \quad V$$

(b)

$$\frac{dv_o(t)}{dt} = -40 \times 12.5e^{-40t} + 12.5 \times 160e^{-160t}$$

$$0 = -40e^{-40t} + 160e^{-160t}$$

$$0 = -e^{-40t} + 4e^{-160t}$$

$$0 = -1 + 4e^{-120t}$$

$$4e^{-120t} = 1$$


$$e^{-120t} = 0.25$$

$$-120t \ln e = \ln 0.25 = -1.386$$


$$t = \frac{1.386}{120} = 11.6 \text{ } \mu\text{s}$$

check with P-spice simulation

(A) bias3.dat (active)

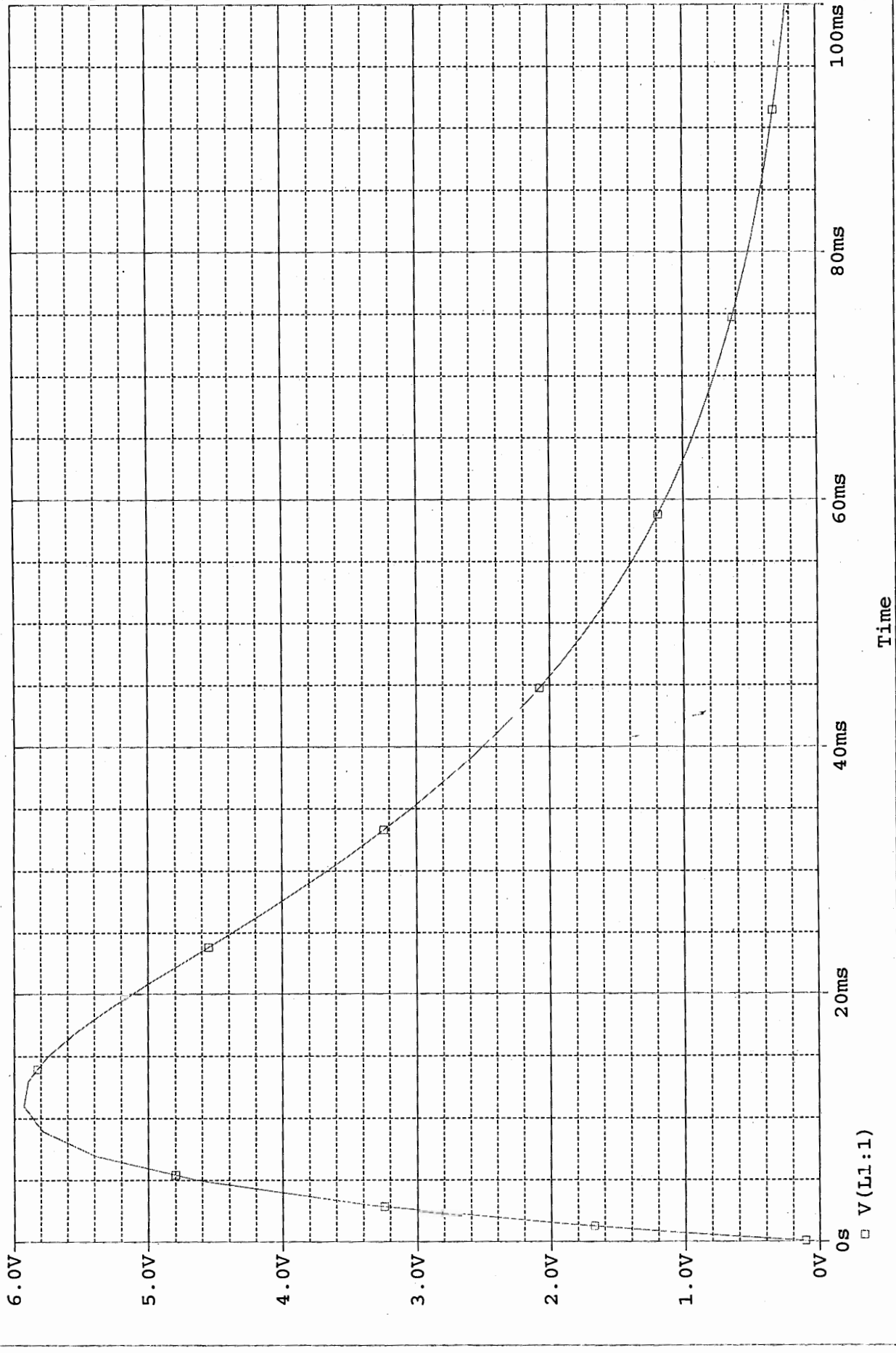

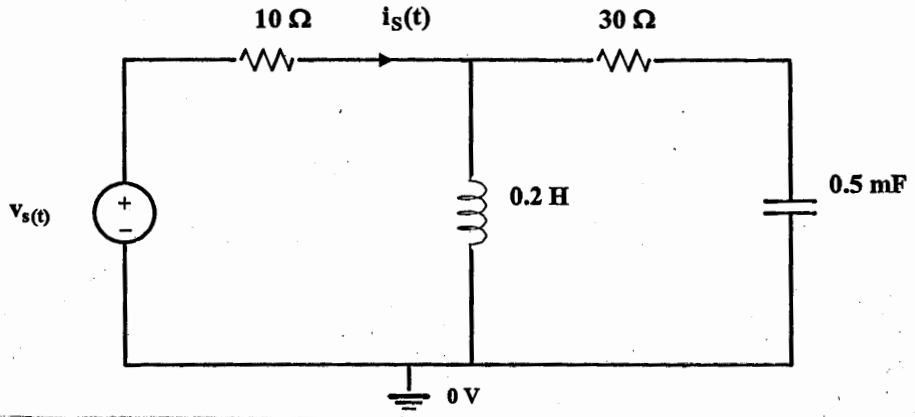- (3) The circuit in Figure 3 is in steady state. Assume $v_s(t) = 20\sin(100t - 40^\circ)$ V.
 (a) Determine the steady state current $i_s(t)$ using a cosine reference.
 (b) Draw the phasor diagram for V_s and I_s .
 (c) Is the voltage V_s leading the current I_s or is I_s leading V_s and by what angle?



$v_s = 20 \sin(100t - 40^\circ)$ change to cosine ref.


$v_s = 20 \cos(100t - 130^\circ)$

$\vec{V}_s = 20 \angle -130^\circ$ V

$0.2 \text{ H} \rightarrow j 100 \times 0.2 \rightarrow j 20 \Omega$

$0.5 \text{ mF} \rightarrow \frac{-j}{100 \times 0.5 \times 10^{-3}} \rightarrow -j 20 \Omega$

Draw Phasor ckt

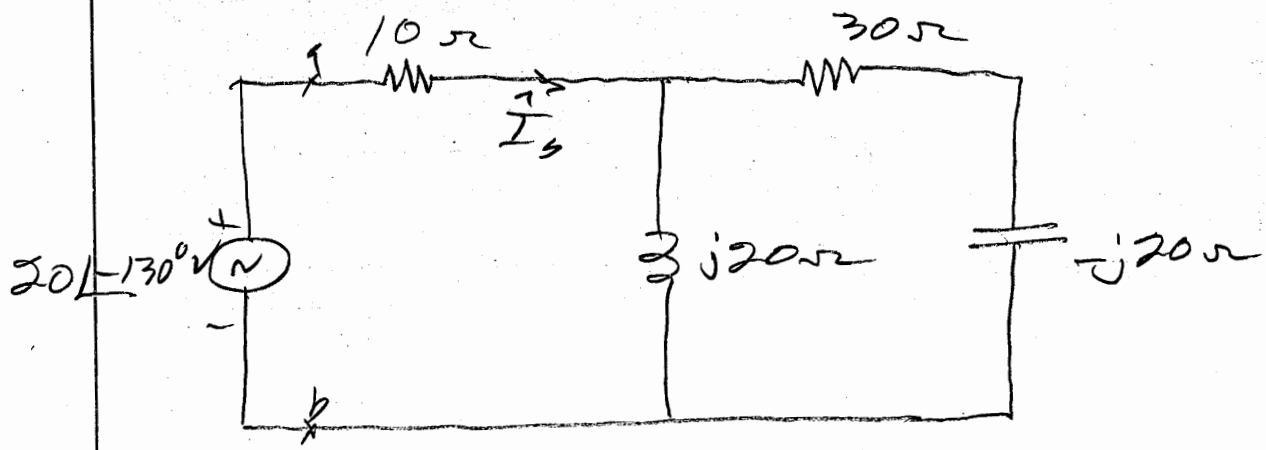

13) cont

$$Z_{ab} = 10 + (30 - j20) \parallel (j20)$$

$$Z_{ab} = 10 + \frac{(30 - j20)(j20)}{30 - j20 + j20}$$


$$Z_{ab} = 30.73 \angle 40.6^\circ \Omega$$

$$\vec{I}_s = \frac{V_s}{Z_{ab}} = \frac{20 \angle -130^\circ}{30.73 \angle 40.6^\circ}$$

$$\vec{I}_s = 0.65 \angle -170.6^\circ \text{ A}$$


$$i_s(t) = 0.65 \cos(100t - 170.6^\circ) \text{ A}$$

(b)

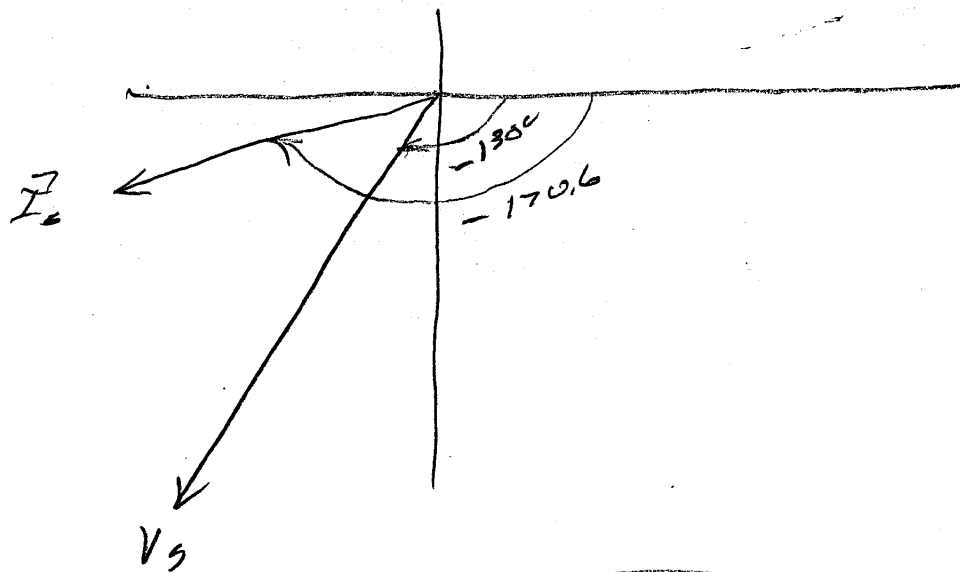

V_s leads I_s by 40°

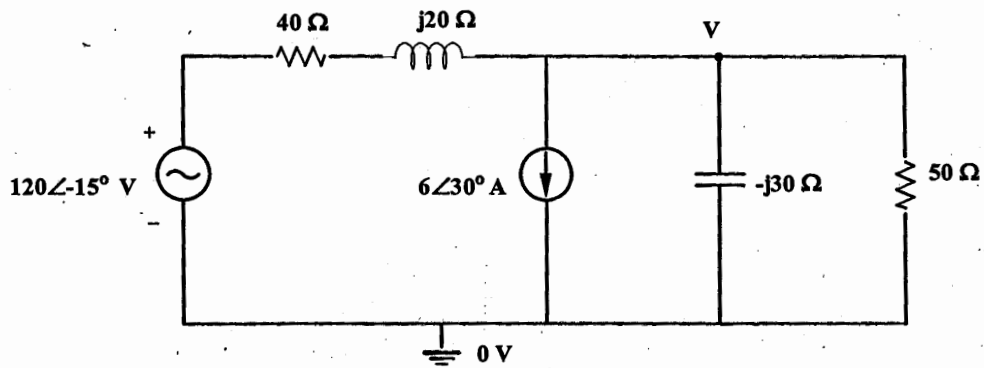(4) Use nodal analysis to find the phasor voltage V in the circuit of Figure 4.



$$\frac{\vec{V} - 120 \angle -15^\circ}{40 + j20} + \frac{\vec{V}}{50} - \frac{\vec{V}}{j30} = -6 \angle 30^\circ$$

$$(0.02 - j0.01)\vec{V} + 2.28 \angle 133.4^\circ$$

$$-j0.6333\vec{V} + 0.2\vec{V} = -6 \angle 30^\circ$$

$$(0.04 + j0.6233)\vec{V} = 6 \angle -150^\circ - 2.28 \angle 133.4^\circ$$

$$\vec{V} = 124.5 \angle -154^\circ \text{ V}$$