

Power #9

Instantaneous Power

$$P(t) = v(t) i(t)$$

$$\text{Let } v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Recall:

$$\cos(A+B) = \cos A \cos B - \sin A \sin B$$


$$\cos(A-B) = \cos A \cos B + \sin A \sin B$$

$$\cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

So

$$V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$
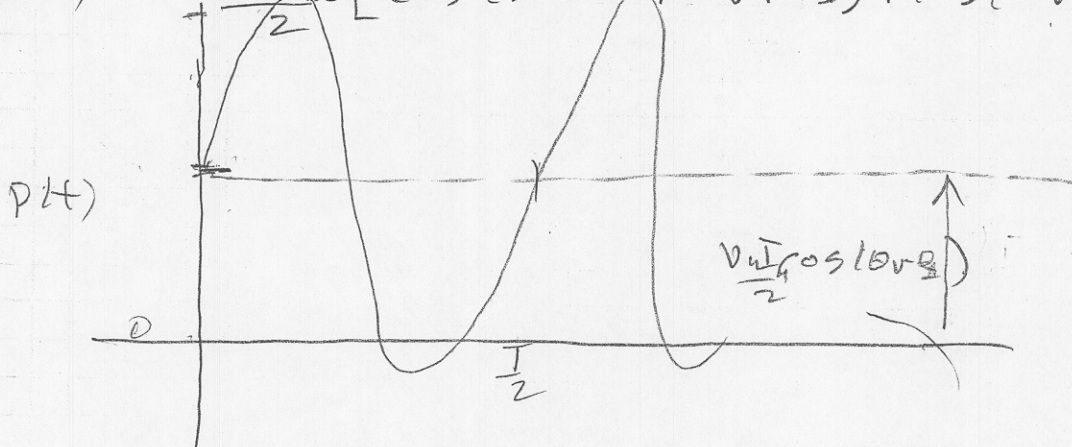
$$P(t) = \frac{V_m I_m}{2} [\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$$



We are really interested in the
Average Power


#9

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) dt -$$

$$+ \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) dt$$
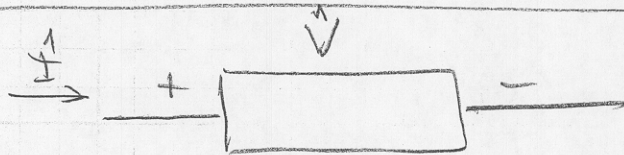
$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$



$$\hat{V} = V_m \angle \theta_v$$

$$\hat{I} = I_m \angle \theta_i$$

If we consider

$\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$ we see this

is the same as


$$\frac{1}{2} \operatorname{Re} [\hat{V} \hat{I}^*] = \frac{1}{2} \operatorname{Re} [V_m \angle \theta_v \times I_m \angle -\theta_i]$$

$$= \frac{1}{2} \operatorname{Re} [V_m I_m e^{j(\theta_v - \theta_i)}]$$

$$= \frac{1}{2} \operatorname{Re} [V_m I_m (\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i))]]$$

If we are talking about a resistor

$$\theta_V = \theta_I$$

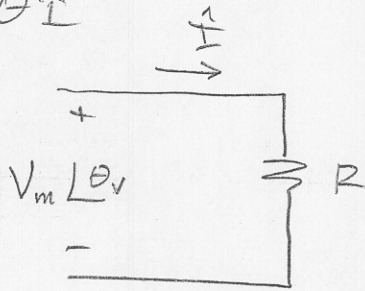

$$\hat{I} = \frac{\hat{V}}{R} = \frac{V_m \angle \theta_V}{R}$$


$$\hat{I} = I_m \angle \theta_I$$

$$I_m = \frac{V_m}{R}, \quad \theta_I = \theta_V$$

$$P = \frac{V_m I_m}{2} = \frac{V_m^2}{2R} = \frac{I_m^2 R}{2}$$

(resistor)

An Inductor

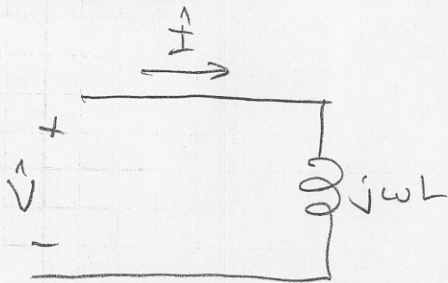

$$\hat{I} = \frac{\hat{V}}{j\omega L} = \frac{V_m \angle \theta_V \cdot \angle -90^\circ}{\omega L}$$

$$\theta_V = \theta_V$$

$$\theta_I = \theta_V - 90^\circ$$

So


$$\cos(\theta_V - \theta_I) = \cos(\theta_V - (\theta_V - 90^\circ)) = \cos 90^\circ = 0$$

$$P_L = \frac{V_m I_m}{2} \cos(90^\circ) = 0 \quad \text{No Average Power}$$

Same for the capacitor, No Average Power

Example

Given

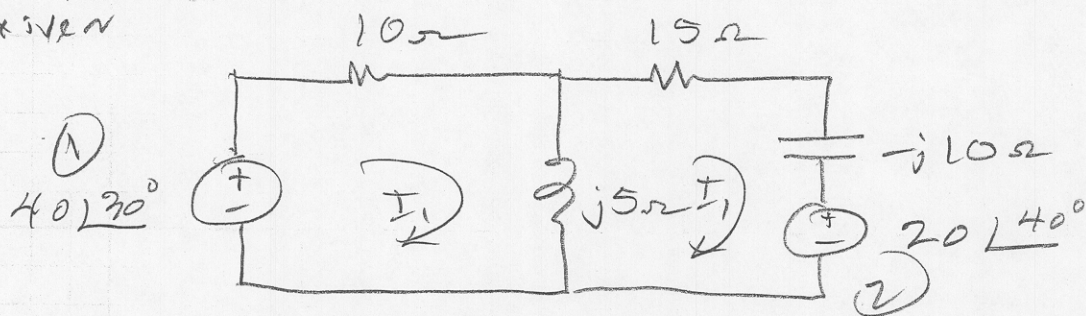

Determine the power

(a) supplied to each resistor

(b) power supplied by each source

$$\begin{bmatrix} 10 + j5 & -j5 \\ -j5 & 15 - j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 40 \angle 30^\circ \\ -20 \angle 40^\circ = 20 \angle -140^\circ \end{bmatrix}$$

$$I_1 = 3.398 - j0.1738 = 3.4024 \angle -2.928^\circ$$

$$I_2 = -0.9498 - j0.0411 = 0.9507 \angle -177.52^\circ$$

$$P_{10} = \frac{(3.4024)^2}{2} \times 10 = 57.88 \text{ W}$$

$$P_{15} = \frac{(0.9507)^2}{2} \times 15 = 6.779$$

$$P_{\text{TOTAL EXT}} = -57.88 + 6.779 = \underline{\underline{64.66 \text{ W}}}$$

$$P_1 = \frac{40 \times 3.4024}{2} \cos(30 + 2.928) = 57.12 \text{ W}$$

$$P_2 = -\frac{20 \times 0.9507}{2} \cos(40 + 177.52) = \underline{\underline{+7.54}} \\ \text{check} \quad 64.66 \text{ W}$$

Maximum Power Transfer

For maximum power transfer we find V_{TH} as before, i.e., open circuit voltage,

$$Z_L = Z_{TH}^*$$

If we are constrained to the load being purely real

$$R_L = |Z_{TH}| = \sqrt{R_{TH}^2 + X_{TH}^2}$$

RMS - The Effective Value

The effective value of a periodic voltage or current is the dc current (voltage) that delivers the same average power to a resistor as the periodic current (voltage)

Power Absorbed by a resistor, d.c. current;

$$P = I_{\text{eff}}^2 R$$

6

Power absorbed by a periodic signal


$$P = \frac{R}{T} \int_0^T i^2 dt$$

$$R I_{\text{eff}}^2 = \frac{R}{T} \int_0^T i^2 dt$$

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

Also
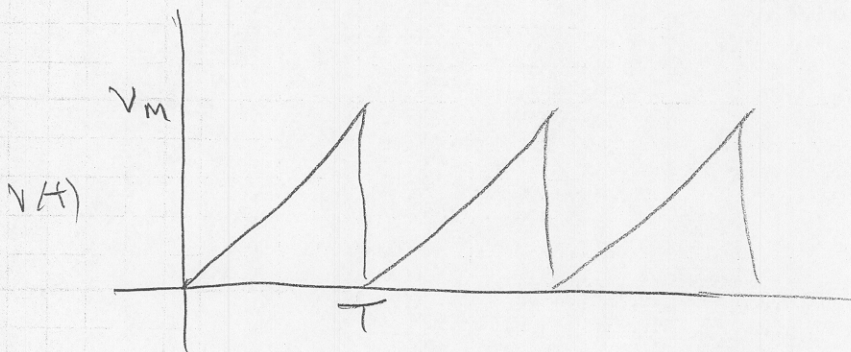
$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$



$$v(t) = \frac{V_m}{T} t$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T \frac{V_m^2}{T^2} t^2 dt}$$

$$= \sqrt{\frac{V_m^2}{T^3} \left[\frac{t^3}{3} \right]_0^T}$$

$$V_{\text{rms}} = \sqrt{\frac{V_m^2}{T^3 \times 3} T^3} = \frac{V_m}{\sqrt{3}}$$

Apparent Power

$$P = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_V - \theta_I)$$

Define Apparent power

$$S = \frac{V_m I_m}{2} = V_{\text{rms}} I_{\text{rms}} \quad \text{units VA}$$

$$\text{We define P.f.} = \frac{P}{S} = \cos(\theta_V - \theta_I)$$


If the current leads the voltage

we have a leading (capacitive)

P.f. current lags, lagging P.f.

Complex Power

8

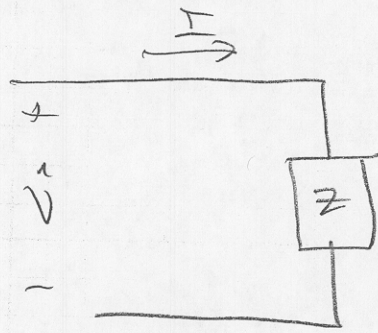

The complex power supplied to the load Z is

$$\hat{S} = \frac{\hat{V} \hat{I}^*}{2} = \underline{\underline{V_{rms} I_{rms}^*}} \quad (A)$$

$$\hat{S} = V_{rms} I_{rms} \angle \theta_V - \theta_I$$

$$\hat{S} = V_{rms} I_{rms} (\cos(\theta_V - \theta_I) + j \sin(\theta_V - \theta_I))$$

$$\hat{S} = P + jQ$$

Express in terms of Z

$$\hat{Z} = \frac{\hat{V}}{\hat{I}} = \frac{V_{rms}}{I_{rms}} \angle \theta_V - \theta_I$$

$$V_{rms} = \hat{Z} I_{rms}$$

Back to (A)

$$\hat{S} = I_{rms} I_{rms}^* \hat{Z} = (I_{rms})^2 \hat{Z}$$

$$S = |I_{rms}|^2 (R + jX)$$


$$S = |I_{rms}|^2 R + j |I_{rms}|^2 X$$

Also

$$|V_{rms}| = |I_{rms}| Z$$

$$I_{rms}^* = \frac{V_{rms}^*}{Z^*}$$

$$S = \frac{V_{rms} V_{rms}^*}{Z^*} = \frac{|V_{rms}|^2}{Z^*}$$

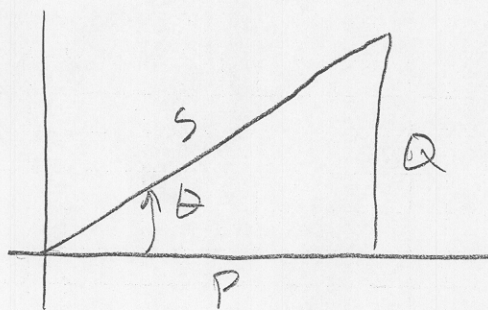


lagging P-f


$$\text{Since } S = |I_{rms}|^2 Z$$

$$\text{angle of } Z = \angle S$$

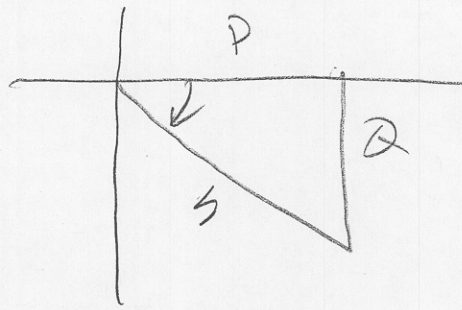
If Z is a capacitive load, I leads V , θ is negative.



leading P.f.

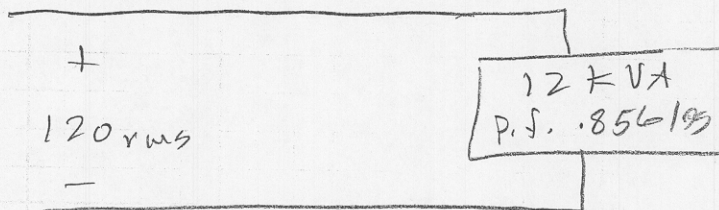Example

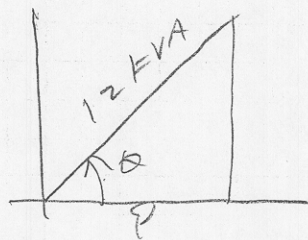- (a) Find the average reactive power to the load
- (b) the peak current
- (c) the load impedance



$$\cos \theta = .856$$

$$\theta = 31.13^\circ$$

$$P = 12 \text{ k} \times 0.856 = 10.272 \text{ kW}$$

$$Q = 12 \text{ k} \sin \theta = 12 \text{ k} \sin 31.13^\circ = 6.204 \text{ kVAR}$$

$$\vec{S} = P + jQ = (10.272 + j6.204) \text{ kVA}$$

$$\vec{S} = \vec{V}_{\text{rms}} \vec{I}_{\text{rms}}^*$$

$$I_{rms}^* = \frac{\dot{S}}{\dot{V}_{rms}} = \frac{(10 + j272 + j6.204) \text{ kVA}}{120 \angle 0}$$

$$I_{rms}^* = 100 \angle 31.13^\circ$$

$$I_{rms} = 100 \angle -31.13$$

$$I_m = \sqrt{2} (I_{rms}) = 141.4 \text{ A}$$


(c)

$$Z = \frac{\dot{V}_{rms}}{\dot{I}_{rms}} = \frac{120 \angle 0}{100 \angle -31.13}$$


$$Z = 1.2 \angle 31.13 \Omega$$

inductive load

Example

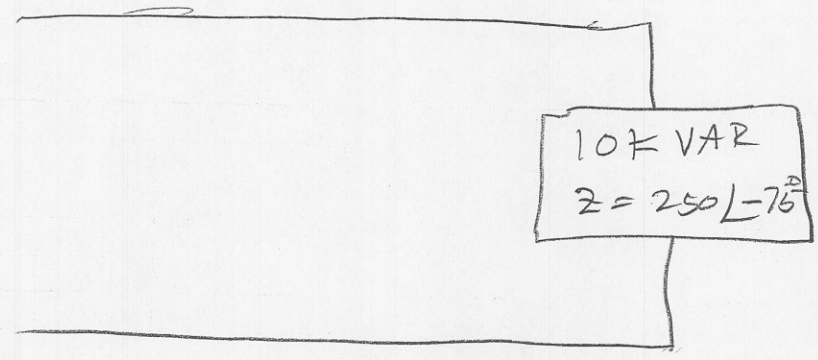

$\angle Z = \text{p.f. angle}$

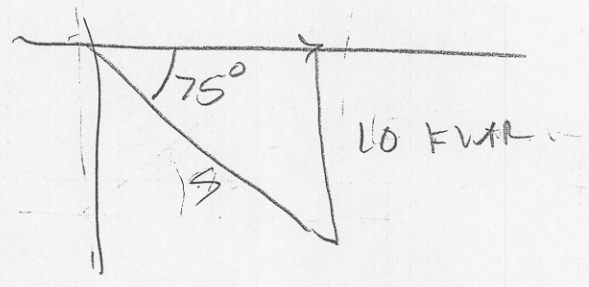

D.f. = $\cos 75^\circ = .2588$ leading

$\sin 75^\circ = \frac{10}{S}$

$S = \frac{10 \text{ kW}}{\sin 75^\circ} = 10.35 \text{ kVA}$

$\frac{V_m^2}{2|Z|^2} = |S|$

$V_m = 2|Z|\sqrt{|S|} = 2 \times 250 \times \sqrt{10.35 \times 10^3}$

$V_m = 1 \times 10^3 \sqrt{5.175} = 2.275 \text{ kV}$

√S