

# Desk Copy


ECE 301  
Fall Semester 2005  
HW # 3

wlg Due: October 4, 2005


Name Caren  
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points.

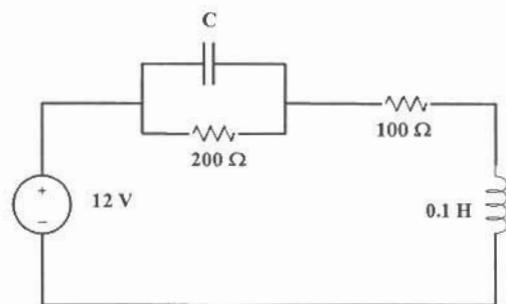
- (1) You are given the circuit shown below. Find C (capacitor value) so that the energy stored in the capacitor equals the energy stored in the inductor. Assume the circuit is in steady state.  
Ans: On your own.



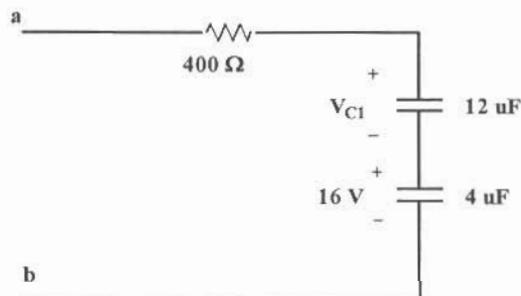
- (2) A certain DC voltage has been applied to terminals a-b in the circuit below. The circuit has reached steady state. (a) Determine  $V_{C1}$ . (b) Determine the voltage  $V_{ab}$ . Ans:  $V_{C1}=5.33V$   
 $V_{ab}=21.55V$ .



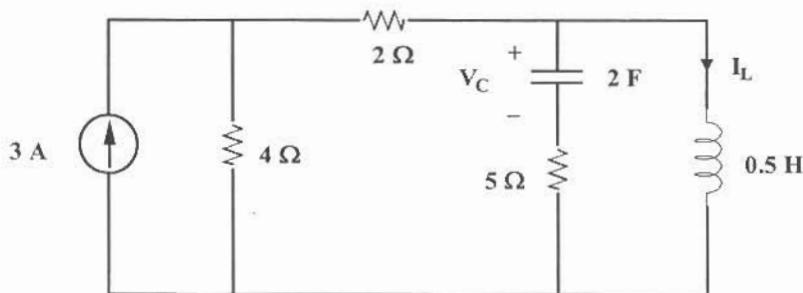
- (3) You are given the circuit below. The circuit has reached steady state. Find the following:  
(a)  $V_c$ , (b)  $I_L$ , (c)  $W_c$ , (d)  $W_L$  Ans:  $V_c = 0$ ,  $I_L = 2A$ ,  $W_c = 0$ ,  $W_L = 1 J$



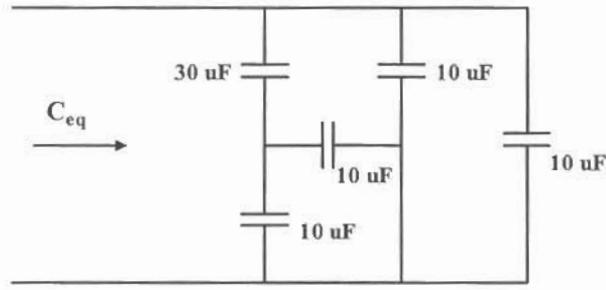
- (4) You are given the circuit shown below. Find  $C_{eq}$ . Ans: On your own.



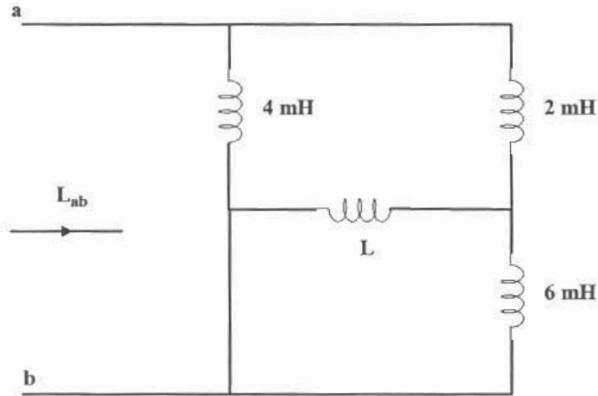- (5) You are given the following circuit. Find L so that  $L_{ab} = 2 \text{ mH}$ . Ans: On your own.



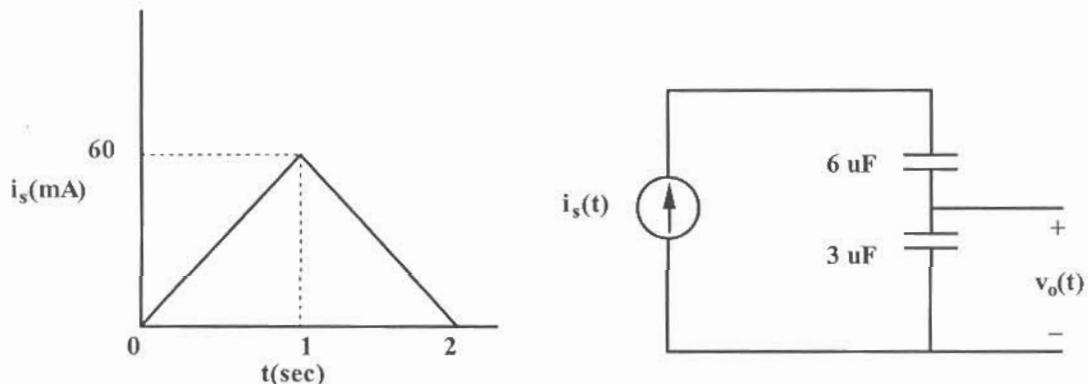- (6) You are given the circuit below. Assume the capacitors are initially uncharged. Find  $v_o(t)$  for  $t > 0$ .




Ans:

$$v_o(t) = 10t^2 10^3 \text{ V} \quad 0 \leq t \leq 1$$

$$v_o(t) = (40t - 10t^2 - 20) 10^3 \text{ V} \quad 1 \leq t \leq 2$$

ECE 301  
HW #3

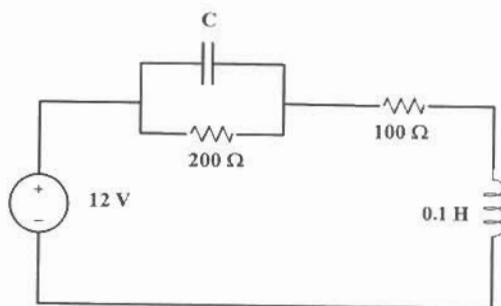- (1) You are given the circuit shown below. Find C (capacitor value) so that the energy stored in the capacitor equals the energy stored in the inductor. Assume the circuit is in steady state.  
Ans: On your own.



In steady state, I from the source

$$\therefore I = \frac{12}{300} = 0.04 \text{ A}$$

$$W_L = \frac{1}{2} L I^2 = \frac{1}{2} \times 0.1 \times (0.04)^2 = 8 \times 10^{-5} \text{ Joules}$$

$$W_L = W_C$$

Capacitor looks like an open circuit  
inductor looks like short circuit.


$$V_C = I \times 200 = 0.04 \times 200 = 8 \text{ V}$$

$$W_C = 8 \times 10^{-5} = \frac{1}{2} C V_C^2$$

$$C = \frac{2 \times 8 \times 10^{-5}}{8^2} = 0.25 \times 10^{-5} \text{ F}$$

$$\boxed{C = 2.5 \mu\text{F}}$$

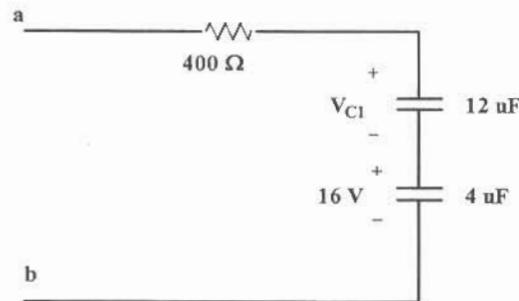- (2) A certain DC voltage has been applied to terminals a-b in the circuit below. The circuit has reached steady state. (a) Determine  $V_{C1}$ . (b) Determine the voltage  $V_{ab}$ . Ans:  $V_{C1}=5.33V$   
 $V_{ab}=21.55V$ .



key:

$$f_{4\mu F} = f_{12\mu F}$$

$$f_{4\mu F} = CV = (4 \times 10^{-6}) \times 16 = 64 \times 10^{-6}$$

$$f_{12\mu F} = 64 \times 10^{-6} = 12 \times 10^{-6} \times V_{C1}$$


$$\boxed{V_{C1} = \frac{64}{12} = 5.33V}$$

$$V_{ab} = V_{C1} + 16$$


$$V_{ab} = 5.33 + 16$$

$$\boxed{V_{ab} = 21.33 V}$$

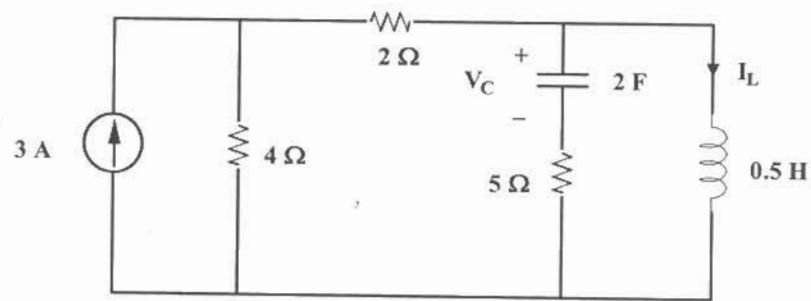- (3) You are given the circuit below. The circuit has reached steady state. Find the following:  
 (a)  $V_c$ , (b)  $I_L$ , (c)  $W_c$ , (d)  $W_L$ . Ans:  $V_c = 0$ ,  $I_L = 2A$ ,  $W_c = 0$ ,  $W_L = 1 J$



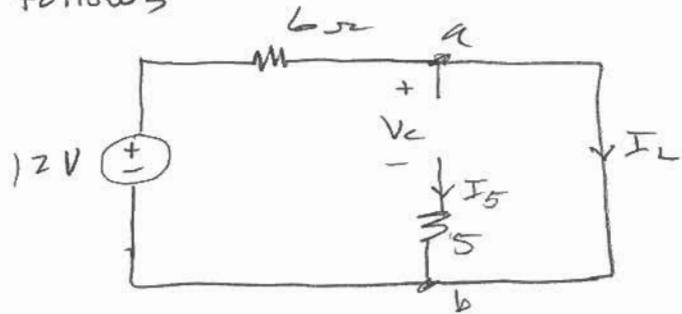In steady state the circuit appears as follows



(a) By inspection, since  $I_5 = 0$  and  $V_{ab} = 0$ ,

$$V_c = 0$$

(b)  $I_L = \frac{12}{6} = 2 A$


(c)  $W_c = \frac{1}{2} C V_c^2 \quad (V_c = 0)$

$$W_c = 0$$


(d)  $W_L = \frac{1}{2} L I_L^2 = \frac{0.5}{2} \times 2^2 = 1 \text{ Joule}$

$$W_L = 1 \text{ J}$$

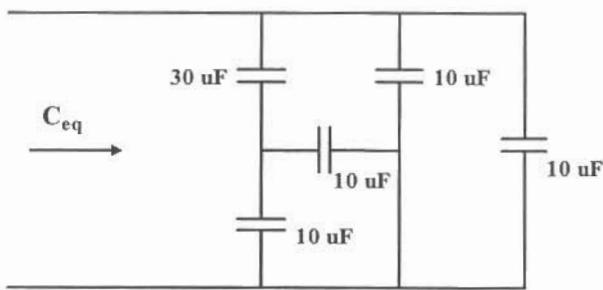
(4) You are given the circuit shown below. Find  $C_{eq}$ . Ans: On your own.



Redraw

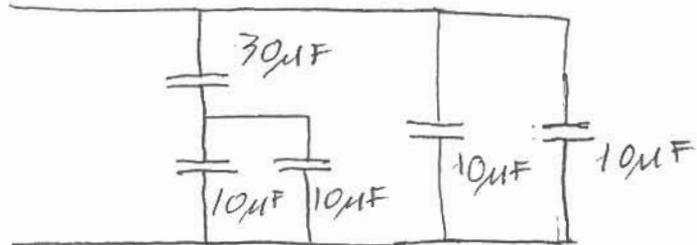


Becomes

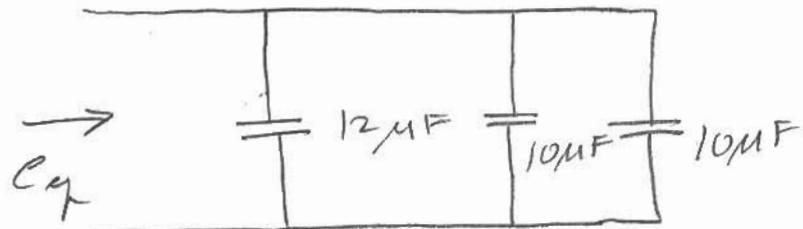


$$C_{eq} = (12 + 10 + 10) \mu F$$

$$\{ C_{eq} = 32 \mu F \}$$

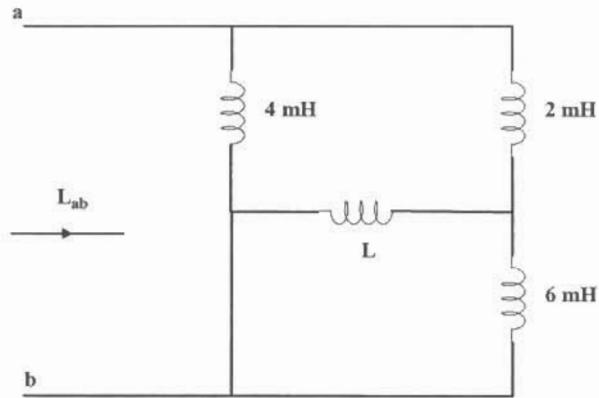- (5) You are given the following circuit. Find L so that  $L_{ab} = 2 \text{ mH}$ . Ans: On your own.



Redraw

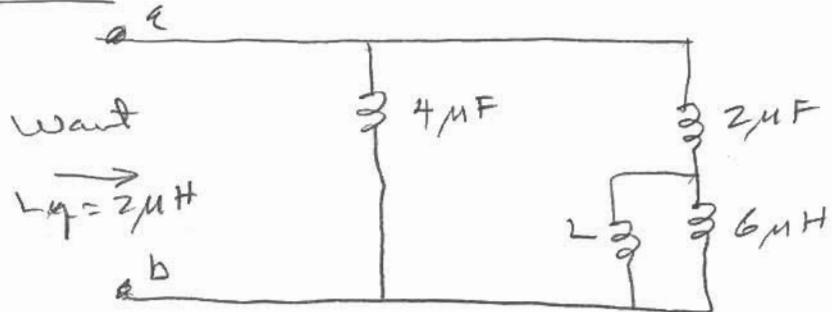

$$L_{eq} = \frac{6 \text{ mH} \times L}{L + 6 \text{ mH}} + 2 \text{ mH} = \frac{6L + 2L + 12}{6 + L}$$

$$L_{eq} = \left( \frac{8L + 12}{6 + L} \right) \text{ mH}$$



$$L_{ab} = \frac{4 \times \left( \frac{8L + 12}{6 + L} \right)}{4 + \left( \frac{8L + 12}{6 + L} \right)} = \left( \frac{32L + 48}{12L + 36} \right) \text{ mH}$$

$$\frac{32L + 48}{12L + 36} \text{ mH} = 2 \mu\text{H}$$

Solve for L

$$\boxed{L = 3 \text{ mH}}$$

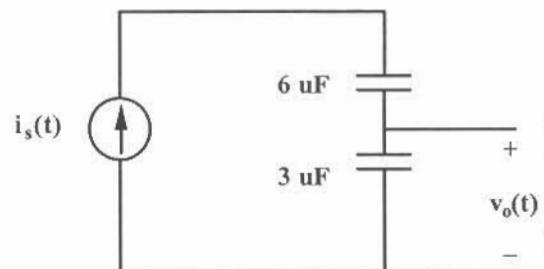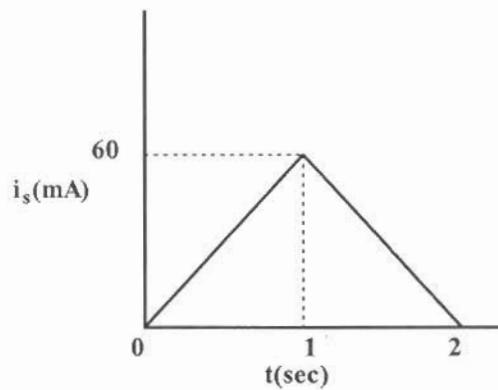- (6) You are given the circuit below. Assume the capacitors are initially uncharged. Find  $v_o(t)$  for  $t > 0$ .



$$1 \geq t > 0$$

Equation of the line

$$i(t) = 60 \times 10^{-3} t$$

$$V = \frac{1}{C} \int_0^t i(t) dt + V(0) \quad V(0) = D$$

$$V = \frac{60 \times 10^{-3}}{3 \times 10^{-6}} \int_0^t t dt = \frac{60 \times 10^{-3}}{6 \times 10^{-6}} t^2$$

$$V(t) = 10 \times 10^3 t^2 \quad 0 \leq t \leq 1$$

Note;

$$V(1) = 10 \times 10^3 \text{ V}$$

$$2 \geq t \geq 1$$

$$i(t) = -60 \times 10^{-3}(t-2)$$

$$\left| \frac{V - V(0)}{t - t_0} \right| = \text{slope}$$

$$i_0 = D, t_0 = 2 \quad \text{slope} = -60 \times 10^{-3}$$

$$V(t) = \frac{-60 \times 10^{-3}}{3 \times 10^{-6}} \int_1^t (t-2) dt + V(1)$$

↑ Note

(6)

$$V(t) = -20 \times 10^3 \left[ \frac{t^2}{2} - 2t \right] + 20 \times 10^3 \left[ \frac{1}{2} - 2 \right] + 10 \times 10^3$$

$$V(t) = \left[ -10 \times 10^3 t^2 + 40 \times 10^3 t \right] - 30 \times 10^3 + 10 \times 10^3$$

40

$$V(t) = \left[ -10 \times 10^3 t^2 + 40 \times 10^3 t - 20 \times 10^3 \right] V$$

DR

$$\boxed{V(t) = [40t - 10t^2 - 20] \times 10^3 V}$$