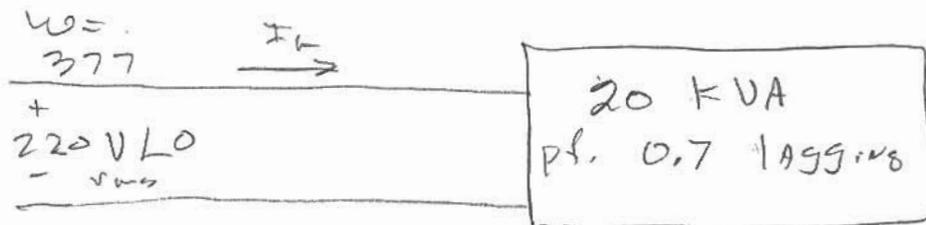


## POWER FACTOR CORRECTION

weg

Suppose we are given the following situation:



(a) Find the  $I_L$  with existing system

Since apparent power is

$$S = V_{rms} I_{rms}$$

and


$$S = 20,000 \text{ VA}$$

$$I_{rms} = \frac{20,000}{220} = 90.91 \text{ A}$$

It is desired to place a capacitor in parallel with the load so that the power factor is changed to 0.97. Find the value of the capacitor and the new value of  $I_L$ .

why

We have

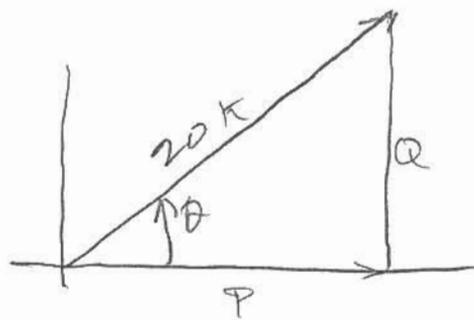

$$\cos \theta = 0.7$$

$$\theta = 45.6^\circ$$

$$P = 20k \cos \theta = 20k \times 0.7 = 14k \text{ W}$$

$$Q_{\text{old}} = 20k \sin 45.6 = 14.29 \text{ kVAR}$$

We want



$$\cos \theta_{\text{new}} = 0.97$$

$$\theta_{\text{new}} = \cos^{-1} 0.97$$

$$\theta_{\text{new}} = 14.07^\circ$$

$$\tan 14.07 = \frac{Q_{\text{new}}}{14k}$$

$$Q_{\text{new}} = 14k \tan 14.07 = 3509 \text{ VAR}$$

$$Q_{\text{cap}} = Q_{\text{old}} - Q_{\text{new}} = 14.29 - 3.509$$

$$Q_{\text{cap}} = 10.78 \text{ VAR}$$

Now,

$$\frac{1}{Z_{\text{cap}}} = \frac{V_{\text{rms}}^2}{Z_{\text{cap}}^*} = \frac{220^2}{j\omega C} = -j 220^2 \omega C$$

but

$$S_{CAP} = -j Q_{CAP} = -j 10.78 \text{ kVAR} = -j 220^2 \omega C$$


90 we have

$$C = \frac{10780}{220^2 \times 377} = 0.6 \text{ mF}$$

$$C = 600 \mu\text{F}$$

A formula
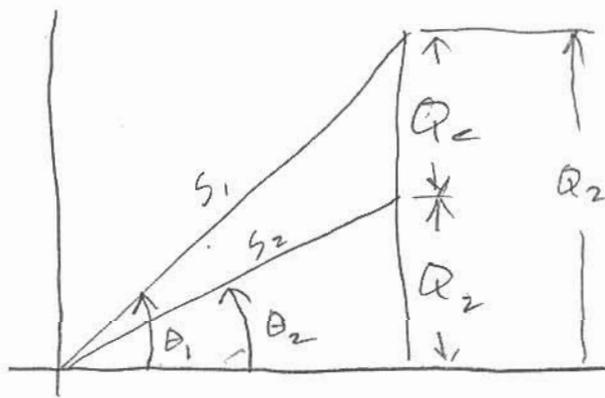
$$C = \frac{P [\tan \theta_1 - \tan \theta_2]}{\omega V_{rms}^2}$$



$$\theta_1 = 45.6^\circ, \quad Q_2 = 14.07$$

$$C = \frac{14,000 [\tan 45.6 - \tan 14.07]}{220^2 \times 377}$$

$$C = 0.0006 \text{ F}$$

Now find  $I_{L_{new}}$

We see that the new load  
Apparent power is

$$\frac{P}{S} = \cos \theta$$

$$S_{new} = \frac{P}{\cos 14.07} = \frac{14,000}{\cos 14.07}$$

$$S_{new} = 14,432 \text{ KVA}$$

$$I_{L_{new}} = \frac{14,432}{220} = 65.6 \text{ A}$$

So we have reduced the  
line current from

$$I_{L_{old}} = 90.91 \text{ A}$$

$$I_{L_{new}} = 65.6 \text{ A}$$