

Work the exam on your own engineering paper. Work on one side of your paper only. Attach your work to the back of this exam sheet and staple in the top left hand corner. You may omit one problem: either problem 1, or 2. Indicate at the top of the exam cover sheet which problem you omit. Each problem counts 25%.

(1) Find the voltage for  $V_o$  for the circuit given in Figure 1. Use any method.

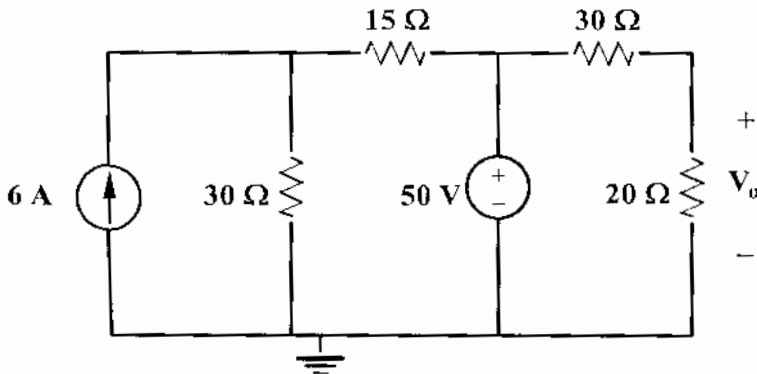


Figure 1: Circuit for problem 1.

(2) You are given the circuit of Figure 2.  
(a) Find the voltage  $V_{ab}$ . Use any method.  
(b) Find the power dissipated in the 10 Ω resistor.

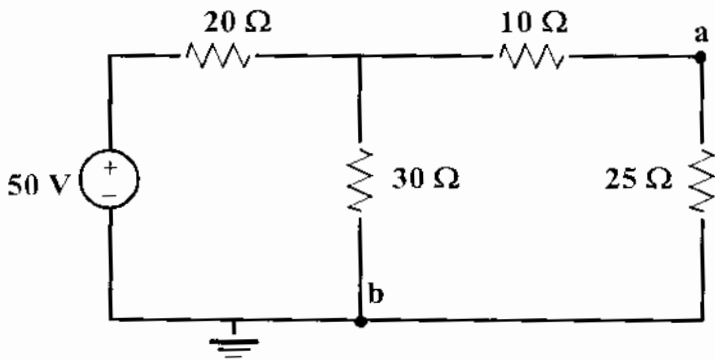


Figure 2: Circuit for problem 2.

- (3) You are given the circuit of Figure 3. Use mesh analysis to find  $I_1$  and  $I_2$ .

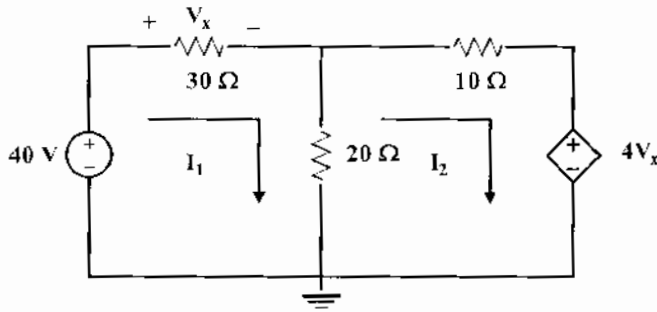


Figure 3: Circuit for problem 3.

- (4) You are given the circuit of Figure 4.  
 (a) Use nodal analysis to find  $V_1$  and  $V_2$ .  
 (b) Find the current  $I_o$  in the  $30\ \Omega$  resistor.

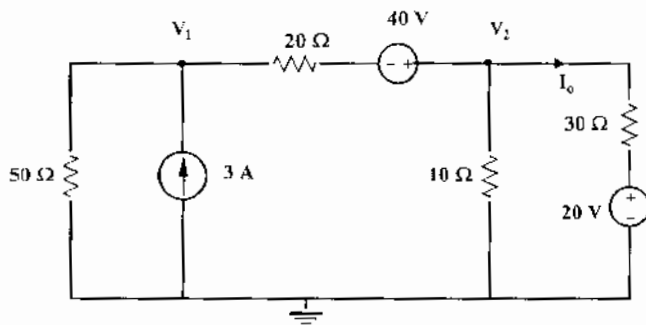


Figure 4: Circuit for problem 4.

- (5) You are given the circuit of Figure 5.  
 (a) Find  $V_{TH}$  and  $R_{TH}$  for the circuit looking into terminals a-b.  
 (b) Draw the Thevenin circuit. Show the terminals a-b on your diagram.  
 (c) Using the information from the Thevenin circuit, draw the Norton equivalent circuit to the left of a-b. Show terminals a-b on your drawing.


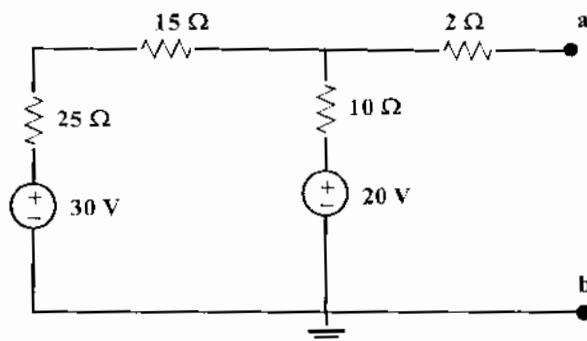


Figure 5: Circuit for problem 5.

Version A

① Find  $V_o$  in the circuit below.

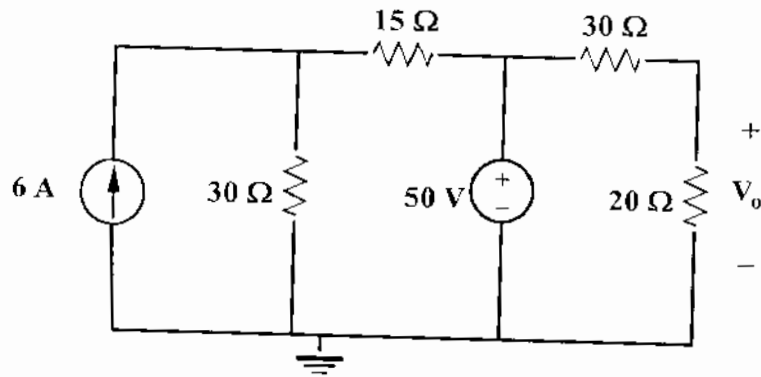


Since the 50V source is directly across the 30Ω and 20Ω resistors, we can use the voltage division rule.

$$V_o = \frac{50 \times 20}{20 + 30}$$

$$V_o = 20V$$

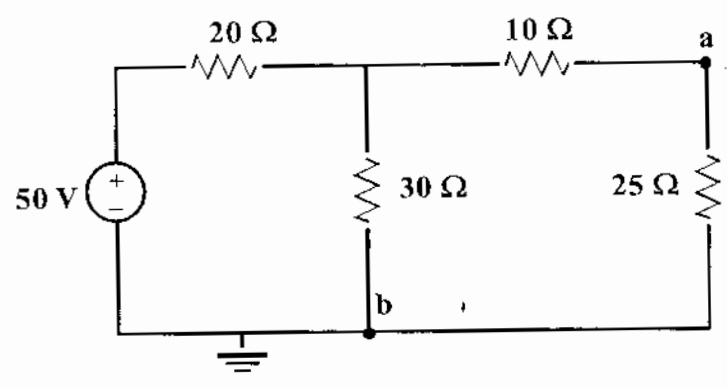
② In the circuit below  
 • find  $V_{ab}$       • find power in  $10\Omega$  resistor



The Thevenin equivalent of the left of  $ab$  is shown below.

$$V_{TH} = \frac{50 \times 30}{20 + 30} = 30V$$
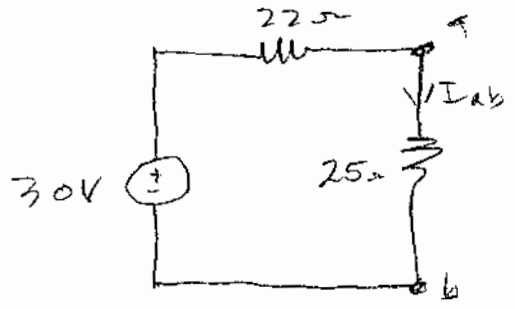
$$R_{TH} = 10 + 20 \parallel 30 = (10 + 12)\Omega$$



$$V_{ab} = \frac{-30 \times 25}{25 + 22} = 15.96V$$


$$V_{ab} = 15.96V$$

$$I_{ab} = I_{10} = \frac{30}{22 + 25} = 0.638A$$

$$P_{10} = (0.638)^2 \times 10$$

$$P_{10} = 4.07W$$

Version A

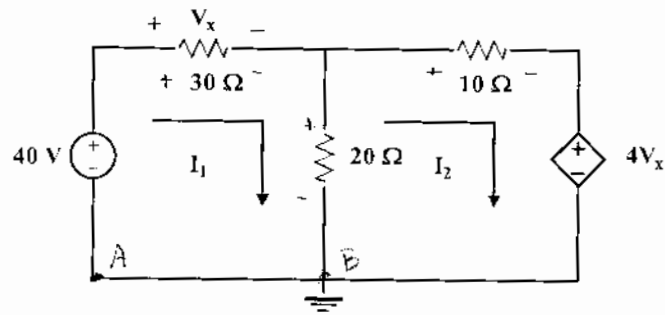③ Use mesh analysis to find  $I_1$  and  $I_2$ .

Start at A, go cw, use drops = 0

$$-40 + 30I_1 + 20(I_1 - I_2) = 0$$

$$\boxed{50I_1 - 20I_2 = 40}$$

Start at B, go cw, use drops = 0

$$-20(I_1 - I_2) + 10I_2 + 4V_x = 0$$

$$\text{but: } V_x = 30I_1$$

$$-20I_1 + 20I_2 + 10I_2 + 4 \times 30I_1 = 0$$

$$\boxed{100I_1 + 30I_2 = 0}$$


$$\begin{bmatrix} 50 & -20 \\ 100 & 30 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \end{bmatrix}$$

$$\boxed{I_1 = 0.343 \text{ A}}$$

$$\boxed{I_2 = -1.143 \text{ A}}$$

Q. 4  
Version A

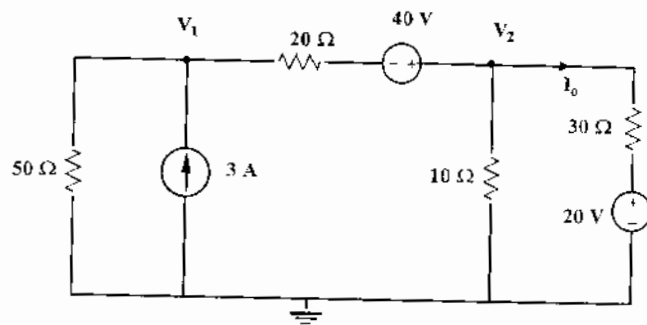- (i) Use nodal analysis to find  $V_1$  and  $V_2$   
(ii) Find  $I_0$  in the  $30\Omega$  resistor.



At  $V_1$

100)

$$\frac{V_1}{50} + \frac{V_1 + 40 - V_2}{20} = 3$$

$$2V_1 + 5V_1 + 200 - 5V_2 = 300$$

$$\boxed{7V_1 - 5V_2 = 100}$$

At  $V_2$

60)

$$\frac{V_2}{10} + \frac{V_2 - 20}{30} + \frac{V_2 - 40 - V_1}{20} = 0$$

$$6V_2 + 2V_2 - 40 + 3V_2 - 120 - 3V_1 = 0$$

$$\boxed{-3V_1 + 11V_2 = 160}$$

$$\begin{bmatrix} 7 & -5 \\ -3 & 11 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 160 \end{bmatrix}$$


$$\boxed{V_1 = 30.65V \quad V_2 = 22.9V}$$

$$I_0 = \frac{V_2 - 20}{30} = 0.097A$$

$$\boxed{I_0 = 0.097A}$$

wkg  
Version A

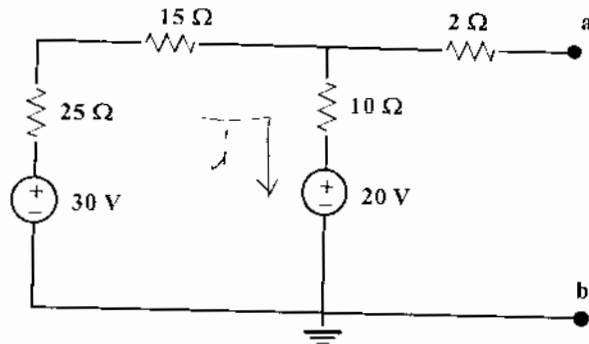- (5) (i) Find  $V_{TH}$ ,  $R_{TH}$ ; show diagram.  
(ii) Give Norton; show diagram.



$R_{TH}$ : Disable 20V and 30V sources:

(i)

$$R_{TH} = 2 + 10 \parallel 40 = 2 + \frac{400}{50} = 10 \Omega$$

$$R_{TH} = 10 \Omega$$

For  $V_{TH}$ :


With a-b open,

$$-30 + 25i + 15i + 10i + 20 = 0$$

$$50i = 10$$


$$i = 0.2 \text{ A}$$
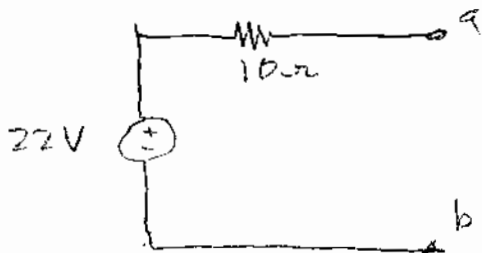
$$V_{ab} = 20 + 10 \times 0.2 = 22 \text{ V} = V_{TH}$$



Thevenin ckt

(ii)

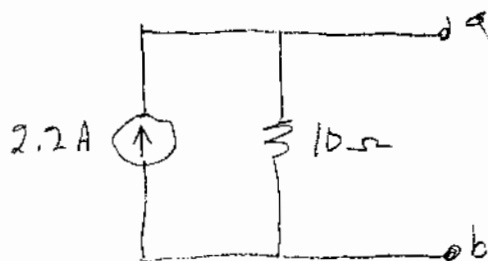

Norton ckt