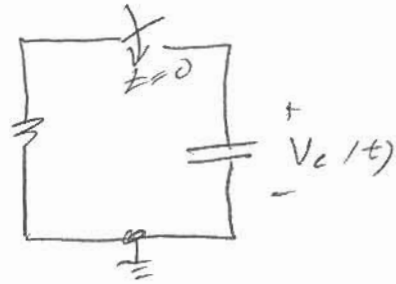


ECE 301  
TRANSIENTS PART II

RC & RL Transients

The force free RC ckt.



$$V_c(0) = V_c$$

$$\frac{V_c}{R} + C \frac{dV_c}{dt} = 0$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = 0$$


$$s + \frac{1}{RC} = 0 \quad \text{ch. eq}$$

$$V_c(t) = k e^{-\frac{t}{RC}} = k e^{-\frac{t}{\tau}}$$

$$\tau = RC$$
$$k = V_c$$

$$V_c(t) = V_c e^{-\frac{t}{RC}}$$

The force free RL ckt

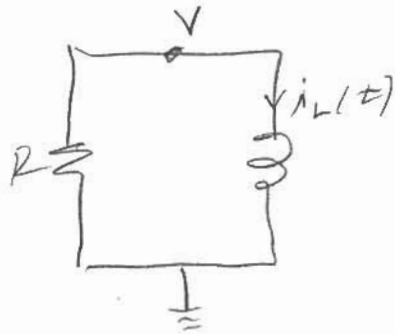

$$i_L(0) = I_L$$

$$\frac{V}{R} + i_L = 0$$

$$V = L \frac{di_L}{dt}$$


$$\frac{L}{R} \frac{di_L}{dt} + i_L = 0$$

$$\frac{di_L}{dt} + \frac{i_L}{L/R} = 0$$

$$\tau = \frac{L}{R}$$

$$i_L(t) = I_L e^{-\frac{Rt}{L}}$$

FORCED RC CKT

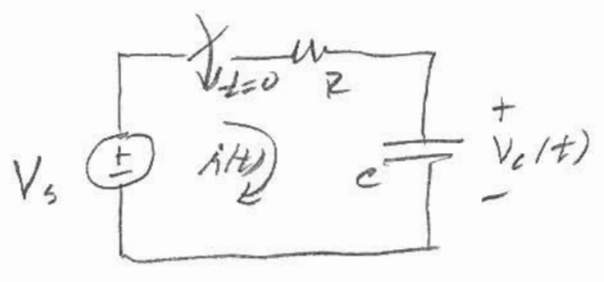

$$V_s = Ri + V_c$$

$$i = C \frac{dV_c}{dt}$$

$$RC \frac{dV_c}{dt} + V_c = V_s$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = \frac{V_s}{RC}$$

$$V_c = V_{pc} + V_{ne}$$

$$V_{pc} = K$$

$$\frac{K}{RC} = \frac{V_s}{RC}$$

$$K = V_s = V_c(\infty)$$

$$V_c(t) = V_s + K_H e^{-\frac{t}{RC}}$$

$$V_c(0) = 0 = V_c(0^+) = V_s + K_H$$

$$K_H = V_c(0^+) - V_s = V_c(0^+) - V_s(\infty)$$

$$V_c(t) = V_s - V_s e^{-\frac{t}{\tau}}$$


Also

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{\tau}}$$

$\tau = RC$ ,  $V_c(\infty) = V_s$ , thus use  $V_c(0) = 0$

$$V_c(t) = V_s - V_s e^{-\frac{t}{RC}}$$

For the forced RL ckt

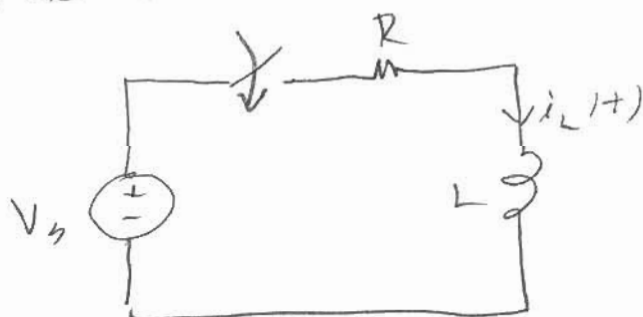

$$V_s = Ri_L + L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} + \frac{i_L}{L/R} = \frac{V_s}{L}$$

differential equation tech.

#

$$i_L = i_{PL} + i_{NL}$$

$$i_{PL} = K$$

$$\frac{RK}{L} = \frac{V_s}{L}$$

$$K = \frac{V_s}{R} = i_L(\infty)$$

$$i_L(t) = \frac{V_s}{R} + K_H e^{-\frac{Rt}{L}}$$

$i_L(0^+) = 0$  (current can't change instantaneously through the inductor)

$$0 = \frac{V_s}{R} + K_H$$

$$K_H = -\frac{V_s}{R}$$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-\frac{Rt}{L}})$$

step-by-step tech.


Also

$$i_L(t) = i_L(\infty) + (i_L(0^+) - i_L(\infty)) e^{-\frac{t}{\tau}}$$

$$i_L(\infty) = \frac{V_s}{R}, \quad i_L(0^+) = 0 \quad (\text{here})$$

Example

GIVEN

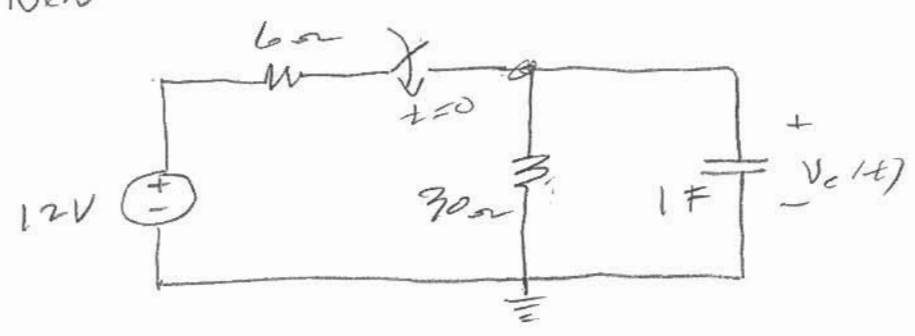

All IC's are zero.

(a) solve for  $V_c(t)$  using d.e. technique

(b) solve for  $V_c(t)$  using step-by-step technique

$t < 0 ; V_c(0^-) = V_c(0^+) = 0$

(a) using nodal analysis:

$$\frac{V_c - 12}{6} + \frac{V_c}{30} + \frac{dV_c}{dt} = 0$$

$$5V_c - 60 + V_c + 30 \frac{dV_c}{dt} = 0$$

$$30 \frac{dV_c}{dt} + 6V_c = 60$$

$$\frac{dV_c}{dt} + \frac{V_c}{5} = 2$$

$$V_c = V_{cp} + V_{cn}$$

$$V_{cp} = K_p$$

$$\frac{k_p}{5} = 2$$

$$k_p = 10$$

$$V_c(t) = 10 + k_H e^{-0.2t}$$

$$0 = 10 + k_H$$

$$V_c(t) = 10 - 10 e^{-0.2t}$$

(b) Step-by-step

$$V_c(0^+) = 0, \quad V_c(\infty) = \frac{12 \times 30}{36}$$

$$V_c(\infty) = 10 \text{ V}$$

$$R_{eq} = \frac{30 \times 6}{30 + 6} = \frac{180}{36} = 5$$

$$R_{eq} C = \tau = 5$$

$$V_c(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{\tau}}$$


$$V_c(t) = 10 - 10 e^{-0.2t}$$

Example 2


For the circuit below, obtain the expression for  $i(t)$  using

(a) d.e. technique

(b) step-by-step technique

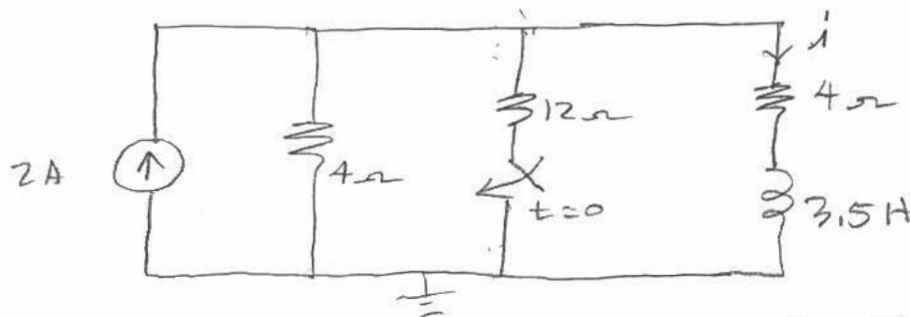

$t < 0$

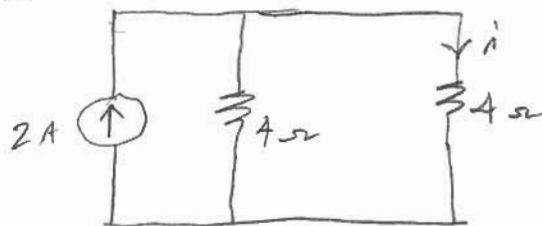

$$i(0^-) = 1 \text{ A} = i(0^+)$$

(a) d.e. approach


Using Thevenin



$$7i + 3.5 \frac{di}{dt} = 6$$

$$\frac{di}{dt} + 2i = \frac{6}{3.5}$$

$t = \infty$

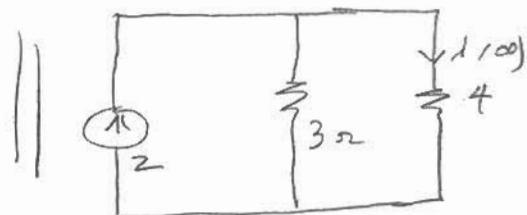

$$\frac{4 \times 12}{4 + 12} = 3 \Omega$$

$$i(\infty) = \frac{2 \times 3}{7} = \frac{6}{7} \text{ A}$$

$$i = i_p + i_N$$

$$i_p = K_p$$

$$2K_p = \frac{6}{3.5}$$

$$K_p = \frac{3}{3.5} = 0.857$$

$$i = \frac{3}{3.5} + K_N e^{-2t} = 1$$

$$K_N = 1 - \frac{3}{3.5} = \frac{0.5}{3.5}$$

$$i(t) = \frac{3}{3.5} + \frac{0.5}{3.5} e^{-2t}$$

(6) Step by step

$$i(\infty) = \frac{2 \times \frac{1}{4}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{4}} = \frac{6}{1+3+3} = \frac{6}{7}$$

$$i(\infty) = \frac{3}{3.5}$$

$$i(0^+) = 1 \text{ A}$$

$$i(t) = \frac{3}{3.5} + \left(1 - \frac{3}{3.5}\right) e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R} = \frac{3.5}{3+4} = \frac{3.5}{7} = \frac{1}{2}$$


$$i(t) = \frac{3}{3.5} + 0.5 e^{-2t}$$




Example 3

Find  $i_o(t)$

6.27

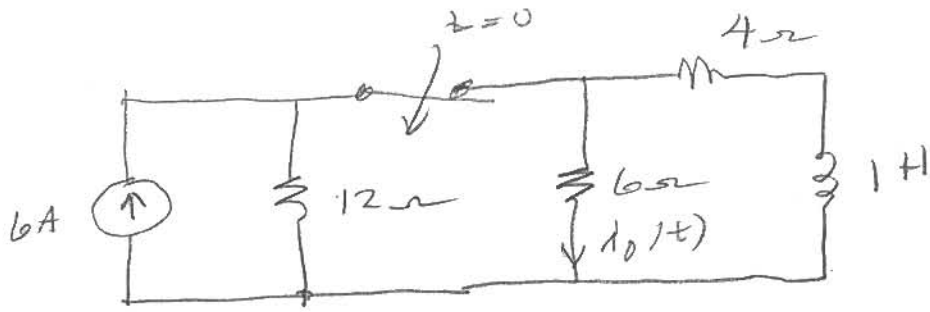


$t < 0$

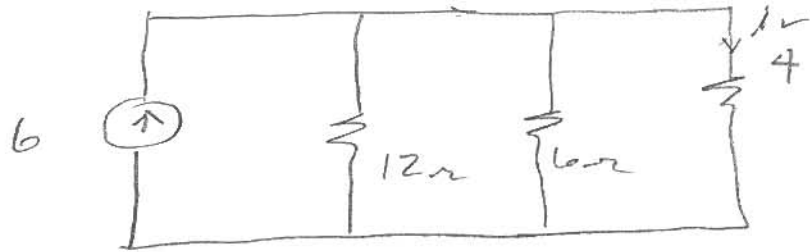

$$i_L(0^-) = i_L(0^+) = \frac{6 \times \frac{1}{4}}{\frac{1}{12} + \frac{1}{6} + \frac{1}{4}}$$


$$i_L(0^+) = \frac{18}{1 + 2 + 3} = \frac{18}{6} = 3 \text{ A}$$

$t > 0$

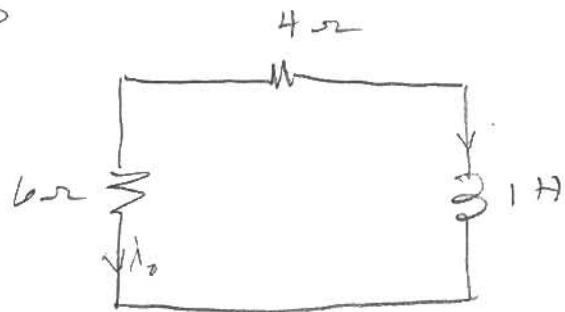

$$i_o = -3e^{-10t}$$

Example 4

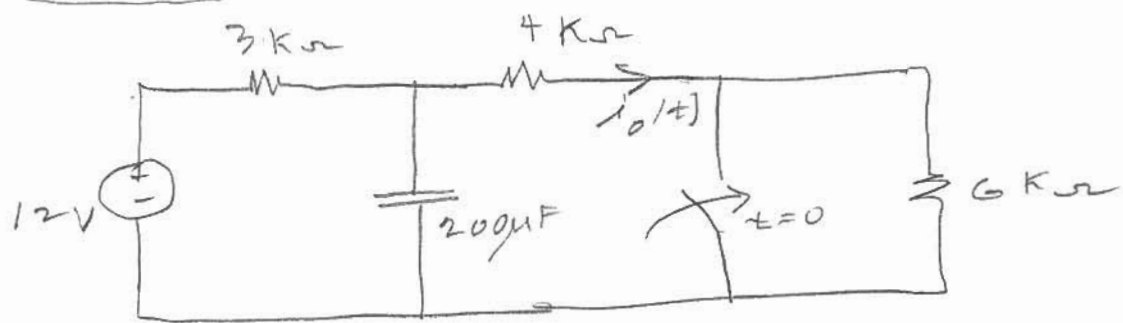

Find  $i_o(t)$ .

ON Your Own.

Ans: (Answer book) Not verified

$$i_o(t) = 2 + 0.5 e^{-3.75t}, \text{ A } t > 0$$