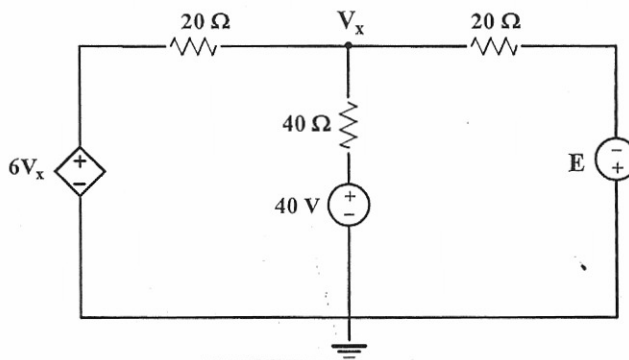


(1) You are given the circuit of Figure 1. Find the value of E that will make $V_x = 0$ volts.



Using Nodal Analysis

At V_x

$$\frac{V_x - 6V_x}{20} + \frac{V_x - 40}{40} + \frac{V_x + E}{20} = 0$$

$$2V_x - 12V_x + V_x - 40 + 2V_x + 2E = 0$$


$$-7V_x - 40 + 2E = 0$$

$$\text{If } V_x = 0,$$


$$2E = 40$$

$$E = 20 \text{ V}$$

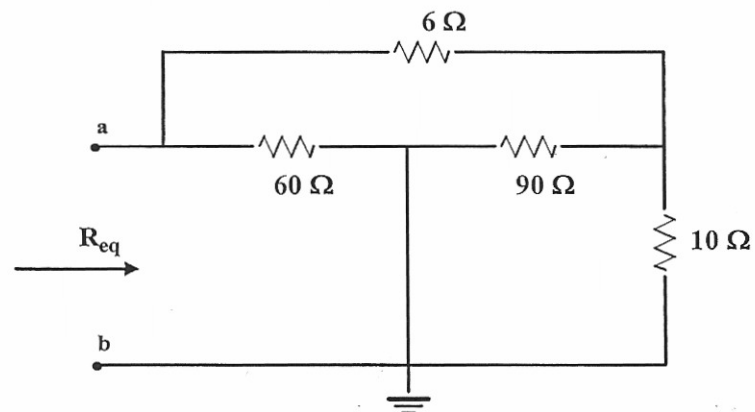(2) You are given the circuit of Figure 2. Solve for R_{eq} , resistance looking into terminals a-b.




Re-draw the circuit:

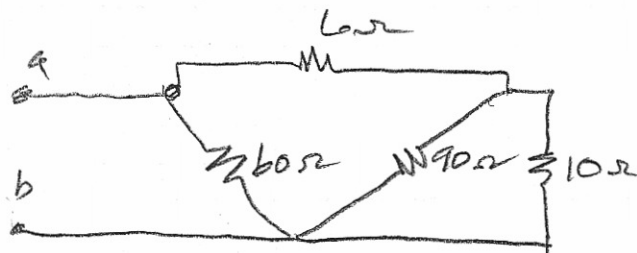

$$(10 \parallel 90 + 6) \parallel 60 = 12 \Omega$$
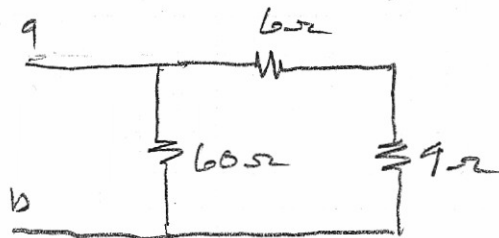
$$90 \parallel 10 = \frac{900}{100} = 9 \Omega$$




$$R_{eq} = R_{ab} = 60 \parallel 15 = \frac{60 \times 15}{60 + 15} = 12 \Omega$$

$$R_{eq} = 12 \Omega$$

(3) You are given the circuit of Figure 3.

(a) Find the power supplied by the 40 V source.

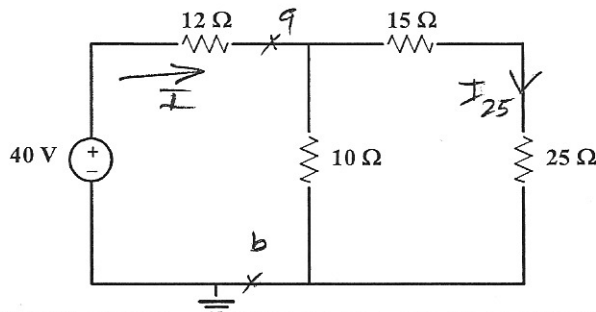(b) Find the power absorbed by the 25 Ω resistor.



Resistance to the right of a-b

$$R_{ab} = 10 \parallel 40 = \frac{400}{10+40} = \frac{400}{50}$$

$$R_{ab} = 8 \Omega$$

Resistance seen by the source = $12 + 8 = 20 \Omega$

$$I = \frac{40}{20} = 2 \text{ A}$$

Using current division

$$I_{25} = \frac{I \times 10}{10 + 40} = \frac{2 \times 10}{50} = 0.4 \text{ A}$$


$$P_{Abs_{25}} = I_{25}^2 \times 25 = (0.4)^2 \times 25 = 4 \text{ W}$$

$$P_{Abs_{25}} = 4 \text{ W}$$

$$P_{sup_{40}} = 40 \times I = 40 \times 2 = 80 \text{ W}$$

$$P_{sup_{40}} = 80 \text{ W}$$

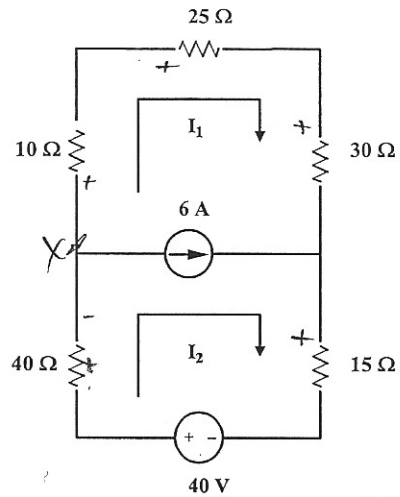(4) You are given the circuit of Figure 4. Use mesh analysis to solve for I_1 and I_2 .



$$10I_1 + 25I_1 + 30I_1 + 15I_2 - 40 + 40I_2 = 0$$

$$65I_1 + 55I_2 = 40$$

CONSTRAINT


$$I_1 - I_2 = -6$$

$$\begin{bmatrix} 65 & 55 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 40 \\ -6 \end{bmatrix}$$

$$I_1 = -2.417 \text{ A}$$

$$I_2 = 3.58 \text{ A}$$

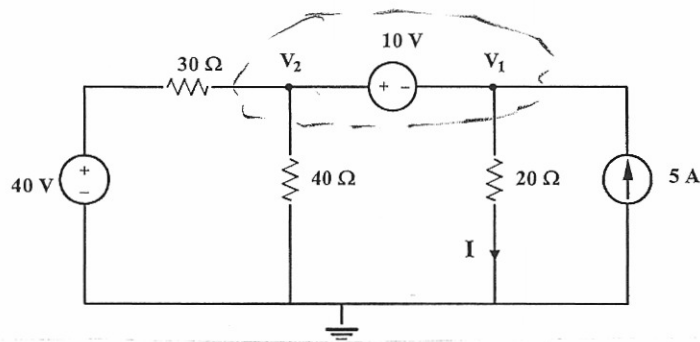(5) You are given the circuit of Figure 5. Use nodal analysis to find the current I as indicated.



Super Mesh

$$120 \quad \frac{V_2 - 40}{30} + \frac{V_2}{40} + \frac{V_1}{20} = 5$$

$$4V_2 - 160 + 3V_2 + 6V_1 = 600$$

$$6V_1 + 7V_2 = 760$$

CONSTRAINT

$$V_2 - 10 - V_1 = 0$$

$$-V_1 + V_2 = 10$$

$$\begin{bmatrix} 6 & 7 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 760 \\ 10 \end{bmatrix}$$

$$V_1 = 53.08V$$

$$V_2 = 63.08V$$

$$I = \frac{V_1}{20} = \frac{53.08}{20}$$

$$I = 2.65A$$