

ECE 301
Test 4A

- (1) You are given the linear transformer circuit shown in Figure 1. Find the input impedance Z_{in} of the circuit.


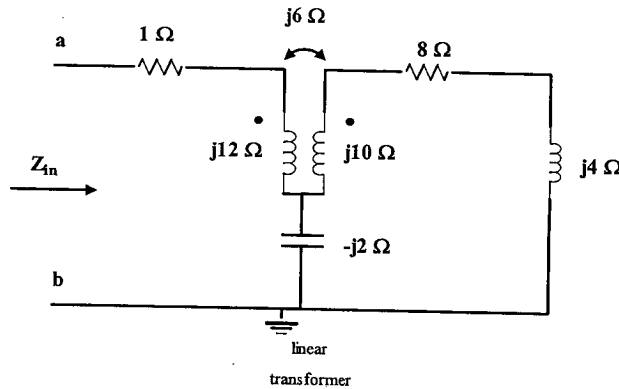


Figure 1: Circuit for problem 1.

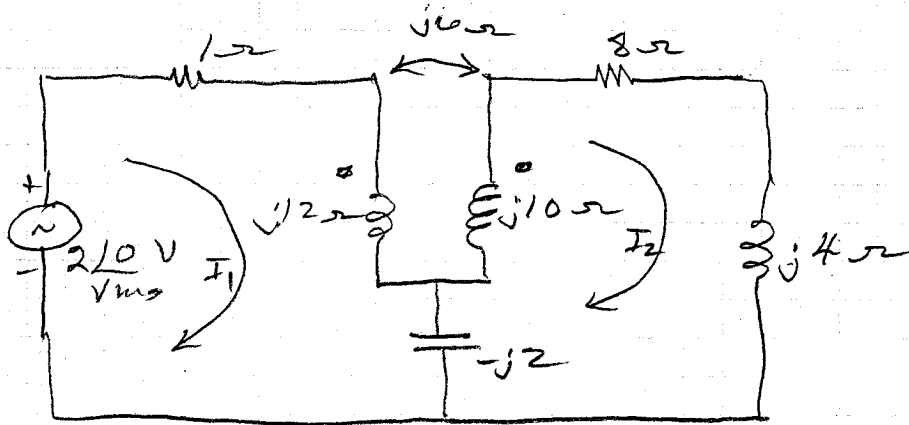

$$(1 + j12 - j2)I_1 + j2I_2 - j6I_2 = 2\angle 0$$

$$(1 + j10)I_1 - j4I_2 = 2\angle 0$$

$$(-j2 + j10 + 8 + j4)I_2 + j2I_1 - j6I_1 = 0$$

$$-j4I_1 + (8 + j12)I_2 = 0$$


$$I_2 = 0.196 \angle -80$$

$$Z_{ab} = \frac{2\angle 0}{0.2169 \angle -80}$$

$$Z_{ab} = 9.22 \angle 80^\circ \Omega$$

A

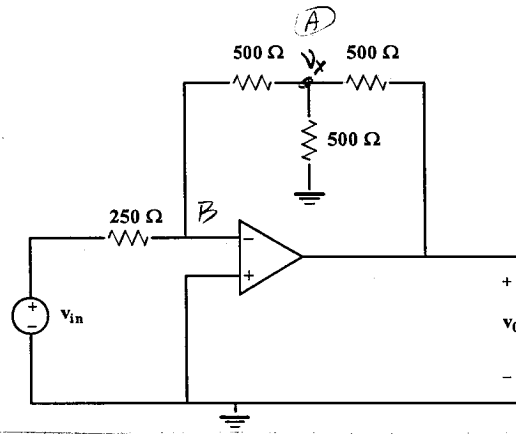(2) Find the output voltage v_0 in terms of the input voltage v_{in} for the op amp circuit of Figure 2.



$$\text{At B} \quad \frac{0 - v_{in}}{250} + \frac{0 - v_x}{500} = 0$$

$$-2v_{in} - v_x = 0$$

$$v_x = -2v_{in}$$


At A

$$\frac{v_x - 0}{500} + \frac{v_x}{500} + \frac{v_x - v_0}{500} = 0$$

$$v_0 = 3v_x$$

$$v_0 = -6v_{in}$$

Counter Example #2

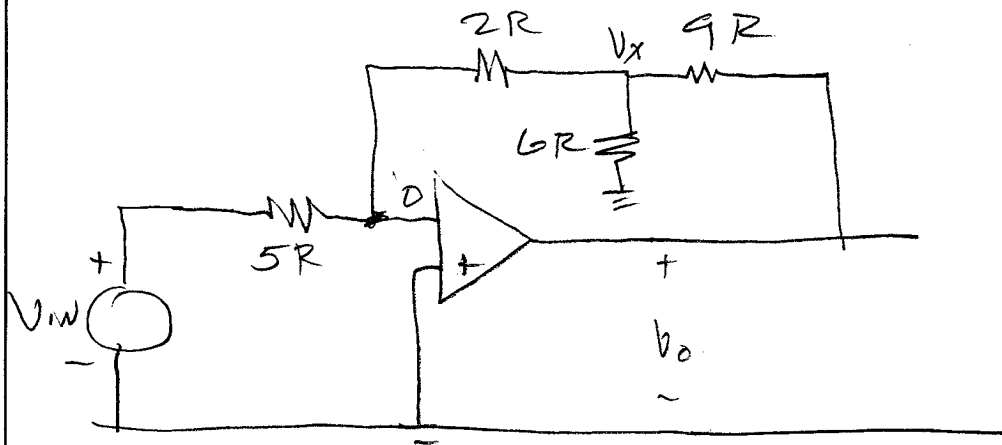

$$-\frac{V_{IN}}{5R} + \frac{-V_X}{2R} = 0 \quad \left(\frac{V_X}{2} = -\frac{V_{IN}}{5} \right)$$

$$\left(V_X = -\frac{2}{5} V_{IN} \right)$$

$$\frac{V_X}{2R} + \frac{V_X}{6R} + \frac{V_X - V_O}{9R} = 0$$

$$54 \left(\frac{V_X}{2R} + \frac{V_X}{6R} + \frac{V_X}{9R} = \frac{V_O}{9R} \right)$$

$$27V_X + 9V_X + 6V_X = 6V_O$$

$$42V_X = 6V_O$$

$$V_O = \frac{42}{6} \left(-\frac{2}{5} \right) V_{IN} = -\frac{84}{30} V_{IN} = -\frac{14}{5} V_{IN}$$


Other way

$$-\frac{V_{IN}}{5R} + \frac{-V_O}{17R} = 0$$

$$V_O = -\frac{17}{5} V_{IN}$$

Does not agree

Counter Example #2

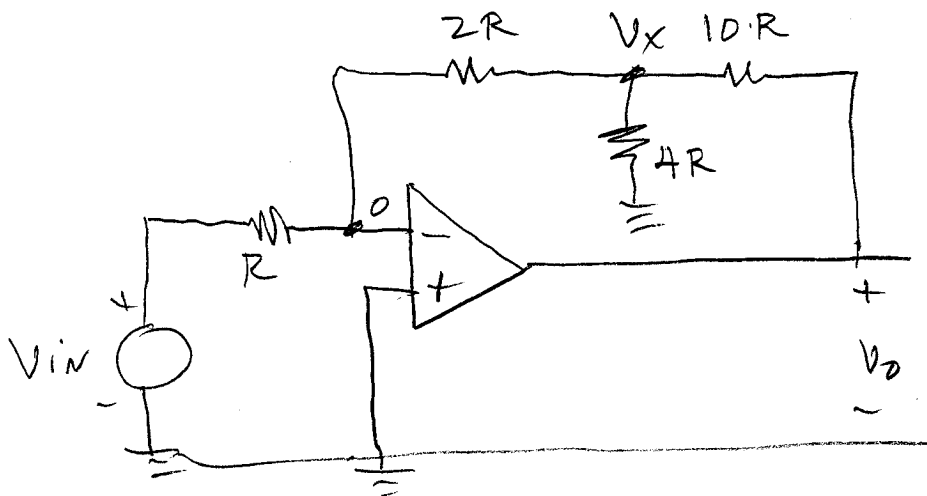

$$-\frac{V_{in}}{R} + \frac{(-V_x)}{2R} = 0$$

$$-2V_{in} - V_x = 0$$

$$\underline{V_x = -2V_{in}}$$

At V_x

$$20 \left(\frac{V_x - 0}{2R} + \frac{V_x}{4R} + \frac{V_x - V_0}{10R} \right) = 0$$

$$10V_x + 5V_x + 2V_x - 2V_0 = 0$$

$$2V_0 = 17V_x = 17(-2V_{in})$$

$$\boxed{V_0 = -17V_{in}}$$


$$-\frac{V_{in}}{R} - \frac{V_0}{16R} = 0$$

$$V_{in} = -\frac{V_0}{16}$$

$$\boxed{V_0 = -16V_{in}}$$

Does not agree

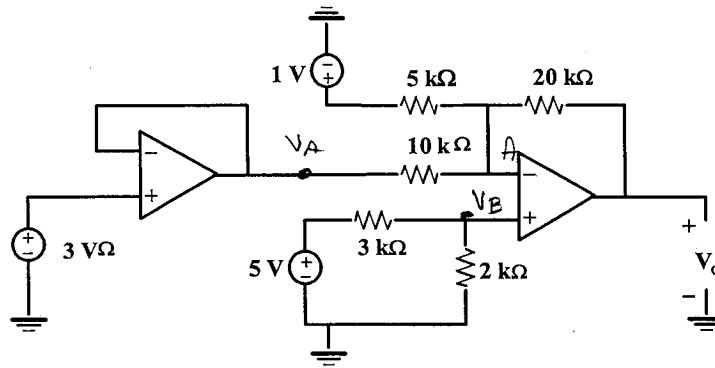(3) Find the output voltage, V_o , for the op amp circuit shown in Figure 3.



$$V_A = 3V$$

$$V_B = \frac{5 \times 2k}{3k + 2k} = 2V$$

At A


$$\frac{V_B - 3}{10k} + \frac{V_B - 1}{5k} + \frac{V_B - V_o}{20k} = 0$$

$$-2 + 4 + 2 - V_o = 0$$


$$V_o = +4V$$

(4) You are given the ideal transformer shown in Figure 4.

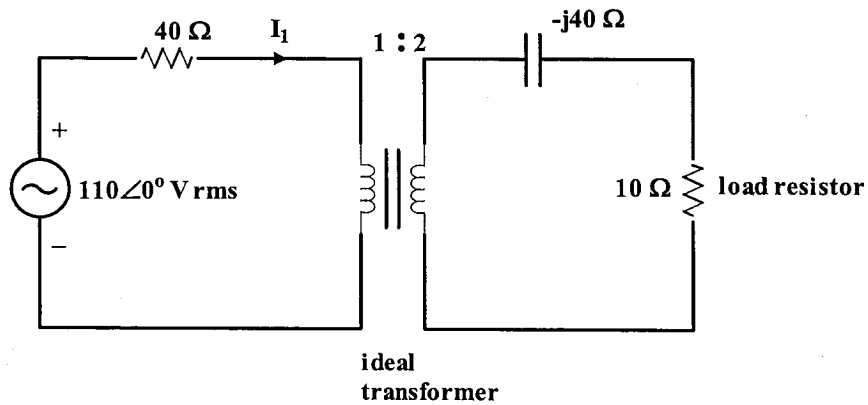- (a) Find the phasor current I_1 .
 (b) Find the power dissipated in the 10Ω load resistor.



Reflect secondary to primary

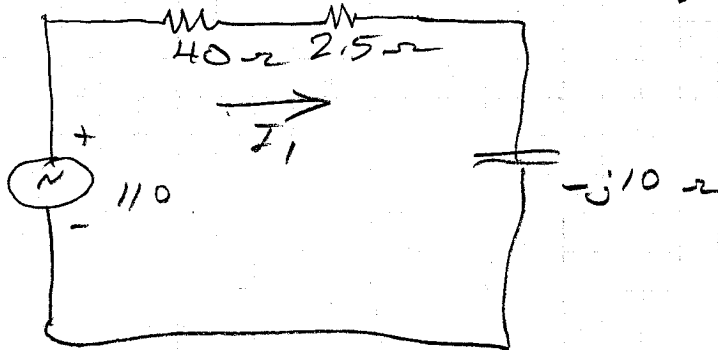

$$\vec{I}_1 = \frac{110 \angle 0^\circ}{42.5 - j10} = 2.52 \angle 13.24^\circ \text{ A rms} = 2.45 + j.577 \text{ A rms}$$


$$\left| \frac{I_1}{I_2} \right| = 2$$

$$|I_2| = 0.5 |I_1| = 1.26 \text{ A rms}$$

$$P_{10} = |I_2|^2 \times 10 = 15.88 \text{ W}$$

(4) This is a tedious and really unnecessary way to work the problem, but I will. One should use reflected impedance

For the answers desired (I_1 & $|I_2|$) it does not matter how I assume dots. I will use the following.

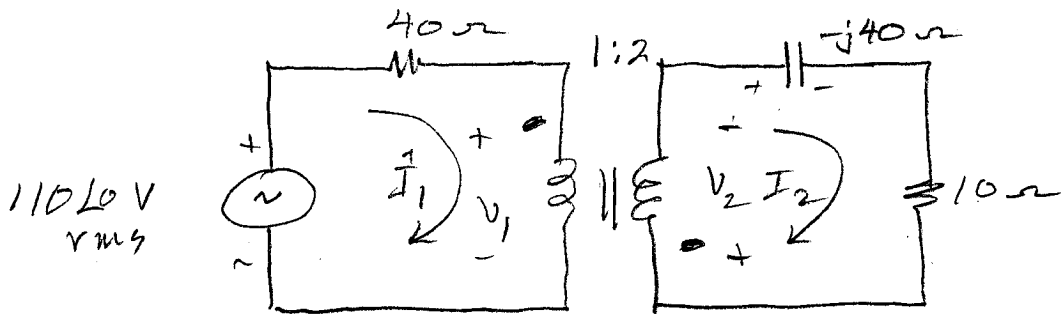

mesh 1

$$V_1 + 40I_1 = 110\angle 0$$

OR

$$40I_1 + 0I_2 + V_1 + 0V_2 = 110\angle 0$$

mesh 2

$$(10 - j40)I_2 + V_2 = 0$$

OR

$$0I_1 + (10 - j40)I_2 + 0V_1 + V_2 = 0$$

$$\frac{V_2}{V_1} = 2$$

OR

$$0I_1 + 0I_2 + 2V_1 - V_2 = 0$$

$$\frac{I_1}{I_2} = -2$$

OR

$$I_1 + 2I_2 + 0V_1 + 0V_2 = 0$$

(7) or

3

$$\begin{bmatrix} 40 & 0 & 1 & 0 \\ 0 & 10 - j40 & 0 & 1 \\ 0 & 0 & 2 & -1 \\ 1 & 2 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 110 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Need I_1 & I_2

$$I_1 = 2.52 \angle 13.2^\circ \text{ A rms}$$

$$I_2 = 1.26 \angle -166.7^\circ \text{ A rms}$$

(6)

$$P_{10} = |I_2|^2 \times 10 = (1.26)^2 \times 10$$

$$P_{10} = 15.88 \text{ W}$$

Real average power always has zero phase angle.