

Example problems using the step by step are presented below.

Example 1:

(From Irwin, p 278, 8th Edition)

In the circuit below, the switch has been open for a long time. It is closed at $t=0$. Find $i(t)$ for $t > 0$. Use the step-by-step method.

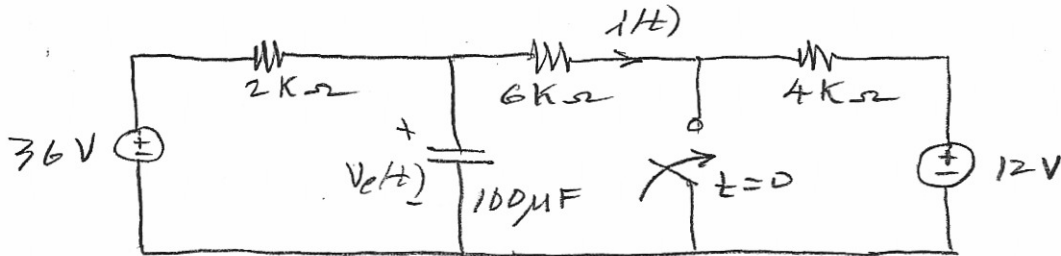


Fig 1

For $t < 0$, we first determine $V_c(0^-)$ from the following circuit

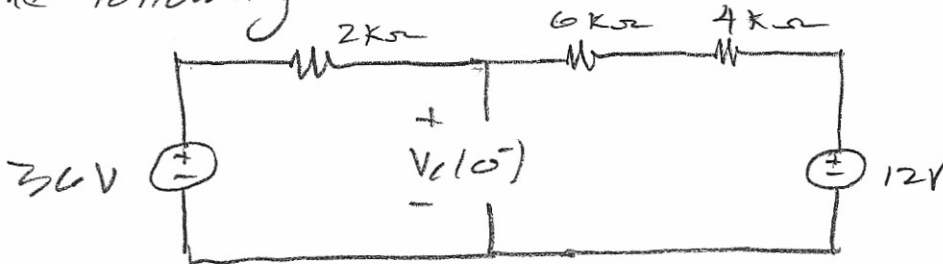


Fig 2

It is easy to find that $V_c(0^-) = 32V$

Now, at $t = 0^+$, we have the following circuit

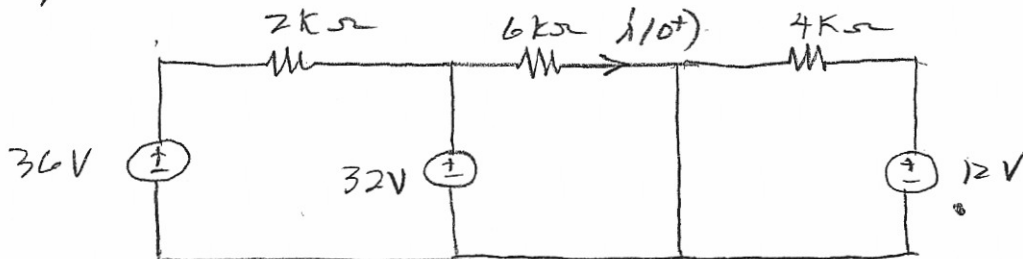


Fig 3.

Example 1 cont.

10X.2

We find that

$$i(10^+) = \frac{32}{6k} = \frac{16}{3} \text{ mA}$$

For $t \rightarrow \infty$, the circuit appears as follows

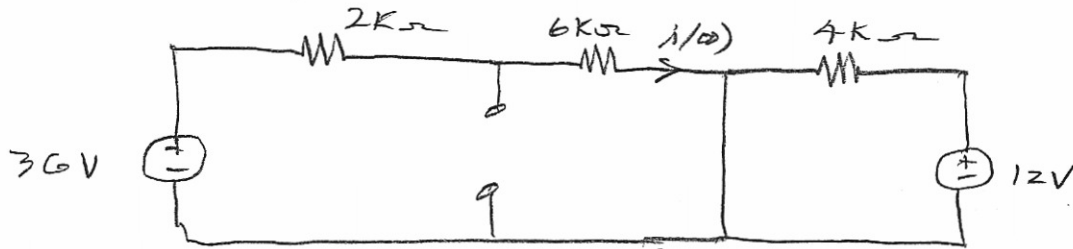


Fig 4

$$i(\infty) = \frac{36}{8} = \frac{9}{2} \text{ mA}$$

To find τ

(Disable all independent sources and look into the terminals where the capacitor is located,

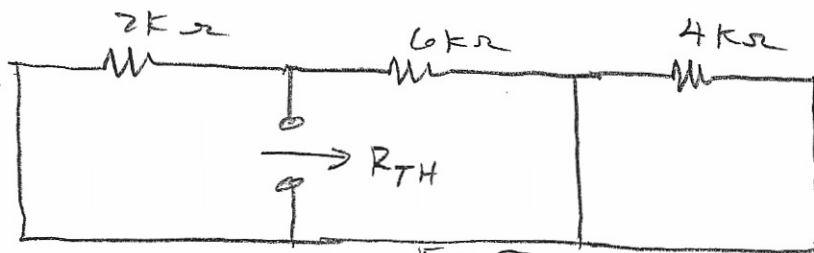


Fig 5


$$R_{TH} = \frac{2k \times 6k}{2k + 6k} = \frac{3}{2} k\Omega \Rightarrow \tau = .15 \text{ sec}$$

Then $i(t) = i(\infty) + [i(10^+) - i(\infty)]e^{-\frac{t}{.15}}$


$$i(t) = \left[\frac{9}{2} + \frac{5}{6} e^{-\frac{t}{.15}} \right] \text{ mA}$$

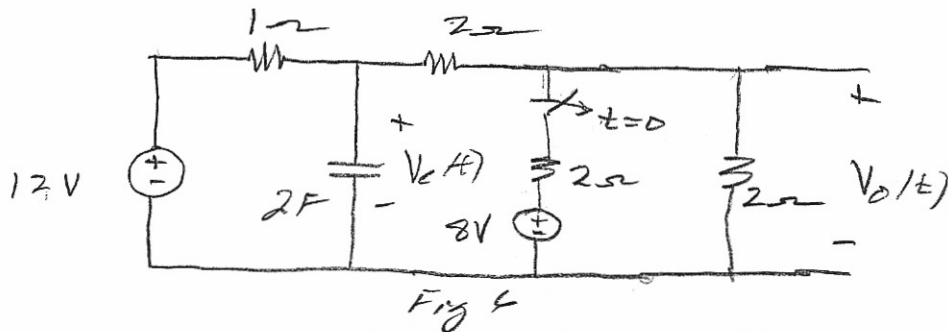Example 2

You are given the following circuit. Find $V_o(t)$ for $t > 0$. Assume the switch has been closed for a long time and is opened at $t = 0$.



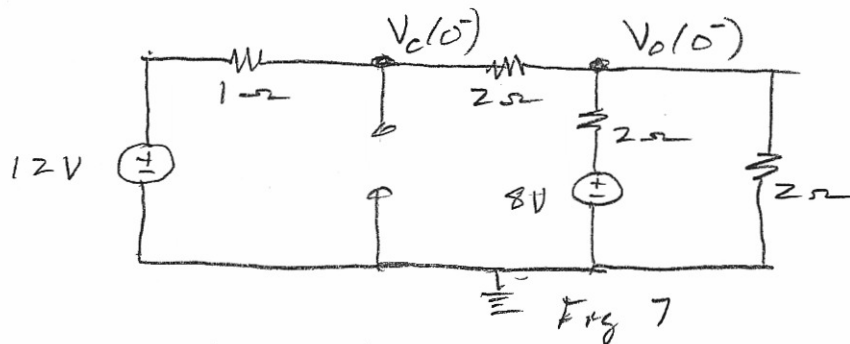We use the following circuit to find $V_o(0^-)$ and $V_c(0^-)$.



By nodal analysis:

$$\text{At } V_c(0^-) \quad \frac{V_c(0^-) - 12}{1} + \frac{V_c(0^-) - V_o(0^-)}{2} = 0$$

$$\text{OR} \quad 2V_c(0^-) - 24 + V_o(0^-) - V_o(0^-) = 0$$

$$\boxed{3V_c(0^-) - V_o(0^-) = 24}$$

At $V_o(0^-)$

$$\frac{V_o(0^-) - V_c(0^-)}{2} + \frac{V_o(0^-) - 8}{2} + \frac{V_o(0^-)}{2} = 0$$

$$\boxed{-V_c(0^-) + 3V_o(0^-) = 8}$$

Example 2; cont.

$$\begin{bmatrix} 3 & -1 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} V_{c5} \\ V_{c0} \end{bmatrix} = \begin{bmatrix} 24 \\ 8 \end{bmatrix}$$

$$V_c(0^-) = V_c(0^+) = 10 \text{ V}$$

$$V_o(0^-) = 6 \text{ V}$$

FOR $t = 0^+$, WE HAVE

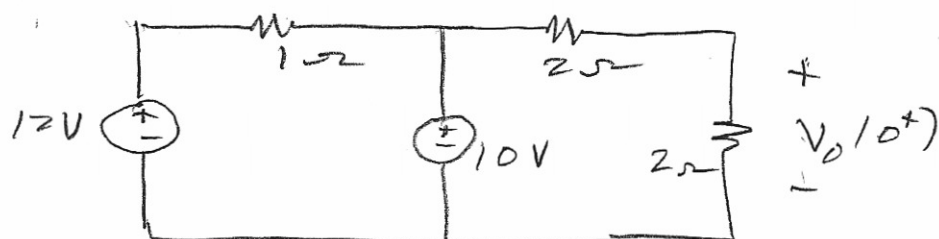


Fig 8

$$V_o(0^+) = \frac{10 \times 2}{2 + 2} = 5 \text{ V}$$

FOR DETERMINING R_{eq}

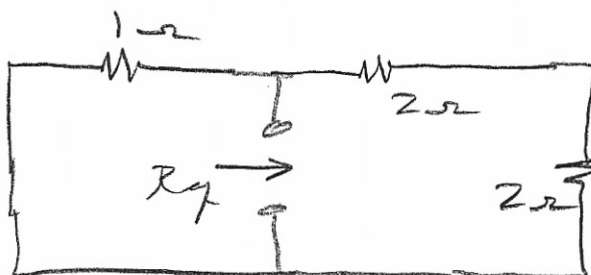


Fig 9

$$R_T = \frac{1 \times 4}{1 + 4} = \frac{4}{5}$$

$$R_T = 0.8 \Omega$$

$$R_{eq} = 2 \times 0.8 = 1.6 \Omega$$

We need $V_o(\infty)$. We find this by assuming the capacitor acts like an open circuit. We use Fig 10 to find $V_o(\infty)$.

Example 2; cont

10x.5

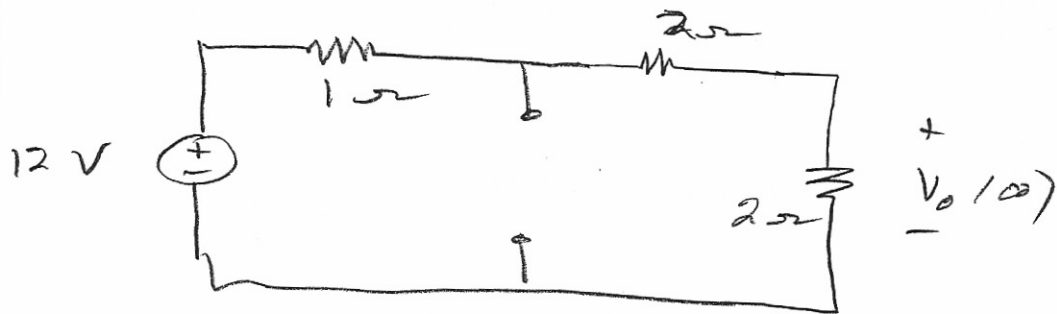


Fig 10

$$V_o(\infty) = \frac{2 \times 12}{1 + 2 + 2} = \frac{24}{5} \text{ V}$$

so


$$V_o(t) = V_o(\infty) + [V_o(0^+) - V_o(\infty)] e^{-\frac{t}{\tau}}$$

$$V_o(0^+) = \frac{24}{5} + \left[5 - \frac{24}{5} \right] e^{-\frac{5}{8}t}$$

$$V_o(t) = \left(\frac{24}{5} + \frac{1}{5} e^{-\frac{5}{8}t} \right) \text{ V, } u(t)$$

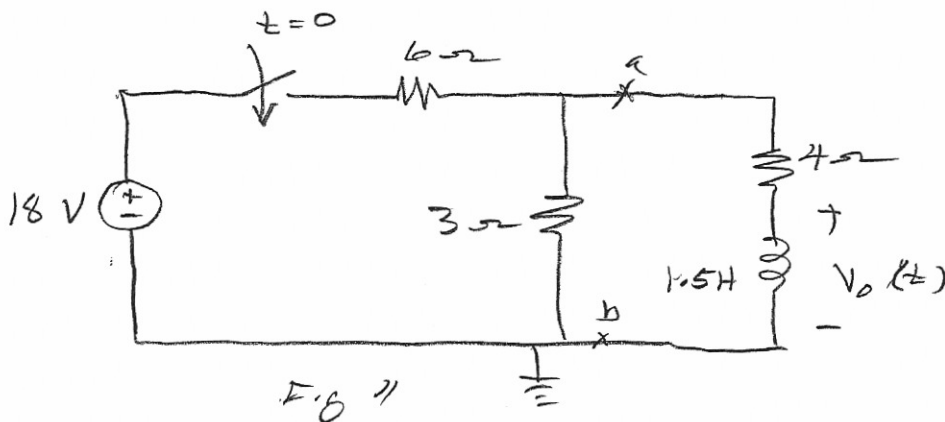Example 3

In the following circuit, find $V_o(t)$.
Sketch the waveform with the time axis calibrated.



For $t < 0$, $V_o(t^-) = 0$, $i(t^-) = 0 = i(t^+)$

Just after the switch is closed ($t = 0^+$)

The inductor looks like an open circuit.

No current flows through the 4Ω resistor.

So the voltage $V_o(t^+) = V_{ab}(t^+)$. We

find

$$V_{ab}(t^+) = V_o(t^+) = \frac{18 \times 3}{3 + 6} = 6V$$

We find R_{eq} in the following ckt.

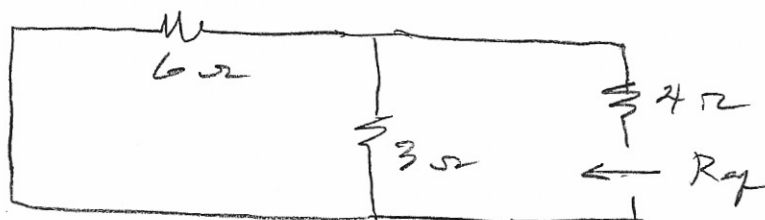


Fig 12

Example 3: cont

Therefore


$$R_{eq} = 4 + 3 \parallel 6 = 4 + 2$$

$$R_T = 6 \Omega$$

$$\tau = \frac{L}{R} = \frac{1.5}{6} = \frac{1}{4}$$

We then have

$$V_o(t) = V_o(\infty) + [V_o(0^+) - V_o(\infty)] e^{-\frac{t}{\tau}}$$

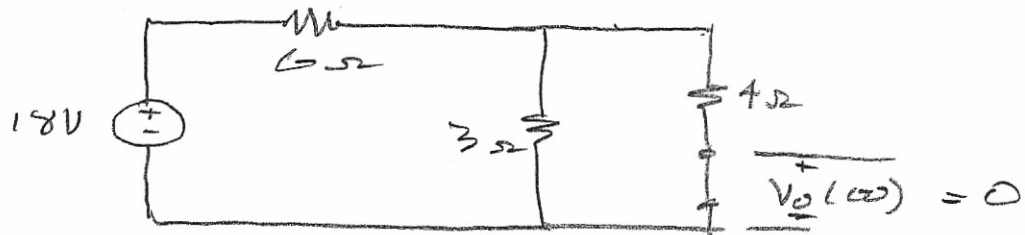We find $V_o(\infty)$ from Fig 13

$$V_o(t) = V_o(0^+) e^{-\frac{t}{\tau}}$$

$$V_o(t) = 6 e^{-4t} \text{ V, } u(t)$$