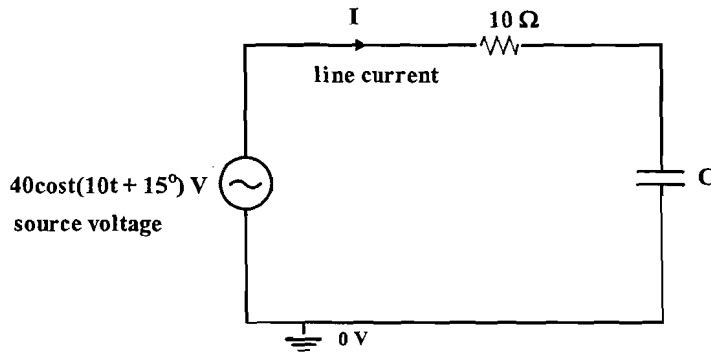


WTV

- (1) You are given the circuit of Figure 1 with the indicated source voltage and line current. The line current is known to be; $\mathbf{I} = 2.83 \angle 60^\circ \text{ A}$. Determine the approximate value of the capacitor C .



$$\mathbf{Z} = \frac{\vec{V}}{\vec{I}}$$

where $\vec{V} = 40 \angle 15^\circ \text{ V}$ $\vec{I} = 2.83 \angle 60^\circ \text{ A}$


$$\mathbf{Z} = \frac{40 \angle 15^\circ}{2.83 \angle 60^\circ} = 9.99 - j9.99$$

$$\mathbf{Z} = R + \frac{1}{j\omega C} = 10 - \frac{j}{\omega C}$$

$$\frac{-j}{\omega C} = -j9.99$$


$$C = \frac{1}{10 \times 10} = 0.01 \text{ F}$$

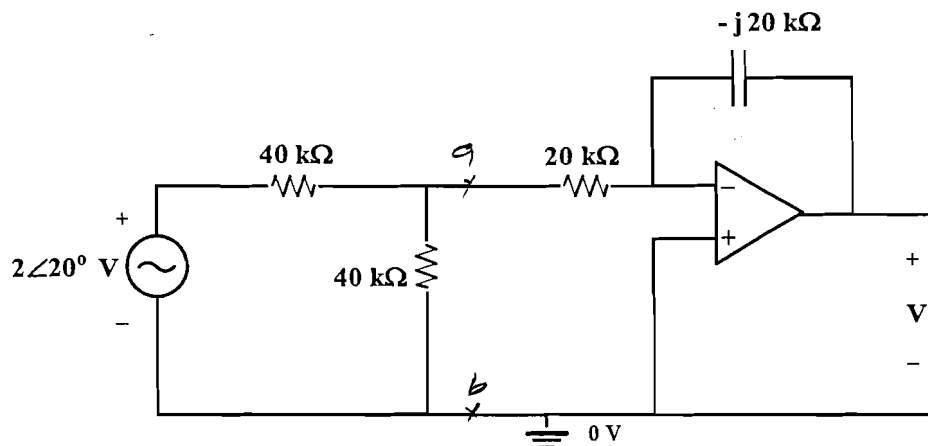- (2) You are given the op-amp circuit of Figure 2. Determine the phasor output voltage V as shown in the circuit diagram. Express V in polar form.



Thevenin to the left of a-b

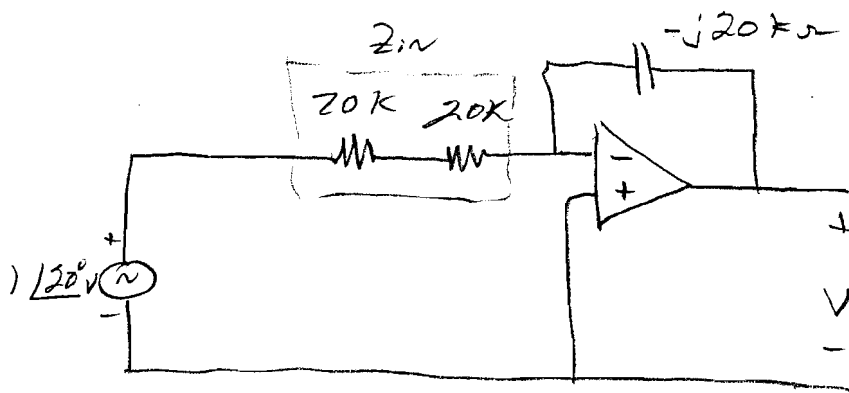
$$V_{TH} = 1\angle 20^\circ \text{ V}; R_{TH} = 20 \text{ k}\Omega$$



$$\vec{V} = -1\angle 20^\circ \times \frac{Z_{FB}}{Z_{IN}} = \frac{1\angle -160 (20\angle -90) \text{ k}}{40 \text{ k}}$$

$$\vec{V} = 0.5\angle 110^\circ \text{ V}$$

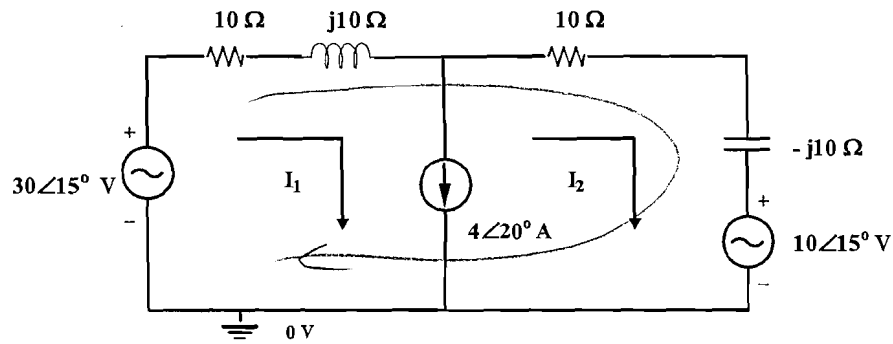- (3) You are given the AC circuit shown in Figure 3. Use mesh analysis to find the mesh currents I_1 and I_2 as indicated in the circuit diagram. Express I_1 and I_2 in polar form.



Supermesh

$$-30\angle 15^\circ + (10 + j10)I_1 + (10 - j10)I_2 + 10\angle 15^\circ = 0$$

$$(10 + j10)I_1 + (10 - j10)I_2 = 20\angle 15^\circ$$

Constraint


$$I_1 - I_2 = 4\angle 20^\circ$$

$$\begin{bmatrix} (10 + j10) & (10 - j10) \\ 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20\angle 15^\circ \\ 4\angle 20^\circ \end{bmatrix}$$

$$I_1 = 3.65\angle -14.9^\circ \text{ A} \quad I_2 = 2.32\angle -95.7^\circ \text{ A}$$

(4) You are given the AC circuit shown in Figure 4.

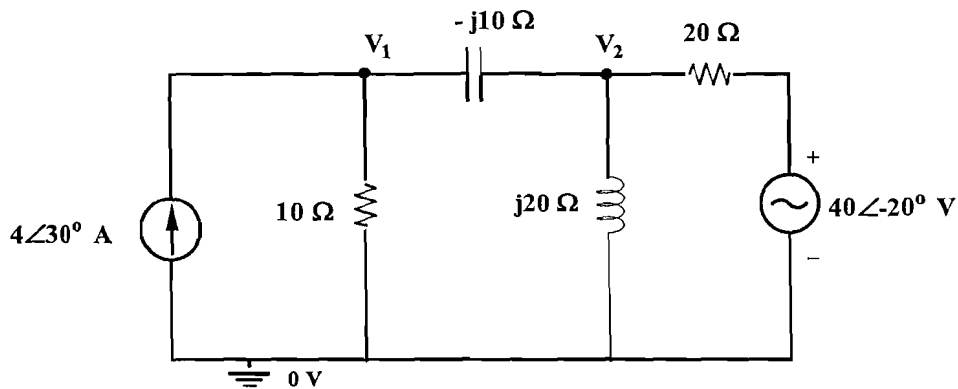- (a) Use nodal analysis to find the node voltages V_1 and V_2 as indicated in the circuit diagram.
Express V_1 and V_2 in polar form.
 (b) Prepare a phasor diagram showing V_1 and V_2 . Which voltage is leading? Explain.



At node V_1 ,

$$\frac{V_1}{10} + \frac{V_1 - V_2}{-j10} = 4\angle 30^\circ$$

$$0.1V_1 + j0.1V_1 - j0.1V_2 = 4\angle 30^\circ$$

$$(0.1 + j0.1)V_1 + (0 - j0.1)V_2 = 4\angle 30^\circ$$

At node V_2

$$\frac{V_2 - V_1}{-j10} + \frac{V_2}{j20} + \frac{V_2 - 40\angle -20^\circ}{20} = 0$$

$$j0.1V_2 - j0.1V_1 - j0.05V_2 + 0.05V_2 = 2\angle -20^\circ$$

$$(0 - j0.1V_1) + (0.05 + j0.05)V_2 = 2\angle -20^\circ$$


$$\begin{bmatrix} (0.1 + j0.1) & (0 - j0.1) \\ (0 - j0.1) & (0.05 + j0.05) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4\angle 30^\circ \\ 2\angle -20^\circ \end{bmatrix}$$

$$V_1 = 34.11 \angle 27.9^\circ \text{ V}$$

$$V_2 = 33.19 \angle 38.1^\circ \text{ V}$$

(4)

3B-4-2

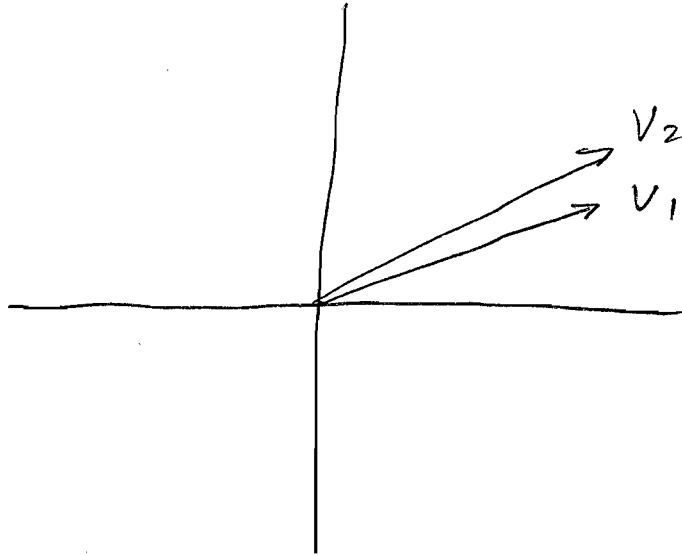


V_2 leads V_1 by $38.1 - 27.9 = 10.2^\circ$

(5) The load for a certain AC circuit is shown in Figure 5.

(a) Find the impedance of this load, Z , as indicated in the diagram. Express Z in polar form.

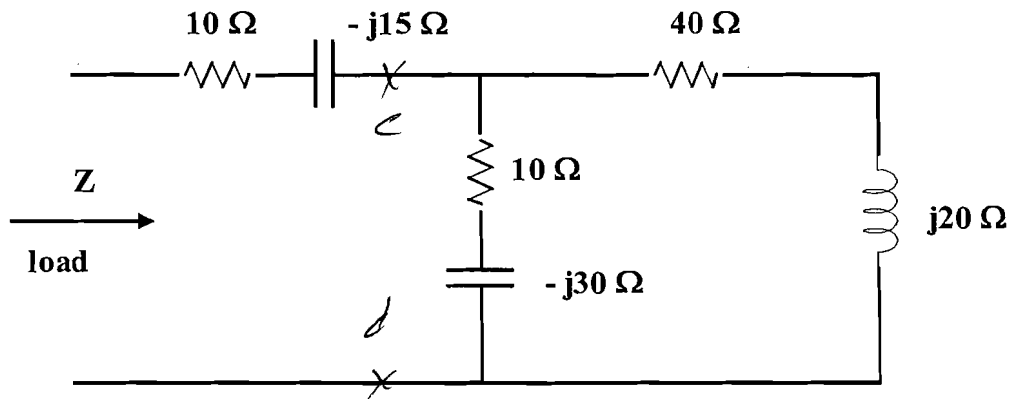(b) Determine whether this is a leading or lagging load. Explain your answer.



$$Z_{cd} = \frac{(40 + j20)(10 - j30)}{40 + j20 + 10 - j30} = \frac{(40 + j20)(10 - j30)}{(50 - j10)}$$

$$Z = 10 - j15 + Z_{cd}$$

$$Z = 44.9 \angle -42.6^\circ \Omega$$