

Desk Copy

ECE 301
Fall Semester, 2007
HW Set # 4

Due: October 9, 2007
wlg

Name Green
Print(last, first)

Use Engineering Paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 15 points.

4.7 (a) $v_c = 50$ for $t < 0$, $= 50e^{-50t}$ V $t > 0$; $v_R = 0$ for $t < 0$, $= 50e^{-50t}$ V $t > 0$

(b) $p_R(t) = 2500e^{-100t}$ W (c) 25 μ J

4.11 $R = 4.33$ M Ω

4.17 (a) $i(0^+) = 1$ mA,

(b) $\frac{di(t)}{dt} + \frac{1}{R} \left[\frac{1}{C_1} + \frac{1}{C_2} \right] i(t) = 0$

(c) 50 msec

(d) $i(t) = e^{-20t}$ mA

(e) 50 V

4.23 $i = 5$ mA, $v_x = 10$ V, $v_c = -15$ V

4.28 $v_R = 0$, $t < 0$ $v_R = 10e^{-0.5t}$ V, $t \geq 0$

4.32 $i(t) = 0$ for $t < 0$; $i(t) = (1 - e^{-20t})$ A, $t \geq 0$

4.35 $i(t) = (0.5 - 0.5e^{-200t})$ A, $t \geq 0$


$v_L = 100e^{-200t}$ V $t \geq 0$

4.48 $i(t) = (1/60)e^{-300t} - (1/60)\cos 300t + (1/60)\sin 300t$ A $t \geq 0$

Use MATLAB to plot the above function. Plot for the time range of $t = 0: 0.001: 0.25$;
A copy of the expected plot is attached to this sheet. Turn in both your plot and a copy of your
MATLAB program.

ECE 301
Homework #4
Fall semester, 2007

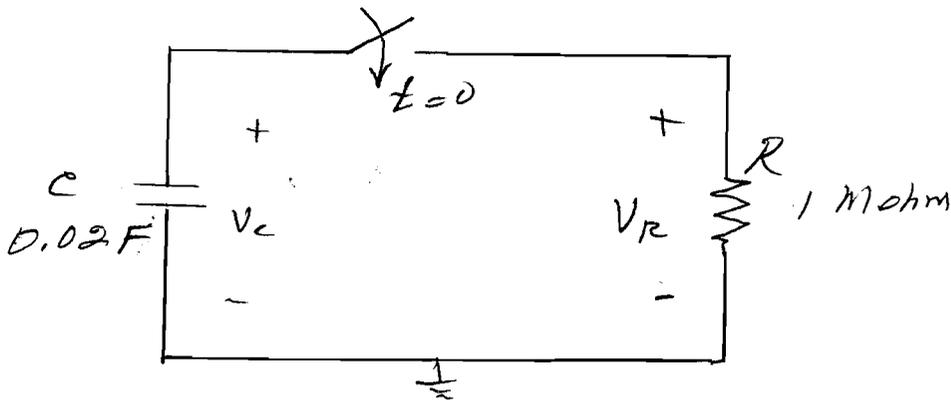4.7 In the circuit below, the capacitor is charged to 50 V prior to closing the switch at $t=0$.



(a) FIND expressions for the voltage across the capacitor and voltage across the resistor using nodal analysis

$$C \frac{dV_c}{dt} + \frac{V_c}{R} = 0$$

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = 0 \quad (1)$$

Assume $V_c = K e^{st}$

Substitute into (1), perform the math leads to

$$s + \frac{1}{RC} = 0$$

4.7 (continue)

2

We have $\tau = RC = 1 \times 10^{-6} \times .02 \times 10^{-6}$

$$\tau = .02 \quad \frac{1}{\tau} = 50$$

so

$$V_c(t) = k e^{-50t}$$

To evaluate k , use initial condition of capacitor voltage.

We know that for the capacitor

$$V_c(0^-) = 50 \text{ V} = V_c(0^+)$$

$$\left. V_c(t) \right|_{t=0} = 50 = \left. k e^{-50t} \right|_{t=0} = k$$

$$\therefore V_c(t) = 50 e^{-50t} \text{ V} \quad t \geq 0$$

From the circuit diagram we know that $V_c(t) = V_R(t)$,

then

$$V_R(t) = 50 e^{-50t} \text{ V} \quad t \geq 0$$

QED

4.7 (cont)

3

(b) Find the expression for the power delivered to the resistor.

We know in general that

$$P_R = \frac{V_R^2}{R} \text{ and for this}$$

case

$$P_R = \frac{[50 e^{-50t}]^2}{1 \times 10^{-6}}$$

$$P_R = \frac{2500 e^{-100t}}{1 \times 10^{-6}} = 2500 e^{-100t} \mu W$$

(c)

$$W = \int_0^{t=\infty} P_R dt = \int_0^{t=\infty} 2500 \times 10^{-6} e^{-100t} dt$$

$$W = \frac{2500 \times 10^{-6}}{-100} e^{-100t} \Big|_0^{\infty}$$

$$W = 0 - \left[\frac{-2500 \times 10^{-6}}{100} \right]$$

$$W = 25 \times 10^{-6} J = 25 \mu J$$

4.7 (cont)

(d) show that energy delivered to the resistor = energy stored in the capacitor.

The initial energy stored in the capacitor is

$$W_C = \frac{1}{2} C V_C^2$$


$$= \frac{1}{2} \times .02 \times 10^{-6} \times 50^2$$

$$= .01 \times 10^{-6} \times 2500$$

$$W_C = 25 \times 10^{-6} \text{ J} = 25 \mu\text{J}$$

QED

Ex 11 Consider the circuit below

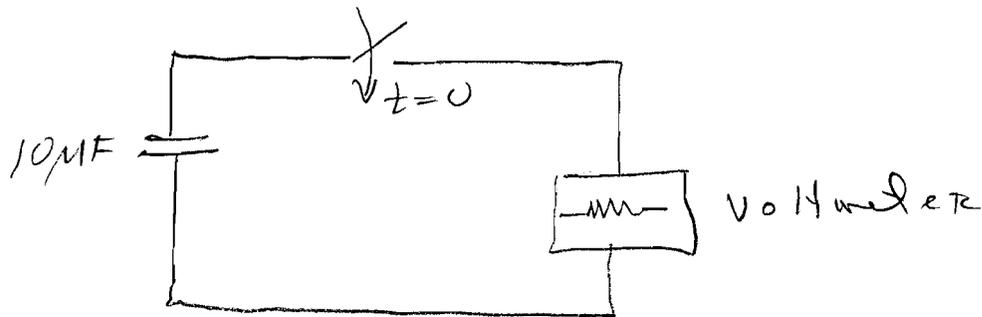

The capacitor is initially charged.
The switch closes at $t=0$. At
 $t=0$, the voltmeter reads 50 V.
The voltmeter can be represented
as a resistor. At $t=30$ sec,
the meter reads 25 V. Find
the value of R for the meter.

Solution

We know

$$V_C(t) = V_R(t) = V_C(0^+) e^{-\frac{t}{RC}}$$

The given values are

$$C = 10 \times 10^{-6} \text{ F}, \quad V_C(0^+) = 50 \text{ V}$$

$$V_C(30) = 25.$$

So

$$25 = 50 e^{-\frac{30}{RC}}$$

4.11 (cont)

so taking the \ln of
both sides

$$\ln(0.5) = \ln\left(e^{-\frac{30}{RC}}\right) = -\frac{30}{RC}$$


$$\therefore 0.69315 = -\frac{30}{RC}$$

$$RC = \frac{30}{0.69315}$$

$$\text{but } C = 10 \times 10^{-6}$$

$$R = \frac{30 \times 10^6}{0.69315} = 4.328 \text{ M}\Omega$$

4.17 We are given the circuit below

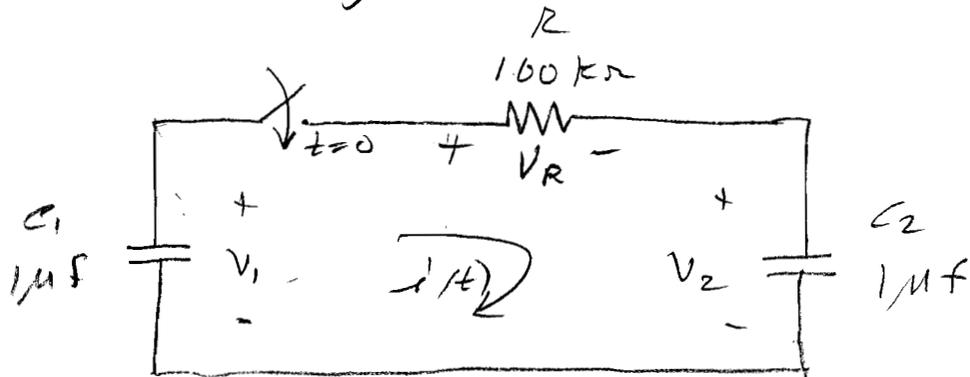

Given initial conditions,

$$V_1(0^-) = 100 \text{ V}, \quad V_2(0^-) = 0 \text{ V}$$

(a) Immediately after the switch is closed, what is $i(0^+)$?

We know

$$i(0^+) = \frac{V_1(0^+) - V_2(0^+)}{R}$$

$$i(0^+) = \frac{100 - 0}{100 \text{ k}} = 1 \text{ mA}$$

(b) Write KVL in terms of $V_1(t)$, $V_2(t)$ and $V_R(t)$

$$-V_1(t) + i(t)R + V_2(t) = 0$$

$$-\left[\frac{1}{C_1} \int_0^t i(t) dt - V_1(0) \right] + i(t)R + \frac{1}{C_2} \int_0^t i(t) dt + V_2(0) = 0$$

Take the derivative of the above w.r.t t .

4.17 (cont)

$$\frac{i(t)}{C_1} + R \frac{di}{dt} + \frac{i(t)}{C_2} = 0$$

$$\frac{di}{dt} + \frac{1}{R} \left[\frac{1}{C_1} + \frac{1}{C_2} \right] i(t) = 0$$

(c) What is the value of the time constant?

The time constant is

$$R C_{eq}$$

so for this case

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\tau = R \frac{C_1 C_2}{C_1 + C_2} = 100 \times 10^3 \times 0.5 \times 10^{-6}$$

$$\tau = 50 \text{ msec}$$

(d) We have

$$\frac{di}{dt} + 20 i(t) = 0$$

$$i(t) = k e^{-20t}$$

$$i(0^+) = 1 \times 10^{-3}$$

$$i(t) = 1 \times 10^{-3} e^{-20t} \text{ A} \quad t \geq 0$$

4.17 cont

3

(e) Find the value that V_2 approaches as t becomes very large.

$$V_2(t) = \frac{1}{L_2} \int_0^t i(t) dt + V_2(0^+)$$

$$V_2(t) = \frac{1}{L_2} \int_0^{\infty} 1 \times 10^{-3} e^{-20t} dt + 0$$

$$= \frac{1 \times 10^{-3}}{1 \times 10^{-6}} \left[-\frac{1}{20} e^{-20t} \right]_0^{\infty} + 0$$


$$V_2(\infty) = \frac{1 \times 10^{-3}}{20} = 50 \text{ V}$$

50

105

4.23

We are given the following circuit

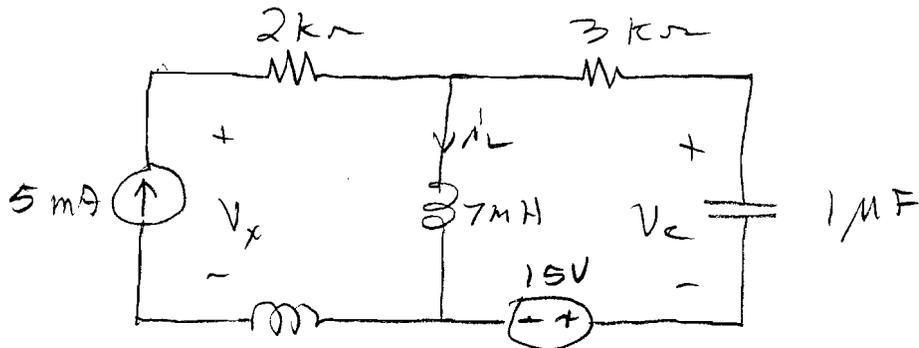


FIND i_L , V_x and V_c in steady state.

Solution

Draw the steady state circuit.

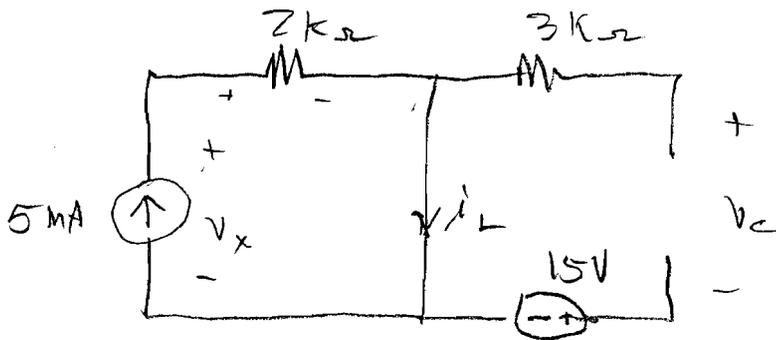coil \rightarrow short capacitor \rightarrow open



$$i_L = 5 \text{ mA} \quad (\text{no current through } 3k)$$

For V_x

write KVL

$$-V_x + 2 \times 10^3 \times 5 \times 10^{-3} = 0 \quad (\text{short is present})$$


$$\boxed{V_x = 10 \text{ V}}$$

For V_c

$$V_c + 15 = 0$$

$$\boxed{V_c = -15 \text{ V}}$$

4.28 We are given the following circuit.

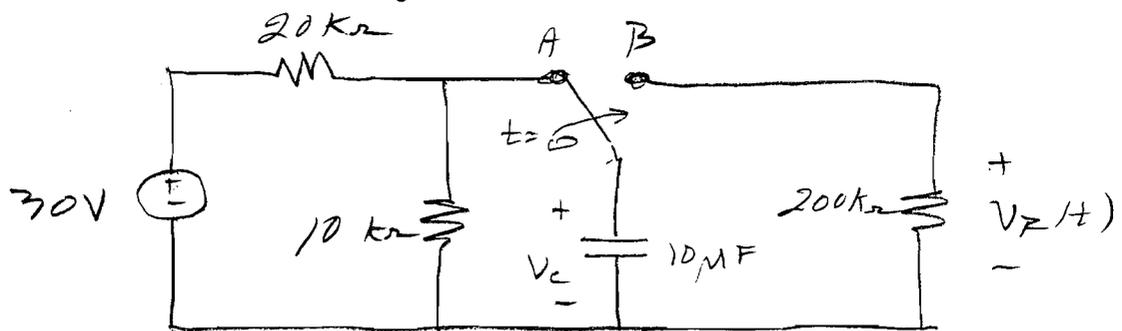

Switch is in the "A" position for a very long time. At $t=0$, it is moved to position B.

Find the expression for $V_R(t)$ and sketch the waveform for $-2 \leq t \leq 10$ s.

Solution


The switch being in position A for a very long time establishes $V_c(0^-) =$ voltage across the 100kΩ resistor. This voltage is easily found by voltage division.

$$V_c(0^-) = V_c(0^+) = 10 \text{ V}$$

Now look at the circuit after switching to B.

4.28 (cont)

2

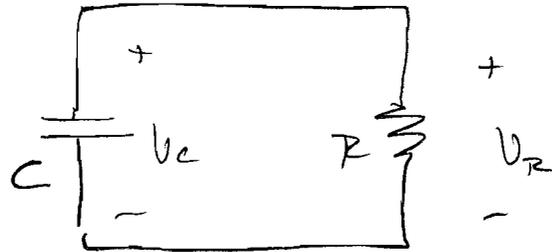

We know from previous work,


$$V_C(t) = V_R(t) = V_C(0^+) e^{-\frac{t}{RC}}$$

$$RC = 200 \times 10^3 \times 10 \times 10^{-6}$$


$$RC = 2000 \times 10^{-3} = 2 \text{ sec} = \tau$$

$$V_R(t) = 10 e^{-0.5t} \text{ V } \quad t \geq 0$$


$$V_R(t) = 0, \quad t < 0$$

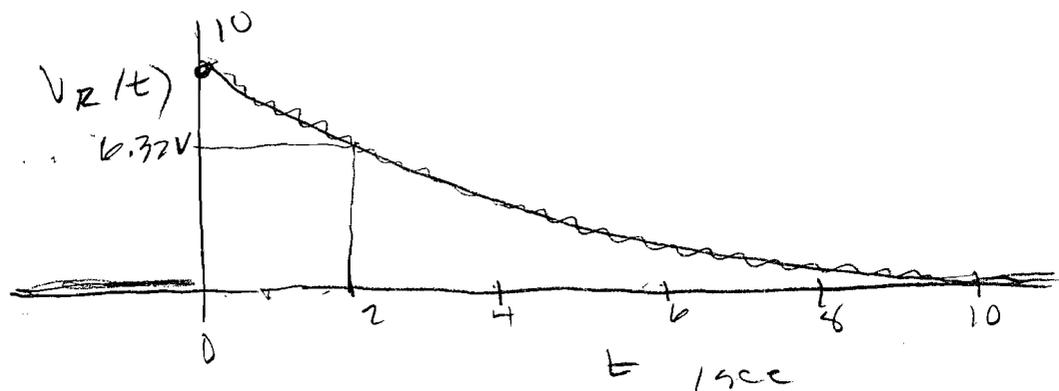

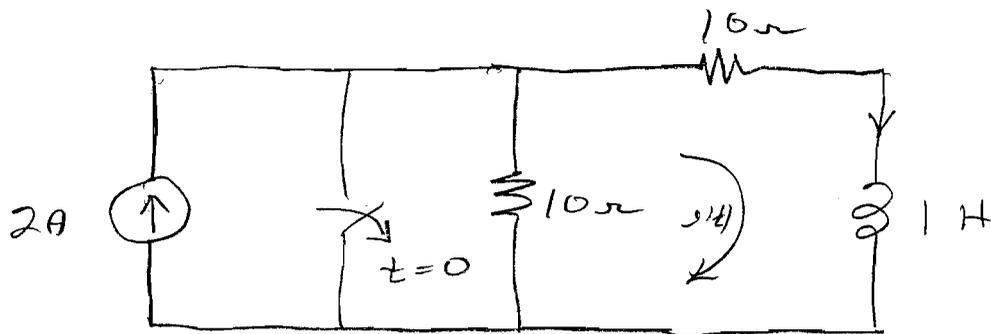4.32 We are given the following circuit which is operating in steady state prior to $t=0$



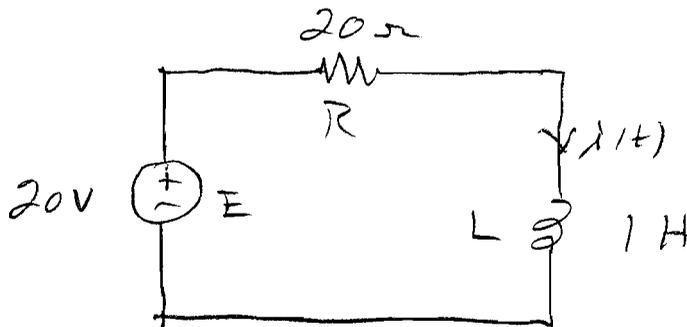Prior to $t=0$, $i(0^-) = 0$ A by inspection (All the 2A goes thru the short)
 After $t=0$, we have, with a source transformation,



We can write

$$E = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} i(t) = \frac{E}{L}$$

4.32 (cont)

putting in numbers

$$\frac{di}{dt} + 20i = 20$$

$$i(t) = i_p + i_c$$

$$i_p = K$$

$$20K = 20$$

$$K = 1$$

find i_c from

$$\frac{di}{dt} + 20i = 0$$

$$i_c(t) = K_c e^{-20t}$$

$$i(t) = 1 + K_c e^{-20t}$$


find K_c using $i_c(0^+)$ We know $i_c(0^-) = i(0^+) = 0A$

$$0 = 1 + K_c e^{-20 \cdot 0} = 1 + K_c$$

$$K_c = -1$$

$$i(t) = 1 - e^{-20t} \quad A \quad t \geq 0$$

4.35 We are given the following circuit.

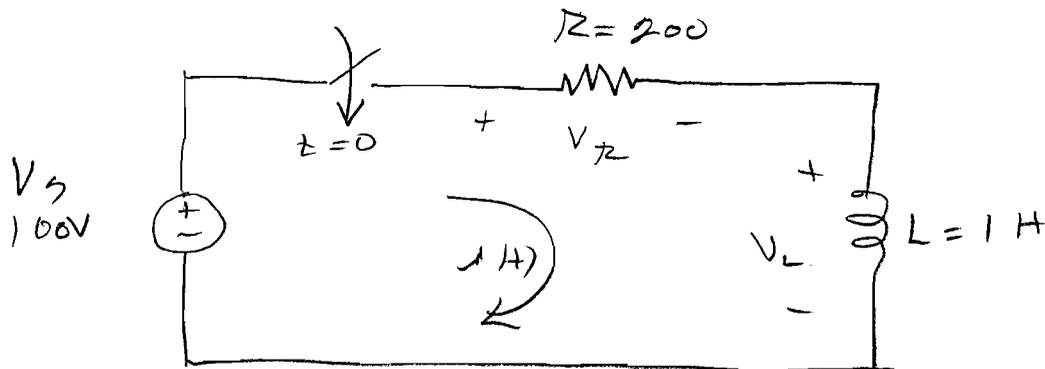

Find $i(t)$, sketch the waveform to scale.

Find an expression for $v_L(t)$
solution

We can write

$$V_s = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} i(t) = \frac{V_s}{L}$$

Putting in numbers

$$\frac{di}{dt} + 200i(t) = 100 \quad (1)$$

$$i(t) = i_p + i_c = i_{ss} + i_t$$

$$i_{ss} = K_{ss}$$

4.35 (cont)

Putting into (1) gives

$$200k_{45} = 100$$

$$k_{45} = 0.5$$

Solve

$$\frac{di'}{dt} + 200i'(t) = 0$$

for i'_t

$$i'_t = k_t e^{-200t}$$

$$i(t) = 0.5 + k_t e^{-200t} \text{ A} \quad (2)$$

$$i(0) = i(0^+) = 0$$

current can't change inst.


so, evaluate (2) at $t=0^+$

$$0 = 0.5 + k_t$$

$$k_t = -0.5$$

then
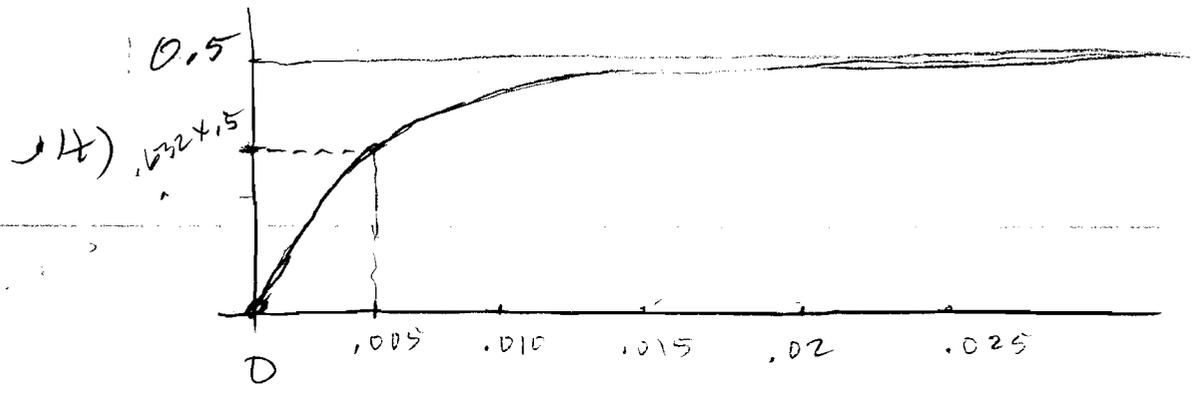
$$i(t) = 0.5 - 0.5 e^{-200t} \text{ A}, \quad t \geq 0$$



t sec


4.35 (cont)

$$V_L = L \frac{di}{dt}$$


$$V_L = 1 \times \frac{d}{dt} [0.5 - 0.5e^{-200t}]$$

$$= 0.5 \times 200 e^{-200t}$$

$$= 100 e^{-200t}$$

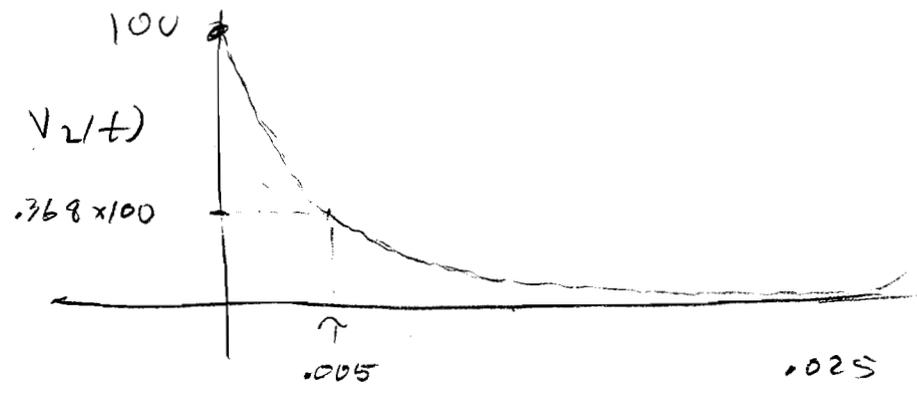

4.45 We are given the circuit below.

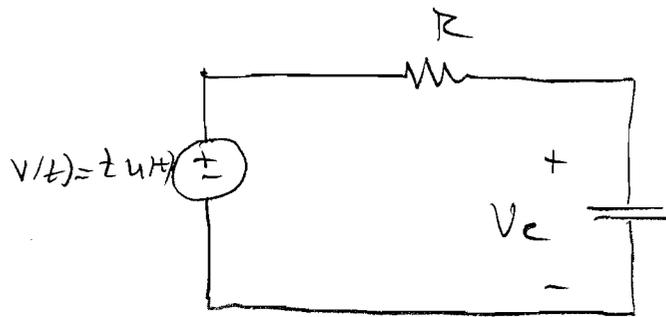

Assume $v_c(0^-) = 0$

Derive an expression for $v_c(t)$, $t \geq 0$,

$$i = C \frac{dv_c}{dt}$$

We write

$$v(t) = Ri(t) + v_c(t)$$

$$v(t) = RC \frac{dv_c}{dt} + v_c(t)$$

$$\frac{dv_c}{dt} + \frac{v_c(t)}{RC} = \frac{t}{RC} \quad (1)$$

$$v_c(t) = v_{c_{ss}} + v_{c_z}$$

$$v_{c_{ss}} = A + Bt$$

put this into (2)

4.45 (cont)

$$\frac{d}{dt} (A + Bt) + \frac{A + Bt}{RC} = \frac{t}{RC}$$

$$B + \frac{A + Bt}{RC} = \frac{t}{RC}$$

$$\left(\frac{A}{RC} + B \right) + \frac{B}{RC} t = \frac{t}{RC}$$

Equate coefficients of like powers.

$$\frac{A}{RC} + B = 0$$

$$\frac{B}{RC} = \frac{1}{RC}$$

$$\therefore B = 1$$

and

$$\frac{A}{RC} = -1$$

$$A = -RC$$

so

$$V_{C_{25}} = -RC + t$$

4.45 (cont)

3

$V_{c,t}$ satisfies

$$\frac{dV_c}{dt} + \frac{V_c}{RC} = 0$$

OR

$$V_{c,t} = K_2 e^{-\frac{t}{RC}}$$

Then

$$V_c(t) = V_{SS} + V_{c,t}$$

$$V_c(t) = -RC + t + K_2 e^{-\frac{t}{RC}}$$


$$V_c(0^-) = V_c(0^+) = 0$$

$$0 = -RC + K_2$$

$$K_2 = RC$$

$$\therefore V_c(t) = -RC + t + RC e^{-\frac{t}{RC}}$$

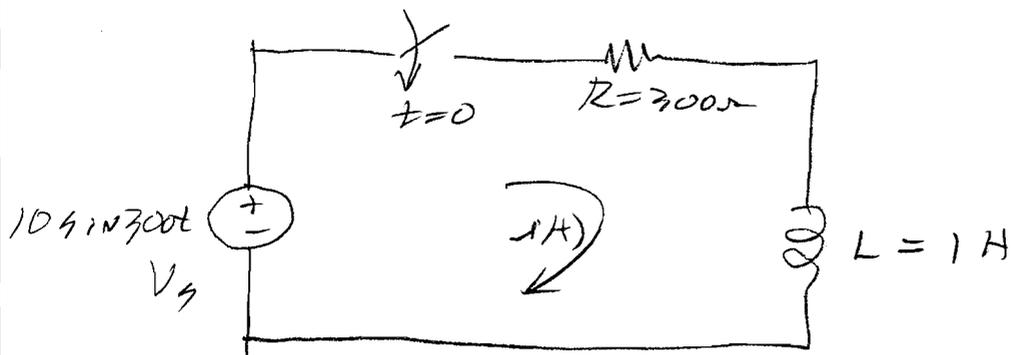4.48 We are given the circuit below. $i(0^+) = 0$



Find the solution for $i(t)$.

We have

$$V_s = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} i(t) = \frac{V_s}{L}$$

with numbers

$$\frac{di}{dt} + 300 i(t) = 10 \sin 300t \quad (1)$$

$$i(t) = i_{ss} + i_t = i_p + i_c$$

$$i_p = A \cos 300t + B \sin 300t$$

Substitute into, group coefficients

4.48 (cont)

2

$$\frac{d}{dt} [A \cos 300t + B \sin 300t] + 300 [A \cos 300t + B \sin 300t] = 10 \sin 300t$$

$$\begin{aligned} -300A \sin 300t + 300B \cos 300t \\ + 300A \cos 300t + 300B \sin 300t \\ = 10 \sin 300t \end{aligned}$$

$$300(A+B) \cos 300t + 300(B-A) \sin 300t = 10 \sin 300t$$

$$300A + 300B = 0$$

OR

$$\boxed{A + B = 0} \quad (3)$$

$$-300A + 300B = 10$$

OR

$$\boxed{-30A + 30B = 1} \quad (4)$$

multiply (3) by 30 and add

$$60B = 1$$

$$B = \frac{1}{60}$$

$$A = -\frac{1}{60}$$

4.48 (cont)

$$i_p = -\frac{1}{60} \cos 300t + \frac{1}{60} \sin 300t$$

$$i_c = K_c e^{-300t}$$

$$i(t) = i_p + i_c$$

$$i(t) = -\frac{1}{60} \cos 300t + \frac{1}{60} \sin 300t + K_c e^{-300t}$$

$$\text{at } t=0, i(0^+) = 0$$

$$0 = -\frac{1}{60} + K_c$$

$$K_c = \frac{1}{60}$$

$$i(t) = \left(-\frac{1}{60} \cos 300t + \frac{1}{60} \sin 300t + \frac{1}{60} e^{-300t} \right) A$$

$$t \geq 0$$

```
% The purpose of this problem is to use MATLAB to plot a
% mixture of cosine, sine and exponential functions. This
% function arises in ECE 301 from HW problem 4.48 in Hambley
% History: wlg; October 2, 2007; Office PC
% program name: trig_functions.m

% set up the span of time and the time stepping

t = 0: 0.001: 0.25;

% define the function to be plotted

i = (1/60)*exp(-300*t) - (1/60)*cos(300*t) + (1/60)*sin(300*t);

% plot the output

plot(t,i)
grid
gtext('Notice how fast the transient is over')
ylabel('i (amps)')
xlabel('t (sec)')
title('Transient response for RL circuit with sinusoidal forcing function')
```

Transient response for RL circuit with sinusoidal forcing function

