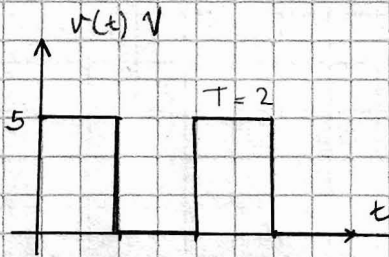


ECE 301


HW # 8 Solutions

5.11.




$$\begin{aligned}
 V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\
 &= \sqrt{\frac{1}{2} \left(\int_0^1 5^2 dt + \int_1^2 0^2 dt \right)} \\
 &= \underline{\underline{3.54 \text{ V}}}
 \end{aligned}$$

5.17

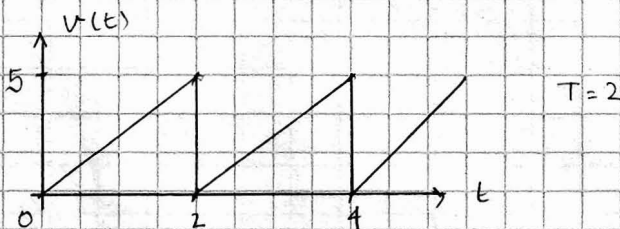

$$\begin{aligned}
 V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\
 &= \sqrt{\frac{1}{2} \int_0^2 (2.5t)^2 dt} \\
 &= \sqrt{\frac{1}{2} \left(0.25 \frac{t^3}{3} \right) \Big|_0^2} = \underline{\underline{2.887 \text{ V}}}
 \end{aligned}$$

5.22

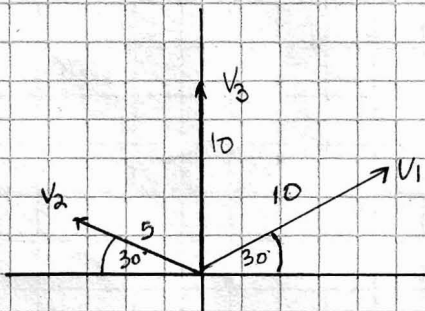

$$f = 200 \text{ Hz}$$

Write each signal in time-domain expression
 $V_m \cos(\omega t + \theta)$

$$\omega = 2\pi f = 400\pi, \text{ therefore:}$$

$$V_1 = 10 \cos(400\pi t + 30^\circ)$$

$$V_2 = 5 \cos(400\pi t + 150^\circ)$$

$$V_3 = 10 \cos(400\pi t + 90^\circ)$$


5.22 cont'd

 V_1 lags V_2 by 120° V_1 lags V_3 by 60° V_3 lags V_2 by 60° # 5.32 State the phase relationship between current & voltage for
a RESISTANCE, for an inductance, & for a CAPACITANCE

FOR a PURE RESISTANCE, CURRENT & VOLTAGE ARE IN PHASE.

" " INDUCTANCE, CURRENT LAGS VOLTAGE BY 90° " " CAPACITANCE, CURRENT LEADS VOLTAGE BY 90°

5.41

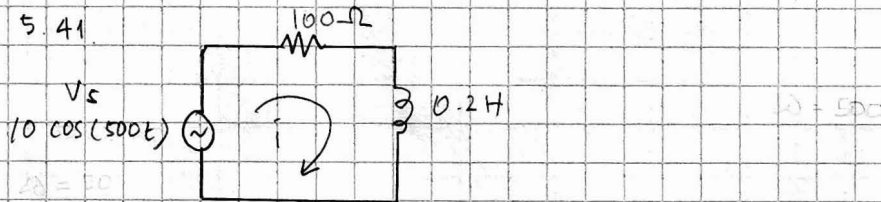

(a) Find phasors for the current & voltages


$$I = \frac{V_s}{R + j\omega L} = \frac{10 \angle 0^\circ}{100 + j100} \quad \omega = 500$$

$$= \underline{\underline{70.71 \angle -45^\circ \text{ mA}}}$$


$$V_R = IR = 7.071 \angle -45^\circ \text{ V}$$

$$V_L = I(j\omega L) = \underline{\underline{7.071 \angle +45^\circ \text{ V}}}$$

(b) Phasor diagram:

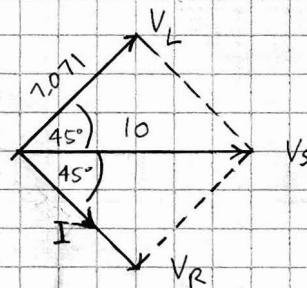(b) I lags V_s by 45°

5.51

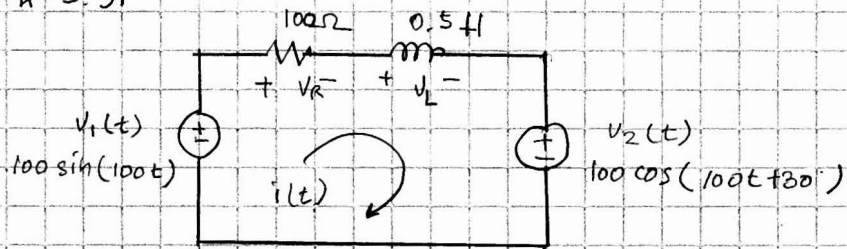

$$(a) \quad \underline{V_1} = 100 \angle -90^\circ$$

$$\underline{V_2} = 100 \angle 30^\circ$$

$$\underline{I} = \frac{\underline{V_1} - \underline{V_2}}{R + j\omega L} \quad \omega = 100$$


$$= \frac{(100 \angle -90^\circ) - (100 \angle 30^\circ)}{100 + j50}$$

$$= \frac{-86.60 - j160}{100 + j50} = \underline{1.549 \angle -146.6^\circ \text{ A}}$$

$$\underline{V_R} = \underline{I} R = \underline{154.9 \angle -146.6^\circ \text{ V}}$$

$$\underline{V_L} = \underline{I} (j\omega L) = \underline{I} (j50) = \underline{77.45 \angle -56.6^\circ \text{ V}}$$

(b) Phasor diagram

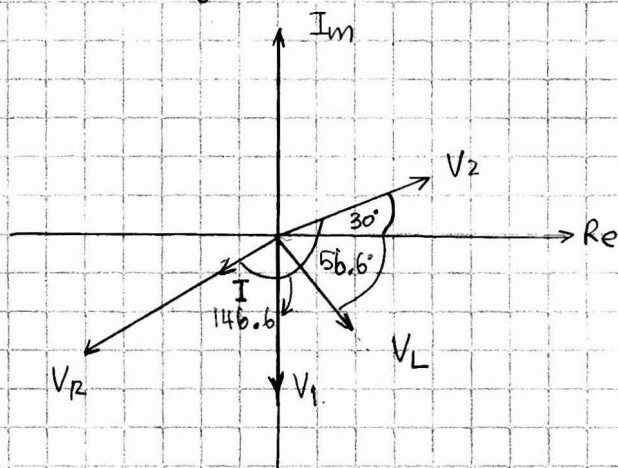

(c) \underline{I} lags $\underline{V_1}$ by 56.6°
 \underline{I} lags $\underline{V_L}$ by 90°