

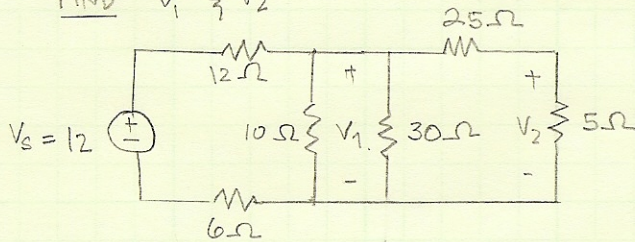


P 2.22.

FIND V_1 & V_2

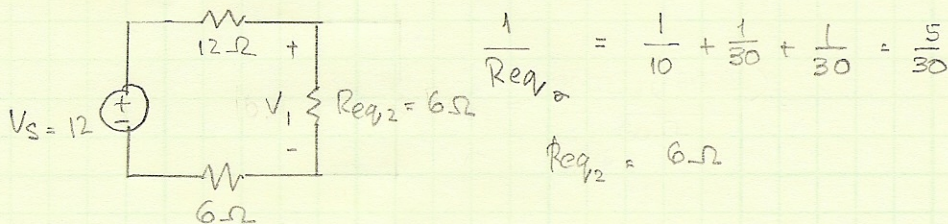

Solution.

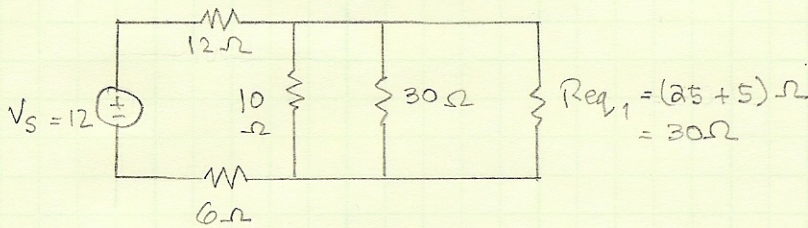


$$R_{TOTAL} = (12 + 6 + 6) \Omega = 24 \Omega$$

$$I = \frac{V_s}{R_{TOTAL}} = \frac{12}{24} = 0.5 \text{ A}$$

$$V_1 = (6)(0.5) \text{ V} = \underline{\underline{3 \text{ V}}}$$


To find V_2 , use the voltage division:

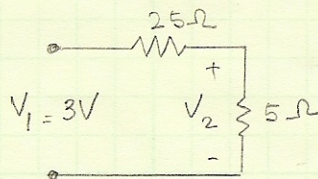

$$V_2 = \frac{5}{5 + 25} (3) \text{ V}$$


$$V_2 = \underline{\underline{0.5 \text{ V}}}$$

Pa. 24

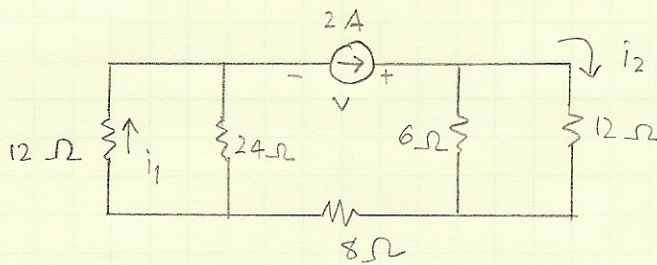

Find V, i_1, i_2 .


Solution

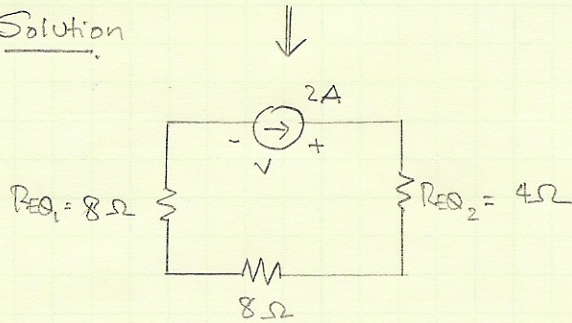

$$R_{EQ1} = \frac{(12)(24)}{36} = 8\Omega$$


$$R_{EQ2} = \frac{(6)(12)}{18} = 4\Omega$$
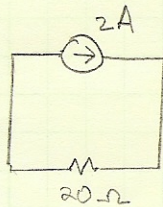
$$R_{TOTAL} = R_{EQ} = (8+8+4)\Omega = 20\Omega$$



$$V = (2)(20) = \underline{\underline{40\text{ V}}}$$


To Find i_1 :

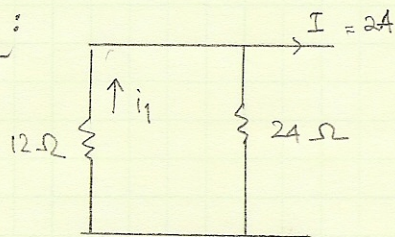

Using current division :

$$i_1 = \frac{24}{12+24} (2) = \underline{\underline{1.333\text{ A}}}$$


To Find i_2 :

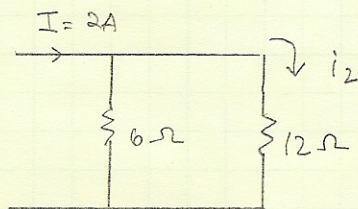

Using current division


$$i_2 = \frac{6}{6+12} (2) = \underline{\underline{0.667\text{ A}}}$$

P2.27.

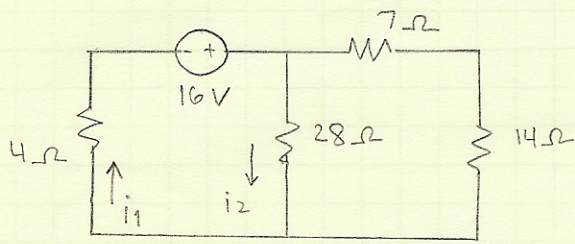

FIND i_1 & i_2

Solution.

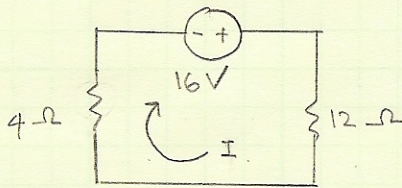

$$R_{EQ1} = \frac{(28)(7+14)}{28+7+14}$$
$$= 12\Omega$$


$$I = \frac{16}{16} = 1A$$

$$\underline{\underline{\hat{i}_1 = I = 1A}}$$

To find \hat{i}_2 , use current division:


$$\hat{i}_2 = \frac{21}{28+21} (1) A$$
$$= \underline{\underline{0.4286 A}}$$

P 2.29

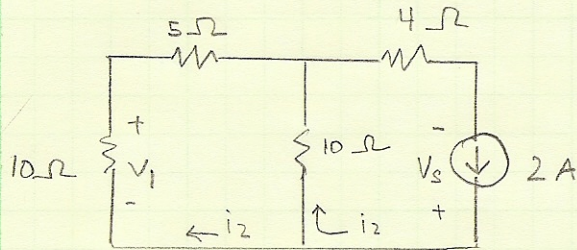

FIND V_s, V_1, i_2

Solution

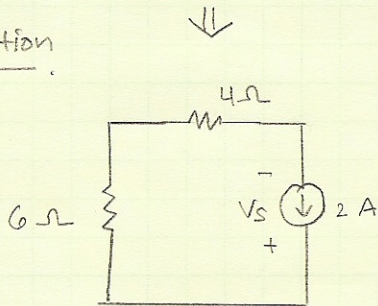

$$R_{EQ} = (10 + 4) \parallel 10$$
$$= \frac{(10+4)(10)}{(10+4)+10} = \frac{150}{25} = 6 \Omega$$


$$V_s = (2)(4+6)$$
$$= \underline{\underline{20V}}$$

USING CURRENT DIVISION:

$$i_1 = (2) \frac{10}{15+10} = \underline{\underline{0.8 A}}$$


$$i_2 = (2) \frac{15}{15+10} = \underline{\underline{1.2 A}}$$

P2.31

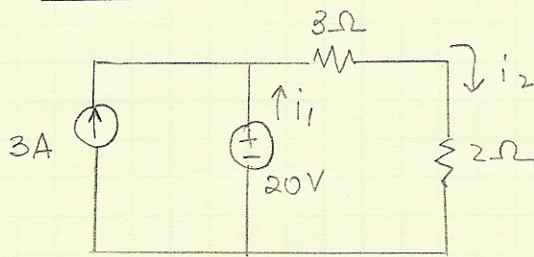

FIND i_1, i_2 & the POWER OF SOURCES.

Solution:

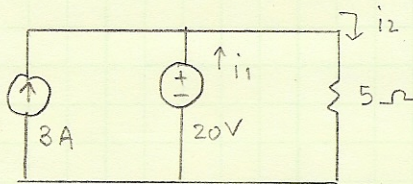

$$i_2 = \frac{20}{5} = \underline{\underline{4A}}$$


$$i_2 = i_1 + 3A \Rightarrow i_1 = i_2 - 3 \\ = 4 - 3 \\ = \underline{\underline{1A}}$$

$$P_{3A} = (3)(20) \\ = \underline{\underline{60W}}$$

$$P_{20V} = (i_1)(20) \\ = (1)(20) \\ = \underline{\underline{20W}}$$

POWER is DELIVERED by both SOURCES

P 2, 34

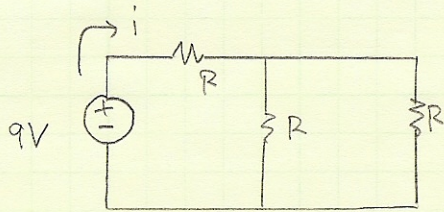

Given 9-V Voltage source
delivers 27 W
Find R

$$I = \frac{P}{V} = \frac{27}{9} = 3 \text{ A}$$

$$R_{EQ} = R + (R // R)$$

$$= R + \frac{R \cdot R}{R + R} = R + \frac{R^2}{2R}$$

$$= R + \frac{1}{2}R = \frac{3}{2}R$$


$$V = i R_{EQ} \Rightarrow V = \frac{3}{2} i R$$

$$9 = \frac{3}{2} (3) R$$

$$\underline{\underline{R = 2 \Omega}}$$


P 2

P 2.39

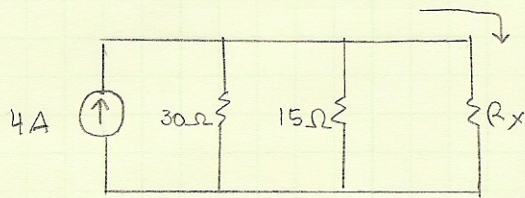

FIND R_x .

Solution :

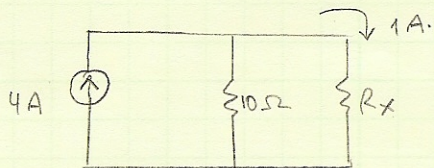


$$R_{30//15} = \frac{(30)(15)}{30+15} = 10\Omega$$

Using current division:

$$1A = \frac{10}{10+R_x} (4) \Rightarrow \underline{\underline{R_x = 30\Omega}}$$

P 2.40

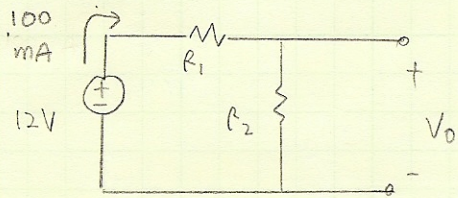


$$V_0 = 5V$$

(a) Find R_1, R_2


(b) Suppose a resistance $200\ \Omega$ is connected across output terminals. Find V_0

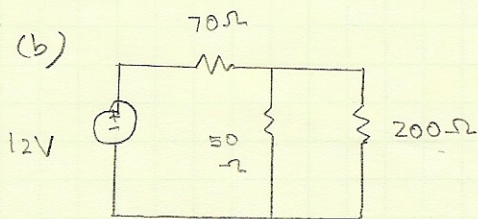(a) FINDING R_1 : $12 = (0.1)R_1 + 5$
 $7 = 0.1R_1$
 $R_1 = \underline{\underline{70\ \Omega}}$

FINDING R_2 : $5 = (0.1)R_2$
 $R_2 = \underline{\underline{50\ \Omega}}$



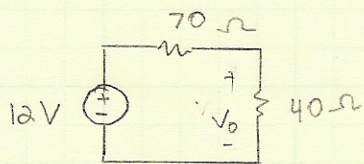
$$R_{50//200} = \frac{(50)(200)}{50+200} = 40\ \Omega$$



To find V_0 , USE voltage division :

$$V_0 = 12 \frac{40}{40+70} = \underline{\underline{4.364\ V}}$$

Pa. 43

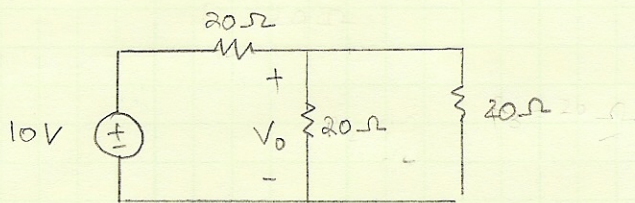


FIND V_0

Solution:

$$R_{20/20} = \frac{(20)(20)}{20+20} = 10\Omega$$

$$V_0 = \frac{10}{10+20} (10) = \underline{\underline{3.333\text{ V}}}$$

Pa. 45

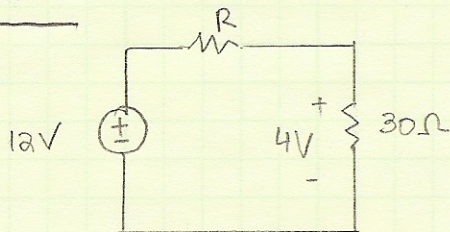

Given 30Ω supplied with 4V, and a 12V voltage source

Draw a suitable circuit with one additional resistor.
FIND R .

Solution

The resistor needs to be placed in series w the load & voltage source.

Using voltage division:

$$4 = \frac{30}{30+R} (12) \Rightarrow \underline{\underline{R = 60\Omega}}$$